


CSE=2021=

COMPUTER=ORGANIZATION

HUGH=CHESSE=R
CSE=B=L0L2U


W9-M

Combined Datapath

 

Control: ALU Control Unit (1)

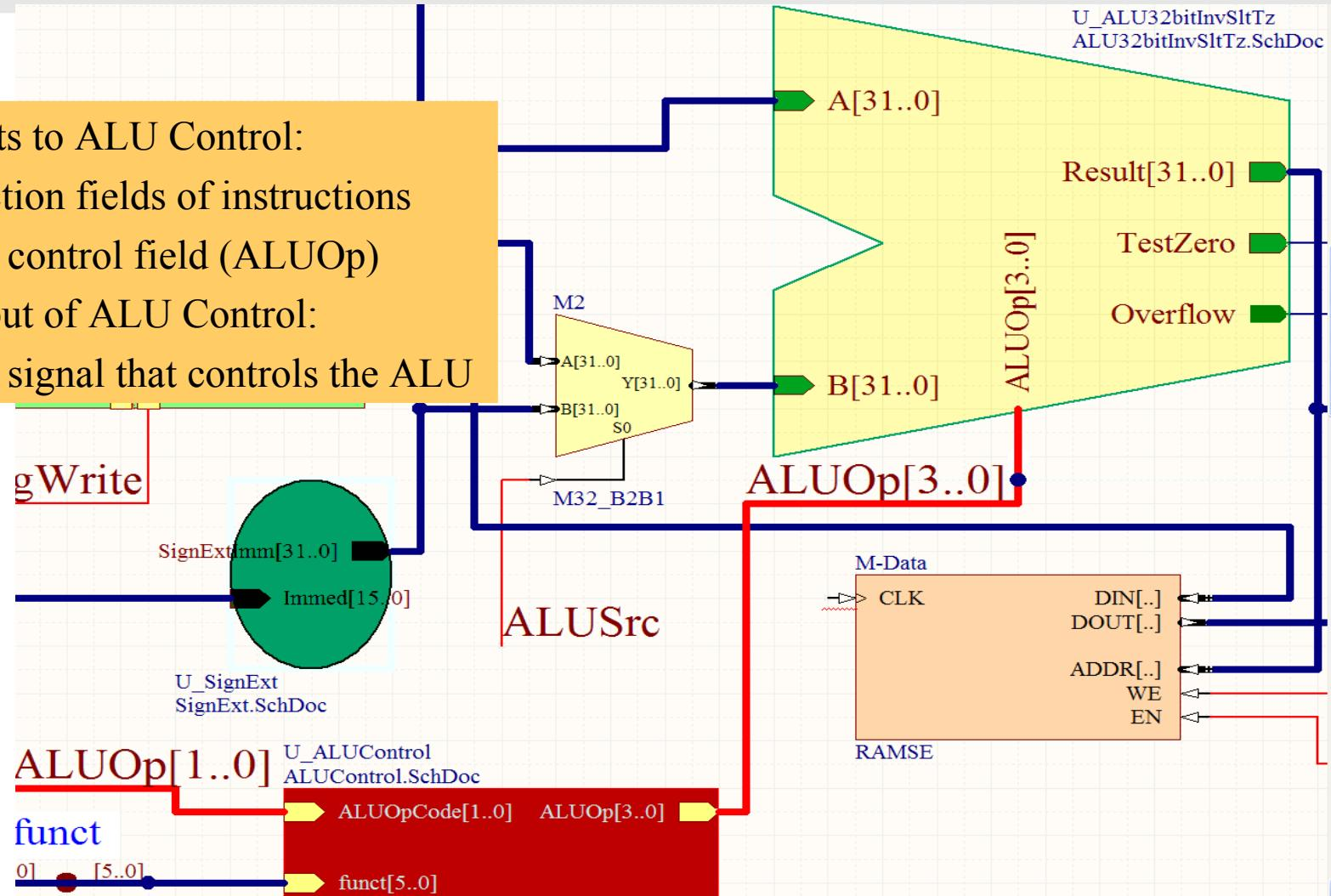- Inputs to ALU Control:
 1. Function fields of instructions
 2. 2-bit control field (ALUOp)
- Output of ALU Control:
 1. 4-bit signal that controls the ALU



Control: ALU Control Unit (4)

Instruction (funct)	Inputs		Desired ALU action	Outputs Operation (Op3 – Op0)
	ALUOp (ALUOp1 – ALUOp0)	Function Field (F5 – F0)		
lw (I)	0 X (0 0)	X X X X X X	add	0 0 1 0
sw (I)	0 X (0 0)	X X X X X X	add	0 0 1 0
beq (I)	X 1 (0 1)	X X X X X X	sub	0 1 1 0
add (32)	1 X (1 0)	X X 0 0 0 0	add	0 0 1 0
sub (34)	1 X (1 0)	X X 0 0 1 0	sub	0 1 1 0
and (36)	1 X (1 0)	X X 0 1 0 0	and	0 0 0 0
or (37)	1 X (1 0)	X X 0 1 0 1	or	0 0 0 1
slt (42)	1 X (1 0)	X X 1 0 1 0	slt	0 1 1 1

Simplified Expressions:

$$\text{Op0} = \overline{\text{ALUOp1}} \cdot (\overline{\text{F0}} + \overline{\text{F3}})$$

$$\text{Op1} = \overline{\text{ALUOp1}} + \overline{\text{F2}}$$

$$\text{Op2} = \text{ALUOp0} + \text{ALUOp1} \cdot \text{F1}$$

Agenda

Topics:

1. A single cycle implementation (complete this)
2. iverilog Example
3. Sample question – add jr instruction

Patterson: Section 4.3, 4.4


Reminder: Quiz #2 – Next Wednesday (November 11)

Control: ALU Control Unit (5)

$$Op0 = \overline{ALUOp1} \cdot (F0 + F3)$$

$$Op1 = \overline{ALUOp1} + \overline{F2} = \overline{ALUOp1} \cdot F2$$

$$Op2 = ALUOp0 + ALUOp1 \cdot F1$$

 


Main Control (1)

R-format:	op (31 – 26)	rs (25 – 21)	rt (20 – 16)	rd (15 – 11)	shamt (10 – 6)	funct (5 – 0)
I-format:	op (31 – 26)	rs (25 – 21)	rt (20 – 16)		Immediate / Offset (15 – 0)	

1. Opcode is contained in bits 31 – 26.
2. Registers specified by rs (bits 25 – 21) and rt (bits 20 – 16) are always read
3. Base register (w/ base address) for lw/sw instruction is specified by rs (bits 25–21)
4. 16-bit offset for **beq**, **lw**, and **sw** is always specified in bits 15 – 0.
5. Destination register is specified in one of the two places:
 - For R-type instructions (add/sub/and/or), destination register is specified by bits (15 – 11)
 - For lw instruction, destination register is specified by bits (20 – 16)

Using information (1 – 5), we can add the instruction labels and additional MUX's to the datapath that we have constructed.

Main Control (2)

 


Number of control lines is 11 (4 for MUX's, 4 for ALU control, 2 for data memory, 1 for register file)

Main Control (3)

Control Input	Effect when Deasserted (0)	Effect when asserted (1)
RegDst	Destination register number comes from bits 20 – 16 of the instruction (sw)	Destination register number comes from bits 15 – 11 of the instruction (add, sub, or, and, slt)
Regwrite	None	Data on the “write data” input is written on the register specified on the “write register” input (lw, add, sub, or, and)
ALUSrc	Second operand to ALU comes from the second register file output (add, sub, or, and, beq, slt)	Second operand to ALU is sign extended, lower 16 bits of instruction(lw,sw)
MemRead	None	Data from memory location specified by “address” input is placed on the “read data” output (lw)
MemWrite	None	Data from “write data” input replaces memory location specified by “address” input (sw)
MemtoReg	Data from the output of ALU is fed into “write data” input of the register file (add, sub, or, and, slt)	Data from the “read data” output of data memory is fed into “write data” input of the register file (lw)
PCSrc	PC is replaced by the output of adder which adds 4 to the existing content of PC (except for beq)	PC is replaced by the output of adder which computes branch target by adding existing content of PC with 2-bit right shifted offset (beq)

Next step in the design of datapath is to add a control unit that generates the control inputs to MUX's

Main Control (4)

 

Main Control (5)

Control Unit Inputs:


Instruction	Opcode in Decimal	Opcode in Binary					
		Op5	Op4	Op3	Op2	Op1	Op0
R-format	0 _{ten}	0	0	0	0	0	0
lw	35 _{ten}	1	0	0	0	1	1
sw	43 _{ten}	1	0	1	0	1	1
beq	4 _{ten}	0	0	0	1	0	0

Outputs of Control Unit:

Instruction	RegDst	ALUSrc	MemtoReg	RegWrite	MemRead	MemWrite	Branch	ALUOp1	ALUOp0
R-format	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0
sw	X	1	X	0	0	1	0	0	0
beq	X	0	X	0	0	0	1	0	1

...above 2 tables constitute the truth table

Main Control (6)

 


Example: R-type Instruction (step1: fetch instruction & increment PC)


Step 1

1. Fetch instruction

2. Add 4 to the value of PC

 

 
Example: R-type Instruction (step2: Read two source registers)




Step 2:

1. Source registers are read from the register file
 2. Control unit uses the opcode to activate units.
- ALUOp = 10 set based on opcode

 Example: R-type Instruction (step3: ALU operates on operands)



 Example: R-type Instruction (step 4: Write result in destination register)



Why is single-cycle implementation not used?

Assuming no delay at adder, sign extension unit, shift left unit, PC, control unit, and MUX:

- Load cycle requires 5 functional units:
instruction fetch, register access, ALU, data memory access, register access
- Store cycle requires 4 functional units:
instruction fetch, register access, ALU, data memory access
- R-type instruction cycle requires 4 functional units:
instruction fetch, register access, ALU, register access
- Path for a branch instruction requires 3 functional units:
instruction fetch, register access, ALU
- Path for a jump instruction requires 1 functional unit:
instruction fetch

Using a clock cycle of equal duration for each instruction is a waste of resources.

iverilog Example

C:\iverilog\Q1.v - Notepad++

```
File Edit Search View Encoding Language Settings Macro Run TextFX Plugins Window
Q1.v testbench.v

1 module eq2_sop
2   (
3     input wire[1:0] a, b,
4     output wire aeqb
5   );
6
7   // internal signal declaration
8   wire p0, p1, p2, p3;
9
10  //sum of product terms
11  assign aeqb = p0 | p1 | p2 | p3;
12
13  // product terms
14  assign p0 = (~a[1] & ~b[1]) & (~a[0] & ~b[0]);
15  assign p1 = (~a[1] & ~b[1]) & (a[0] & b[0]);
16  assign p2 = (a[1] & b[1]) & (~a[0] & ~b[0]);
17  assign p3 = (a[1] & b[1]) & (a[0] & b[0]);
18
endmodule
```

C:\iverilog\testbench.v - Notepad++

```
File Edit Search View Encoding Language Settings Macro Run TextFX Plugins Window ?
Q1.v testbench.v

1 module testbench;
2   reg [1:0] test_a, test_b;
3   wire test_c;
4
5   eq2_sop uut_eq2(test_a, test_b, test_c);
6
7   initial
8   begin
9     #200
10    test_a = 2'b10;
11    test_b = 2'b10;
12    #1 $display($time, " a = %d, b = %d, c = %d", test_a, test_b, test_c);
13    #200
14    test_a = 2'b00;
15    test_b = 2'b10;
16    #1 $display($time, " a = %d, b = %d, c = %d", test_a, test_b, test_c);
17
18 endmodule
```

cmd.exe

```
C:\iverilog>iverilog Q1.v testbench.v
C:\iverilog>vvp a.out
      201 a = 2, b = 2, c = 1
      402 a = 0, b = 2, c = 0

C:\iverilog>
```


Activity (Sample Quiz, Exam Q)

We wish to add jr (jump register) to the single cycle datapath from the previous slide. Add the necessary connections to the single cycle datapath block diagram to implement the jr instruction. Also, append the table below to add the necessary control signals needed for the jr instruction.

Instruction	RegDst	ALUSrc	MemtoReg	RegWrite	MemRead	MemWrite	Branch	ALUOp1	ALUOp0
R-format	1	0	0	1	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0
sw	X	1	X	0	0	1	0	0	0
beq	X	0	X	0	0	0	1	0	1

Answer (Part 1):

Modify the datapath as shown

 

Answer (Part 2):

... append the table below to add the necessary control signals needed for the jr instruction.

Instruction	RegDst	ALUSrc	MemtoReg	RegWrite	MemRead	MemWrite	Branch	JumpReg	ALUOp1	ALUOp0
R-format	1	0	0	1	0	0	0	0	1	0
lw	0	1	1	1	1	0	0	0	0	0
sw	X	1	X	0	0	1	0	0	0	0
beq	X	0	X	0	0	0	1	0	0	1
jr	X	0	X	0	0	0	0	1	0	1