

# CSE 2021 COMPUTER ORGANIZATION

HUGH CHESSER  
CSE B 1012U

# Agenda

## Topics:

1. Register files, Decoder, Data Memory, Instruction Memory – Building Blocks
2. Complete hardware implementation of goal instructions

Patterson: Appendix C, Section 4.1, 4.2, 4.3

Reminder: Next week make-up for Labs A-D


# Overview (1)

**Goal:** Implement a subset of core instructions from the MIPS instruction set, given below

Category	Instruction	Example	Meaning	Comments
Arithmetic and Logical	<b>add</b>	<code>add \$s1, \$s2, \$s3</code>	$\$s1 \leftarrow \$s2 + \$s3$	
	<b>subtract</b>	<code>sub \$s1, \$s2, \$s3</code>	$\$s1 \leftarrow \$s2 - \$s3$	
	<b>and</b>	<code>and \$s1, \$s2, \$s3</code>	$\$s1 \leftarrow \$s2 \& \$s3$	<b>&amp; =&gt; and</b>
	<b>or</b>	<code>or \$s1, \$s2, \$s3</code>	$\$s1 \leftarrow \$s2   \$s3$	<b>  =&gt; or</b>
	<b>slt</b>	<code>slt \$s1, \$s2, \$s3</code>	If $\$s1 < \$s3$ , $\$s1 \leftarrow 1$ else $\$s1 \leftarrow 0$	
Data Transfer	<b>load word</b>	<code>lw \$s1, 100(\$s2)</code>	$\$s1 \leftarrow \text{Mem}[\$s2 + 100]$	
	<b>store word</b>	<code>sw \$s1, 100(\$s2)</code>	$\text{Mem}[\$s2 + 100] \leftarrow \$s1$	
Branch	<b>branch on equal</b>	<code>beq \$s1, \$s2, L</code>	if $(\$s1 == \$s2)$ go to L	
	<b>unconditional jump</b>	<code>j 2500</code>	go to 10000	
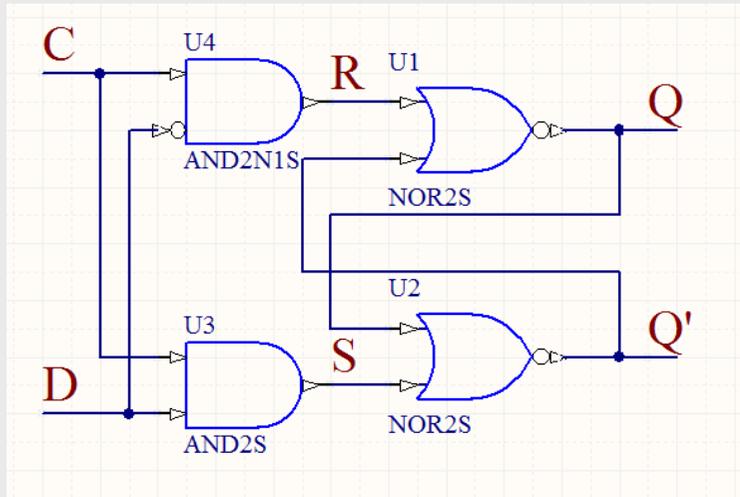
# Basics: Clocked D Latch (4)

- For a D-latch: output  $Q = 1$  when  $D = 1$  (set condition)  
output  $Q = 0$  when  $D = 0$  (reset condition)




Logic Diagram


Inputs		Outputs		Comments
C	D	Q	$Q' = \bar{Q}$	
0	X	Unchanged		
1	0	0	1	Reset
1	1	1	0	Set

Function Table

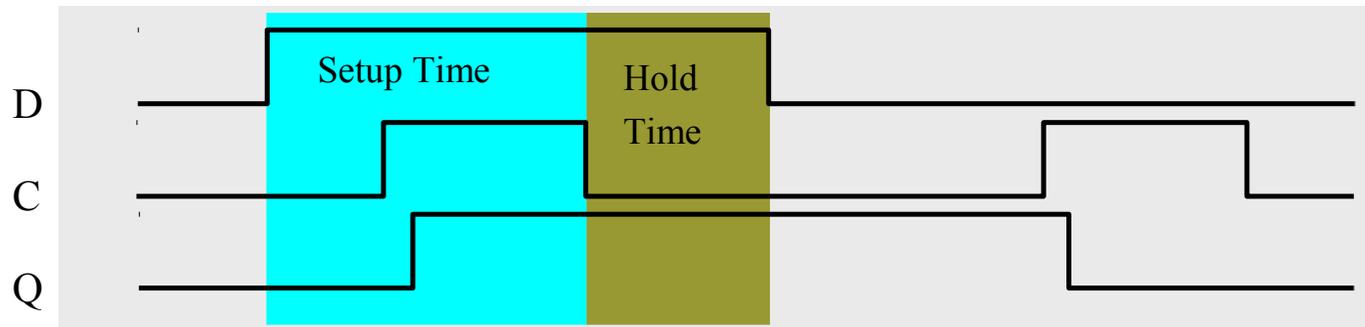- D Latch requires clock to be asserted for output to change



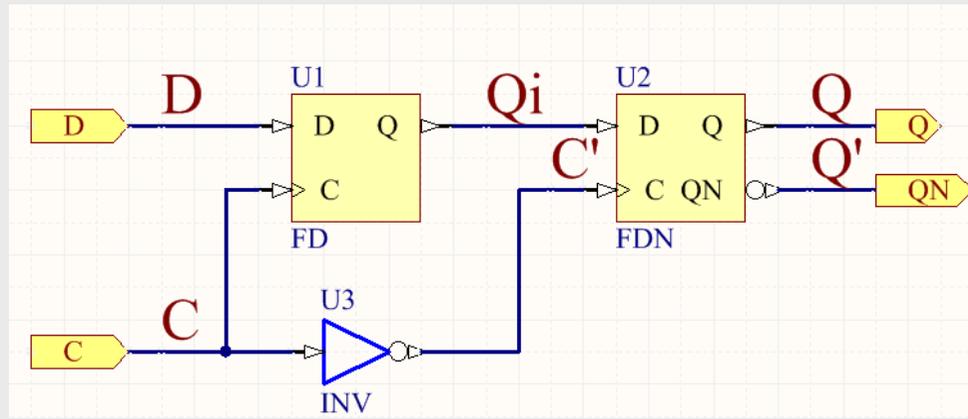
# Basics: Falling Edge Triggered D flip-flop (5)



Logic Diagram


Latch changes state on falling edge of clock

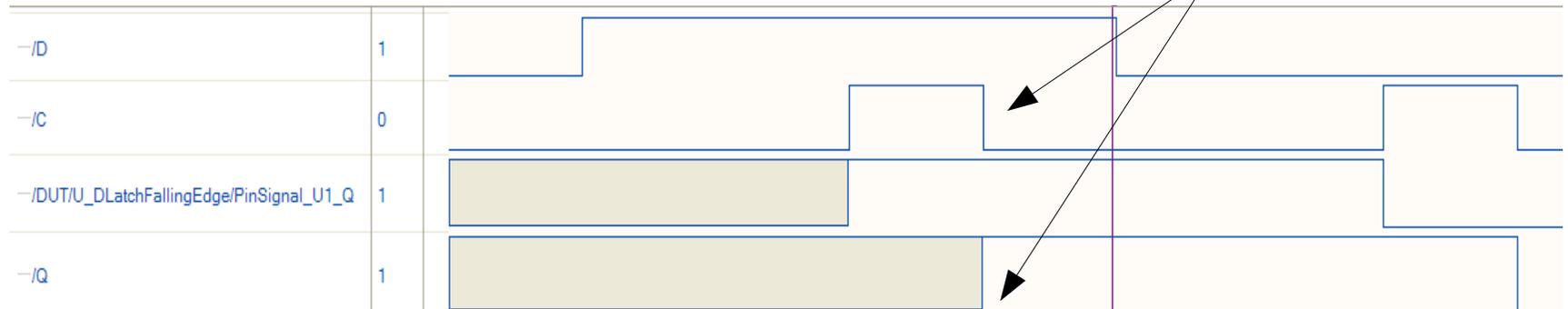Output Q follows D but changes only at the clock falling edge



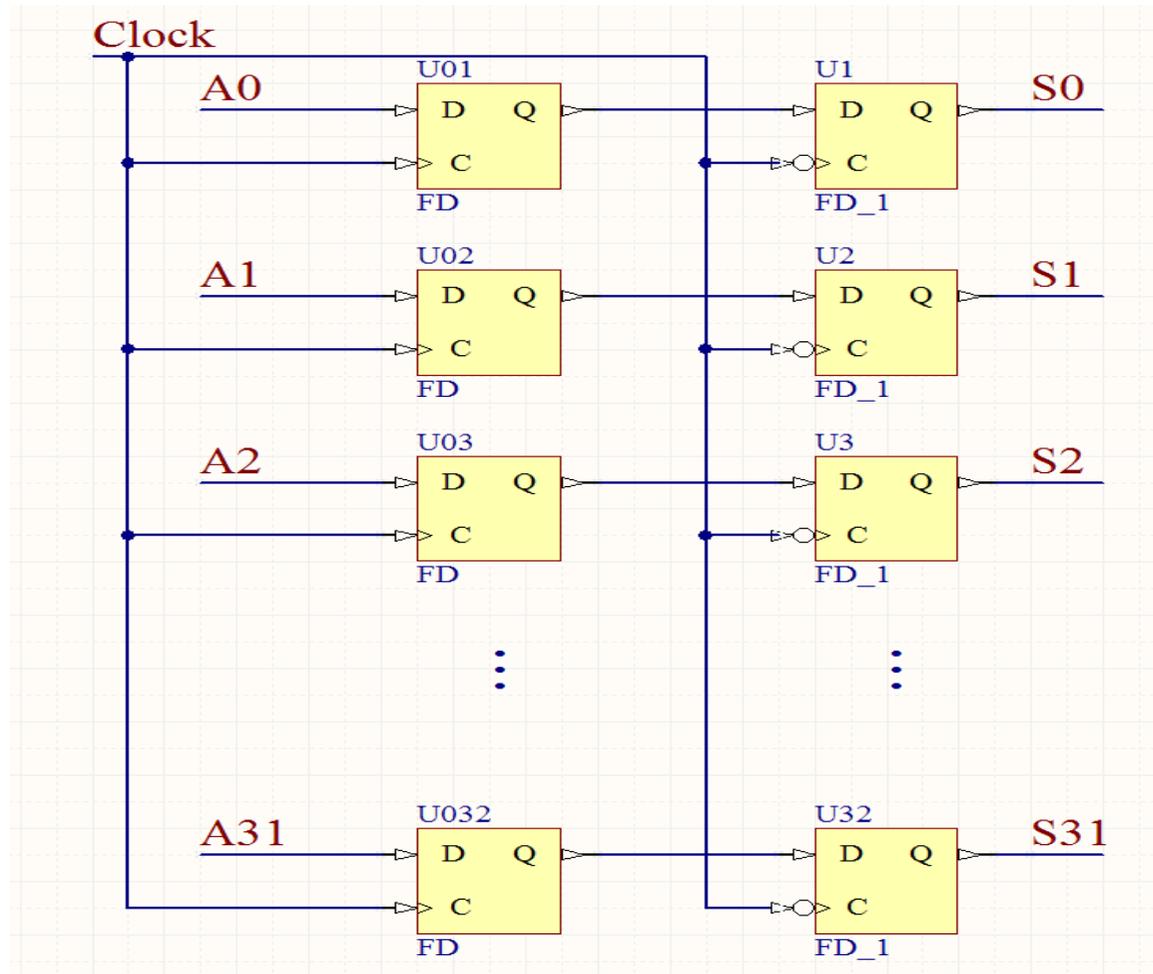
# Basics: 32-bit Registers (6)

Falling edge triggered D flip-flops can be combined to form a register



## Basics: Register Files (6)


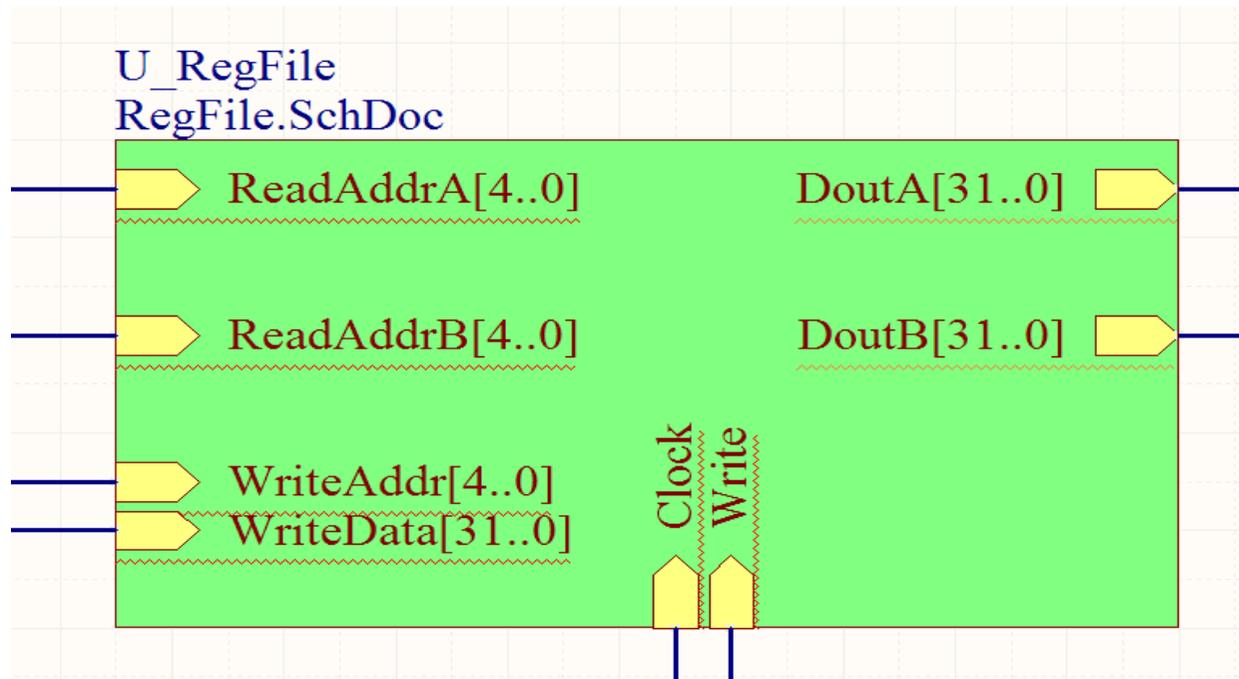
1. Register files consist of a set of registers that can be read or written individually
2. In MIPS, register file contains 32 registers
3. Two registers can be read simultaneously
4. One register can be written at one time



# Basics: Write Enabled 1-bit Register (7)
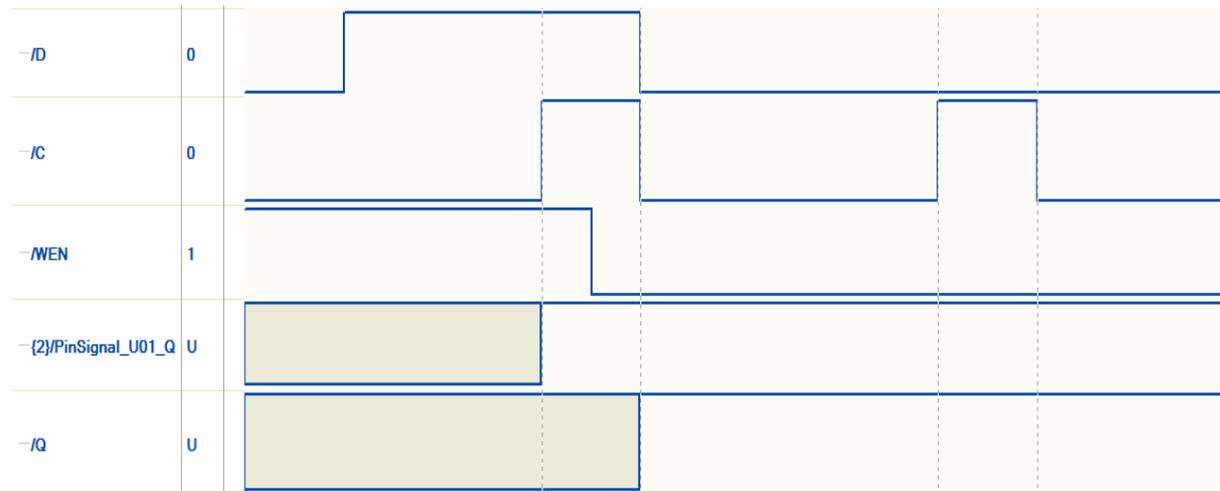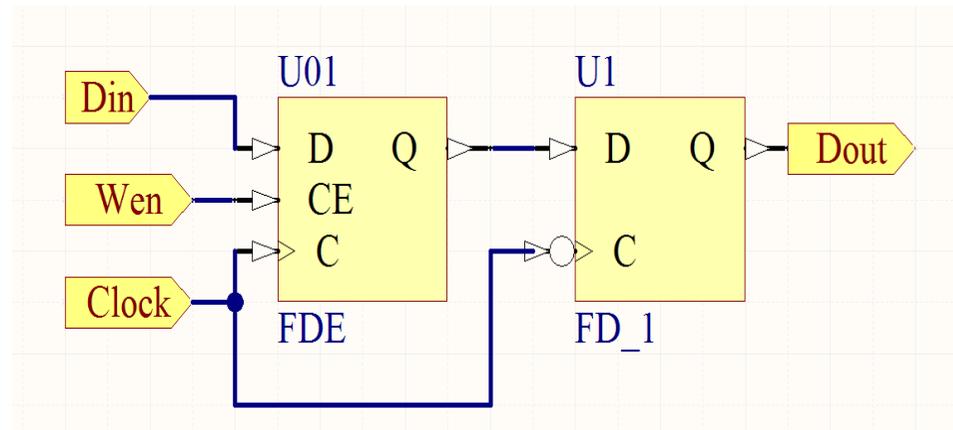
## Write Operation:


- Slight change to D flip-flop to include a "Write" input
- Din (Data input) changes flip-flop state only if "Wen" (Write enable) is true
- Clock that controls the write operation timing



# Basics: 32-bit Register (8)
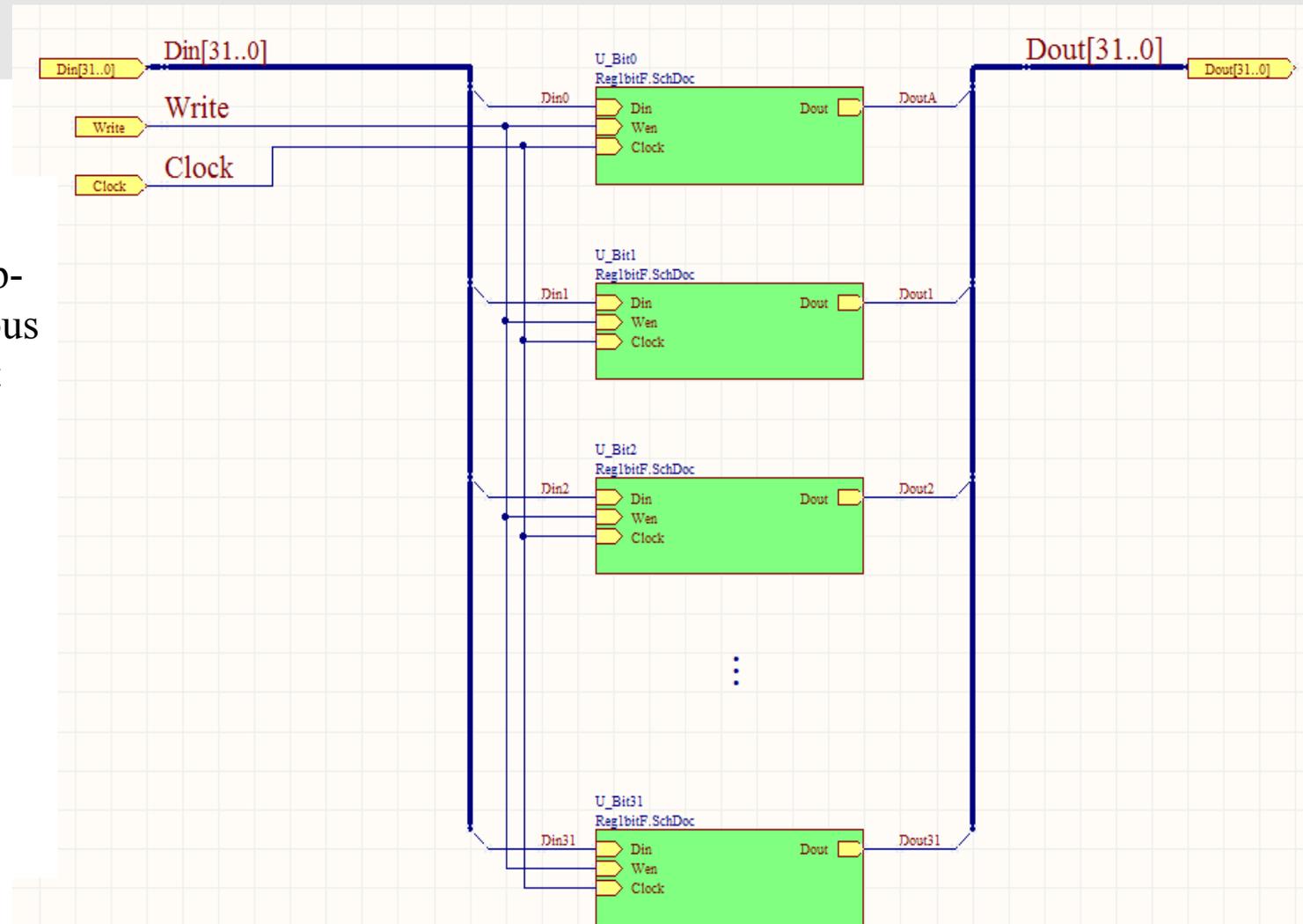
## Register:

- We duplicate the Flip-flops from the previous slide to form a 32-bit register
- Each bit receives the same “Write” and Clock inputs which enable the writing of data “Din”
- A single set of Dout lines allows the register to be read




# Basics: Write Operation in Register Files (9)

We now duplicate the 32-bit registers from the previous slide to provide 32 registers of the Register File
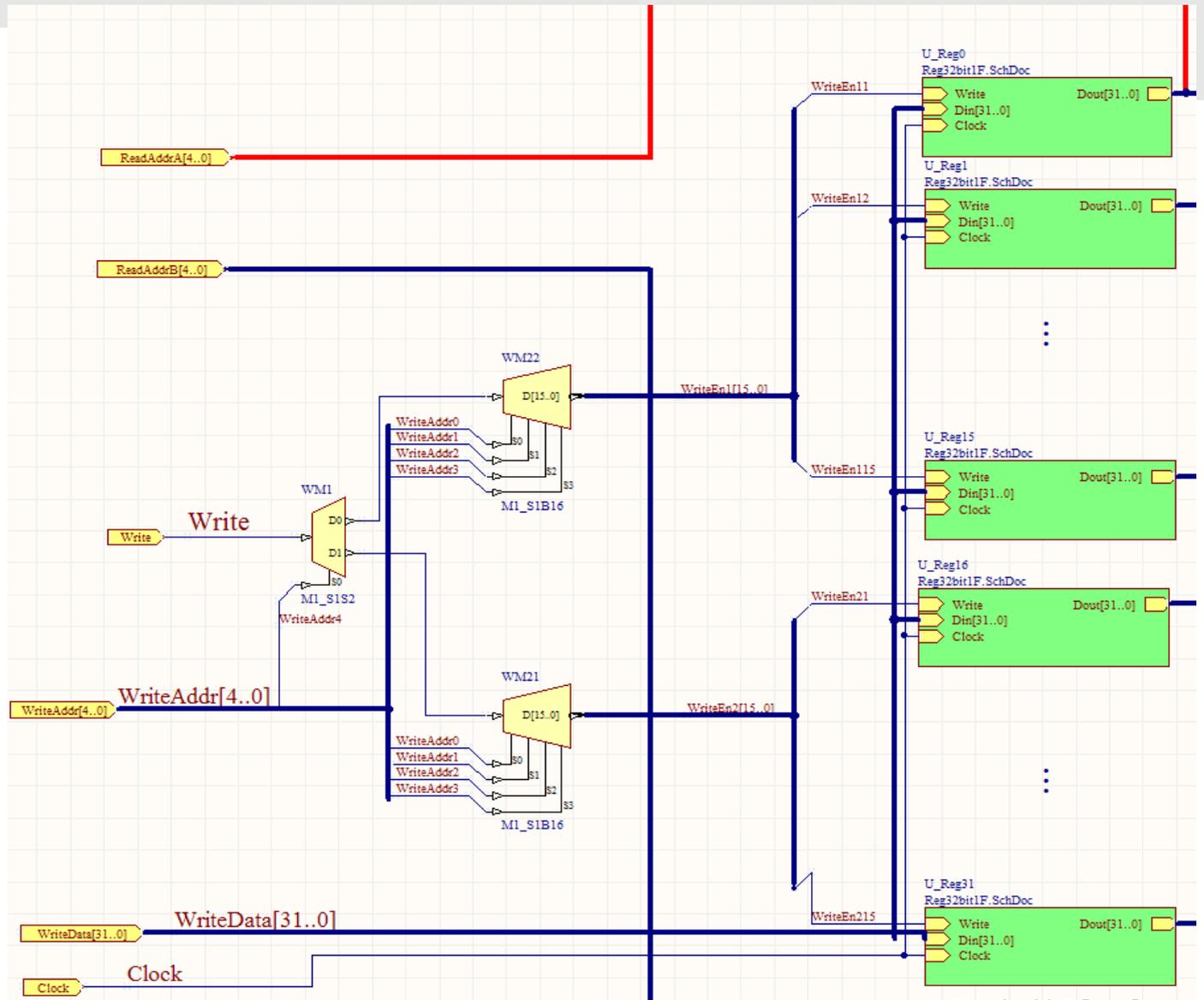
## Write Operation:


- Register number of the register to be written is one input (WriteAddr bus)
- Data to be written is the second input (WriteData bus)
- Clock that controls the write operation is the third input
- **Decoders** are used in the write operation




# Basics: Read Operation in Register File (10)
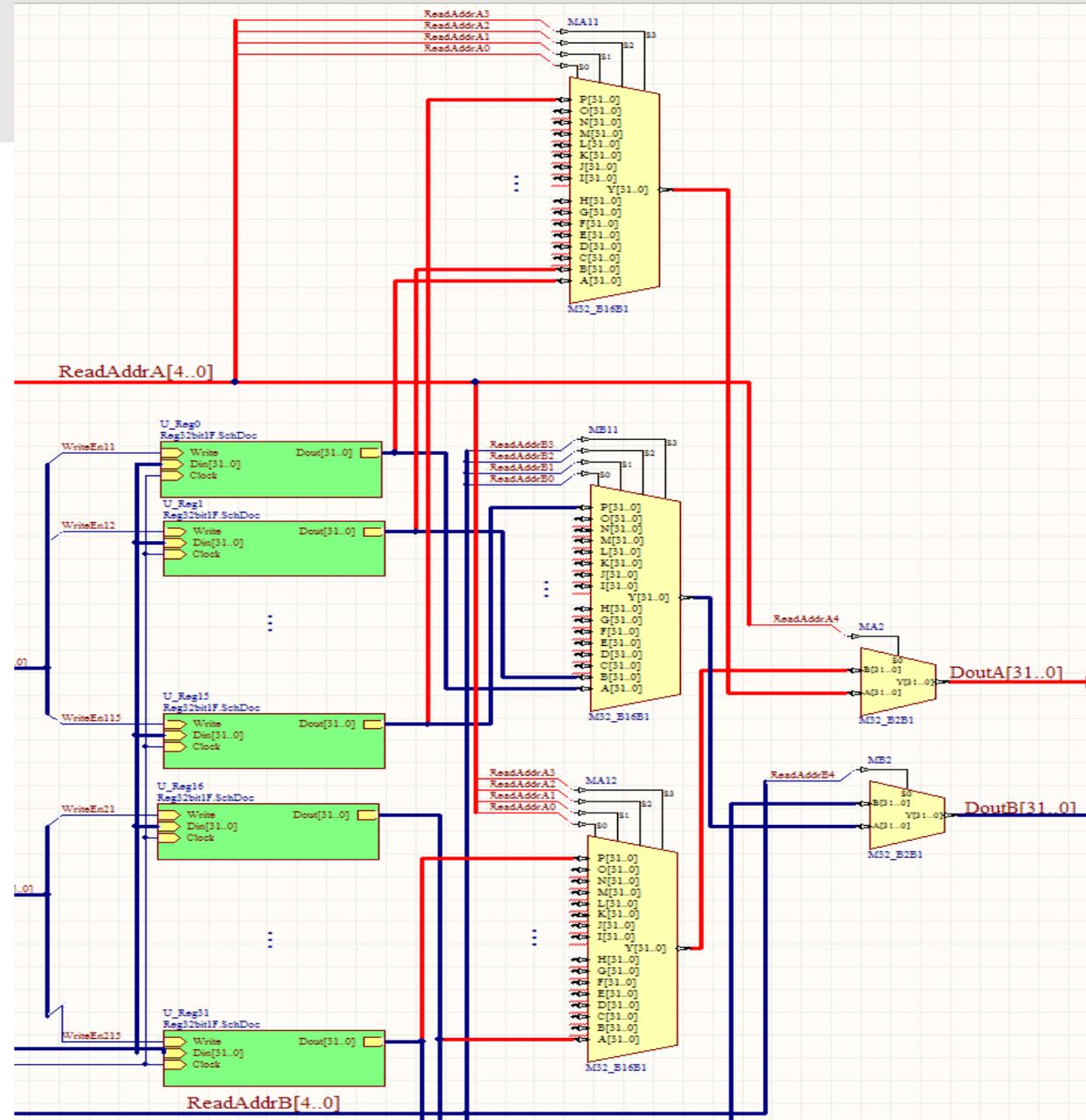
## Read Operation:


- Register number (address) of the register to be read is provided as input
- Content of the read register is the output of the register file
- Multiplexers (2 stages shown) are used in the read operation




# Basic Building Blocks (1)

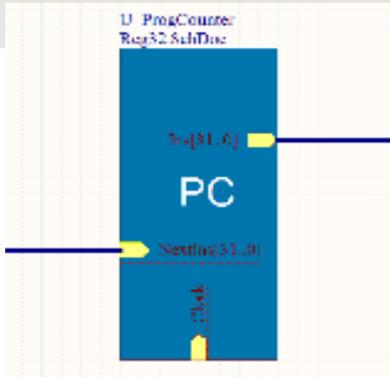

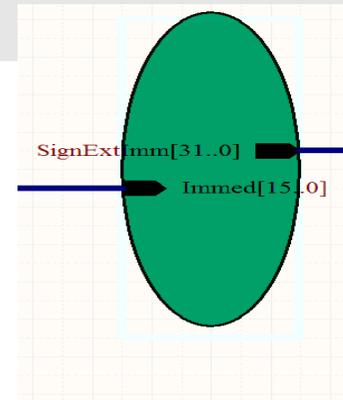
1. Program counter:  
contains address of next instruction



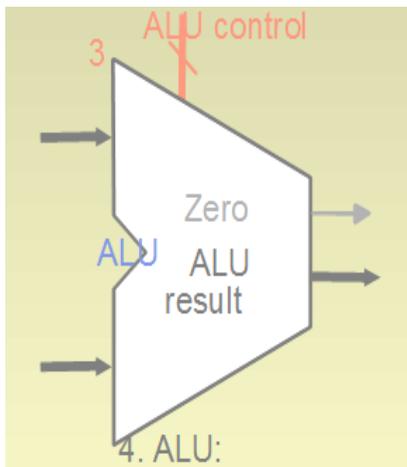2. Sign-extension unit:  
extends a 16-bit integer to a 32-bit integer




3. Adder:  
adds two 32-bit integers

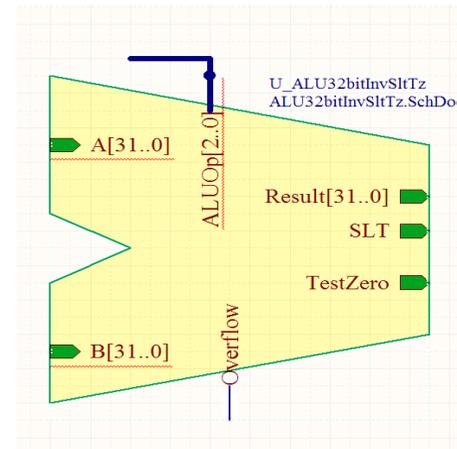


4. ALU:  
add/subtract/and/or/compare two 32-bit integers


# Basic Building Blocks (2)

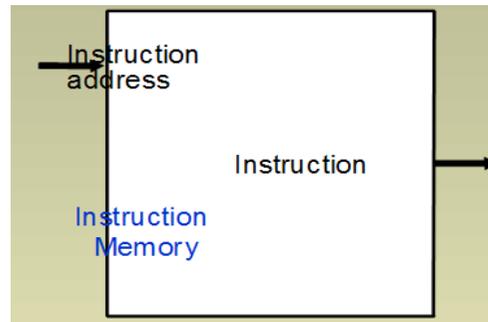

5. Instruction memory

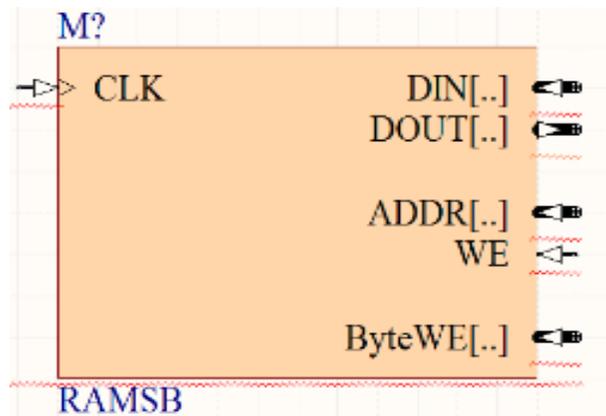


6. Data memory unit

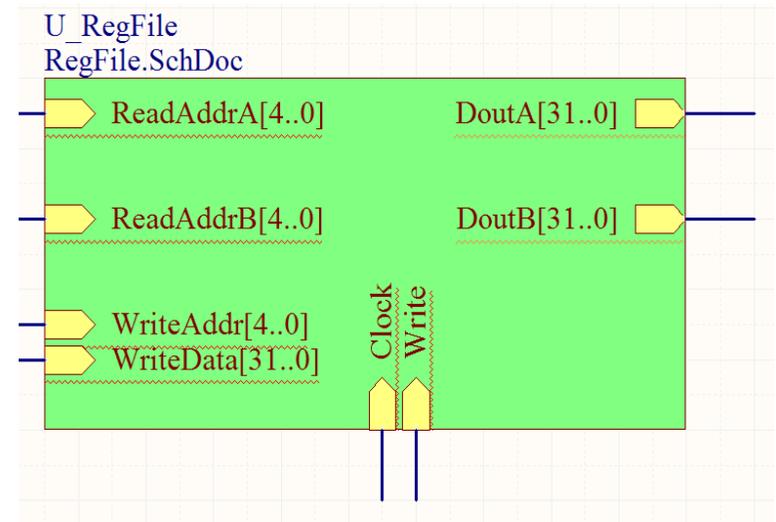

7. Register File

# Datapath: Fetch Instruction

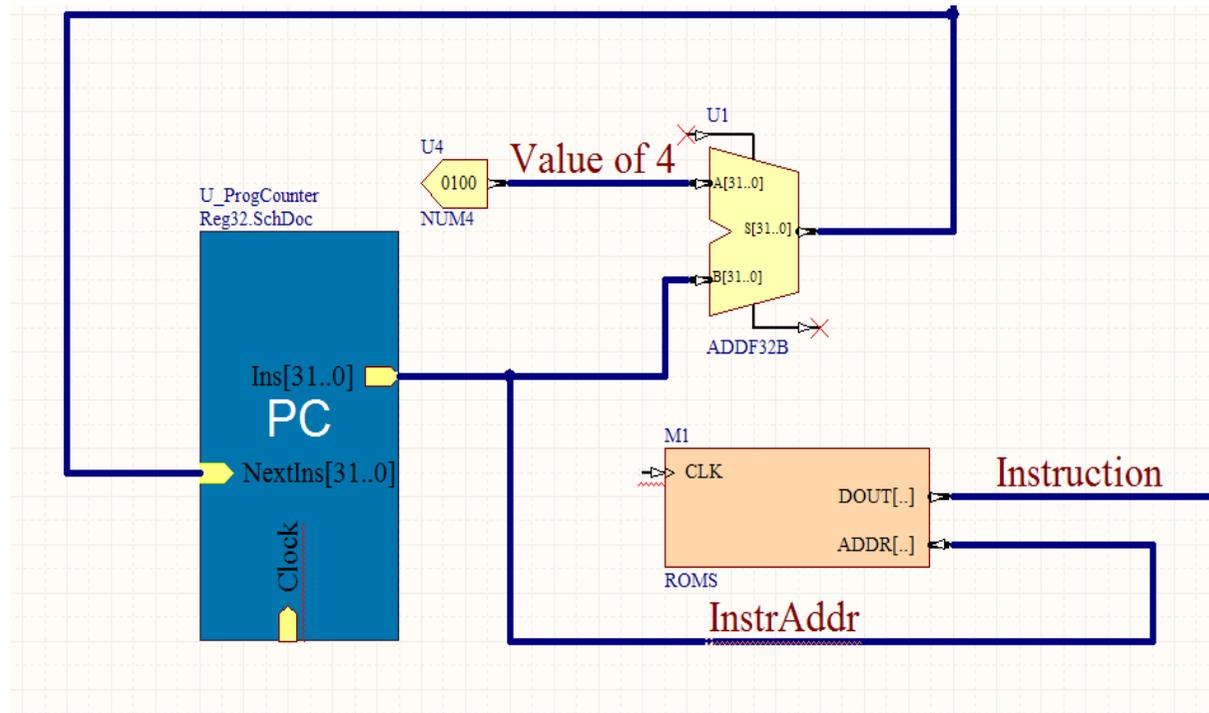1. Provide address from PC to Instruction Memory
2. Increment PC by 1 word (4 bytes)
3. Fetch the instruction




# Datapath: R-type Instructions

R-type instructions include arithmetic and logical instructions (add, sub, or, and, slt)

Example: `add $s1,$s2,$s3`

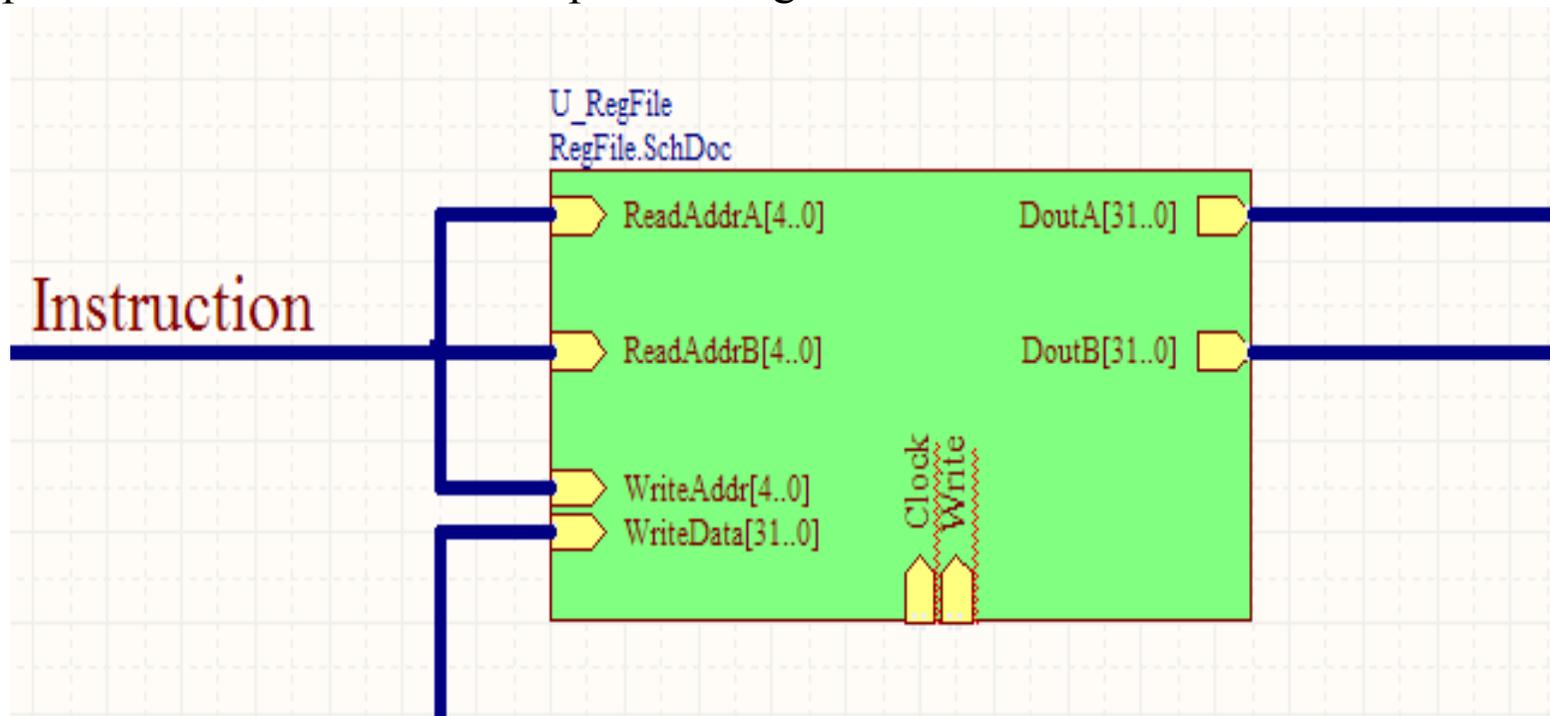1. Read two registers (`$s2`, `$s3`) specified in the instruction
2. ALU performs the required operation (`add`) on the two operands
3. Output of ALU is written to the specified register (`$s1`)




# Datapath: Data transfer Instruction (1)

Store instruction:

`sw $s1, offset($s2)`

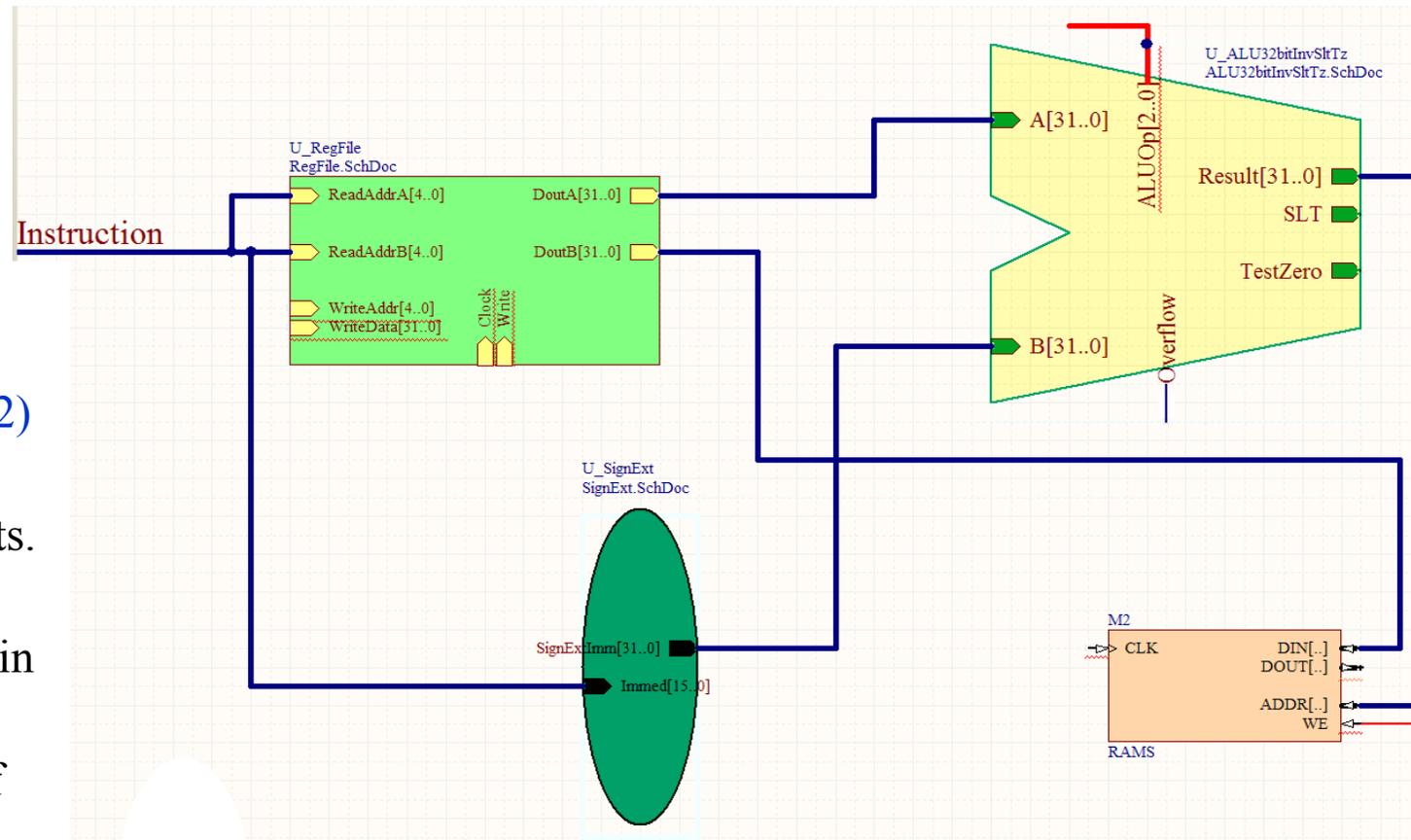
1. Read two registers ( $\$s1, \$s2$ ) specified in the instruction.
2. Offset is extended to 32 bits.
3. ALU adds offset with specified register ( $\$s2$ ) to obtain data memory address.
4. Address along with data of the register ( $\$s1$ ) to be stored passed to data memory.



# Datapath: Data transfer Instruction (2)


Load instruction `lw $s1, offset($s2)`

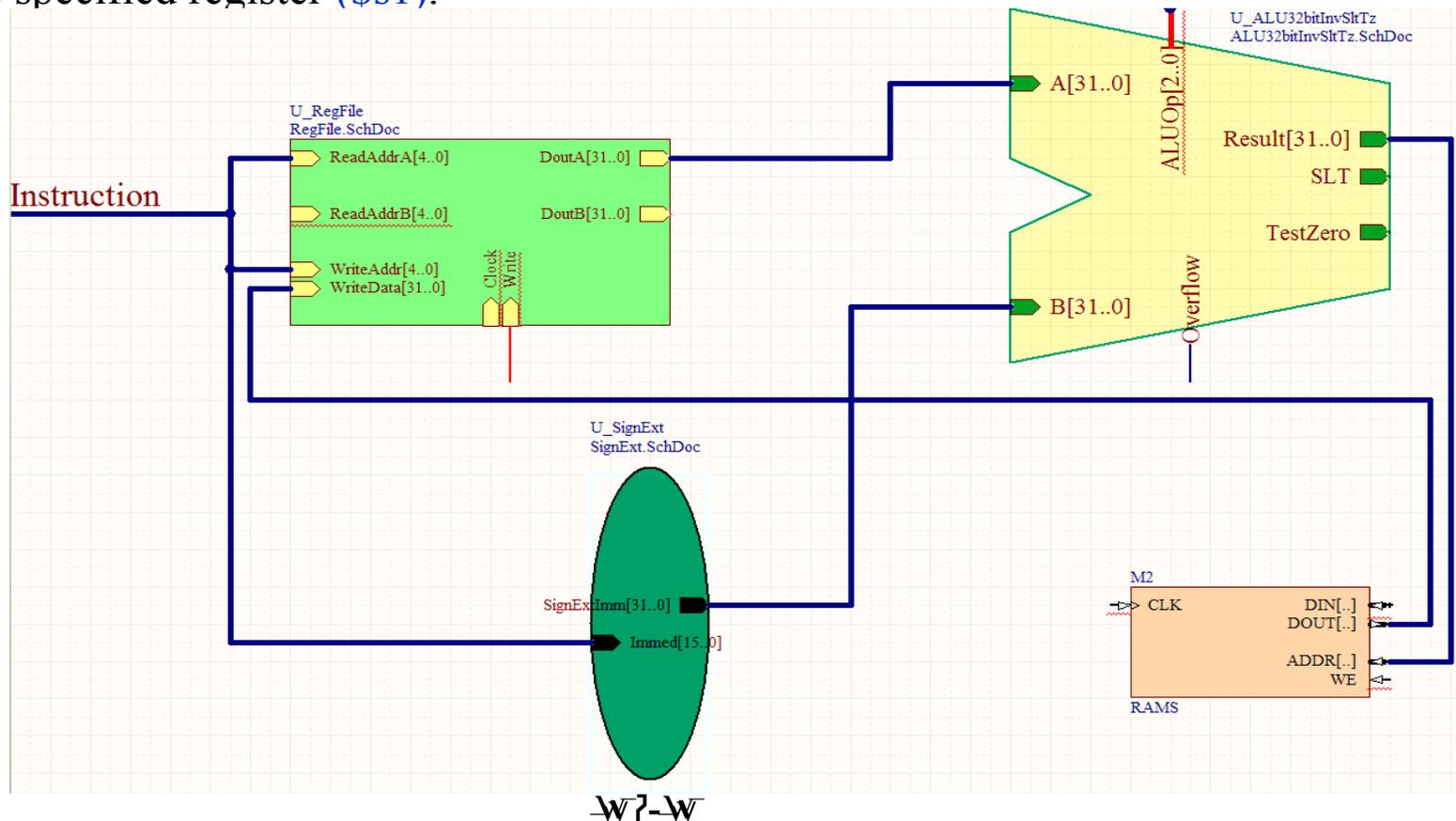1. Read register (`$s2`) specified in the instruction.
2. Offset is extended to 32 bits.
3. ALU adds offset with specified register (`$s2`) to obtain data memory address.
4. Data memory transfers data from provided address to Register file where it is stored in the specified register (`$s1`).



# Datapath: Data transfer Instruction (3)

Load and store instruction combined

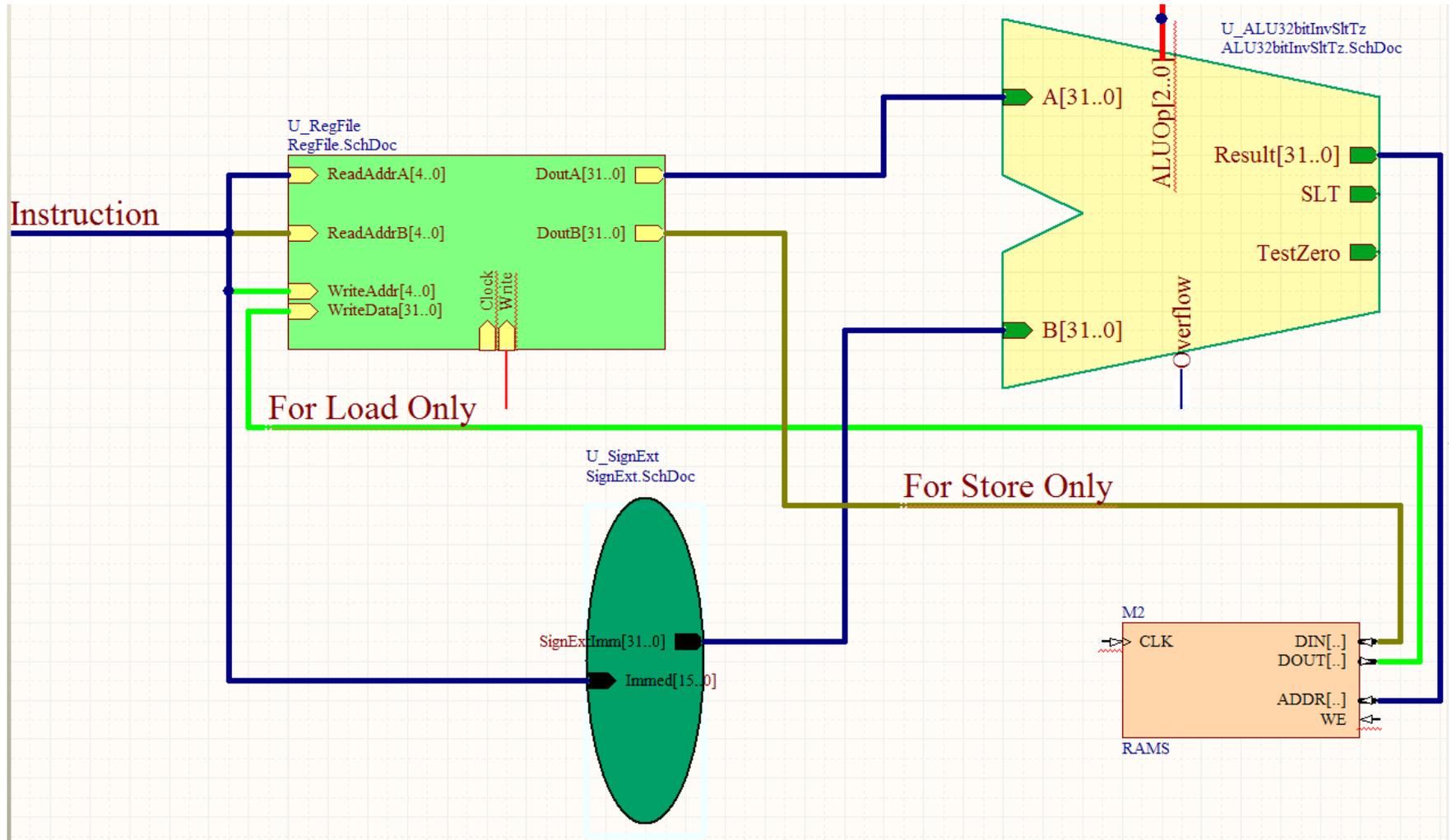

# Datapath: Branch Instructions

Example: `beq $s1,$s2,Loop`

Compiler translation:

`beq $s1,$s2,w_offset`

`#if $s1==$s2, goto (PC+4+4*w_offset)`

1. Read two registers (`$s2,$s3`) specified in the instruction
2. ALU compares content of specified registers (`$s1,$s2`)
3. Adder computes the branch address
4. If equal (zero = 1), branch address is copied to PC

