

ENG2200



Electric Circuits


Chapter 9

Sinusoidal Steady State Analysis

Objectives

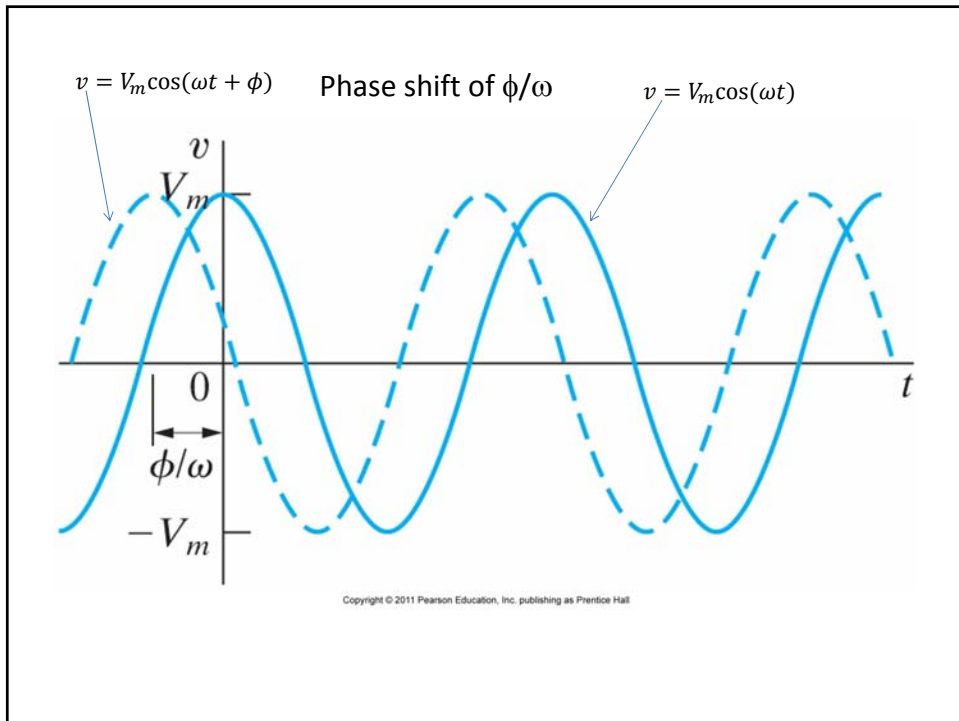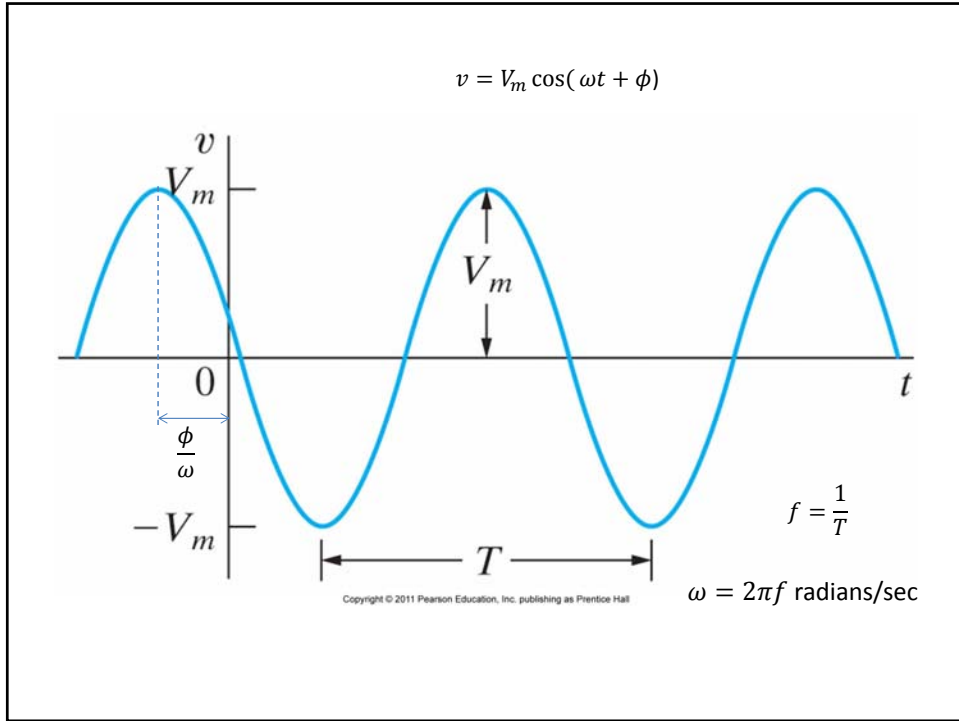- Understanding phasor concept and be able to perform phasor transform and inverse phasor transform.
- Be able to transform a circuit with sinusoidal source into the frequency domain using phasor transform
- Know how to use circuits analysis techniques to solve circuits in the frequency domain.
- Be able to use phasor in analyzing circuits with ideal transformers.



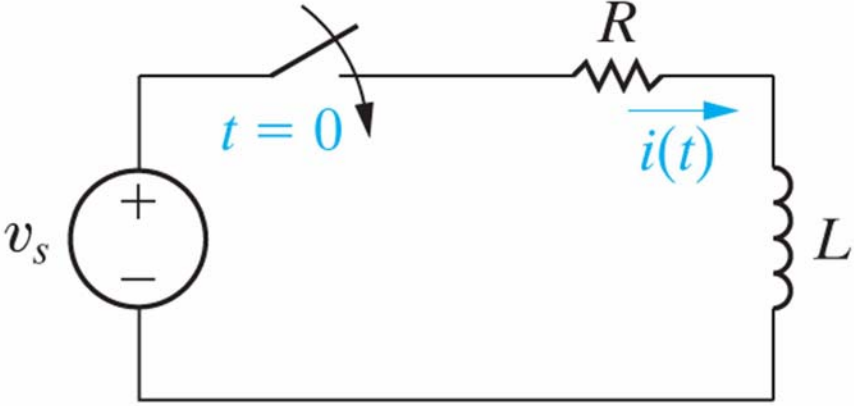

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

$$L \frac{di}{dt} + iR = V_m \cos(\omega t + \phi)$$

$$i = \frac{-V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\phi - \theta) e^{-(R/L)t} + \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta)$$

RMS value

$$V_{rms} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} V_m^2 \cos^2(\omega t + \phi) dt}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

Why RMS?


The Phasor


- The phasor is a complex number that carries the amplitude and phase angle information of a sinusoidal function.
- Euler's identity $e^{\pm j\theta} = \cos \theta \pm j \sin \theta$

$$\cos \theta = \Re\{e^{j\theta}\} \quad v = V_m \cos(\omega t + \phi)$$

$$\sin \theta = \Im\{e^{j\theta}\} \quad v = \Re\{V_m e^{j\phi} e^{j\omega t}\}$$

$$Ae^{j\phi} = A \angle \phi^\circ$$

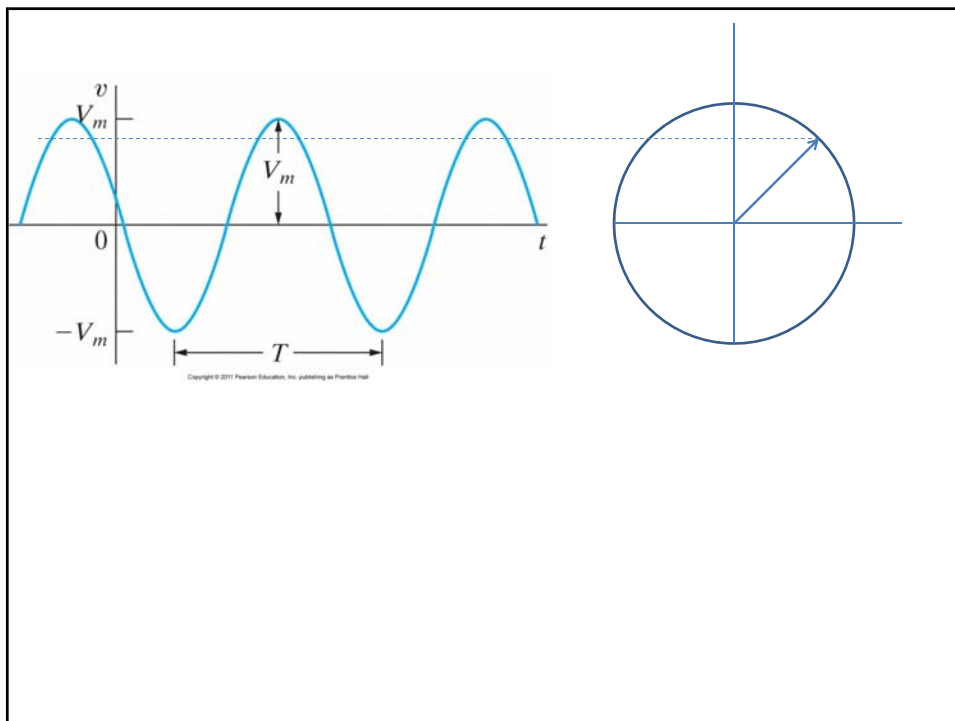

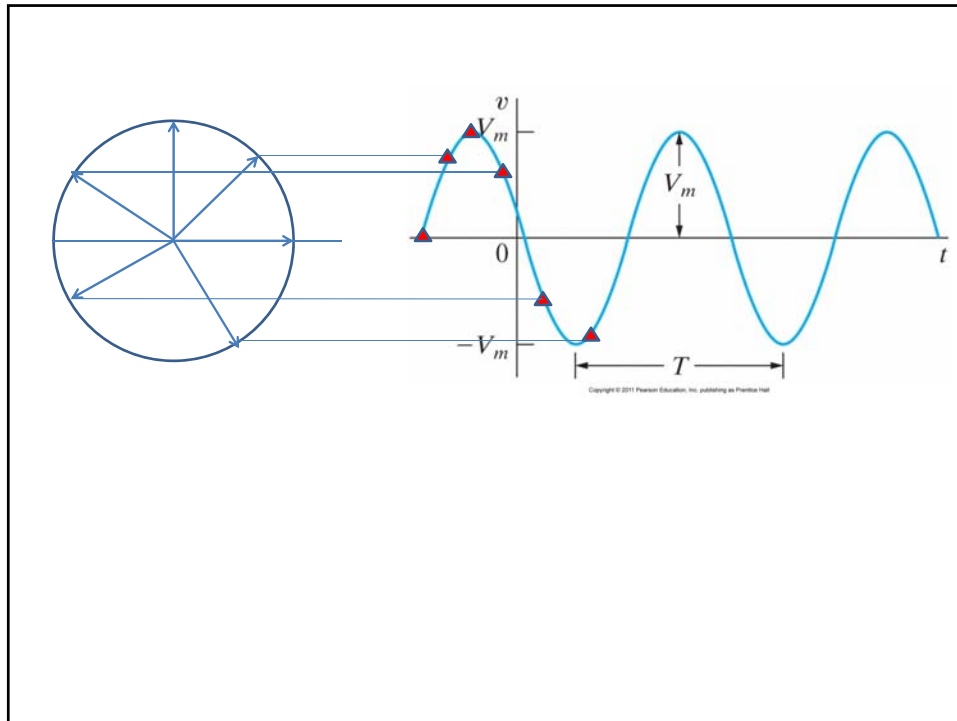

The inductor

$$v = L \frac{di}{dt}$$

$$v = V_m \cos(\omega t)$$

$$di = \frac{1}{L} V_m \cos(\omega t) dt$$


$$i = \frac{1}{L} V_m \int \cos(\omega t) dt$$

$$i = \frac{V_m}{\omega L} \sin(\omega t) = \frac{V_m}{\omega L} \cos(\omega t - \frac{\pi}{2})$$

$$I = \frac{V_m}{\omega L} e^{-j\pi/2} = \frac{V_m}{\omega L} \angle -\pi/2$$

$$Z = \frac{v}{i} = \omega L \angle \pi/2 = \textcircled{j\omega L}$$

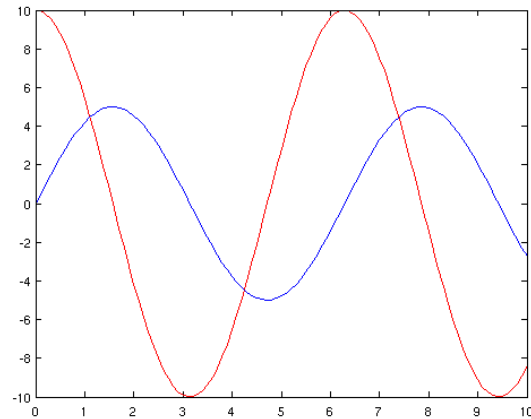A plot showing the phase relationship between the current and voltage at the terminals of an inductor



The Capacitor

$$i = C \frac{dv}{dt}$$

$$v = V_m \cos(\omega t)$$


$$i = CV_m \frac{d}{dt} \cos(\omega t)$$

$$i = -C\omega V_m \sin(\omega t) = \omega CV_m \cos(\omega t + \frac{\pi}{2})$$

$$I = \omega CV_m e^{j\pi/2} = \omega CV_m \angle \pi/2$$


$$Z = \frac{v}{i} = \frac{1}{\omega C} \angle -\pi/2 = \frac{-j}{\omega C} = \frac{1}{j\omega C}$$

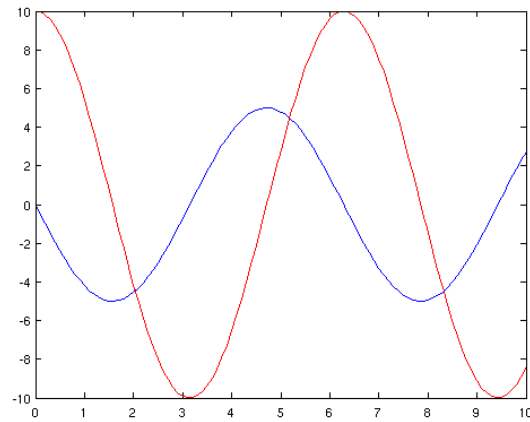A plot showing the phase relationship between the current and voltage at the terminals of a capacitor



Adding Complex Numbers
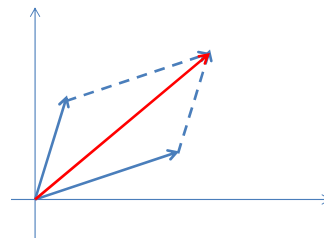
$$\pm \begin{array}{l} x_1 + jy_1 \\ x_2 + jy_2 \\ \hline (x_1 + x_2) \pm j(y_1 + y_2) \end{array}$$



Multiplication

$$\begin{array}{r} \times \quad \begin{array}{c} x_1 + jy_1 \\ x_2 + jy_2 \\ \hline \end{array} \\ (x_1 x_2 - y_1 y_2) + j(x_1 y_2 + x_2 y_1) \end{array}$$

$$A_1 \angle \theta_1 \times A_2 \angle \theta_2 = A_1 A_2 \angle \theta_1 + \theta_2$$

Example


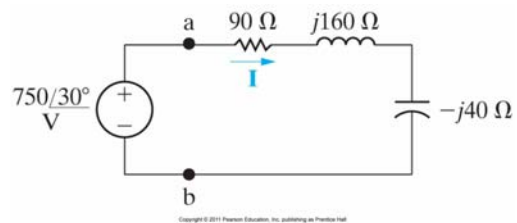
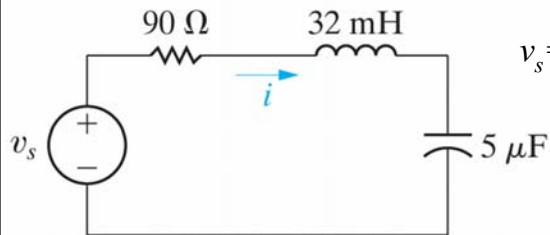


Figure 9.18 The circuit for Example 9.7.

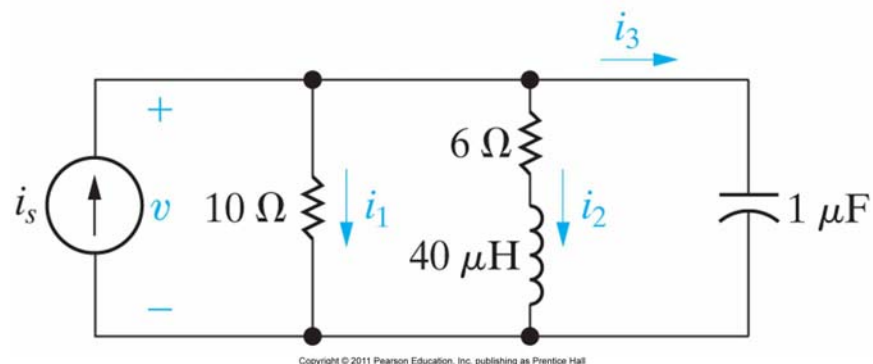

$$i_s = 8 \cos 200,000t$$

Figure 9.19 The frequency-domain equivalent circuit.

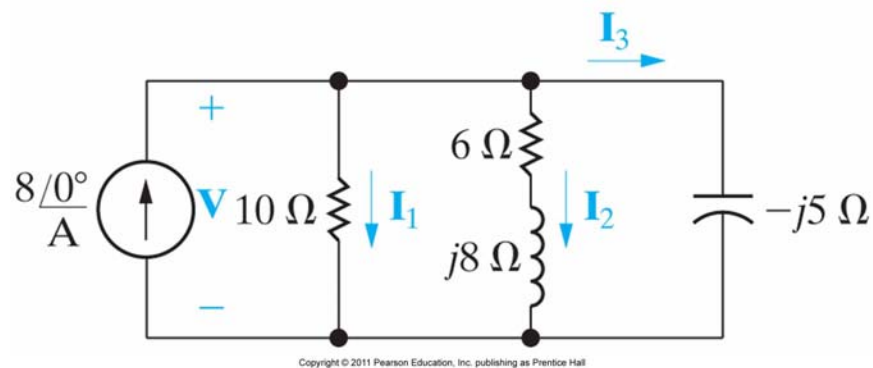


Figure 9.24 A source transformation in the frequency domain.

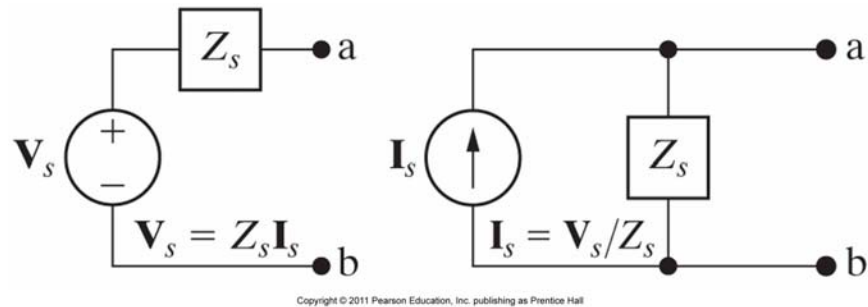


Figure 9.25 The frequency-domain version of a Thévenin equivalent circuit.

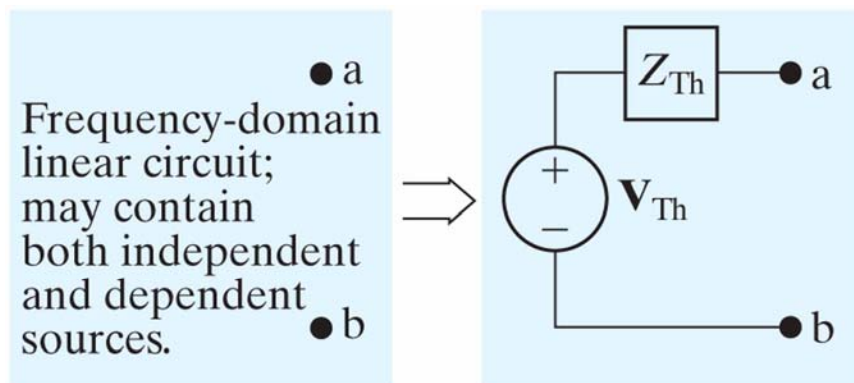


Figure 9.26 The frequency-domain version of a Norton equivalent circuit.

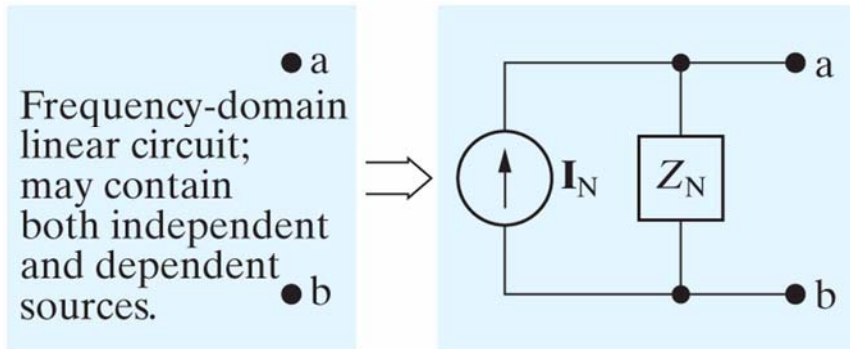


Figure 9.27 The circuit for Example 9.9.

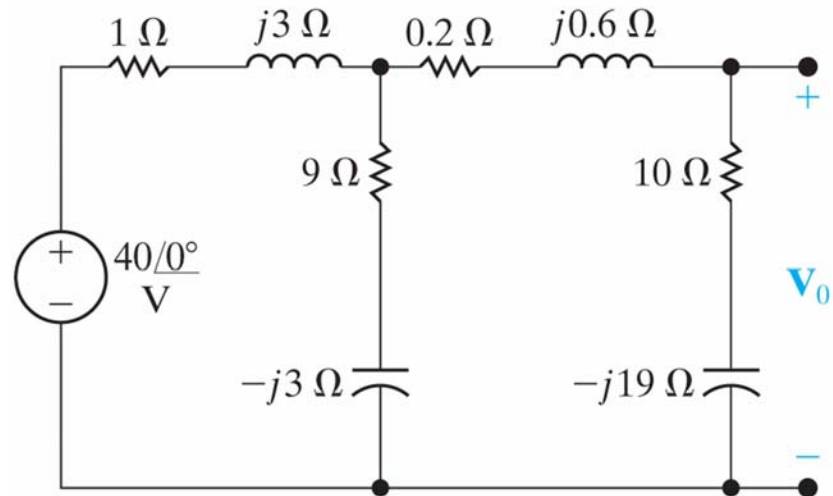


Figure 9.28 The first step in reducing the circuit shown in Fig. 9.27


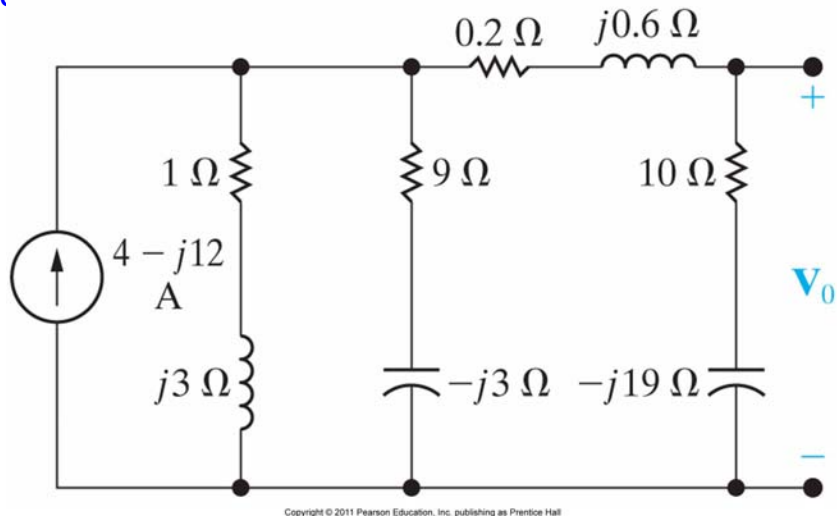


Figure 9.29 The second step in reducing the circuit shown in Fig. 9.27.

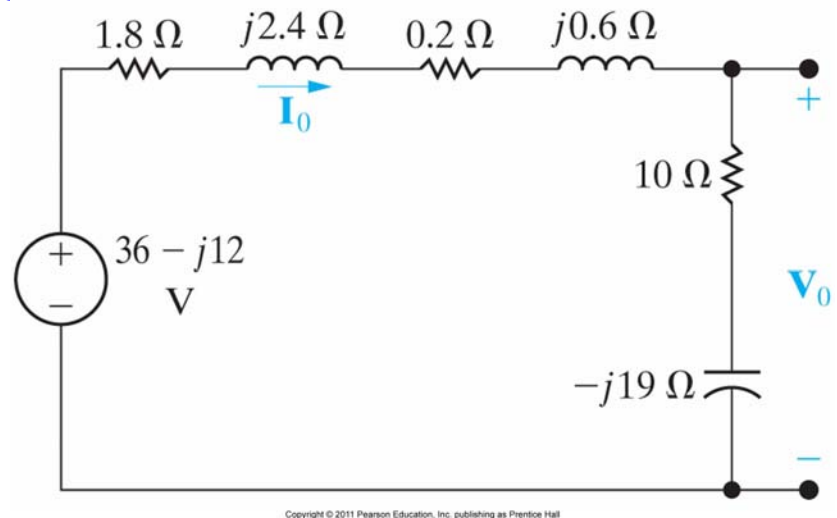

Copyright © 2011 Pearson Education, Inc. publishing as Pearson Hall

$$V_s = I_1(Z_s + R_1 + j\omega L_1) - I_2 j\omega M$$

$$0 = -j\omega M I_1 + I_2(R_2 + j\omega L_2 + Z_L)$$

$$j\omega M I_1 = I_2(R_2 + j\omega L_2 + Z_L)$$

$$I_2 = \frac{j\omega M I_1}{(R_2 + j\omega L_2 + Z_L)}$$

$$Z_{11} = Z_s + R_1 + j\omega L_1$$

$$Z_{22} = Z_L + R_2 + j\omega L_2$$

$$I_1 = \frac{Z_{22}}{Z_{11}Z_{22} + \omega^2 M^2} V_s$$

$$\frac{V_2}{I_1} = Z_{total} = Z_{11} + \frac{\omega^2 M^2}{Z_{22}}$$

Impedance in the primary loop Reflected impedance

Copyright © 2011 Pearson Education, Inc. publishing as Pearson Hall

$$Z_{reflected} = \frac{\omega^2 M^2}{Z_{22}}$$

$$Z_{reflected} = \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L}$$

$$Z_{reflected} = \frac{\omega^2 M^2}{R_2 + j\omega L_2 + R_L + j\omega X_L}$$

$$Z_{reflected} = \frac{\omega^2 M^2}{(R_2 + R_L) + j\omega(L_2 + X_L)}$$

$$Z_{reflected} = \frac{\omega^2 M^2}{|Z_{22}|^2} [(R_2 + R_L) - j\omega(L_2 + X_L)]$$

The complex conjugate of the self impedance of the secondary circuit scaled by a factor