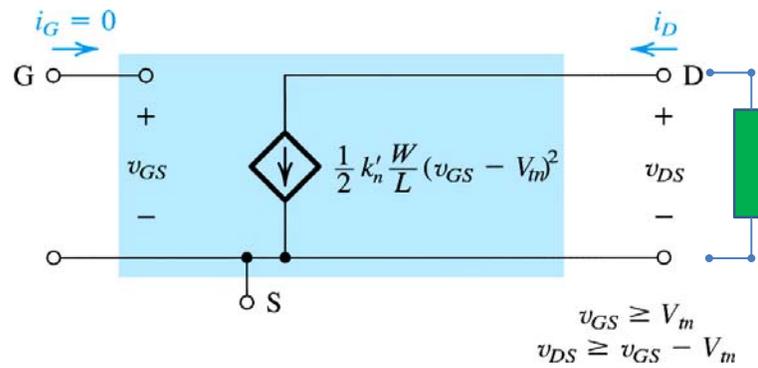


Large Signal Equivalent Circuit




Operating in Saturation

Ideal, back to this point later

Figure 5.15 Large-signal equivalent-circuit model of an *n*-channel MOSFET operating in the saturation

Finite Output Resistance


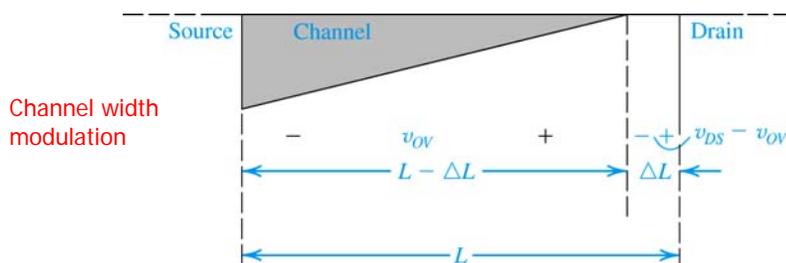


Channel width modulation



- As v_{DS} increases, the channel *pinch off* moves away from the drain (L gets smaller).
- Voltage across the channel remains v_{ov}
- A voltage drop of $v_{DS} - v_{ov}$ appears across the small depletion region
- This voltage accelerates the electrons that reach the drain (increases current)

$$i_D = \frac{1}{2} k'_n \left(\frac{W}{L} \right) V_{ov}^2$$

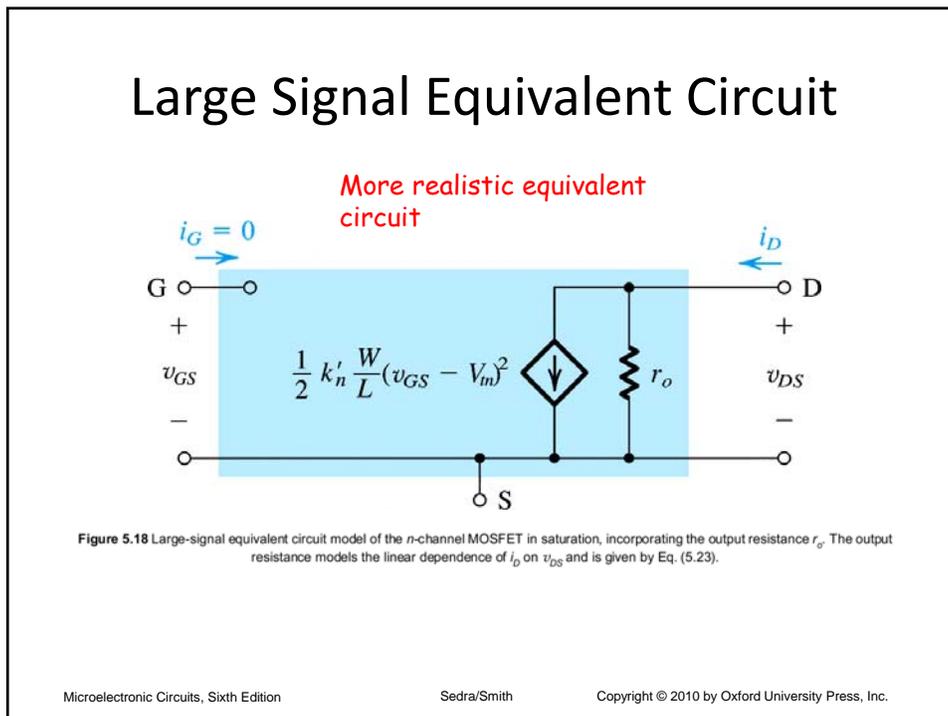
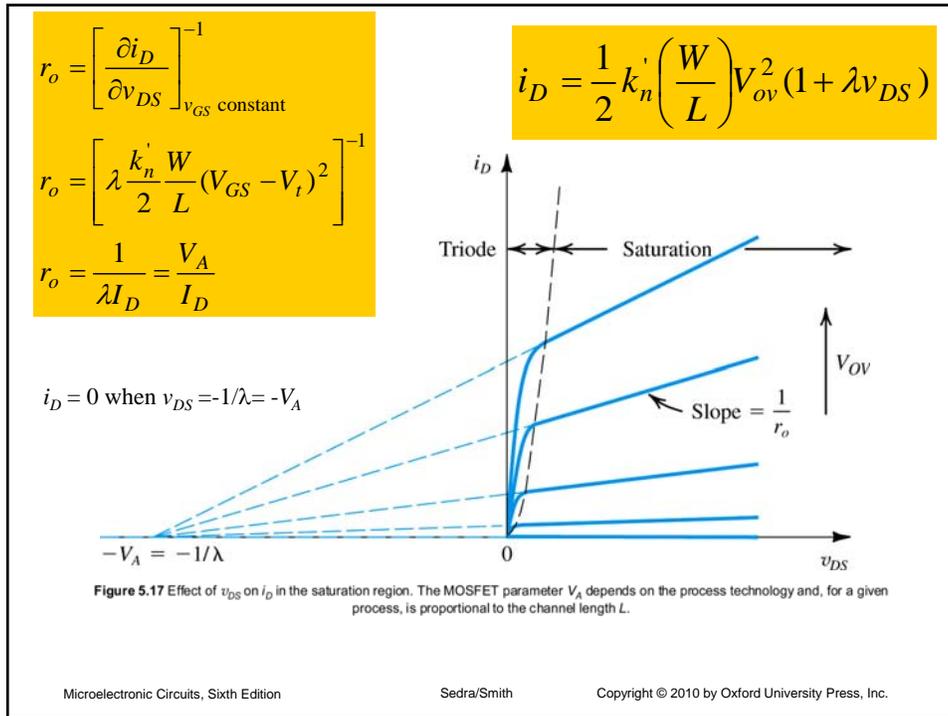
$$i_D = \frac{1}{2} k'_n \left(\frac{W}{L} \right) V_{ov}^2 (1 + \lambda v_{DS})$$







PMOS

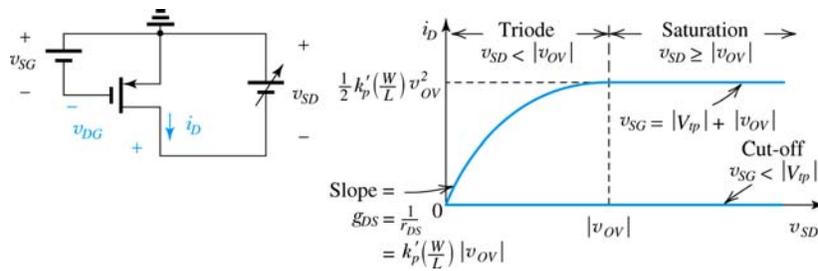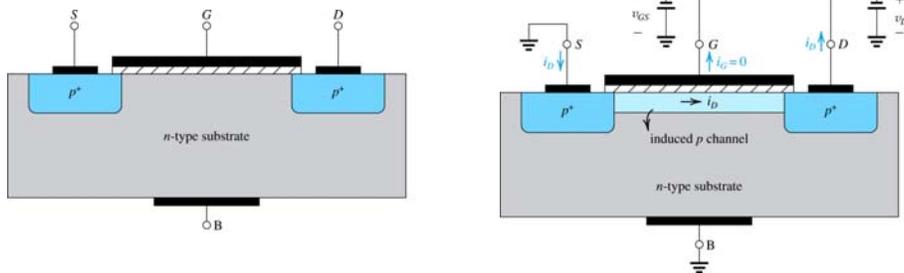

PMOS vs. NMOS

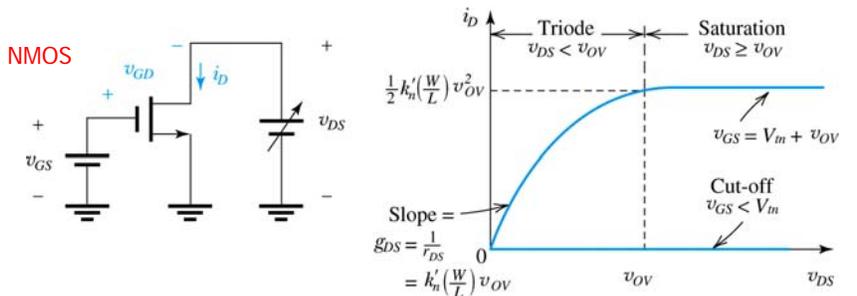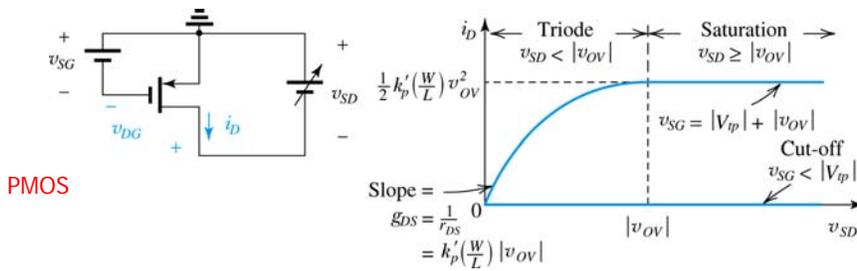

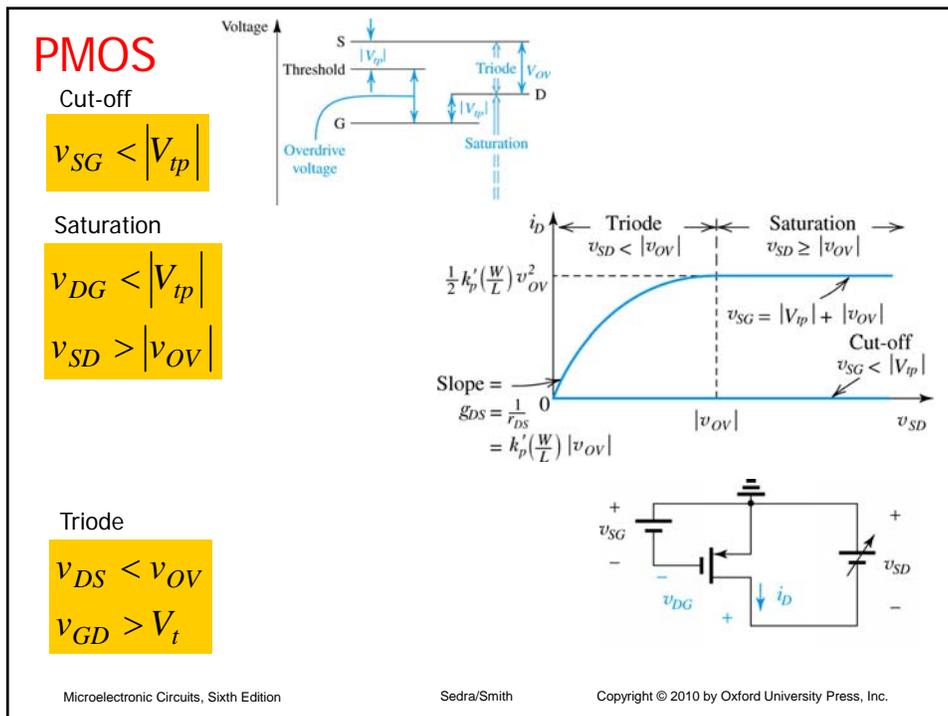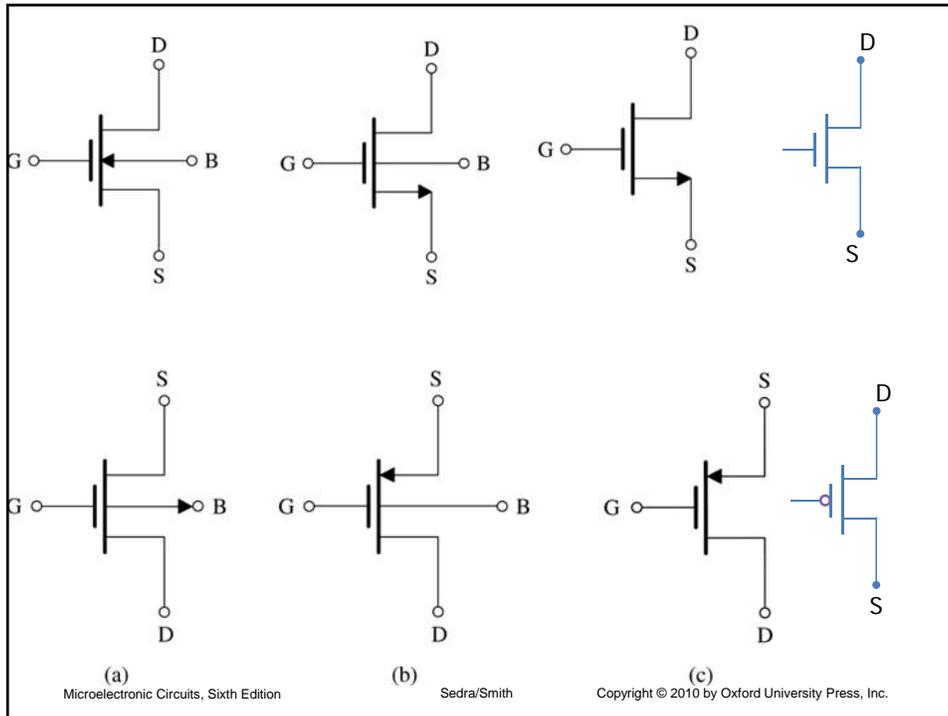

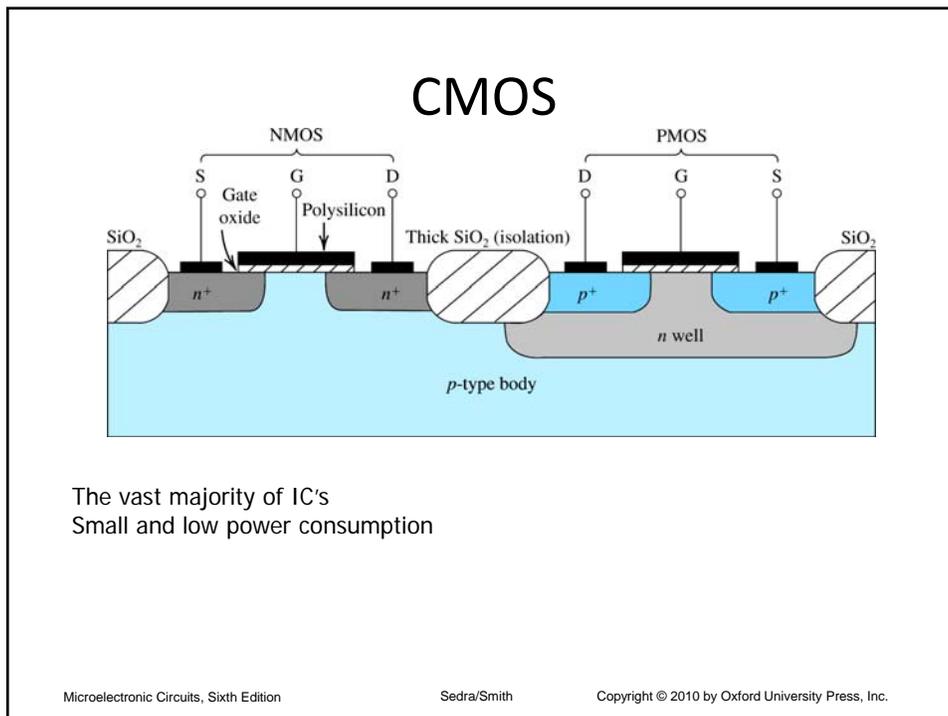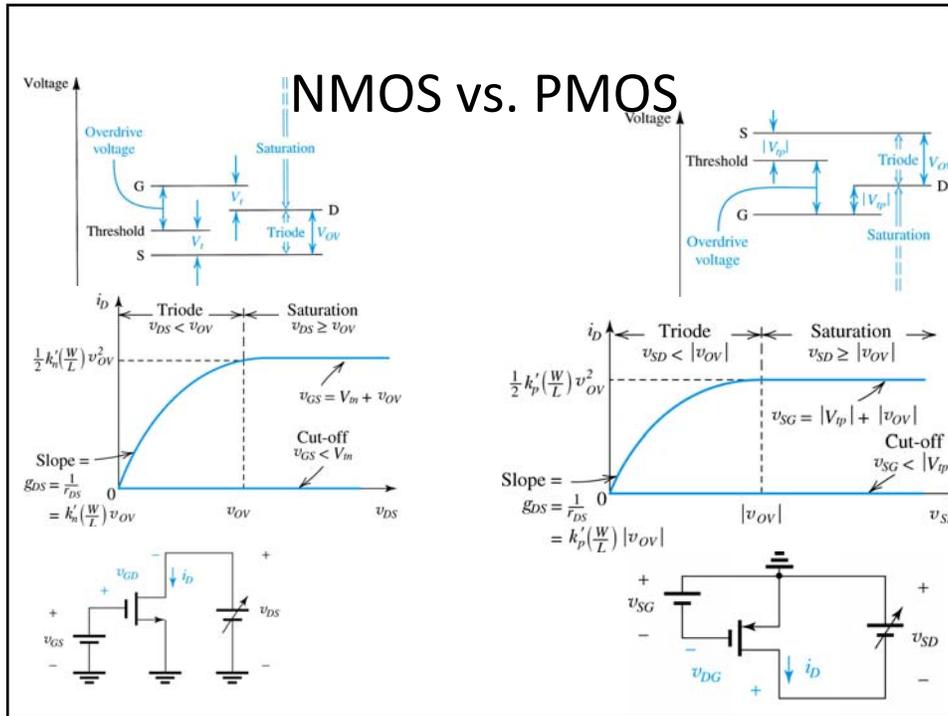

EXAMPLE

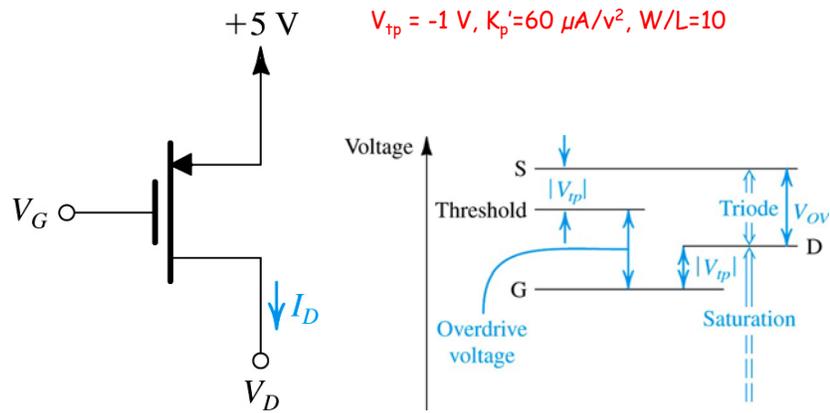


Figure E5.7

Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.

Example

- Find R_s and R_d such that
- $I_d = 0.4\text{ mA}$, $V_D = +0.5\text{ V}$
- $V_t = 0.7\text{ V}$, $\mu_n C_{ox} = 100\ \mu\text{A}/\text{V}^2$
- $L = 1\ \mu\text{m}$, $W = 32\ \mu\text{m}$.

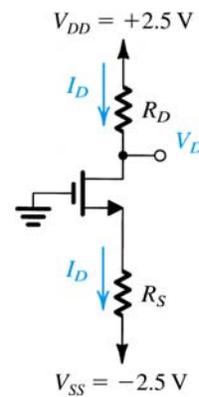


Figure 5.21 Circuit for Example 5.3.

Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.

