

Emitter voltage =  $-0.7$  V, if  $\beta=50$  find  
 $I_E$ ,  $I_B$ ,  $I_C$  and  $V_C$


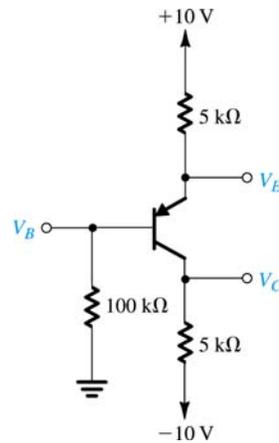


Figure E6.14


## Graphical Representation

Just like regular diodes, the BE voltage determines the collector current

$$i_C = I_s e^{v_{BE}/V_T}$$

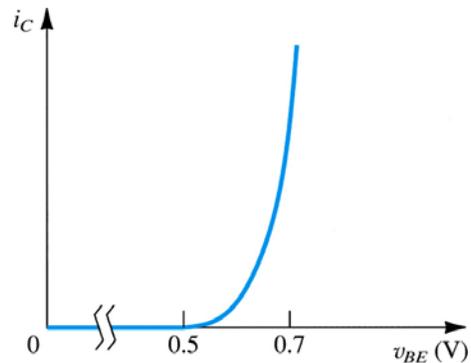

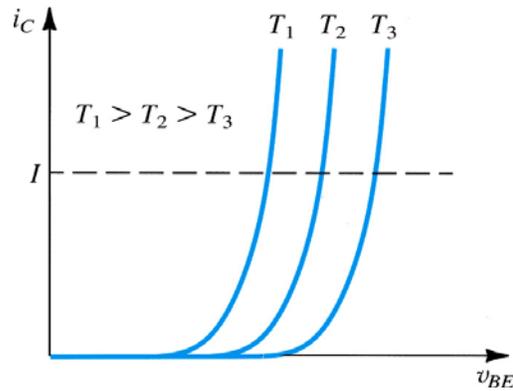At a constant collector current, the BE voltage decrease by  $-2 \text{ mV}/^\circ\text{C}$




### Common Emitter $i_C$ - $V_{CE}$ C/C



Practically, the collector current is not constant as we change CE voltage. This is called the **early Effect**.



$$i_C = I_s e^{v_{BE}/V_T} \left( 1 + \frac{v_{CE}}{V_A} \right)$$

$$r_o = \left[ \frac{\partial i_C}{\partial v_{CE}} \Big|_{v_{BE} \text{ constant}} \right]^{-1}$$
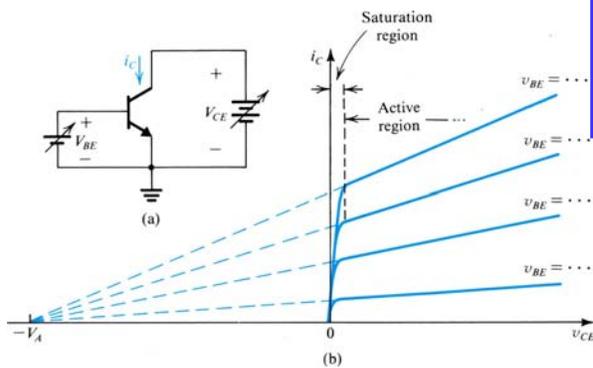
$$r_o = \frac{V_A + V_{CE}}{I_C} \approx \frac{V_A}{I_C}$$



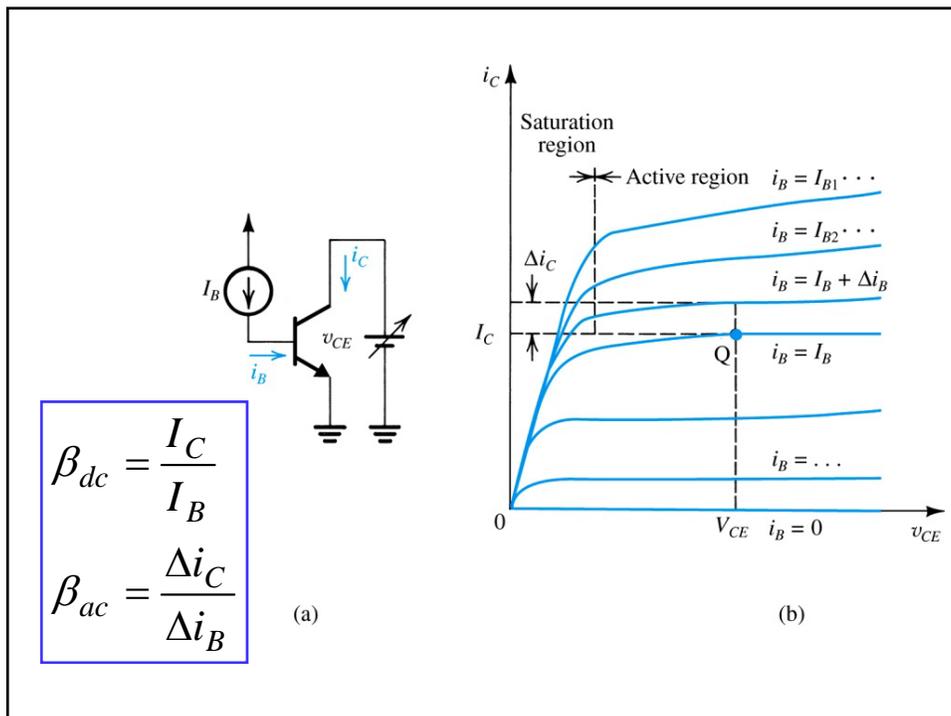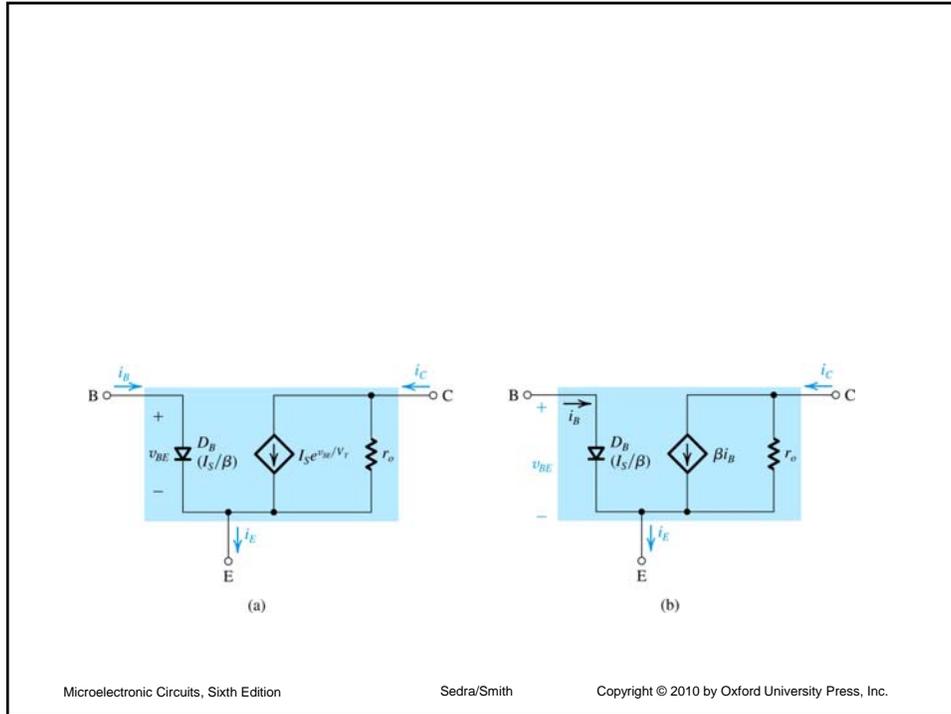

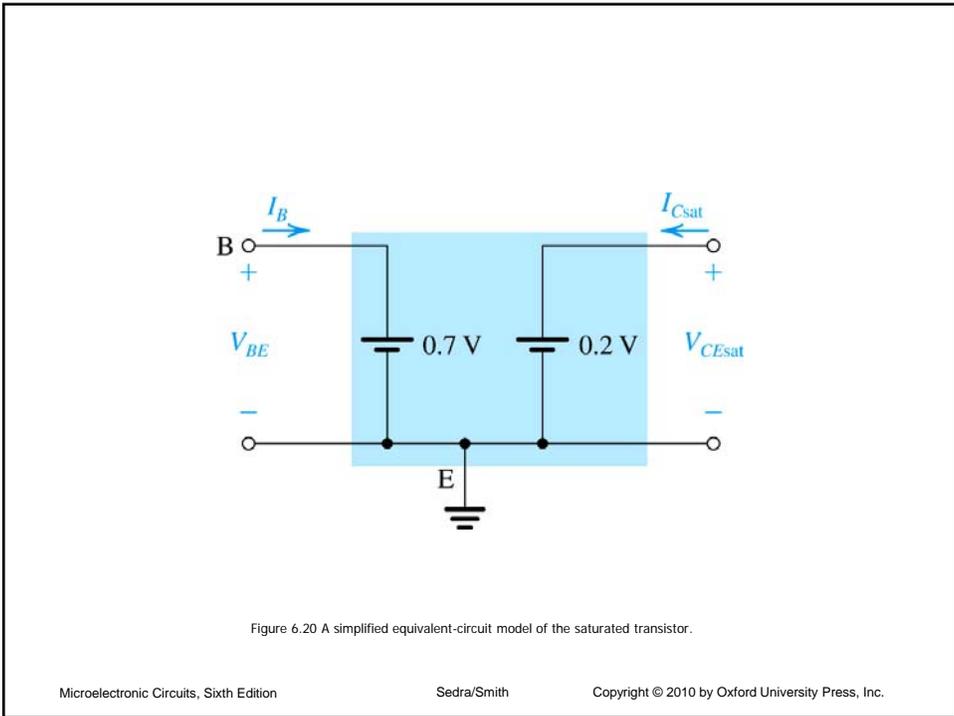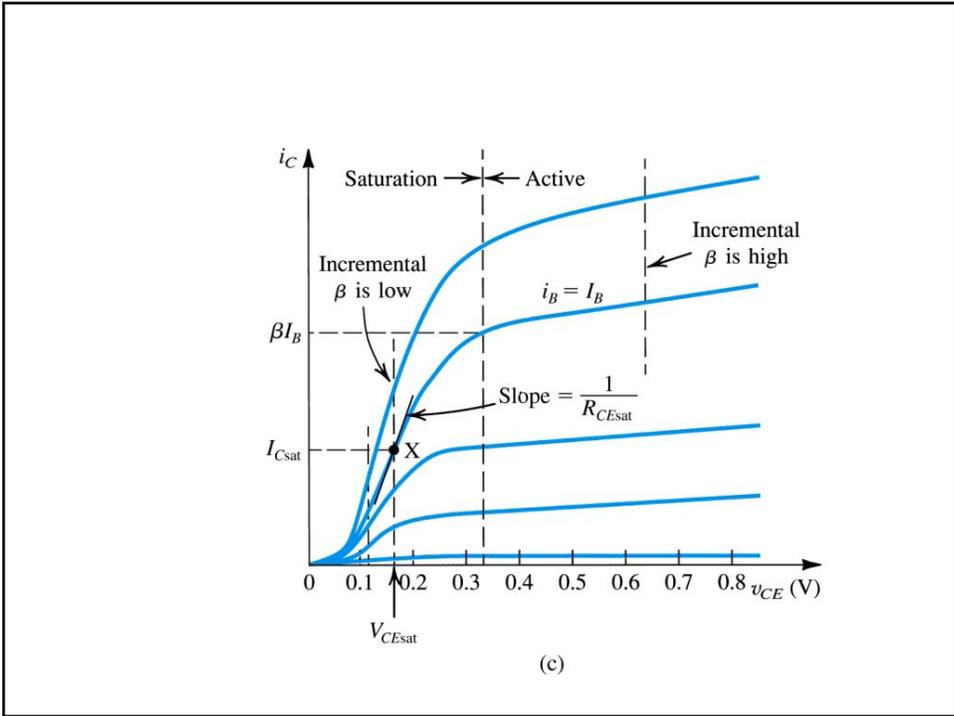

Find  $V_{BB}$ , Assume  $V_{BE}=0.7V$  and  $\beta=50$   
 (a) Active mode with  $V_{CE}=5V$   
 (b) Edge of Saturation  
 (c) Deep in saturation  $\beta=10$

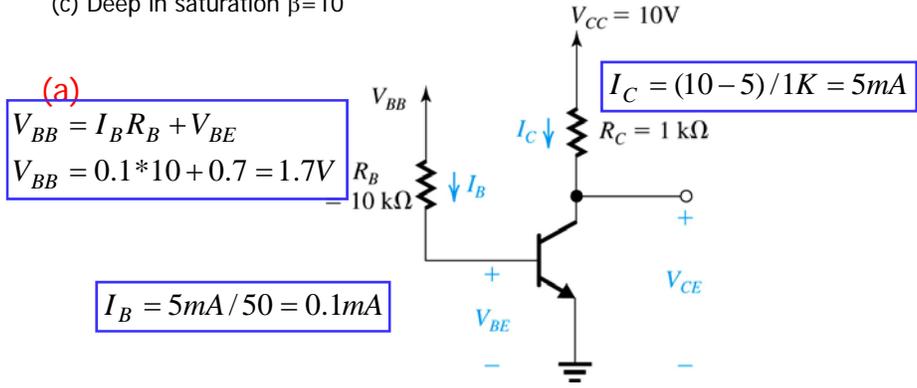


Figure 6.21 Circuit for Example 6.3.

Find  $V_{BB}$ , Assume  $V_{BE}=0.7V$  and  $\beta=50$   
 (a) Active mode with  $V_{CE}=5V$   
 (b) Edge of Saturation  
 (c) Deep in saturation  $\beta=10$

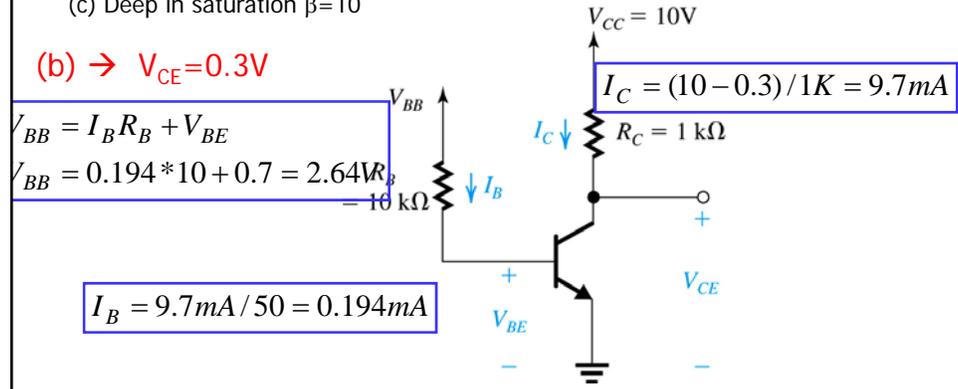


Figure 6.21 Circuit for Example 6.3.

Find  $V_{BB}$ , Assume  $V_{BE}=0.7V$  and  $\beta=50$   
 (a) Active mode with  $V_{CE}=5V$   
 (b) Edge of Saturation  
 (c) Deep in saturation  $\beta=10$

(c)  $\rightarrow V_{CE}=0.2V$

$$V_{BB} = I_B R_B + V_{BE}$$

$$V_{BB} = 0.98 \times 10 + 0.7 = 10.5V$$

$$I_B = 9.8mA / 10 = 0.98mA$$

$V_{CC} = 10V$

$$I_C = (10 - 0.2) / 1K = 9.8mA$$

$R_C = 1k\Omega$

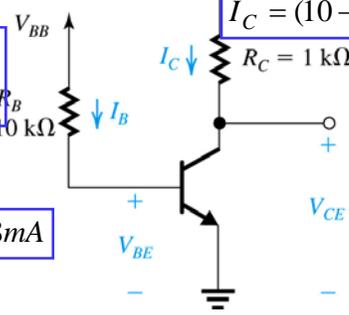


Figure 6.21 Circuit for Example 6.3.

## Cutoff


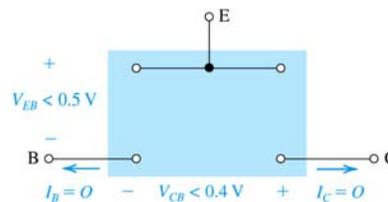
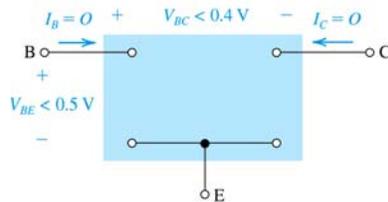
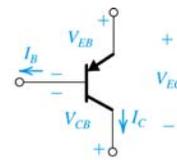
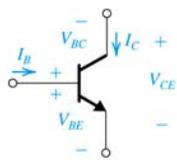


Table 6.3 Conditions and Models for the Operation of the BJT in Various Modes (continued)

Active

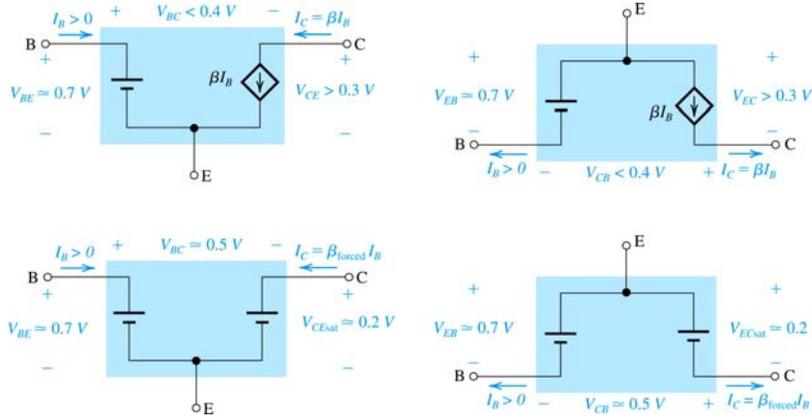

Saturation

Table 6.3 (continued)

Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.


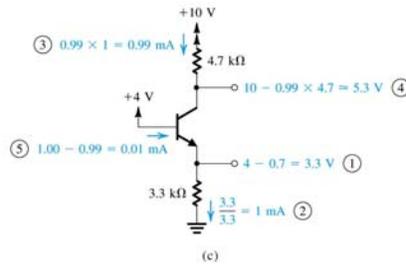
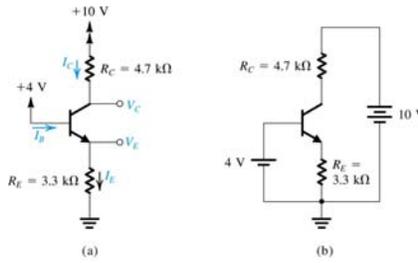


Figure 6.22 Analysis of the circuit for Example 6.4: (a) circuit; (b) circuit redrawn to remind the reader of the convention used in this book to show connections to the power supply; (c) analysis with the steps numbered.

Microelectronic Circuits, Sixth Edition



Sedra/Smith


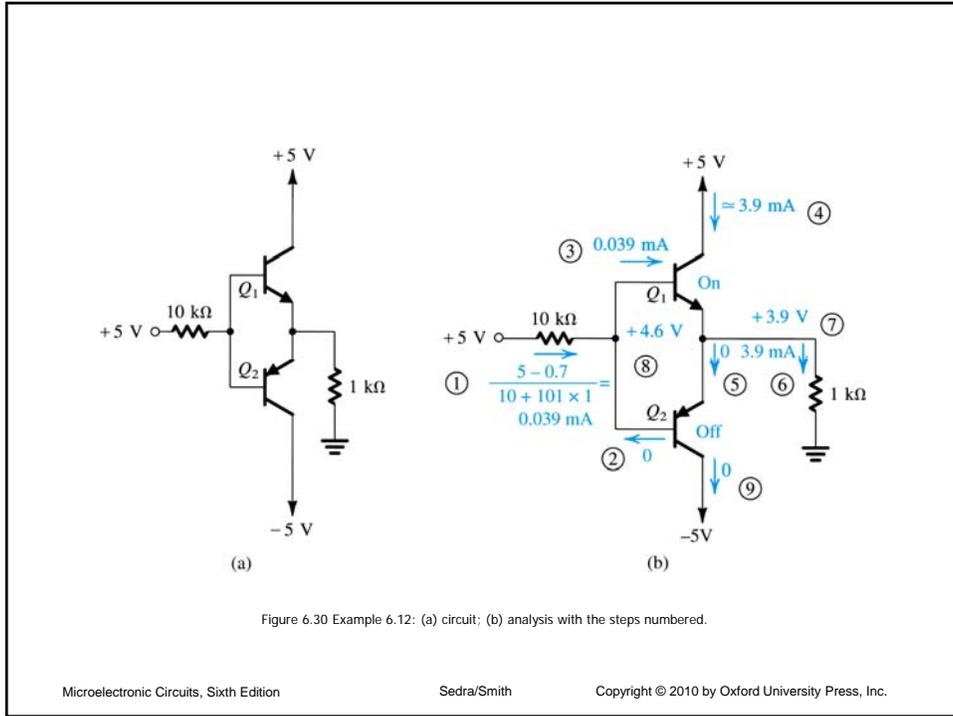
Copyright © 2010 by Oxford University Press, Inc.





## BJT as Amplifiers

$$v_o = V_{CC} - R_C I_s e^{v_i/V_T}$$

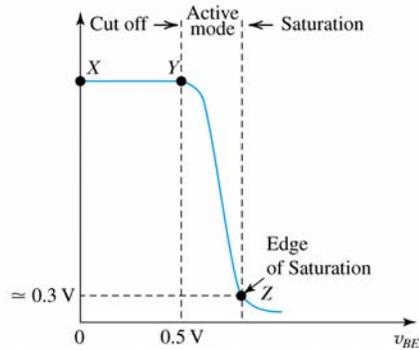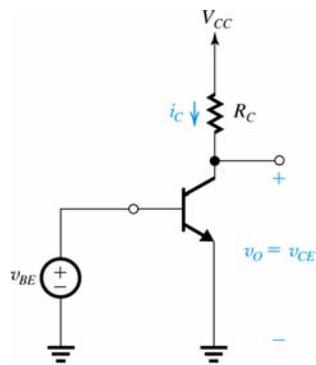

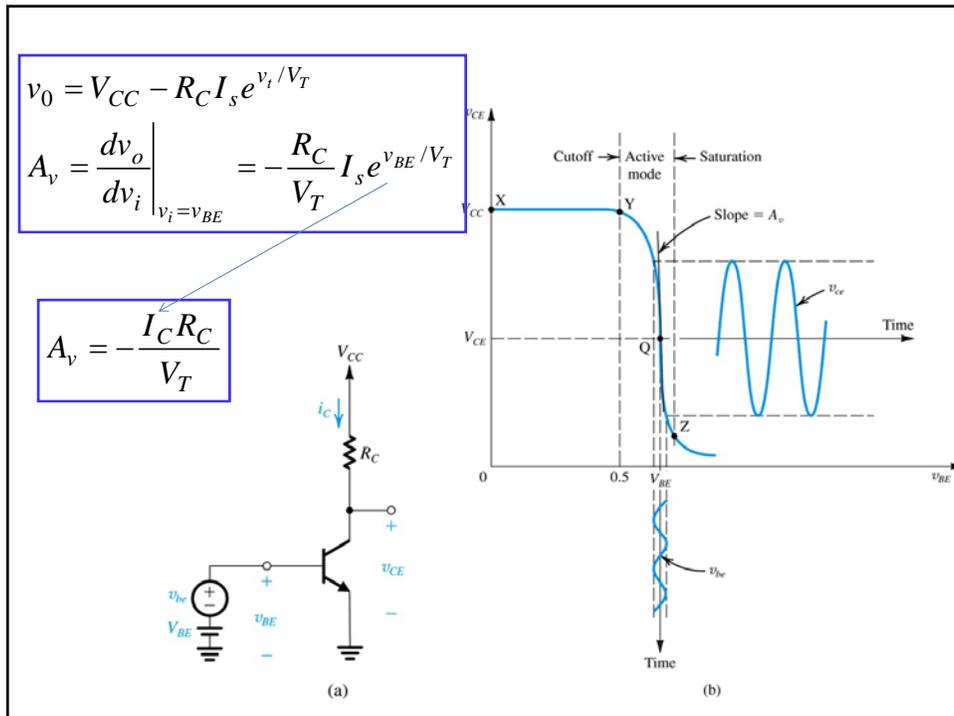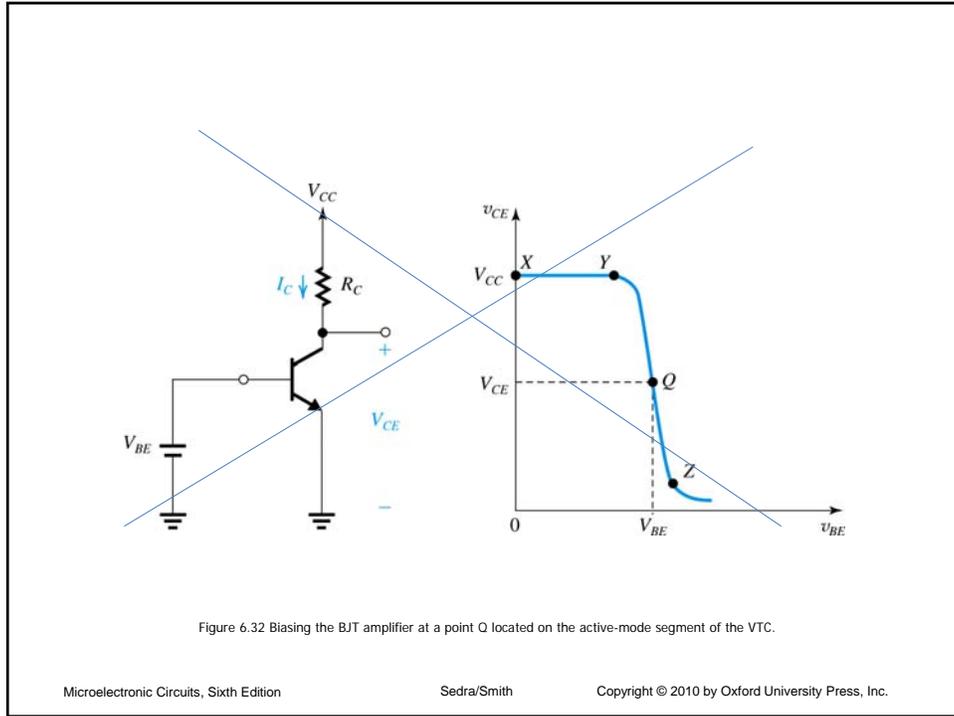

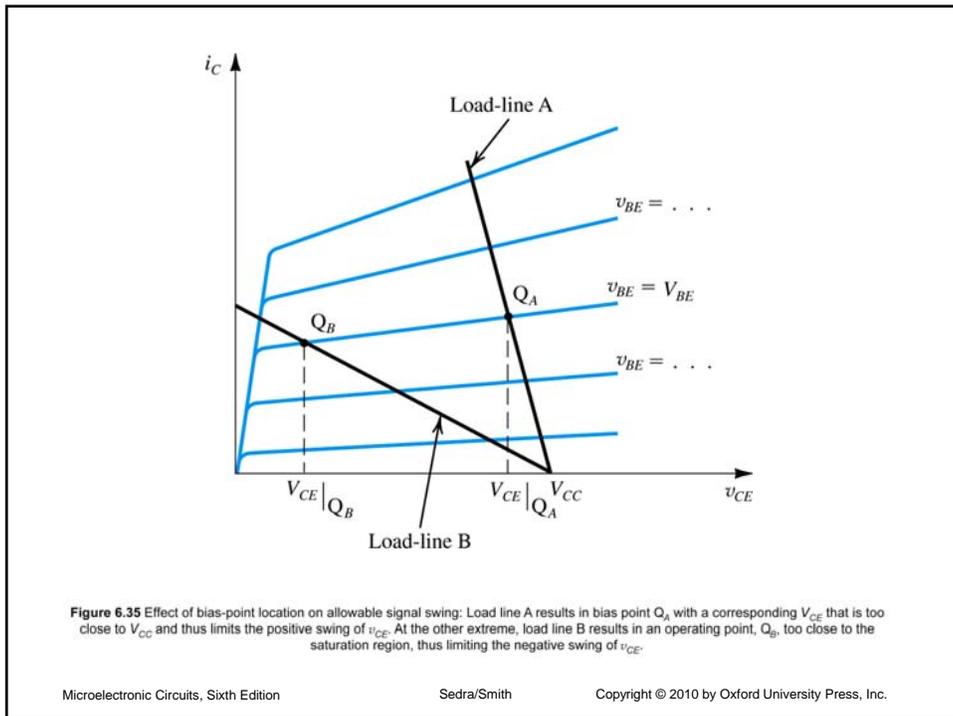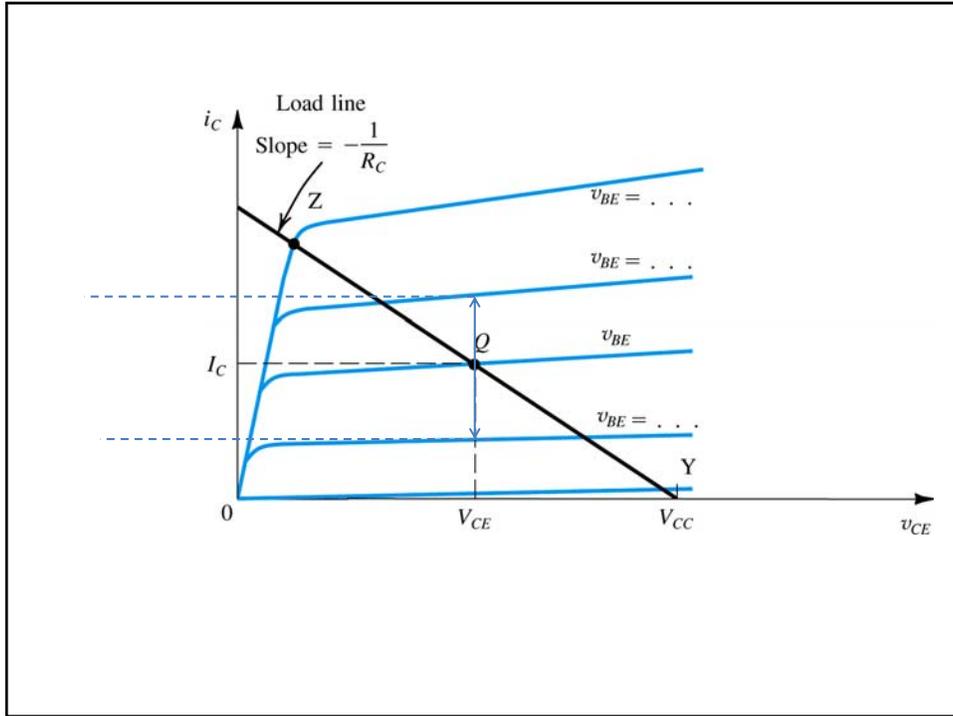

**Figure 6.35** Effect of bias-point location on allowable signal swing: Load line A results in bias point  $Q_A$  with a corresponding  $V_{CE}$  that is too close to  $V_{CC}$  and thus limits the positive swing of  $v_{CE}$ . At the other extreme, load line B results in an operating point,  $Q_B$ , too close to the saturation region, thus limiting the negative swing of  $v_{CE}$ .