

## CSE 2021 Computer Organization

### Appendix C

#### The Basics of Logic Design

## Outline

- Fundamental Boolean operations
- Deriving logic expressions from truth tables
- Boolean Identities
- Simplifying logic expressions using Boolean identities
- Combinational and sequential circuits
- Verilog basics




2

## Boolean Algebra

- Boolean algebra is the basic math used in digital circuits and computers.
- A Boolean variable takes on only 2 values: {0,1} , {T,F}, {Yes, No}, etc.
- There are 3 fundamental Boolean operations:
  - AND, OR, NOT

3

## Fundamental Boolean Operations

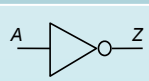AND	OR	NOT																																				
																																						
$Z=A*B \text{ (AB)}$	$Z=A+B$	$Z=\bar{A}$																																				
Truth Table	Truth Table	Truth Table																																				
<table><tr><th>A</th><th>B</th><th>Z</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	Z	0	0	0	0	1	0	1	0	0	1	1	1	<table><tr><th>A</th><th>B</th><th>Z</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	Z	0	0	0	0	1	1	1	0	1	1	1	1	<table><tr><th>A</th><th>Z</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	A	Z	0	1	1	0
A	B	Z																																				
0	0	0																																				
0	1	0																																				
1	0	0																																				
1	1	1																																				
A	B	Z																																				
0	0	0																																				
0	1	1																																				
1	0	1																																				
1	1	1																																				
A	Z																																					
0	1																																					
1	0																																					

4

## Boolean Algebra


- A *truth table* specifies output signal logic values for every possible combination of input signal logic values
- In evaluating Boolean expressions, the *Operation Hierarchy* is: 1) NOT 2) AND 3) OR. Order can be superseded using ( ... )
- Example:*  $A = T, B = F, C = T, D = T$
- What is the value of  $Z = (\bar{A} + B) \cdot (C + \bar{B} \cdot D)$ ?

$$\begin{aligned} Z &= (\bar{T} + F) \cdot (C + \bar{B} \cdot D) = (F + F) \cdot (C + \bar{B} \cdot D) \\ &= F \cdot (C + \bar{B} \cdot D) = F \end{aligned}$$

5
 
## Deriving Logic Expressions From Truth Tables

Light must be ON when both switches A and B are OFF, or when both of them are ON.



Truth Table:

A	B	Z
0	0	1
0	1	0
1	0	0
1	1	1

- What is the Boolean expression for Z?

6

## Minterms and Maxterms

- Minterms
  - AND term of all input variables.
  - For variables with value 0, apply complements
- Maxterms
  - OR factor with all input variables
  - For variables with value 1, apply complements

A	B	Z	Minterms	Maxterms
0	0	1	$\bar{A} \cdot \bar{B}$	$A + B$
0	1	0	$\bar{A} \cdot B$	$A + \bar{B}$
1	0	0	$A \cdot \bar{B}$	$\bar{A} + B$
1	1	1	$A \cdot B$	$\bar{A} + \bar{B}$

7

## Minterms and Maxterms

- A function with  $n$  variables has  $2^n$  minterms (and Maxterms) – exactly equal to the number of rows in truth table
- Each minterm is true for exactly one combination of inputs
- Each Maxterm is false for exactly one combination of inputs

A	B	Z	Minterms	Maxterms
0	0	1	$\bar{A} \cdot \bar{B}$	$A + B$
0	1	0	$\bar{A} \cdot B$	$A + \bar{B}$
1	0	0	$A \cdot \bar{B}$	$\bar{A} + B$
1	1	1	$A \cdot B$	$\bar{A} + \bar{B}$

8

## Equivalent Logic Expressions

- Two equivalent logic expressions can be derived from Truth Tables:

### 1. Sum-of-Products (SOP) expressions:

- Several AND terms OR'd together, e.g.

$$\overline{A}BC + \overline{A}B\overline{C} + ABC$$

### 2. Product-of-Sum (POS) expressions:

- Several OR terms AND'd together, e.g.

$$(\overline{A} + \overline{B} + C)(A + B + \overline{C})$$

9

## Rules for Deriving SOP Expressions

- Find each row in TT for which output is 1 (rows 1 & 4)
- For those rows write a **minterm** of all input variables.
- OR together all **minterms** found in (2):  
Such an expression is called a *Canonical SOP*

A	B	Z	Minterms	Maxterms
0	0	1	$\overline{A}.\overline{B}$	$A+B$
0	1	0	$\overline{A}.B$	$A+\overline{B}$
1	0	0	$A.\overline{B}$	$\overline{A}+B$
1	1	1	$AB$	$\overline{A}+\overline{B}$

$$Z = \overline{A}\overline{B} + AB$$

10

## Rules for Deriving POS Expressions

- Find each row in TT for which output is 0 (rows 2 & 3)
- For those rows write a **maxterm**
- AND together all **maxterm** found in (2):  
Such an expression is called a *Canonical POS*.

A	B	Z	Minterms	Maxterms
0	0	1	$\overline{A}.\overline{B}$	$A+B$
0	1	0	$\overline{A}.B$	$A+\overline{B}$
1	0	0	$A.\overline{B}$	$\overline{A}+B$
1	1	1	$AB$	$\overline{A}+\overline{B}$

$$Z = (A + \overline{B})(\overline{A} + B)$$

11

## CSOP and CPOS

- Canonical SOP:  $Z = \overline{A}\overline{B} + AB$
- Canonical POS:  $Z = (A + \overline{B})(\overline{A} + B)$
- Since they represent the same truth table, they should be identical

Verify that

$$Z = \overline{A}\overline{B} + AB \equiv (A + \overline{B})(\overline{A} + B)$$

- CPOS and CSOP expressions for the same TT are logically equivalent. Both represent the same information.*

12

## Activity 1

Derive SOP and POS expressions for the following TT.

A	B	Carry
0	0	0
0	1	0
1	0	0
1	1	1

13

## Boolean Identities

## Boolean Identities

- Useful for simplifying logic equations.

	(a)	(b)
1	$\overline{\overline{A}} = A$	$\overline{\overline{A}} = A$
2	$A + \text{false} = A \quad (A + 0 = A)$	$A \cdot \text{true} = A \quad (A \cdot 1 = A)$
3	$A + \text{true} = \text{true} \quad (A + 1 = 1)$	$A \cdot \text{false} = \text{false} \quad (A \cdot 0 = 0)$
4	$A + \overline{A} = \text{true} \quad (A + \overline{A} = 1)$	$A \cdot \overline{A} = \text{false} \quad (A \cdot \overline{A} = 0)$
5	$A + A = A$	$A \cdot A = A$
6	$A + B = B + A$	$A \cdot B = B \cdot A$
7	$A + B + C = (A + B) + C = A + (B + C)$	$A \cdot B \cdot C = (A \cdot B) \cdot C = A \cdot (B \cdot C)$
8	$A \cdot (B + C) = A \cdot B + A \cdot C$	$A + B \cdot C = (A + B)(A + C)$
9	$\overline{A + B} = \overline{A} \cdot \overline{B}$	$\overline{A \cdot B} = \overline{A} + \overline{B}$
10	$A \cdot B + A \cdot \overline{B} = A$	$(A + B)(A + \overline{B}) = A$
11	$A + A \cdot B = A$	$A(A + B) = A$
12	$A(\overline{A} + B) = A \cdot B$	$A + \overline{A} \cdot B = A + B$
13	$A \cdot B + \overline{A} \cdot C + B \cdot C = A \cdot B + \overline{A} \cdot C$	$(A + B)(\overline{A} + C)(B + C) = (A + B)(\overline{A} + C)$

↑ Duals ↑

15

## Boolean Identities

Identities	Property
1-5	Single variable, foundations of Boolean manipulation
6	Commutative
7	Associative
8	Distributive
9	De Morgan's
10	Combining
11	Absorption
13	Consensus

16

## Boolean Identities

- The right side is the dual of the left side

- Duals formed by replacing

AND  $\rightarrow$  OR  
 OR  $\rightarrow$  AND  
 0  $\rightarrow$  1  
 1  $\rightarrow$  0


- The dual of any true statement in Boolean algebra is also a true statement.

17

 
## Boolean Identities

- DeMorgan's laws very useful: 9a and 9b

$$\overline{A+B} = \overline{A} \cdot \overline{B}$$


 
$$\overline{AB} = \overline{A} + \overline{B}$$



18

## Activity 2

Proofs of some Identities:


12b:  $A + \overline{AB} = A + B$

13a:  $AB + \overline{AC} + BC = AB + \overline{AC}$

19

## Simplifying Logic Expressions Using Boolean Identities

## Simplifying Logic Equations – Why?

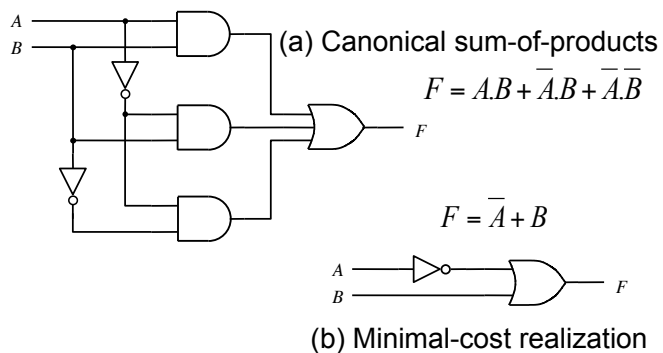

21

## Simplifying Logic Equations

- Simplifying logic expressions can lead to using smaller number of gates (parts) to implement the logic expression
- Can be done using
  - Boolean Identities (algebraic)
  - Karnaugh Maps (graphical)
- A *minimum SOP* (MSOP) expression is one that has no more AND terms or variables than any other equivalent SOP expression.
- A *minimum POS* (MPOS) expression is one that has no more OR factors or variables than any other equivalent POS expression.
- There may be several MSOPs of an expression

22

## Example of Using Boolean Identities

- Find an MSOP for

$$\begin{aligned}
 F &= \bar{X}W + Y + \bar{Z}(Y + \bar{X}W) \\
 &= \bar{X}W + Y + \bar{Z}Y + \bar{Z}\bar{X}W \\
 &= \bar{X}W(1 + \bar{Z}) + Y(1 + \bar{Z}) \\
 &= \bar{X}W + Y
 \end{aligned}$$

23

## Activity 3

- Find an MSOP for

$$F = V\bar{W}XY + VWYZ + V\bar{X}YZ$$

24

## CSE 2021 Computer Organization

### Combinational and Sequential Circuits

## Digital Circuit Classification

- Combinational circuits
  - Output depends only solely on the current combination of circuit inputs
  - Same set of input will always produce the same outputs
  - Consists of AND, OR, NOR, NAND, and NOT gates
- Sequential circuits
  - Output depends on the current inputs and state of the circuit (or past sequence of inputs)
  - Memory elements such as flip-flops and registers are required to store the "state"
  - Same set of input can produce completely different outputs


26

## CSE 2021 Computer Organization

### Combinational Circuits
 
## Multiplexer


- A multiplexer (MUX) selects data from one of  $N$  inputs and directs it to a single output, just like a railway switch
  - 4-input Mux needs 2 select lines to indicate which input to route through
  - $N$ -input Mux needs  $\log_2(N)$  selection lines



28

## Multiplexer (2)


- An example of 4-input Mux

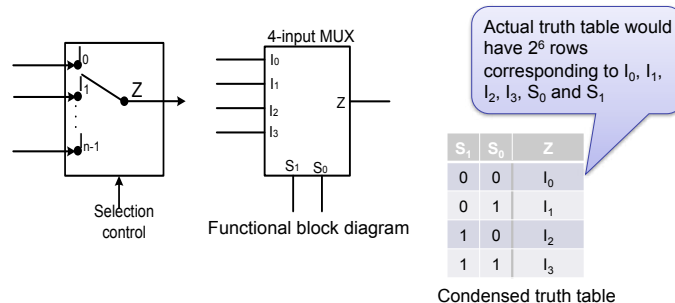

29
 
## Decoder

- A decoder is a circuit element that will decode an  $N$ -bit code.
- It activates an appropriate output line as a function of the applied  $N$ -bit input code



30

## CSE 2021 Computer Organization

### Sequential Circuits


## Why Bit Storage ?

 3.2

- Flight attendant call button
  - Press call: light turns on
    - Stays on** after button released
  - Press cancel: light turns off
- Logic gate circuit to implement this?



Doesn't work.  $Q=1$  when  $Call=1$ , but doesn't stay 1 when  $Call$  returns to 0  
Need some form of "memory" in the circuit




32


 
## Bit Storage Using SR Latch

- Simplest memory elements are Latch and Flip-Flops
- SR (set-reset) latch is an **un-clocked** latch
  - Output Q=1 when S=1, R=0 (set condition)
  - Output Q=0 when S=0, R=1 (reset condition)
  - Problem - Q is undefined if S=1 and R=1




33

## Clocks

- Clock period:** time interval between pulses
  - example: period = 20 ns
- Clock frequency:** 1/period
  - example: frequency =  $1 / 20 \text{ ns} = 50 \text{ MHz}$
- Edge-triggered clocking:** all state changes occur on a clock edge.


Freq	Period
100 GHz	0.01 ns
10 GHz	0.1 ns
1 GHz	1 ns
100 MHz	10 ns
10 MHz	100 ns

 

34
 
## Clock and Change of State


- Clock controls when the state of a memory element changes
- Edge-triggered clocking:** all state changes occur on a clock edge.



35
 
## Clock Edge Triggered Bit Storage


- Flip-flop** - Bit storage that stores on clock edge, not level
- D Flip-flop
  - Two latches, master and slave latches.
  - Output of the first goes to input of second, slave latch has inverted clock signal (falling-edge trigger)



36
 
## Setup and Hold Time


- Setup time
  - The minimum amount of time the data signal should be held steady before the clock edge arrives.
- Hold time
  - The minimum amount of time the data signal should be held steady after the clock edge.



37
 
## N-Bit Register

- Cascade  $N$  number of D flip-flops to form a  $N$ -bit register
- An example of 8-bit register formed by 8 edge-triggered D flip-flops



38

## CSE 2021 Computer Organization

### Verilog Basics

## What is an HDL?

- A Hardware Description Language (HDL) is a software programming language used to model the intended operation of a piece of hardware.
- The difference between an HDL and “C”
  - Concurrency
  - Timing
- A powerful feature of the Verilog HDL is that we can use the same language for describing, testing and debugging the system.

40

## An Example

```

module pound_one;
reg [7:0] a,a$b,b,c; // register declarations
reg clk;

initial
begin
    clk=0; // initialize the clock
    c = 1;
    forever #25 clk = !clk;
end
/* This section of code implements
a pipeline */
always @ (posedge clk)
begin
    a = b;
    b = c;
end
endmodule

```

41

## Identifiers

- Identifiers are names assigned by the user to Verilog objects such as modules, variables, tasks etc.
- An identifier may contain any sequence of letters, digits, a dollar sign '\$', and the underscore '\_' symbol.
- The first character of an identifier must be a letter or underscore; it cannot be a dollar sign '\$', for example. We cannot use characters such as '-' (hyphen), brackets, or '#' in Verilog names (*escaped identifiers* are an exception).

42

## Escaped Identifiers

- The use of escaped identifiers allow any character to be used in an identifier.
  - Escaped identifiers start with a backslash (\) and end with white space (White space characters are space, tabs, carriage returns).
  - Gate level netlists generated by EDA tools (like DC) often have escaped identifiers
- Examples:
  - Vclock = 0;
  - \a\*b = 0;
  - \5-6
  - \bus\_a[0]
  - \bus\_a[1]

43

```

module identifiers; /* Multiline comments in Verilog look like C comments
and // is OK in here. */
// Single-line comment in Verilog.

reg legal_identifier, two__underscores;
reg _OK,OK,_OK,$_OK,123,CASE_SENSITIVE, case_sensitive;
reg Vclock ,\a*b ; // Add white_space after escaped identifier.
//reg $_BAD,123_BAD; // Bad names even if we declare them!
initial begin
    legal_identifier = 0; // Embedded underscores are OK,
    two__underscores = 0; // even two underscores in a row.
    _OK = 0; // Identifiers can start with underscore
    OK_ = 0; // and end with underscore.
    OK$ = 0; // $ sign is OK.
    OK_123 = 0; // Embedded digits are OK.
    CASE_SENSITIVE = 0; // Verilog is case-sensitive (unlike VHDL).
    case_sensitive = 1;
    Vclock = 0; // An escaped identifier with \ breaks rules
    \a*b = 0; // but be careful to watch the spaces!
    $display("Variable CASE_SENSITIVE= %d",CASE_SENSITIVE);
    $display("Variable case_sensitive= %d",case_sensitive);
    $display("Variable Vclock = %d",Vclock );
    $display("Variable \a*b = %d",\a*b );
end
endmodule

```

An Example

44

## Simulation Result of the Example

Variable CASE\_SENSITIVE= 0

Variable case\_sensitive= 1

Variable /clock = 0

Variable \a\*b = 0

45

## Logic values

- Verilog has 4 logic Values:
  - '0' represents zero, low, false, not asserted.
  - '1' represents one, high, true, asserted.
  - 'z' or 'Z' represent a high-impedance value, which is usually treated as an 'x' value.
  - 'x' or 'X' represent an uninitialized or an unknown logic value--an unknown value is either '1', '0', 'z', or a value that is in a state of change.

46

## Data Types

- Three data type classes:
  - Nets
    - Physical connections between devices
    - Example: **wire** a, b;
  - Registers
    - Storage devices, variables.
    - Example: **reg** a; **reg** [7:0] bus;
  - Parameters
    - Constants
    - Example: **parameter** width=32;  
**parameter** A\_string ="hello";

47

## CSE 2021 Computer Organization

### Code Structure

**Design Entities**  
**Verilog Module Basics**

## Design Entities

- The **module** is the basic unit of code in the Verilog language.

- Example

```
module holiday_1(sat, sun, weekend);
  input sat, sun;
  output weekend;
  assign weekend = sat | sun;
endmodule
```

49

## Verilog Module

- Modules contain

- **declarations**
- **functionality**
- **timing**

```
module name (port_names);
  module port declarations
  data type declarations
  procedural blocks
  continuous assignments
  user defined tasks & functions
  primitive instances
  module instances
  specify blocks
endmodule
```

syntax:

```
module module_name (signal, signal,... signal) ;
  .      ; //content of module
  .
  ..
  .
endmodule
```

50

## Module Port Declarations

- Scalar (1bit) port declarations:
  - *port\_direction port\_name, port\_name ... ;*
- Vector (Multiple bit) port declarations:
  - *port\_direction [port\_size] port\_name, port\_name ... ;*
- *port\_direction* : input, inout (bi-directional) or output
- *port\_name* : legal identifier
- *port\_size* : is a range from [msb:lsb]

```
input a, into_here, george; // scalar ports
input [7:0] in_bus, data;    // vectored ports
output [31:0] out_bus;      // vectored port
inout [maxsize-1:0] a_bus; // parameterized port
```

51

## Module Instances

- A module may be instantiated within another module.
- There may be multiple instances of the same module.

syntax for instantiation:

```
module_name instance_name (signal, signal,...);
```

```
module example (a,b,c,d);
  input a,b;
  output c,d;
  .
  .
endmodule
```

```
example ex_inst_1(in_1, in_2, w, z);
example ex_inst_2(in_1, in_2, , z); // skip a port
```

52

## Gate-level Primitives


- Verilog has pre-defined primitives that implement basic logic functions.
- Structural modeling with the primitives is similar to schematic level design.

and	nand	or	nor	xor	xnor
buf	not	bufif0	bufif1	notif0	notif1

```
module
gate_level_ex(in_1,in_2,c);
output c;
input in_1,in_2;

nand(a,in_1,in_2);
not(b,a);
or_or_1(c,in_2,b);


endmodule
```

 

53
 
## Activity 4

Given the circuit below, develop a Verilog module for the circuit



54

## User-Defined Primitives

- We can define primitive gates (a **user-defined primitive** or **UDP**) using a truth-table specification. The first port of a UDP must be an output port, and this must be the only output port (we may not use vector or inout ports).

- An example

```
primitive Adder(Sum, InA, InB);
output Sum;
input InA, InB;
table // inputs : output
00 : 0;
01 : 1;
10 : 1;
11 : 0;
endtable
endprimitive
```

55

## Operators

- Verilog operators (in increasing order of precedence)

- ?: (conditional)
- || (logical or)
- && (logical and)
- | (bitwise or)
- ~| (bitwise nor)
- ^ (bitwise xor)
- ^~ ^ (bitwise xnor, equivalence)
- & (bitwise and)
- ~& (bitwise nand)
- == (logical) != (logical) === (case) !== (case)
- < (lt)
- <= (lt or equal)
- > (gt)
- >= (gt or equal)
- << (shift left)
- >> (shift right)
- +
- 
- \*
- /
- % (modulus)

56

## CSE 2021 Computer Organization

**Procedural Assignment**  
**Continuous Assignment**  
**Control Statement**

## Procedures

- A Verilog **procedure** is an **always** or **initial** statement, a task , or a function .
- The statements within a sequential block (statements that appear between a **begin** and an **end** ) that is part of a procedure execute sequentially in the order in which they appear, but the procedure executes concurrently with other procedures.

58

## Procedural Blocks

- There are two types of procedural blocks:
  - initial blocks - executes only once
  - always blocks - executes in a loop
- Multiple Procedural blocks may be used, if so the multiple blocks are concurrent.
- Procedural blocks may have:
  - Timing controls - which delays when a statement may be executed
  - Procedural assignments
  - Programming statements

59

## Procedural Statement Groups

- When there is more than one statement within a procedural block the statements must be grouped.
- Sequential grouping: statements are enclosed within the keywords **begin** and **end**.
- An example
 

```
always
begin
  a = 5;           // executed 1st
  c = 4;           // executed 2nd
  wake_up = 1;    // executed 3rd
end
```

60

## Timing Controls (procedural delays)

- **#delay** - simple delay
  - Delays execution for a specific number of time steps.  
`#5 reg_a = reg_b;`
- **@ (edge signal)** - edge-triggered timing control
  - Delays execution until a transition on **signal** occurs.
  - **edge** is optional and can be specified as either **posedge** or **negedge**.
  - Several **signal** arguments can be specified using the keyword **or**.
  - An example : `always @ (posedge clk) reg_a = reg_b;`
- **wait (expression)** - level-sensitive timing control
  - Delays execution until **expression** evaluates true.
  - `wait (cond_is_true) reg_a = reg_b;`

61

## Procedural assignments

- Assignments made within procedural blocks are called procedural assignments.
  - Value of the RHS of the equal sign is transferred to the LHS
  - LHS must be a register data type (reg, integer, real). NO NETS!
  - RHS may be any valid expression or signal

```
always @ (posedge clk)
begin
  a = 5;           // procedural assignment
  c = 4*32/6;      // procedural assignment
  wake_up =$time; // procedural assignment
end
```


62

## Continuous Assignment

- Continuous assignment assigns a value to a **wire** in a similar way that a real logic gate drives a real wire.
- The main use for continuous assignments is to model combinatorial logic.

**syntax:** Explicit continuous assignment:  
`assign net_name = expression;`  
 where **net\_name** is a **net** that has been previously declared
 
```
module continuous (Ain, Aout);
  input Ain;
  output Aout;
  assign Aout = ~Ain //continuous assignment.
endmodule
```



63

## Illustration of Assignment Statements

### module assignments

//... Continuous assignments go here.

**always** // beginning of a procedure

**begin** // beginning of sequential block

//... Procedural assignments go here.

**end**

**endmodule**

64



## Control Statements

- Two types of programming statements:
  - Conditional
  - Looping
- Programming statements only used in procedural blocks

65

## if and if-else

### syntax:

#### **if(expression) statement**

If the expression evaluates to true then execute the statement

#### **if(expression) statement1**

#### **else statement2**

If the expression evaluates to true then execute statement1, if false, then execute statement2.

```
module if_ex(clk);
  input clk;
  reg red,blue,pink,yellow,orange,color,green;
  always @ (posedge clk)
  if (red || (blue && pink))
  begin
    $display ("color is mixed up");
    color <= 0; // reset the color
  end
  else if (blue && yellow)
    $display ("color is greenish");
  else if (yellow && (green || orange))
    $display ("not sure what color is");
  else $display ("color is black");
endmodule
```

66

## for

### syntax:

#### **for (assignment\_init; expression; assignment) statement or statement\_group**

- The **assignment\_init** is executed once at the start of the loop.
- Loop executes as long as **expression** is true.
- The **assignment** is executed at the completion of each loop.

```
module for_ex1 (clk);
  input clk;
  reg [31:0] mem [0:9]; // 10x32 memory
  integer i;
  always @ (posedge clk)
  for (i = 9; i >= 0; i = i-1)
    mem[i] = 0; // init the memory to zeros
endmodule
```

67

## Simulating the Verilog Code

- Verilog code of NAND Latch

```
Module simple_latch (q, qBar, set, clear);
```


```
  input set, clear;
```

```
  output q, qBar;
```

```
  nand #2 n1(q,qBar,set);
```

```
  nand #2 n2(qBar,q,clear);
```

```
endmodule
```

 

68

## Testbench

- A testbench generates a sequence of input values (we call these **input vectors** ) that test or **exercise** the verilog code.
- It provides stimulus to the statement that will monitor the changes in their outputs.
- Testbenches do not have a port declaration but must have an instantiation of the circuit to be tested.

69

## A testbench for NAND Latch

```
Module test_simple_latch;
  wire q, qBar;
  reg set, clear;
  simple_latch SL1(q,qBar,set,clear);
  initial
  begin
    #10 set = 0; clear = 1;
    #10 set = 1;
    #10 clear = 0;
    #10 clear = 1;
    #10 $stop;
    #10 $finish;
  end
  initial
  begin
    $monitor ("%d set= %b clear= %b q=%b qBar=%b", $time,
              set, clear, q, qBar);
  end
endmodule
```

70