

CSE 2021 Computer Organization

Appendix C Part 2

Basic Arithmetic Logic Unit -- Adder

Half Adders

- Need to add *bits* $\{0,1\}$ of A_i and B_i .

- Associate

- binary bit 0 \leftrightarrow logic value F (0)

- binary bit 1 \leftrightarrow logic value T (1)

- This leads to the following truth table

| A_i | B_i | Sum_i | $Carry_{i+1}$ |
|-------|-------|---------|---------------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

$$SUM_i = \overline{A_i}B_i + A_i\overline{B_i} = A_i \oplus B_i$$


$$CARRY_{i+1} = A_i B_i$$

$$\begin{array}{c} C_{i+1} \\ A: A_n \dots A_{i+1} A_i \dots A_0 \\ B: B_n \dots B_{i+1} B_i \dots B_0 \\ S_i \end{array}$$

Half Adder Circuit

$$SUM_i = \overline{A_i}B_i + A_i\overline{B_i} = A_i \oplus B_i$$

$$CARRY_{i+1} = A_i B_i$$

 


Half Adder Limitations

- Half adder circuits do not suffice for general addition because they do not include the carry bit from the previous stage of addition, e.g.

| | | | | | |
|-------|---|---|---|---|---|
| Carry | | 0 | 1 | 1 | 0 |
| A | | 0 | 1 | 1 | 0 |
| B | + | 0 | 0 | 1 | 1 |
| SUM | | 1 | 0 | 0 | 1 |

Full Adders (1-Bit ALU)

 - Full adders can use the carry bit from the previous stage of addition



| A_i | B_i | C_i | S_i | C_{i+1} |
|-------|-------|-------|-------|-----------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

Full Adder Logic Expressions

Sum

$$\begin{aligned}
 \text{SUM} &= \bar{A}_i \bar{B}_i C_i + \bar{A}_i B_i \bar{C}_i + A_i \bar{B}_i \bar{C}_i + A_i B_i C_i \\
 &= \bar{A}_i (\bar{B}_i C_i + B_i \bar{C}_i) + A_i (\bar{B}_i \bar{C}_i + B_i C_i) \\
 &= \bar{A}_i (B_i \oplus C_i) + A_i (\bar{B}_i \oplus \bar{C}_i) \\
 &= A_i \oplus B_i \oplus C_i
 \end{aligned}$$


Carry

$$\begin{aligned}
 C_{i+1} &= A_i B_i + A_i \bar{B}_i C_i + \bar{A}_i B_i C_i \\
 &= A_i B_i + C_i (A_i \bar{B}_i + \bar{A}_i B_i) \\
 &= A_i B_i + C_i (A_i \oplus B_i)
 \end{aligned}$$

Full Adder Circuit

$$SUM = (A_i \oplus B_i) \oplus C_i$$
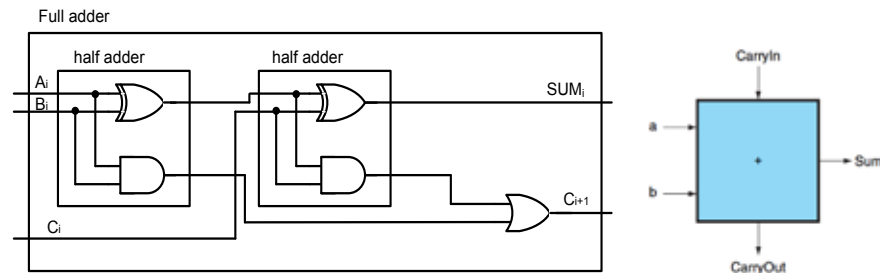
$$C_{i+1} = A_i B_i + C_i (A_i \oplus B_i)$$




Note: A full adder adds 3 bits. Can also consider as first adding first two and then the result with the carry

Enhancement to 1-bit Adder(1)

- 1-bit ALU with AND, OR, and addition
 - Supplemented with AND and OR gates
 - A multiplexer controls which gate is connected to the output


| Operation | Result |
|-----------|----------|
| 00 | AND |
| 01 | OR |
| 10 | Addition |

 

Enhancement to 1-bit Adder(2)

- 1-bit ALU for subtraction
 - Subtraction is performed using 2's complement, i.e.

$$a - b = a + \bar{b} + 1$$

 


| Binvert | CarryIn | Operation | Result |
|---------|---------|-----------|-------------|
| 0 | 0 | 00 | AND |
| 0 | 0 | 01 | OR |
| 0 | 0 | 10 | Addition |
| 1 | 1 | 10 | Subtraction |

Enhancement to 1-bit Adder(3)

- 1-bit ALU for NOR operation
- A MIPS ALU also needs a NOR function

 
$$\overline{(a + b)} = \bar{a} \cdot \bar{b}$$



| Ainvert | Binvert | CarryIn | Operation | Result |
|---------|---------|---------|-----------|-------------|
| 0 | 0 | 0 | 00 | AND |
| 1 | 1 | 0 | 00 | NOR |
| 0 | 0 | 0 | 01 | OR |
| 0 | 0 | 0 | 10 | Addition |
| 1 | 1 | 1 | 10 | Subtraction |


Enhancement to 1-bit Adder(4)

 - 1-bit ALU for SLT operations
- `slt $s1, $s2, $s3`
 - If $(\$s2 < \$s3)$, $\$s1 = 1$, else $\$s1 = 0$
- adding one input *less*
 - if $(a < b)$, set *less* to 1
 - or if $(a - b) < 0$, set *less* to 1
 - If the result of subtraction is negative, set *less* to 1
- How to determine if the result is negative?




Enhancement to 1-bit Adder(5)

 - How to determine if the result is negative?
 - Negative \rightarrow Sign bit value = 1
- Create a new output "Set" and used only for `slt`
- An overflow detection is included



N-Bit Adders (Ripple Carry)

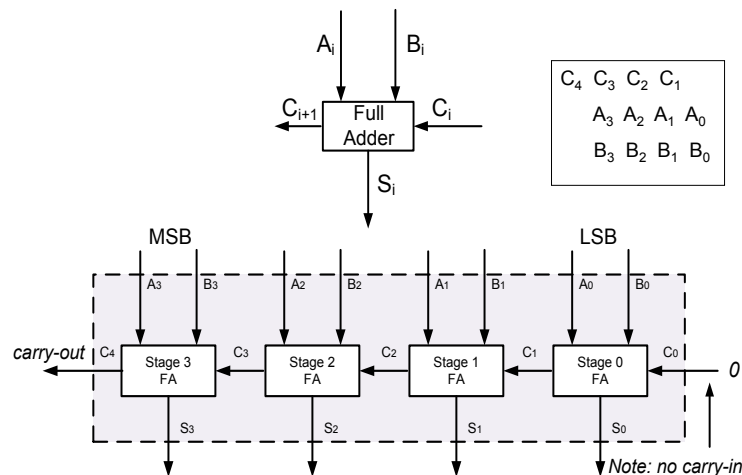

Ripple Carry Adders

- 4 FA's cascaded to form a 4-bit adder
- In general, N FA's can be used to form a N -bit adder
- Carry bits have to propagate from one stage to the next. Inherent propagation delays associated with this
- Output of each FA is therefore not stable until the carry-in from the previous stage is calculated

32-Bit ALU

- OR and INV gates are added to support conditional branch instruction, i.e. test the result of a-b if the result is 0.

| ALU control lines | Function |
|-------------------|------------------|
| 0000 | AND |
| 0001 | OR |
| 0010 | add |
| 0110 | subtract |
| 0111 | set on less than |
| 1100 | NOR |

