
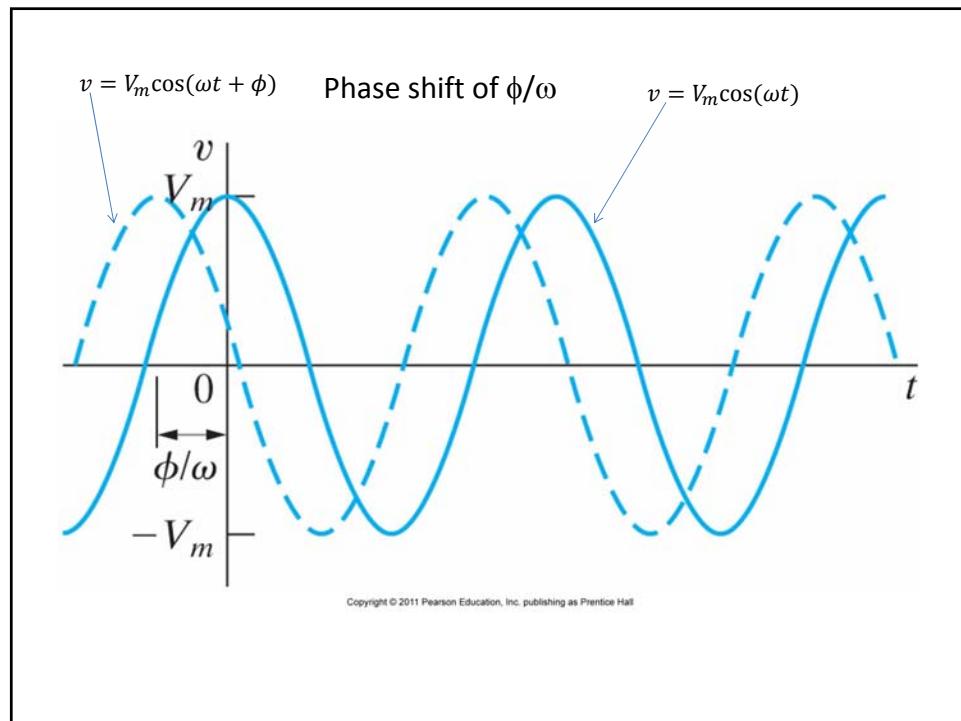



ENG2200 Electric Circuits

Chapter 9 Sinusoidal Steady State Analysis

Objectives

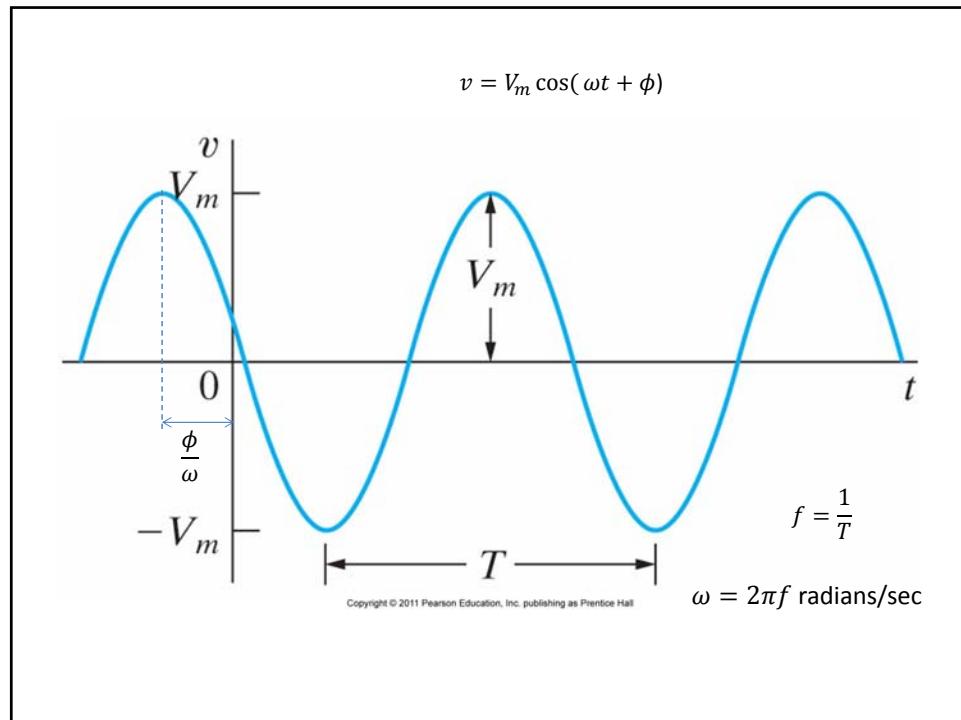- Understanding phasor concept and be able to perform phasor transform and inverse phasor transform.
- Be able to transform a circuit with sinusoidal source into the frequency domain using phasor transform
- Know how to use circuits analysis techniques to solve circuits in the frequency domain.
- Be able to use phasor in analyzing circuits with ideal transformers.



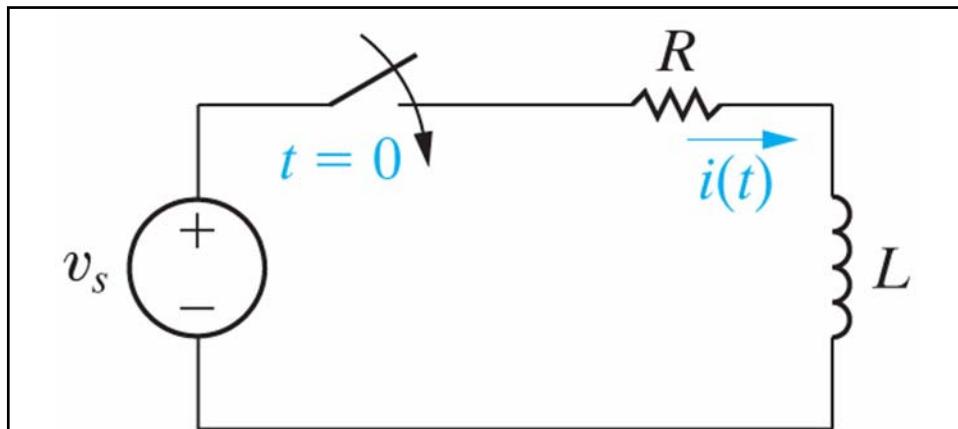

$$L \frac{di}{dt} + iR = V_m \cos(\omega t + \phi)$$

$$i = \frac{-V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\phi - \theta) e^{-(R/L)t} + \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta)$$

RMS value

$$V_{rms} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} V_m^2 \cos^2(\omega t + \phi) dt}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

Why RMS?


The Phasor


- The phasor is a complex number that carries the amplitude and phase angle information of a sinusoidal function.
- Euler's identity $e^{\pm j\theta} = \cos \theta \pm j \sin \theta$

$$\begin{aligned}\cos \theta &= \Re\{e^{j\theta}\} \\ \sin \theta &= \Im\{e^{j\theta}\}\end{aligned}$$

$$\begin{aligned}v &= V_m \cos(\omega t + \phi) \\ v &= \Re\{V_m e^{j\phi} e^{j\omega t}\}\end{aligned}$$

$$Ae^{j\phi} = A\angle\phi^\circ$$

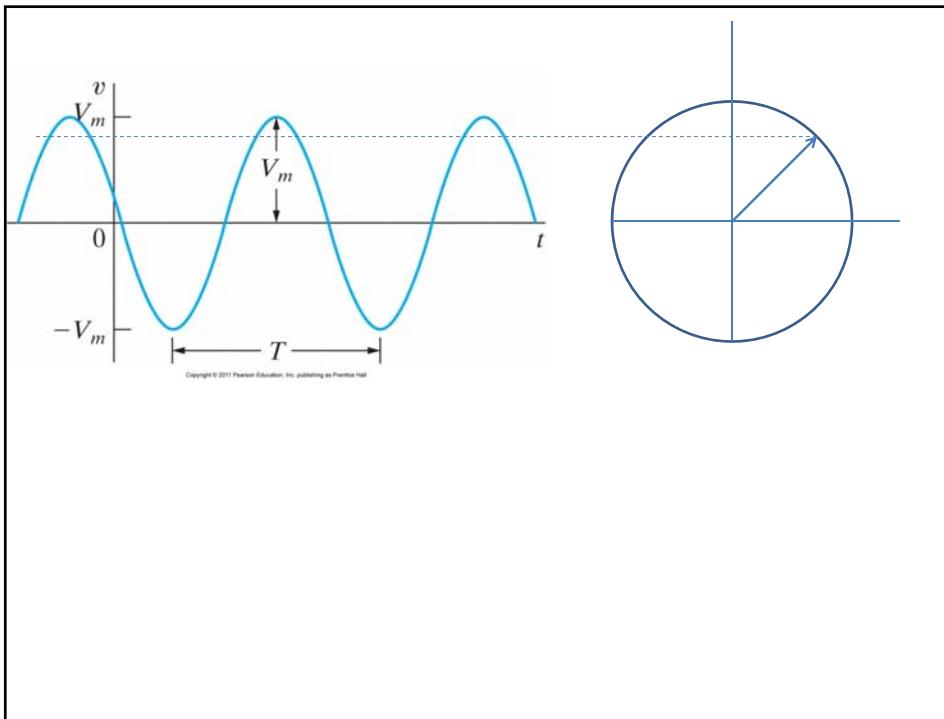

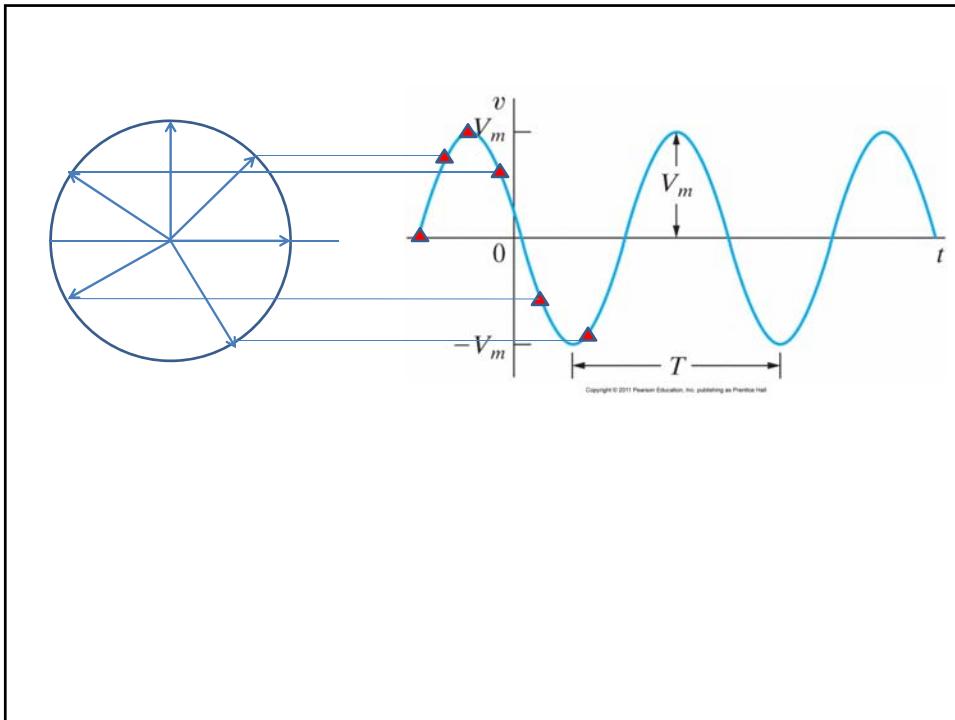

The inductor

$$v = L \frac{di}{dt}$$

$$v = V_m \cos(\omega t)$$

$$di = \frac{1}{L} V_m \cos(\omega t) dt$$


$$i = \frac{1}{L} V_m \int \cos(\omega t) dt$$

$$i = \frac{V_m}{\omega L} \sin(\omega t) = \frac{V_m}{\omega L} \cos(\omega t - \frac{\pi}{2})$$

$$I = \frac{V_m}{\omega L} e^{-j\pi/2} = \frac{V_m}{\omega L} \angle -\pi/2$$

$$Z = \frac{v}{i} = \omega L \angle \pi/2 = j\omega L$$

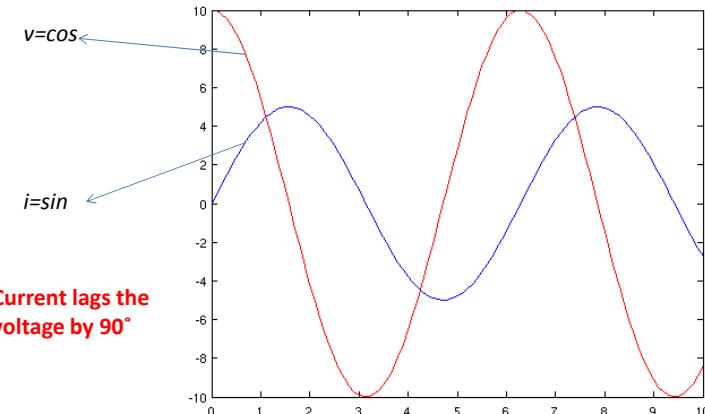A plot showing the phase relationship between the current and voltage at the terminals of an inductor



The Capacitor

$$i = C \frac{dv}{dt}$$

$$v = V_m \cos(\omega t)$$


$$i = CV_m \frac{d}{dt} \cos(\omega t)$$

$$i = -C\omega V_m \sin(\omega t) = \omega CV_m \cos(\omega t + \frac{\pi}{2})$$

$$I = \omega CV_m e^{j\pi/2} = \omega CV_m \angle \pi/2$$


$$Z = \frac{v}{i} = \frac{1}{\omega C} \angle -\pi/2 = \frac{-j}{\omega C} = \frac{1}{j\omega C}$$

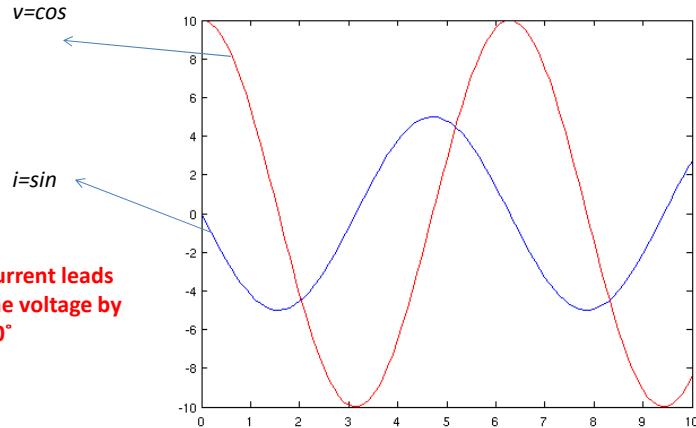A plot showing the phase relationship between the current and voltage at the terminals of a capacitor



Adding Complex Numbers


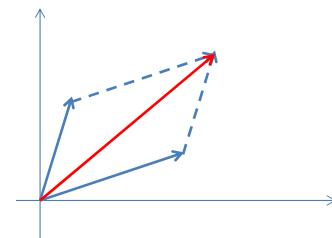
$$\begin{array}{r} x_1 + jy_1 \\ \pm \quad x_2 + jy_2 \\ \hline (x_1 + x_2) \pm j(y_1 + y_2) \end{array}$$




Multiplication

$$\begin{array}{r} \times \quad \quad \quad x_1 + jy_1 \\ \quad \quad \quad x_2 + jy_2 \\ \hline (x_1 x_2 - y_1 y_2) + j(x_1 y_2 + x_2 + y_1) \end{array} \quad A_1 \angle \theta_1 \times A_2 \angle \theta_2 = A_1 A_2 \angle \theta_1 + \theta_2$$

Example

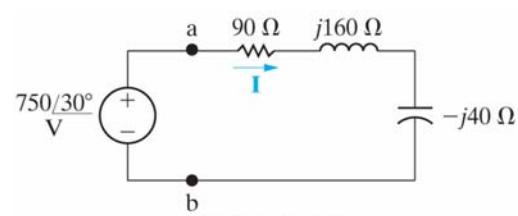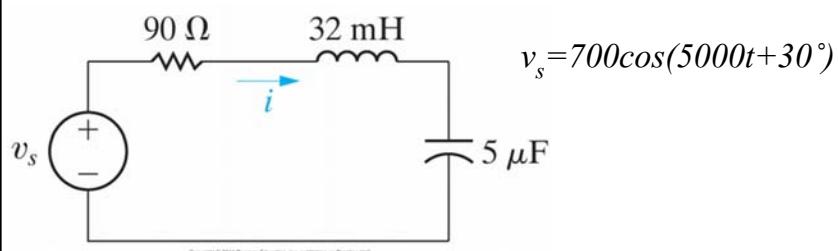

Example

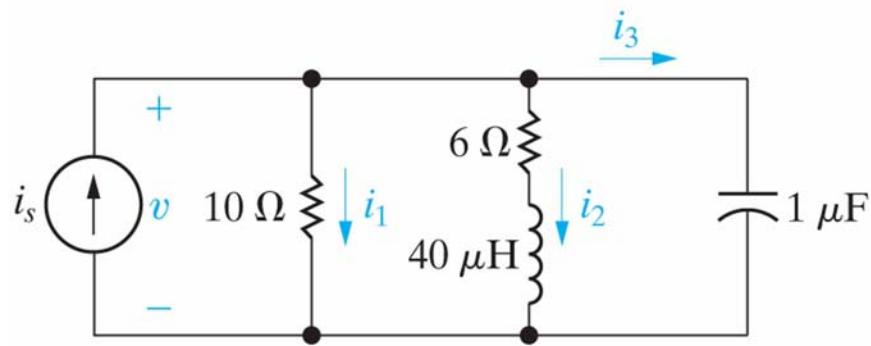

$$i_s = 8 \cos 200,000t$$

Example



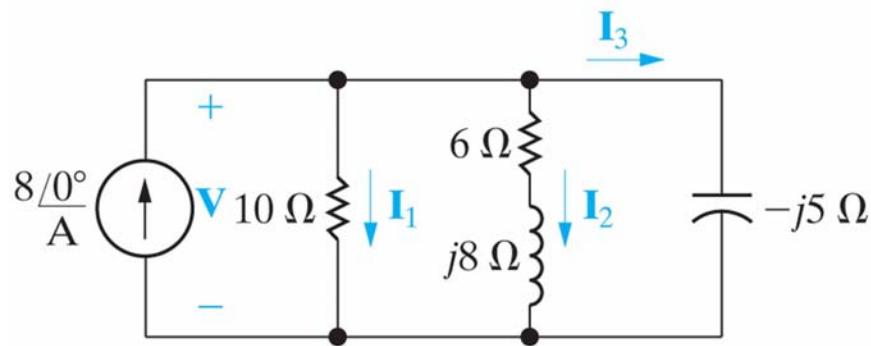


Figure 9.24 A source transformation in the frequency domain.

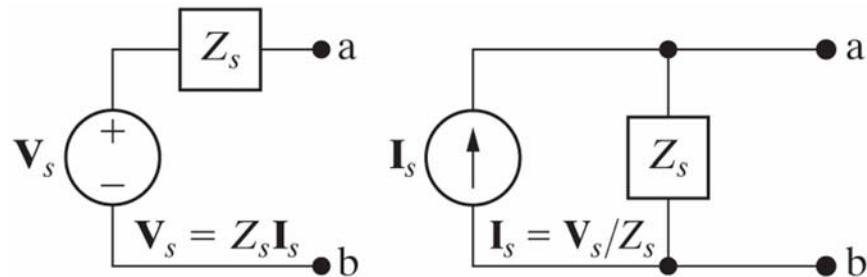

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Figure 9.27 The circuit for Example 9.9.

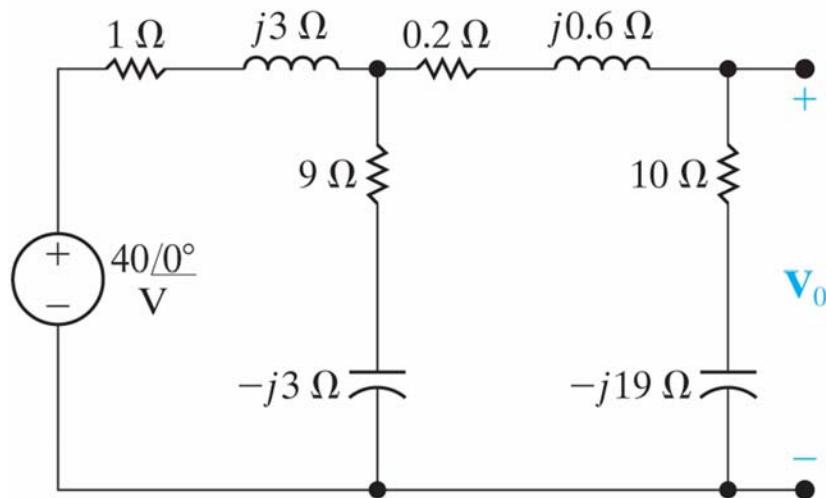

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Figure 9.28 The first step in reducing the circuit shown in Fig. 9.27.

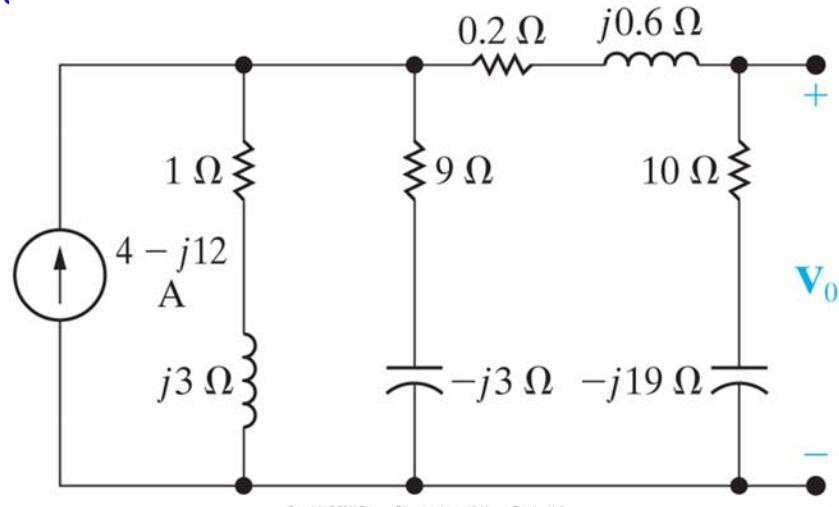


Figure 9.29 The second step in reducing the circuit shown in Fig. 9.27.

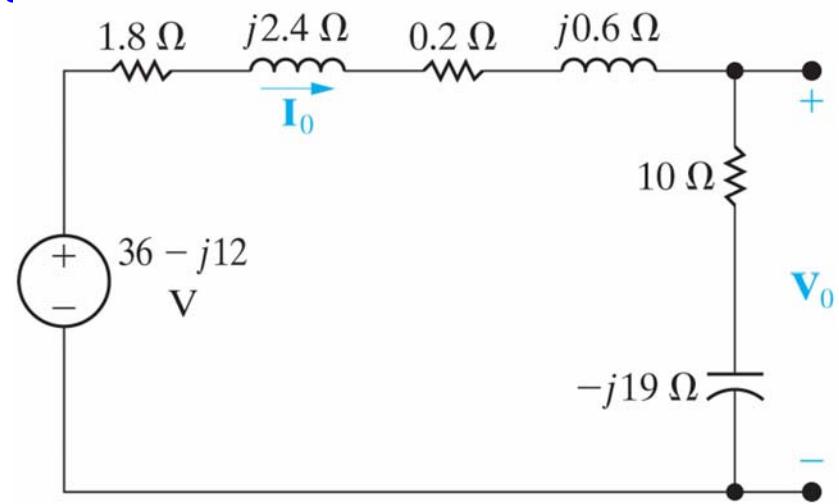
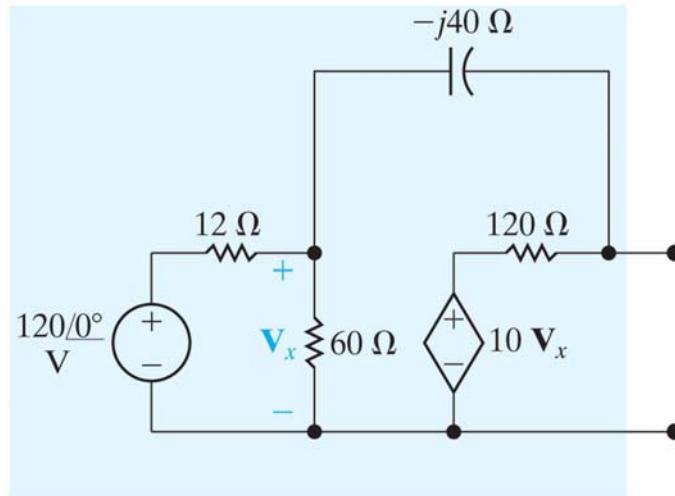
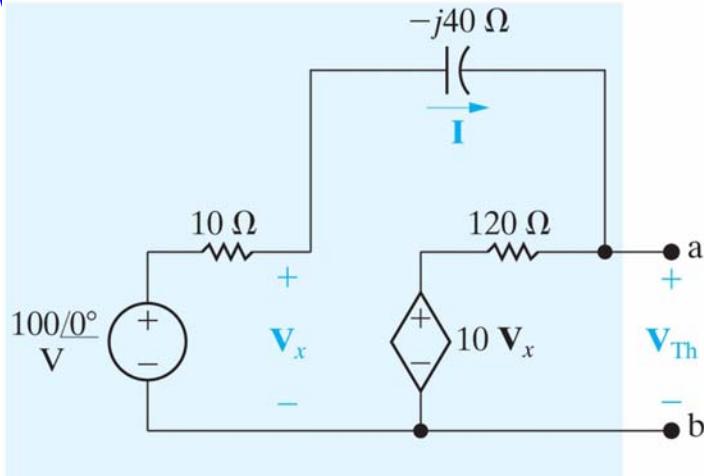



Figure 9.30 The circuit for Example 9.10.

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Figure 9.31 A simplified version of the circuit shown in Fig. 9.30


Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Figure 9.32 A circuit for calculating the Thévenin equivalent impedance.

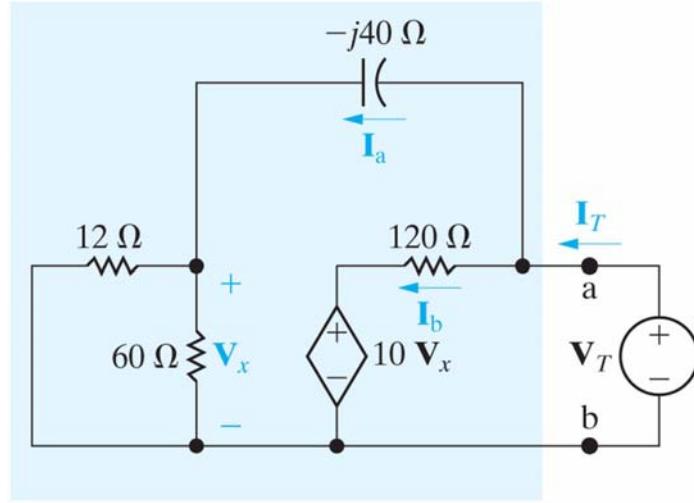


Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall


Figure 9.33 The Thévenin equivalent for the circuit shown in Fig. 9.30.

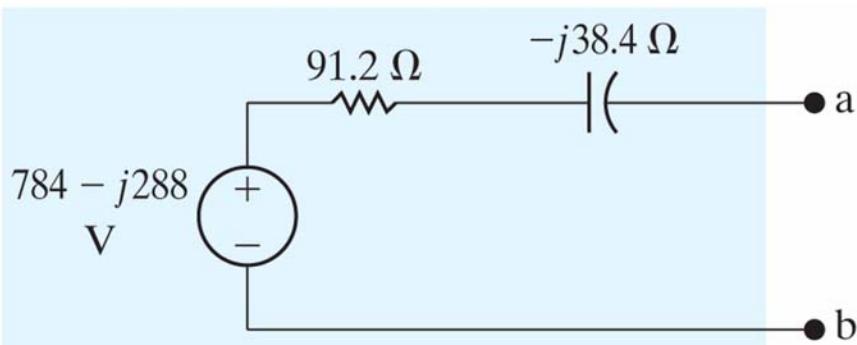


Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

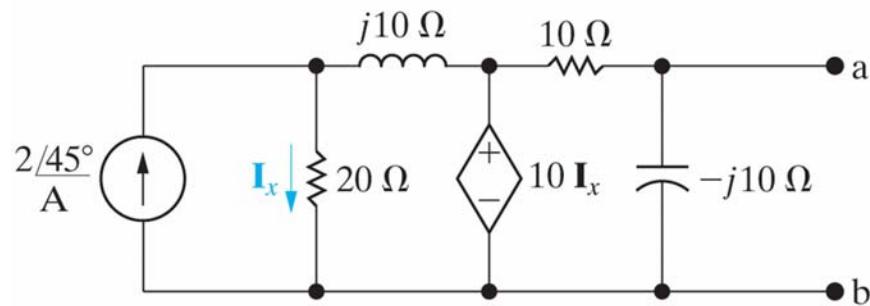Figure 9.34 The circuit for Example 9.11.


Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

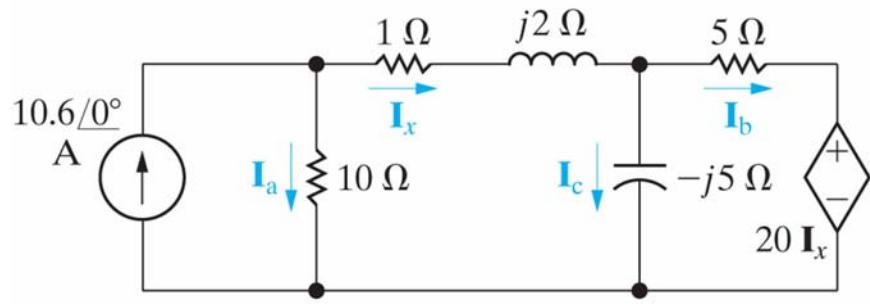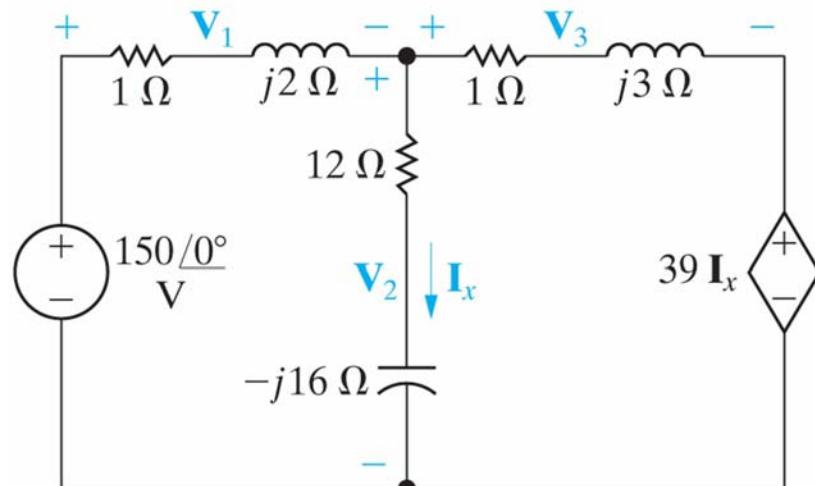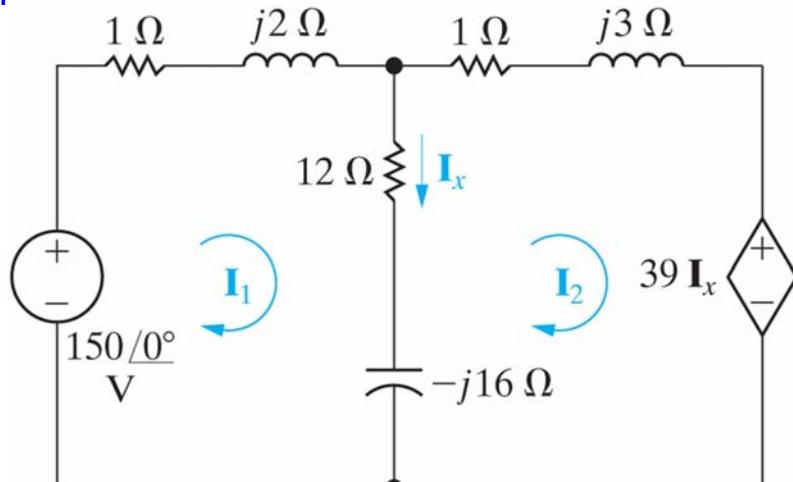Figure 9.35 The circuit shown in Fig. 9.34, with the node voltages defined.

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Figure 9.36 The circuit for Example 9.12.

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Figure 9.37 Mesh currents used to solve the circuit shown in Fig. 9.36

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

