

Solutions to CSE3201 Assignment 4

1. 5.21 (From the textbook, as with the remainder of the questions)
Ans. in textbook

2. 5.22 (Just do the code and only show what's in the always block, absolutely no structural code, use only non-blocking assignments.)

```
module johnson8 (Resetn, Clock, Q);
  input Resetn, Clock;
  output reg [7:0] Q;
  reg [7:0] Q;

  always @(negedge Resetn, posedge Clock)
    if (!Resetn)
      Q <= 0;
    else
      Q <= {{Q[6:0]}, {~Q[7]}};

endmodule
```

3. 5.23



// Ring counter with synchronous reset

```
module ripplen (Resetn, Clock, Q);
  parameter n = 8;
  input Resetn, Clock;
  output reg [n-1:0] Q;

  always @(posedge Clock)
    if (!Resetn)
      begin
        Q[7:1] <= 0;
        Q[0] <= 1;
      end
    else
      Q <= {{Q[6:0]}, {Q[7]}};

endmodule
```


4. 5.25

  

5. 5.26

Ans. in textbook

 
6. 5.28 (Just draw the diagram after carefully looking at the code and show the counting sequence).



7. 6.1 (Note: the book writes its state assignment table a little differently than we have, it denotes the inputs with the variable w and places different settings for it in different columns, our notation made it look just like a traditional truth table).

Ans. in textbook

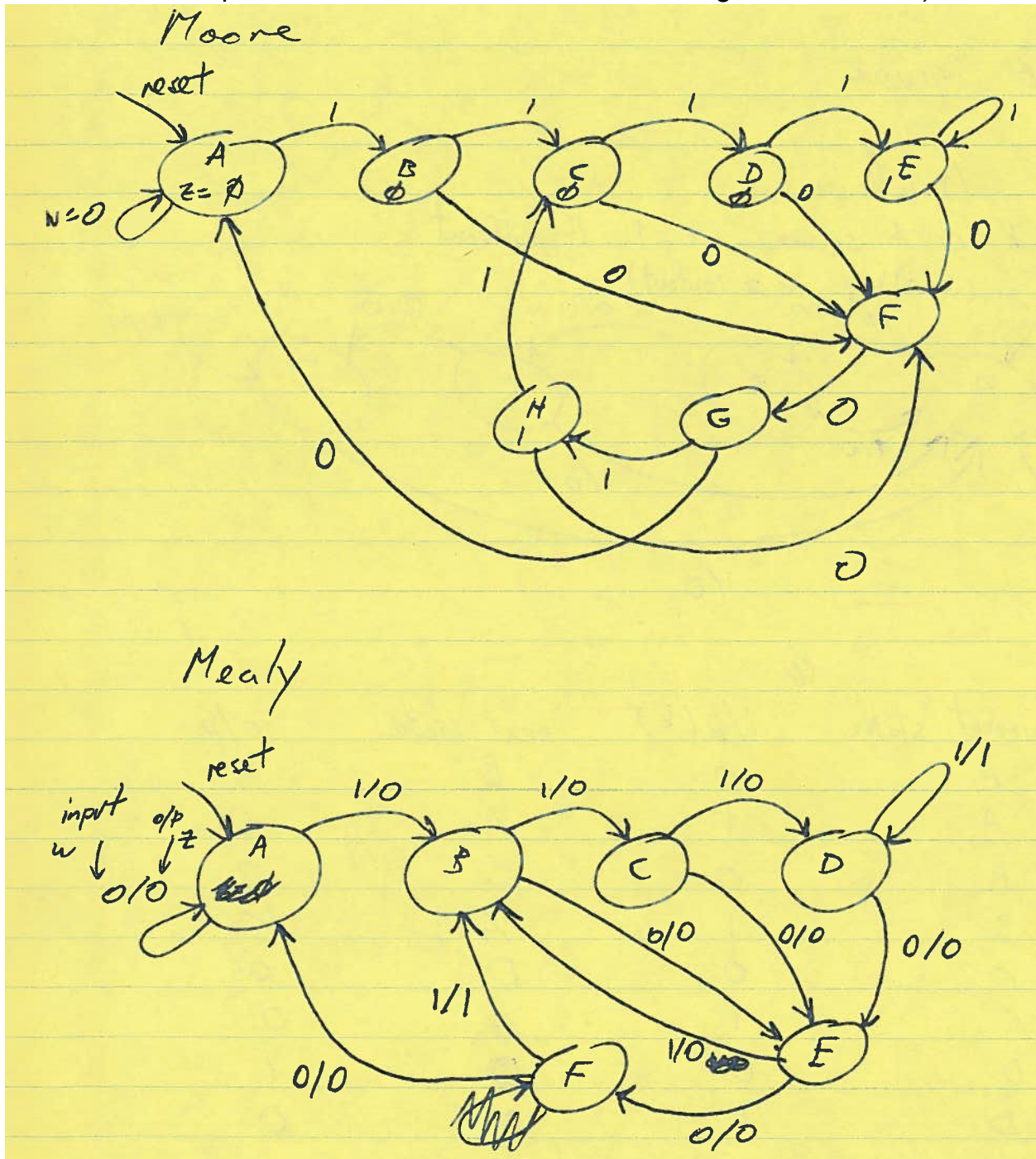
8. 6.3 (Just draw the state transition diagram – no tables please –, label your states in alphabetical order A,B,C, etc. with A being the reset state).



9. 6.5
Ans. in textbook

10. 6.6
Ans. in textbook

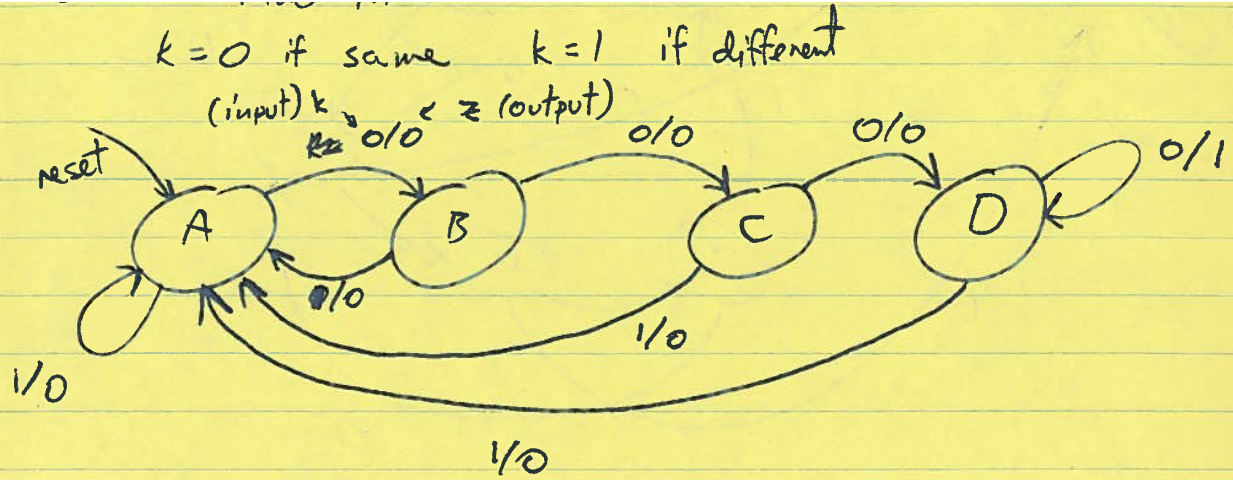11. 6.9 (Use the same labeling approach as for 6.3)



current state	i/p (k)	next state	o/p
A	0	B	0
A	1	A	0
B	0	C	0
B	1	A	0
C	0	D	0
C	1	A	0
D	0	D	1
D	1	A	0

	$S_1 S_0$	
A	00	} mapping to 4 bits states
B	01	
C	10	
D	11	

Mealy State transition & O/P table

S_1	S_0	k	S_1'	S_0'	$Y = Z$
current state			next state		O/P
0	0	0	0	1	0
0	0	1	0	0	0
0	1	0	1	0	0
0	1	1	0	0	0
1	0	0	1	1	0
1	0	1	0	0	0
1	1	0	1	1	1
1	1	1	0	0	0

	$S_1 S_0$			
	00	01	11	10
k	0	0	1	1
	1	0	0	0

$$S_1' = S_0 \bar{k} + S_1 k$$

	$S_1 S_0$			
	00	01	11	10
k	0	1	1	1
	1	0	0	0

$$S_0' = \bar{S}_0 \bar{k} + S_1 k$$

$$Y = S_1 S_0 \bar{k}$$


12. 6.10

```
module prob8_10 (Clock, Resetn, w1, w2, z);
  input Clock, Resetn, w1, w2;
  output reg z;
  reg [2:1] y, Y;
  wire k;
  parameter [2:1] A = 2'b00, B = 2'b01, C = 2'b10, D = 2'b11;

  // Define the next state and output combinational circuits
  assign k = w1 ^ w2;
  always @(k, y)
    case (y)
      A: if (k) begin
           Y = A; z = 0;
         end
        else begin
           Y = B; z = 0;
         end
      B: if (k) begin
           Y = A; z = 0;
         end
        else begin
           Y = C; z = 0;
         end
      C: if (k) begin
           Y = A; z = 0;
         end
        else begin
           Y = D; z = 0;
         end
      D: if (k) begin
           Y = A; z = 0;
         end
        else begin
           Y = D; z = 1;
         end
    endcase

  // Define the sequential block
  always @(negedge Resetn, posedge Clock)
    if (Resetn == 0) y <= A;
    else y <= Y;
endmodule
```

13. 6.14

 

14. 6.15

Ans. in textbook

15. 6.20

present counter state	next counter state	output	input w can be the clock
0	1	0	
1	2	2	
2	3	1	
3	0	3	

map to bits

S ₁ S ₀	S' ₁ S' ₀	Y ₁ Y ₀
0 0	0 1	0 0
0 1	1 0	1 0
1 0	1 1	0 1
1 1	0 0	1 1

$S'_1 = S_1 \oplus S_0$
 $S'_0 = \overline{S_0}$
 $Y_1 = S_0$
 $Y_0 = S_1$

16. 6.23

present state	input	next state	$S_2 S_1 S_0$	w	$S_2' S_1' S_0'$
0	0	0	000	0	000
0	1	1	000	1	001
1	0	1	001	0	001
1	1	2	001	1	010
2	0	2	010	0	010
2	1	3	010	1	011
3	0	3	011	0	011
3	1	4	011	1	100
4	0	4	100	0	100
4	1	5	100	1	101
5	0	5	101	0	101
5	1	0	101	1	000

$S_2 S_1$ / $S_0 w$

00	01	11	10
00		X	1
01		X	1
11	1	X	
10		X	1

 $S_2' = S_2 S_0 + S_2 \bar{w} + S_1 S_0 w$

$S_2 S_1$ / $S_0 w$

00	01	11	10
00	1	X	
01	1	X	
11	1	X	
10	1	X	

 $S_1' = S_1 \bar{S}_0 + S_1 \bar{w} + \bar{S}_2 \bar{S}_1 S_0 w$

$S_2 S_1$ / $S_0 w$

00	01	11	10
00		X	
01	1	1	X
11		X	0
10	1	1	X

 $S_0' = \bar{S}_0 w + S_0 \bar{w}$

output \Rightarrow is just the current state in this simple case

$$[S_2 S_1 S_0] = [Y_2 Y_1 Y_0]$$

17. 6.29

Ans. in textbook

18. 6.30

```
module prob8_30 (Clock, Resetn, D, N, z);
  input Clock, Resetn, D, N;
  output z;
  reg [3:1] y, Y;
  wire [1:0] K;
  parameter [3:1] S1 = 3'b000, S2 = 3'b001, S3 = 3'b010, S4 = 3'b011, S5 = 3'b100;

  // Define the next state combinational circuit
  assign K = {D, N};
  always @(K, y)
    case (y)
      S1: if (K == 2'b00) Y = S1;
          else if (K == 2'b01) Y = S3;
          else if (K == 2'b10) Y = S2;
          else Y = 3'bxxx;
      S2: if (K == 2'b00) Y = S2;
          else if (K == 2'b01) Y = S4;
          else if (K == 2'b10) Y = S5;
          else Y = 3'bxxx;
      S3: if (K == 2'b00) Y = S3;
          else if (K == 2'b01) Y = S2;
          else if (K == 2'b10) Y = S4;
          else Y = 3'bxxx;
      S4: if (K == 2'b00) Y = S1;
          else Y = 3'bxxx;
      S5: if (K == 2'b00) Y = S3;
          else Y = 3'bxxx;
      default: Y = 3'bxxx;
    endcase

  // Define the sequential block
  always @(negedge Resetn, posedge Clock)
    if (Resetn == 0) y <= S1;
    else y <= Y;

  // Define output
  assign z = (y == S4) | (y == S5);

endmodule
```

19. 6.31

```

module prob8_31 (Clock, Resetn, D, N, z);
  input Clock, Resetn, D, N;
  output z;
  reg [3:1] y;
  wire [1:0] K;
  parameter [3:1] S1 = 3'b000, S2 = 3'b001, S3 = 3'b010, S4 = 3'b011, S5 = 3'b100;

  assign K = {D, N};
  // Define the sequential block
  always @(negedge Resetn, posedge Clock)
    if (Resetn == 0) y <= S1;
    else
      case (y)
        S1: if (K == 2'b00) y <= S1;
            else if (K == 2'b01) y <= S3;
            else if (K == 2'b10) y <= S2;
            else y <= 3'bxxx;
        S2: if (K == 2'b00) y <= S2;
            else if (K == 2'b01) y <= S4;
            else if (K == 2'b10) y <= S5;
            else y <= 3'bxxx;
        S3: if (K == 2'b00) y <= S3;
            else if (K == 2'b01) y <= S2;
            else if (K == 2'b10) y <= S4;
            else y <= 3'bxxx;
        S4: if (K == 2'b00) y <= S1;
            else y <= 3'bxxx;
        S5: if (K == 2'b00) y <= S3;
            else y <= 3'bxxx;
        default: y <= 3'bxxx;
      endcase

  // Define output
  assign z = (y == S4) | (y == S5);
endmodule

```

20. 6.40

