



## Chapter 6

### Pipelining and Parallel Processing

Instructor: Prof. Peter Lian  
Department of Electrical  
Engineering & Computer Science  
Lassonde School of Engineering  
York University
  
## Introduction

- Pipelining
  - Pipelining is a set of data processing elements connected in series, where the output of one stage is the input of the next one.
  - Leads to a reduction in the critical path
  - Either increases the clock speed (or sampling speed) or reduces the power consumption at same speed in a DSP system.




# Introduction

- Parallel processing
  - Multiple outputs are computed in parallel in a clock period.
  - The effective sampling speed is increase by the level of parallelism.
  - Can also be used to reduce the power consumption.




# Pipelining vs Parallel

 

## Pipelining
 
### Example of a 3-tap FIR Filter

$$y(n] = a * x(n) + b * x(n-1) + c * x(n-2)$$




The critical path here is two additions  
and one multiplication

$$T_s = 2T_{add} + T_{mul} \quad , \quad f_s = \frac{1}{(2T_{add} + T_{mul})}$$


## How to increase $f_s$ ?

- What if the application requires a faster input rate?
- Pipelining: reduce the effective critical path by introducing pipelining latches along the critical data path.
- Parallel processing: increases the sampling rate by replicating hardware so that several inputs can be processed in parallel and several outputs can be produced at the same time

## 2-Level Pipelining and Parallel

 


# Pipelining

 
 
# Pipelined Implementation

- By introducing 2 additional latches in the filter, the critical path is reduced from  $2T_{add} + T_{mul}$  to  $T_{add} + T_{mul}$ .



Clock	Input	Node 1	Node 2	Node 3	Output
0	$x(0)$	$ax(0)+bx(-1)$	—	—	—
1	$x(1)$	$ax(1)+bx(0)$	$ax(0)+bx(-1)$	$cx(-2)$	$y(0)$
2	$x(2)$	$ax(2)+bx(1)$	$ax(1)+bx(0)$	$cx(-1)$	$y(1)$
3	$x(3)$	$ax(3)+bx(2)$	$ax(2)+bx(1)$	$cx(0)$	$y(2)$

## Pipelining Pros and Cons

- Advantages
  - Could be used to reduce power and/or to increase clock rate (speed)
- Disadvantages
  - Increases number of delay elements (latches or flip-flops)
  - Increases latency (the difference in the availability of the first output data in the pipelined system and the sequential system)

## Pipelining Latches

- The speed of an architecture is limited by the longest path between any 2 latches or between an input and a latch or between a latch and an output or between the input and output
- This longest path or the “critical path” can be reduced by suitably placing the pipelining latches in the architecture.
- The pipelining latches can only be placed across any feed-forward cutset of the graph.

## Definition of Cutset

- **Cutset**: is a set of edges of a graph if removed, the graph becomes disjoint.
- **Feed forward cutset**: a cutset where the data moves in the forward direction on all the edges in the cutset.
- We can place latches on a **feed-forward cutset** without affecting the functionality of the graph.

## Activity 1

In the signal-flow graph (SFG) in Fig. a, the computation time for each node is assumed to be 1 u.t.

- (1) Calculate the critical path computation time.
- (2) The critical path has been reduced to 2 u.t. by inserting 3 extra latches as shown in Fig. b. Is this a valid pipelining? If not, how to get a valid one.

 


Fig. a


 



Fig. b
 
## Transposed FIR Filter SFG

- Reversing the direction of all the edges in a given SFG, and interchanging the input and output preserves the functionality of the system.



## Data Broadcast Structure

 


$T_M + T_a$

## Fine-Grain Pipelining


Multiplication time = 10

Addition time = 2

Critical path = ?

 

## Fine Grain Pipelining

 

## Parallel Processing

## Parallel Processing

- Parallel processing and pipelining techniques are duals each other: if a computation can be pipelined, it can also be processed in parallel. Both of them exploit concurrency available in the computation in different ways.
- Example for parallel FIR system
  - A single-input single-output (SISO) FIR filter can be converted into an multiple-input multiple-output system (MIMO) in order to obtain a parallel processing structure


## Parallel Processing Example

$$y(n) = ax(n) + bx(n-1) + cx(n-2)$$

$$y(3k) = ax(3k) + bx(3k-1) + cx(3k-2)$$

$$y(3k+1) = ax(3k+1) + bx(3k) + cx(3k-1)$$

 
$$y(3k+2) = ax(3k+2) + bx(3k+1) + cx(3k)$$




## Parallel Processing

- Parallel processing system is also called block processing, and the number of inputs processed in a clock cycle is referred to as the block size.
- In the example, at the  $k$ -th clock cycle, 3 inputs  $x(3k)$ ,  $x(3k+1)$ , and  $x(3k+2)$  are processed and 3 samples  $y(3k)$ ,  $y(3k+1)$  and  $y(3k+2)$  are generated at the output.


## Parallel Processing of a Filter

 

## Complete Parallel System

 


## S/P and P/S Converter

 
 
## Parallel Processing

- Why use parallel processing? It increases the hardware.
- There is a limit for the use of pipelining, you may not be able to pipeline a functional unit beyond a certain limit
- Also, I/O usually imposes a bound on the cycle time (communication bound)



**Low Power Design  
Exploring Pipelining and  
Parallel Processing**

## Low Power

- Two important formulas:
  - Power consumption & propagation delay

$$P = C_{total} V_o^2 f$$

$$T_{pd} = \frac{C_{charge} V_o}{k(V_o - V_t)^2}$$

$C_{total}$  is the total capacitance of the circuit,  $V_o$  is the supply voltage.  $C_{charge}$  is the capacitance to be charged/discharged in a single clock cycle.

- Pipelining and parallel processing could be used to minimize power or execution time.


## Pipelining for Low Power

- The power consumption in the original sequential FIR filter

$$P_{seq} = C_{total} V_o^2 f, \quad f = \frac{1}{T_{seq}}$$

- In  $M$ -level pipelining FIR filter, critical path is reduced to  $1/M$  of its original length.

Sequential (critical path):

 


Pipelined: (critical path when  $M=3$ )



- If the same clock speed is maintained, then pipelined circuit can be “slow”.

 
## Pipelining for Low Power

- Goal of traditional pipelining: Maximum performance





## Pipelining for Low Power

- Goal: Low-Power, Fixed Throughput

 

## Slow Circuit → Low Voltage

  

- Lowering Vdd increases delay
- Lowering Vdd improves energy consumption

## Pipelining for Low Power

- In  $M$ -level pipelined filter running at the same clock rate as non-pipelined design, the power consumption is given by:

$$P_{pip} = C_{total} (\beta V_o)^2 f = \beta^2 C_{total} V_o^2 f = \beta^2 P_{seq}, \quad 0 < \beta < 1$$

- How to find  $\beta$ ?

$$T_{seq} = \frac{C_{charge} V_o}{k(V_o - V_t)^2}, \quad T_{pip} = \frac{\frac{C_{charge}}{M} \beta V_o}{k(\beta V_o - V_t)^2}$$


$$T_{seq} = T_{pip} \rightarrow \frac{C_{charge} V_o}{k(V_o - V_t)^2} = \frac{C_{charge} \beta V_o}{kM(\beta V_o - V_t)^2}$$

$$\rightarrow M(\beta V_o - V_t)^2 = \beta(V_o - V_t)^2$$

## Parallel processing

- What happen for  $L$  parallel System?
- Total capacitance increased by  $L$
- Same performance, increase  $T$  by  $L$
- More time to charge  $C_{charge} \rightarrow$  decrease  $V$

Sequential(critical path):

 

## Parallel processing

- The propagation delay of the L-parallel system is

$$LT_{seq} = L \frac{C_{charge} V_o}{k(V_o - V_t)^2}, \quad T_{par} = \frac{C_{charge} \beta V_o}{k(\beta V_o - V_t)^2}$$

$$LT_{seq} = T_{par} \rightarrow L \frac{C_{charge} V_o}{k(V_o - V_t)^2} = \frac{C_{charge} \beta V_o}{k(\beta V_o - V_t)^2}$$

$$\rightarrow L(\beta V_o - V_t)^2 = \beta(V_o - V_t)^2$$


- Power of parallel system is

$$P_{par} = (LC_{total})(\beta V_o)^2 \frac{f}{L} = \beta^2 P_{seq}, \quad 0 < \beta < 1$$

## Examples

- Example of pipelined system
  - Please read textbook for Example 3.4.1 on page 75.
- Example of parallel system
  - Please read the Example 3.4.2 in the textbook on page 77.


## Parallel for Low Power

 

- Critical path delay:
  - $T_{\text{adder}} + T_{\text{comparator}} = 25\text{ns} \rightarrow f_{\text{ref}} = 40\text{MHz}$
- Total capacitance being switched =  $C_{\text{ref}}$
- $V_{\text{dd}} = V_{\text{ref}} = 5\text{V}$
- Power for reference datapath:  $P_{\text{ref}} = C_{\text{ref}} V_{\text{ref}}^2 f_{\text{ref}}$

\*Chandrakasan, IEEE JSSC' 92

## Parallel as a Low Power Tool

 

- The clock rate can be reduced by half with the same throughput  $\rightarrow f_{\text{par}} = f_{\text{ref}}/2$
- $V_{\text{par}} = V_{\text{ref}}/1.7$ ,  $C_{\text{par}} = 2.15C_{\text{ref}}$
- $P_{\text{par}} = (2.15C_{\text{ref}})(V_{\text{ref}}/1.7)^2(f_{\text{ref}}/2) = 0.36P_{\text{ref}}$

## Parallel as a Low Power Tool

Architecture type	Voltage	Area	Power
Simple datapath (no pipelining or parallelism)	5V	1	<b>1</b>
Pipelined datapath	2.9V	1.3	0.39
Parallel datapath	2.9V	3.4	0.36
Pipeline-Parallel	2.0V	3.7	<b>0.2</b>