

Chapter 8

Folding


Instructor: Prof. Peter Lian
Department of Electrical
Engineering & Computer Science
Lassonde School of Engineering
York University

Introduction to Folding

- Folding is a technique to reduce the silicon area by time-multiplexing many algorithm operations into single functional unit.
- The hardware is reduced by a factor of N , the time is increased by the same factor.
- In general, the data on the input of a folded realization is assumed to be valid for N cycles before changing.
- May lead to a large number of registers, thus need to minimize the registers.


A Folding Example

$$y(n) = a(n) + b(n) + c(n)$$

 

Valid for 2
cycles

(a)

 

(b)


Cycle	A	B	E	C	D
0	a(0)	b(0)	a(0)+b(0)	—	—
1	a(0)+b(0)	c(0)	a(0)+b(0)+c(0)	a(0)+b(0)	—
2	a(1)	b(1)	a(1)+b(1)	a(0)+b(0)+c(0)	a(0)+b(0)+c(0)
3	a(1)+b(1)	c(1)	a(1)+b(1)+c(1)	a(1)+b(1)	—
4	a(2)	b(2)	a(2)+b(2)	a(1)+b(1)+c(1)	a(1)+b(1)+c(1)
5	a(2)+b(2)	c(2)	a(2)+b(2)+c(2)	a(2)+b(2)	—
6	a(3)	b(3)	a(3)+b(3)	a(2)+b(2)+c(2)	a(2)+b(2)+c(2)

Folding Transformation

- The objective is to provide a systematic technique for designing control circuits for hardware where several algorithm operations are mapped to the same piece of hardware via time-multiplexing of course.
- The folding transformation starts with a DFG for the algorithm.

Definitions in Folding Transformation

 
- U and V are two nodes in the original DFG.
- U and V are connected via an edge e with a delay $w(e)$, i.e. $U \xrightarrow{w(e)} V$



- Folding factor is N
- Node U (computation): l^{th} iteration is performed at time $Nl + u$
- Node V (computation): l^{th} iteration is performed at time $Nl + v$
- u and v are folding order of the nodes U and V that satisfy $0 \leq u, v \leq N-1$

Definitions in Folding Transformation

 - H_u and H_v are the hardware units used at U and V for performing computation.
- H_u and H_v are pipelined by P_u and P_v stages



Folding Transformation

- The results of the l^{th} iteration of node U is available at $Nl+u+P_u$
- Since there are $w(e)$ delays between U and V, the result of the l^{th} iteration of the node U is used by the $(l+w(e))^{th}$ iteration of the node V, which is executed at $N(l+w(e))+v$.

- The result must be stored for


$$\begin{aligned}D_F(U \xrightarrow{e} V) &= [N(l+w(e))+v] - [Nl+P_u+u] \\ &= Nw(e) - P_u + v - u\end{aligned}$$

Folding Set

- Is an ordered set of operations executed by the same functional unit.
- Each folding set contains N entries (some of which may be null operations)
- The j^{th} position within the folding set is executed during the time partition j
 - For example the folding set $S_1 = \{A_1, 0, A_2\}$ for $N=3$
 - A_1 is performed during the 0^{th} time partition $S_1|0$, while A_2 is done in the 2^{nd} time partition $S_1|2$
 - Due to null operation in position 1, the function unit is not used at time instances $3l+1$
- Folding set is obtained using a scheduling and allocation algorithm

Writing Folding Equations
 
$$D_F(U \xrightarrow{e} V) = Nw(e) - P_u + v - u$$




Folded Biquad Filter

Nodes 1, 2, 3, 4 are adders
Nodes 5, 6, 7, 8 are multipliers

$$D_F(U \xrightarrow{e} V) = Nw(e) - P_u + v - u$$

- $D_F(1 \rightarrow 2) = 4(1) - 1 + 1 - 3 = 1$
- $D_F(1 \rightarrow 5) = 4(1) - 1 + 0 - 3 = 0$
- $D_F(1 \rightarrow 6) = 4(1) - 1 + 2 - 3 = 2$
- $D_F(1 \rightarrow 7) = 4(1) - 1 + 3 - 3 = 3$
- $D_F(1 \rightarrow 8) = 4(2) - 1 + 1 - 3 = 5$
- $D_F(3 \rightarrow 1) = 4(0) - 1 + 3 - 2 = 0$
- $D_F(4 \rightarrow 2) = 4(0) - 1 + 1 - 0 = 0$
- $D_F(5 \rightarrow 3) = 4(0) - 2 + 2 - 0 = 0$
- $D_F(6 \rightarrow 4) = 4(1) - 2 + 0 - 2 = 0$
- $D_F(7 \rightarrow 3) = 4(1) - 2 + 2 - 3 = 1$
- $D_F(8 \rightarrow 4) = 4(1) - 2 + 0 - 1 = 1.$

 

Folding Condition

- For a folded system to be realizable, $D_F \geq 0$ must hold for all of the edges in the DFG.
- What if some of the D_F 's are negative?
 - Of course we can not implement it.
- We can apply retiming to the original graph to get a valid D_F 's
- Recall, retiming equation $U \rightarrow V$

$$w_r(e) = w(e) + r(V) - r(U) \geq 0$$

Retiming for Folding

$D'_F(U \xrightarrow{e} V)$ is the delays in the folded retimed graph

$$D_F(U \xrightarrow{e} V) = Nw(e) - P_u + v - u$$

$$D'_F(U \xrightarrow{e} V) = N(w(e) + r(V) - r(U)) - P_u + v - u$$

$$D'_F(U \xrightarrow{e} V) = Nw(e) - P_u + v - u + Nr(V) - Nr(U)$$

$$D'_F(U \xrightarrow{e} V) = D_F(U \xrightarrow{e} V) + Nr(V) - Nr(U) \geq 0$$

$$r(U) - r(V) \leq \frac{D_F(U \xrightarrow{e} V)}{N}$$


$$r(U) - r(V) \leq \left\lceil \frac{D_F(U \xrightarrow{e} V)}{N} \right\rceil$$

Retiming for Folding

- We can use the techniques in Chapter 4 to solve for retiming.
- Then we fold the retimed DFG

Activity 1

 Given the biquad filter below, (1) find folding equations, (2) can it be folded? If not, retiming it.



Register Minimization


Registers Minimization Techniques

- The objective is to minimize the number of registers in the implementation of a DSP algorithm.
- Techniques involved
 - Life time analysis
 - Data allocation using forward-backward register allocation
 - Register minimization in folded architecture

Life Time Analysis


- A data sample (variable) is alive from the time it is produced, until the time it is consumed (dead).
- During that time, the variable is stored in a register.
- The maximum number of live variables at any time is the minimum number of registers required for the implementation.
- We use the convention that the variable is not alive during the cycle it is produced in, and alive during the cycle it is consumed in.

Linear Lifetime Chart

 

 Example

$$\begin{bmatrix} a & b & c \\ d & e & f \\ g & h & i \end{bmatrix} \xrightarrow{\text{Transpose}} \begin{bmatrix} a & d & g \\ b & e & h \\ c & f & i \end{bmatrix}$$



Example

Output time with zero latency


$$T_{diff} = T_{zout} - T_{input}$$

Sample	T_{input}	T_{zout}	T_{diff}	T_{output}	Life
a	0	0	0	4	0 → 4
b	1	3	2	7	1 → 7
c	2	6	4	10	2 → 10
d	3	1	-2	5	3 → 5
e	4	4	0	8	4 → 8
f	5	7	2	11	5 → 11
g	6	2	-4	6	6 → 6
h	7	5	-2	9	7 → 9
i	8	8	0	12	8 → 12

$$+T_{lat} = -(-4)$$


The latency, T_{lat} , is the most negative value of T_{diff}

Example

 

Circular Life-Time Chart

 - Useful to represent the periodic nature of the DSP programs
- The point marked l ($0 \leq l \leq N-1$) represents the time partition l and all time instances $Nl+i$
- Variable produced during time unit j and consumed during time unit k is shown to be alive from $j+1$ to k
- The numbers in the bracket in the adjacent figure correspond to the number of live variable at each time partition.



Data Allocation

- Step 1: Determine the min. number of registers using lifetime analysis
- Step 2: Input each variable at the time step corresponding to the beginning of its lifetime. If multiple variables are input in a given cycle, use multiple registers such that the variable with longest lifetime is allocated to the initial register.
- Step 3: Each variable is allocated in a forward manner until it is dead or reaches the last register

Data Allocation

- Step 4: Since the allocation is periodic, the allocation of the current iteration also repeats itself after N .
- Step 5: For variables that reach the last register and not yet dead, the remaining life period is calculated, and these variables are allocated to a register in a backward manner on a first-come first-served basis. (if more than one, choose one that has been allocated backward before, then forward again and so on).
- Step 6: Repeat steps 4 and 5 until the allocation is complete.

Data Allocation Example

cycle	input	R1	R2	R3	R4	output
0	a					
1	b	a				
2	c	b	a			
3	d	c	b	a		
4	e	d	c	b	a	a
5	f	e	d	c	b	d
6	g	f	e	d	c	g
7	h	f	e	d	c	
8	i	h	f	e	d	e
9		i	h	f	e	h
10			i	h	f	
11				i	h	
12					i	i

Sample

a
b
c
d
e
f
g
h
i

Life period

0→4
1→7
2→10
3→5
4→8
5→11
6→6
7→9
8→12

Note: Hashing is done to avoid conflict during backward allocation

Data Allocation Example

Sample

a
b
c
d
e
f
g
h
i


Life period

0→4
1→7
2→10
3→5
4→8
5→11
6→6
7→9
8→12

Note: Hashing is done to avoid conflict during backward allocation

cycle	input	R1	R2	R3	R4	output
0	a					
1	b	a				
2	c	b	a			
3	d	c	b	a		
4	e	d	c	b	a	a
5	f	e	d	c	b	d
6	g	f	e	d	c	g
7	h	c	f	e	b	b
8	i	h	c	f	e	e
9		i	h	c	f	h
10			i	h	c	c
11				i	h	f
12					i	i

Synthesized Architecture

 

cycle	input	R1	R2	R3	R4	output
0	a					
1	b	a				
2	c	b	a			
3	d	c	b	a		
4	e	d	c	b	a	a
5	f	e	d	c	b	d
6	g	f	e	d	c	g
7	h	c	f	e	b	b
8	i	h	c	f	e	e
9		i	h	c	f	h
10			i	f	c	c
11				i	f	f
12					i	i

Activity 2

Given the linear lifetime chart below, (1) derive the data allocation using forward-backward register allocation; (2) synthesis the architecture.


cycle	a_0	b_0	c_0	# live
0				0
1	█			1
2	█	█		2
3	█	█	█	2
4	○	█	█	2
5		█	█	2
6			█	2+0=2
7		○	○	2+1=3

Register Minimization for Folded Architecture

- Step 1: Perform retiming for folding
- Step 2: Write the folding equations
- Step 3: Use the folding equations to construct a lifetime table
- Step 4: Draw the lifetime chart and determine the minimum number of registers
- Step 5: Perform forward-backward register allocation
- Step 6: Draw the folded architecture that uses the minimum number of registers

 Example: Biquad Filter

- Consider the Biquad filter example presented in slide 10.



- Steps 1 & 2 have already been done.

Step 3: Construct a lifetime table

Node U produces data at time $u + P_u : T_{input} = u + P_u$,

T_{out} for node $U = u + P_u + \max_V \{D_F(U \rightarrow V)\}$

$$D_F(U, V) = Nw(e) - P_u + v - u$$

Example: Node 1 is created at time 4 and consumed at $4 + \max(1, 0, 2, 3, 5) = 9$

$$D_F(1 \rightarrow 2) = 4(1) - 1 + 1 - 3 = 1$$

$$D_F(1 \rightarrow 5) = 4(1) - 1 + 0 - 3 = 0$$

$$D_F(1 \rightarrow 6) = 4(1) - 1 + 2 - 3 = 2$$

$$D_F(1 \rightarrow 7) = 4(1) - 1 + 3 - 3 = 3$$

$$D_F(1 \rightarrow 8) = 4(2) - 1 + 1 - 3 = 5$$

$$D_F(3 \rightarrow 1) = 4(0) - 1 + 3 - 2 = 0$$

$$D_F(4 \rightarrow 2) = 4(0) - 1 + 1 - 0 = 0$$

$$D_F(5 \rightarrow 3) = 4(0) - 2 + 2 - 0 = 0$$


$$D_F(6 \rightarrow 4) = 4(1) - 2 + 0 - 2 = 0$$

$$D_F(7 \rightarrow 3) = 4(1) - 2 + 2 - 3 = 1$$

$$D_F(8 \rightarrow 4) = 4(1) - 2 + 0 - 1 = 1$$

Node	$T_{input} \rightarrow T_{output}$
1	4 → 9
2	-----
3	3 → 3
4	1 → 1
5	2 → 2
6	4 → 4
7	5 → 6
8	3 → 4

Step 4: Construct lifetime chart

 


Synthesize

- To synthesize the architecture, which is shown in the previous slide, let's build partial architecture by considering each edge based on the folding equations.
- The final architecture is the combination of these partial architectures.

$$\begin{aligned}
 D_F(1 \rightarrow 2) &= 4(1) - 1 + 1 - 3 = 1 \\
 D_F(1 \rightarrow 5) &= 4(1) - 1 + 0 - 3 = 0 \\
 D_F(1 \rightarrow 6) &= 4(1) - 1 + 2 - 3 = 2 \\
 D_F(1 \rightarrow 7) &= 4(1) - 1 + 3 - 3 = 3 \\
 D_F(1 \rightarrow 8) &= 4(2) - 1 + 1 - 3 = 5 \\
 D_F(3 \rightarrow 1) &= 4(0) - 1 + 3 - 2 = 0 \\
 D_F(4 \rightarrow 2) &= 4(0) - 1 + 1 - 0 = 0 \\
 D_F(5 \rightarrow 3) &= 4(0) - 2 + 2 - 0 = 0 \\
 D_F(6 \rightarrow 4) &= 4(1) - 2 + 0 - 2 = 0 \\
 D_F(7 \rightarrow 3) &= 4(1) - 2 + 2 - 3 = 1 \\
 D_F(8 \rightarrow 4) &= 4(1) - 2 + 0 - 1 = 1.
 \end{aligned}$$


1 → 2 delay 1 (Adder to adder)

 - N1 is produced at time 0 ($4l+0$) needed by N2 at time 1 (a delay of 1)
- An edge from R1 (where the result will be available after 1 time unit) to node 2 (adder) that switches at time $4l+1$
- Also, input is switched at $4l+3$ and output at $4l+2$




1 → 5 delay 0 (adder to multiplier)

 - created at 0 consumed at 0
- A path from output of adder to input of multiplier switches at $4l+0$




1 → 6 (adder to multiplier)

 - N1 produces at time 0, needed after a delay of 2 at multiplier at 2
- Need a switch to move it from adder to R1 at 0, R1 to R2 at 1, R2 to multiplier at 2




1 → 7 delay of 3 (A to M)

 - N1 produced at 0, needed after 3 at 3
- We need a switch to go from adder to R1 at 0, R1 → R2 at 1, R2 → R2 at 2, R2 → multiplier at 3




1 → 8 delay of 5 (A to M)

 - N1 produces result at 0, needed after 5 at multiplier $4I+1$
- Need a switch to go from Adder to R1 at 0, R1 → R2 at 1, R2 → R2 at 2, R2 → R2 at 3, R2 → R2 at 4 ($4I+0$), R2 → Multiplier at 5 ($4I+1$)




3 → 1 delay of 0 (A to A)

 - N3 (adder) produces result at 3, needed at 3 at adder




4 → 2 delay of 0 (A to A)

 - N4 produces result at 1, needed at adder at 1 no delay
- Switch from output of adder to input of adder with no delay at 1




5 → 3 delay of 0 (M to A)

 - N5 produces at 2, needed at adder with no delay
- A switch from output of multiplier to input of adder at 2




6 → 4 delay of 0 (M to A)

 - N6 produces at 4 i.e. $4l+0$, needed with no delay at adder
- A switch from output of multiplier to input of adder at 0




7 → 3 delay of 1 (M to A)

 - N7 produces at 5, i.e. $4l+1$, needed after 1 delay at adder
- A switch from multiplier to R1 at 1, R1 → adder at 2



8 → 4 delay of 1 (M to A)

 - N8 produces at 3 needed after one delay to input of adder
- A switch from Multiplier → R1 at 3 and R1 → adder at 0



Final structure

- Superimposing the switches produces the final architecture
- Note that constants a,b,c,d are muxed into multiplier at {0,2,3,1}

