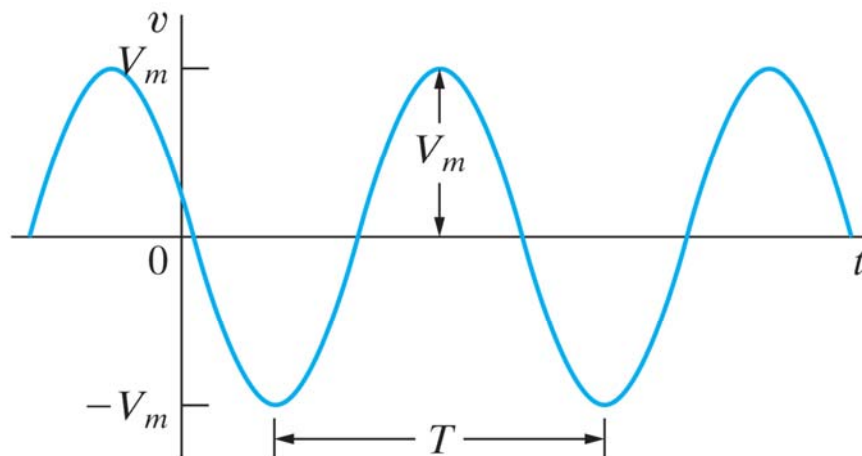


Chapter Objective


- Understanding phasor concept and be able to perform phasor transform and inverse phasor transform.
- Be able to transform a circuit with sinusoidal source into the frequency domain using phasor transform
- Know how to use circuits analysis techniques to solve circuits in the frequency domain.
- Be able to use phasor in analyzing circuits with ideal transformers.

Figure 9.1 A sinusoidal voltage.




Copyright ©2015 Pearson Education, All Rights Reserved

Figure 9.2 The sinusoidal voltage from Fig. 9.1 shifted to the right when $\phi = 0$.

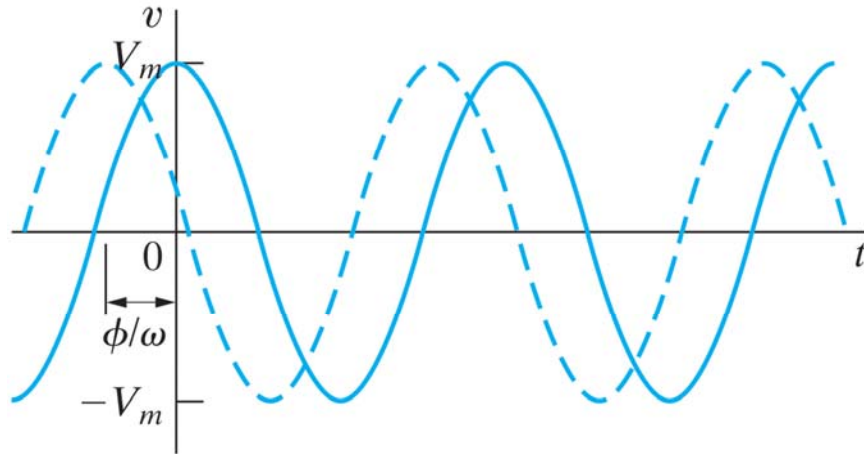



Copyright ©2015 Pearson Education, All Rights Reserved

Figure 9.3 Periodic triangular current.

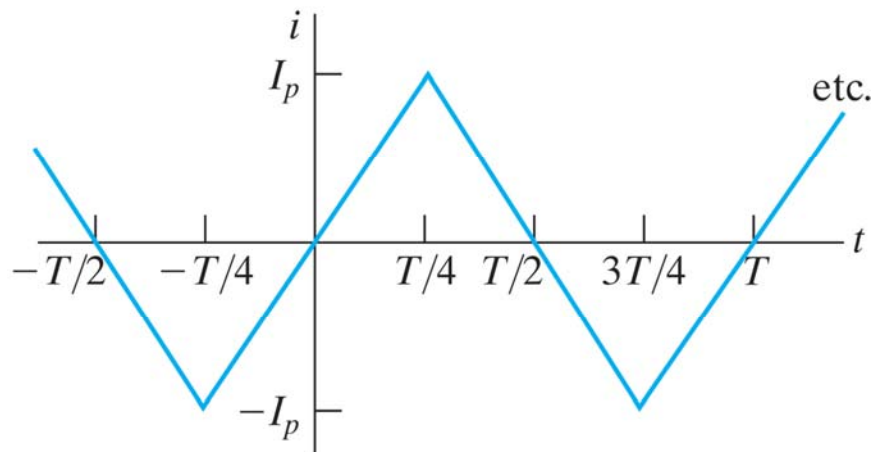

Copyright ©2015 Pearson Education, All Rights Reserved

Figure 9.4 i^2 versus t .

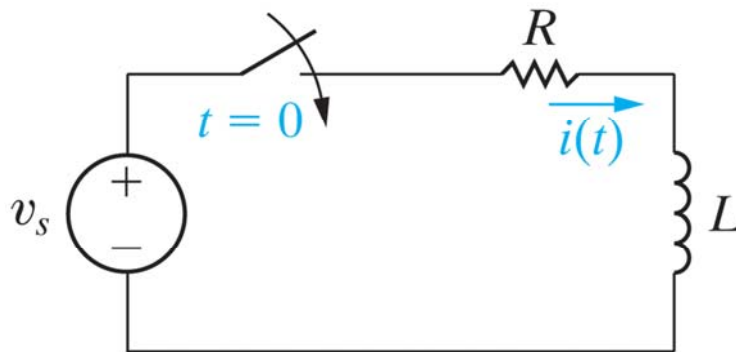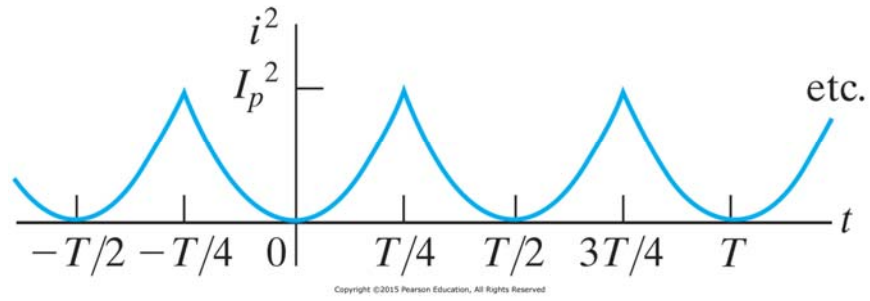

$$L \frac{di}{dt} + iR = V_m \cos(\omega t + \phi)$$

$$i = \frac{-V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\phi - \theta) e^{-(R/L)t} + \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta)$$

RMS Values

- Why RMS

$$V_{rms} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} V_m^2 \cos^2(\omega t + \phi) dt}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

The Phasor

- The phasor is a complex number that carries the amplitude and phase angle information of a sinusoidal function.
- Euler's identity $e^{\pm j\theta} = \cos \theta \pm j \sin \theta$



$$\cos \theta = \Re\{e^{j\theta}\}$$

$$\sin \theta = \Im\{e^{j\theta}\}$$

$$v = V_m \cos(\omega t + \phi)$$

$$v = \Re\{V_m e^{j\phi} e^{j\omega t}\}$$

$$Ae^{j\phi} = A\angle\phi^\circ$$

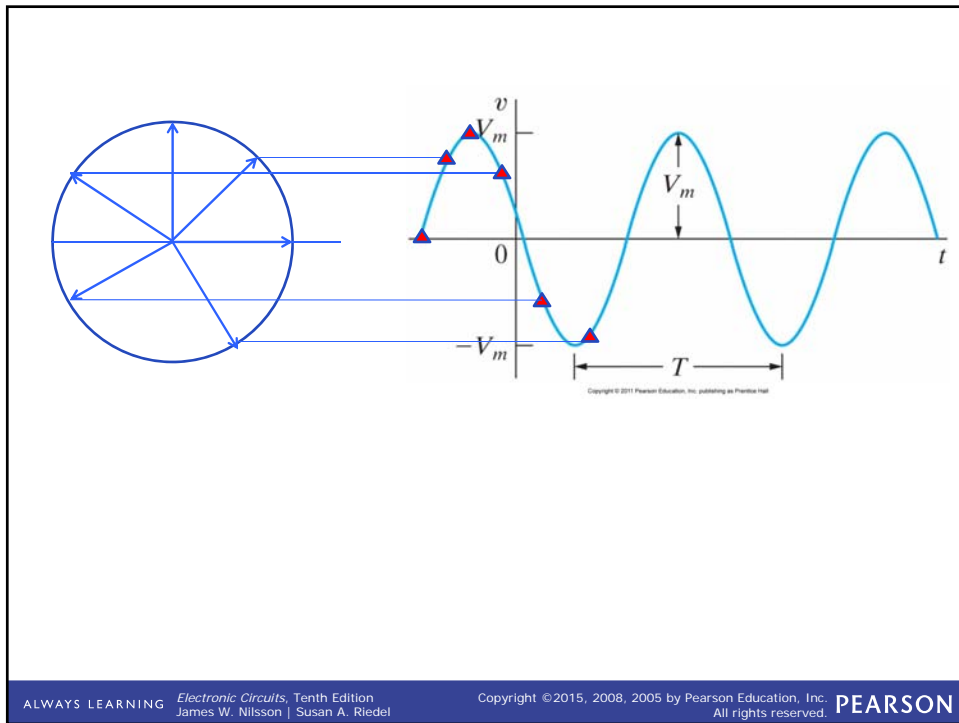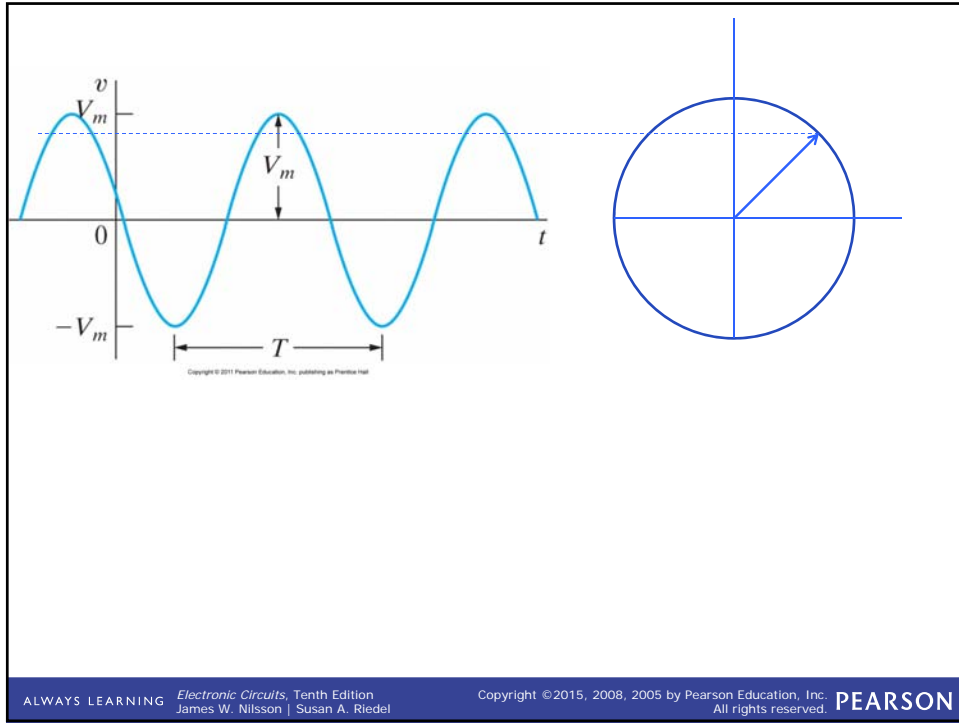

The inductor

$$v = L \frac{di}{dt}$$

$$v = V_m \cos(\omega t)$$

$$di = \frac{1}{L} V_m \cos(\omega t) dt$$


$$i = \frac{1}{L} V_m \int \cos(\omega t) dt$$

$$i = \frac{V_m}{\omega L} \sin(\omega t) = \frac{V_m}{\omega L} \cos(\omega t - \frac{\pi}{2})$$

$$I = \frac{V_m}{\omega L} e^{-j\pi/2} = \frac{V_m}{\omega L} \angle -\pi/2$$

$$Z = \frac{v}{i} = \omega L \angle \pi/2 = j\omega L$$

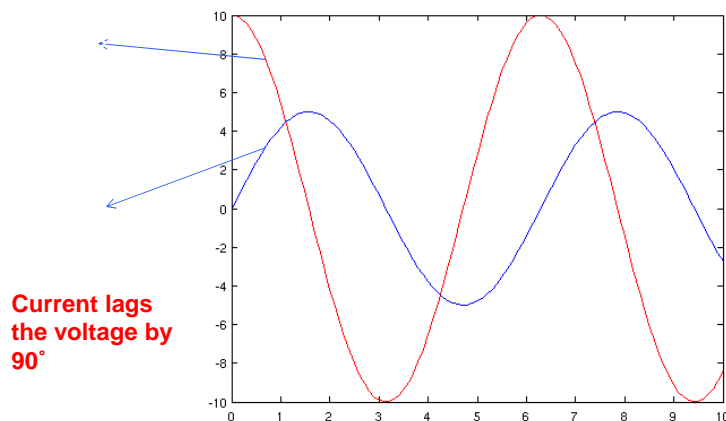A plot showing the phase relationship between the current and voltage at the terminals of an inductor



The Capacitor

$$i = C \frac{dv}{dt}$$

$$v = V_m \cos(\omega t)$$


$$i = CV_m \frac{d}{dt} \cos(\omega t)$$

$$i = -C\omega V_m \sin(\omega t) = \omega CV_m \cos\left(\omega t + \frac{\pi}{2}\right)$$


$$I = \omega CV_m e^{j\pi/2} = \omega CV_m \angle \pi/2$$

$$Z = \frac{v}{i} = \frac{1}{\omega C} \angle -\pi/2 = \frac{-j}{\omega C} = \frac{1}{j\omega C}$$

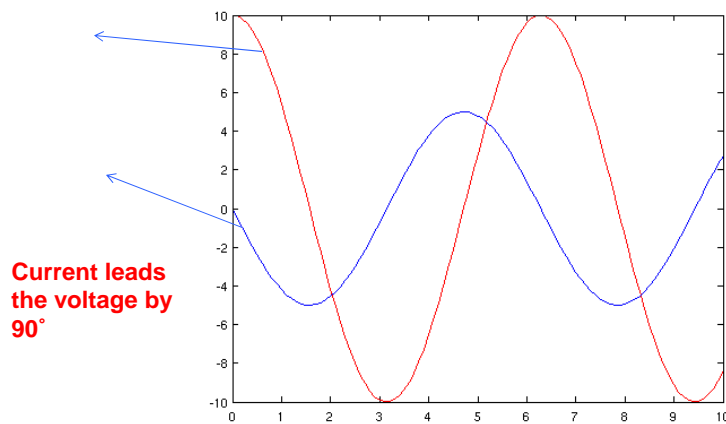A plot showing the phase relationship between the current and voltage at the terminals of a capacitor



Adding Complex Numbers

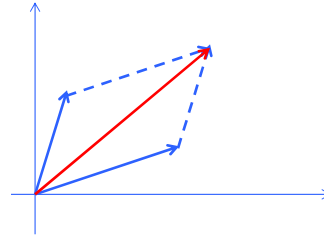


Multiplication

$$\begin{array}{r} \times \quad \begin{array}{l} x_1 + jy_1 \\ x_2 + jy_2 \\ \hline \end{array} \\ (x_1 x_2 - y_1 y_2) + j(x_1 y_2 + x_2 y_1) \end{array}$$

$$A_1 \angle \theta_1 \times A_2 \angle \theta_2 = A_1 A_2 \angle \theta_1 + \theta_2$$

TABLE 9.1 Impedance and Reactance Values


Circuit Element	Impedance	Reactance
Resistor	R	—
Inductor	$j\omega L$	ωL
Capacitor	$j(-1/\omega C)$	$-1/\omega C$

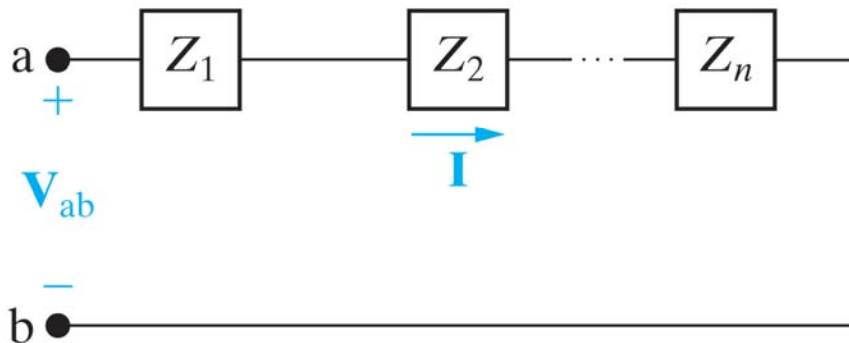Figure 9.14 Impedances in series.

Copyright ©2015 Pearson Education, All Rights Reserved

Figure 9.15 The circuit for Example 9.6.

$$v_s = 700 \cos(5000t + 30^\circ)$$

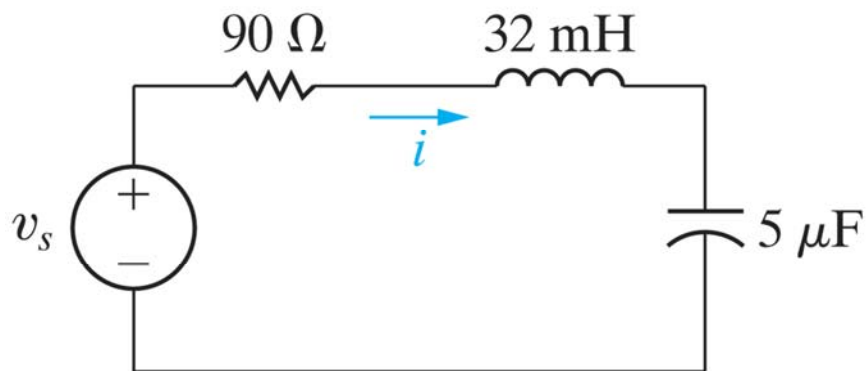


Copyright ©2015 Pearson Education, All Rights Reserved

ALWAYS LEARNING *Electronic Circuits*, Tenth Edition
James W. Nilsson | Susan A. Riedel

Copyright ©2015, 2008, 2005 by Pearson Education, Inc.
All rights reserved. PEARSON

Figure 9.16 The frequency-domain equivalent circuit of the circuit shown in Fig. 9.15.

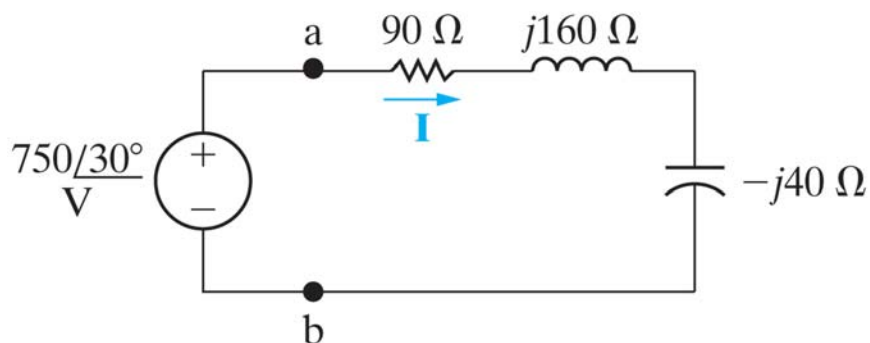

Copyright ©2015 Pearson Education, All Rights Reserved


ALWAYS LEARNING *Electronic Circuits*, Tenth Edition
James W. Nilsson | Susan A. Riedel

Copyright ©2015, 2008, 2005 by Pearson Education, Inc.
All rights reserved. PEARSON

TABLE 9.2 Admittance and Susceptance Values

Circuit Element	Admittance (Y)	Susceptance
Resistor	G (conductance)	—
Inductor	$j(-1/\omega L)$	$-1/\omega L$
Capacitor	$j\omega C$	ωC


Figure 9.17 Impedances in parallel.

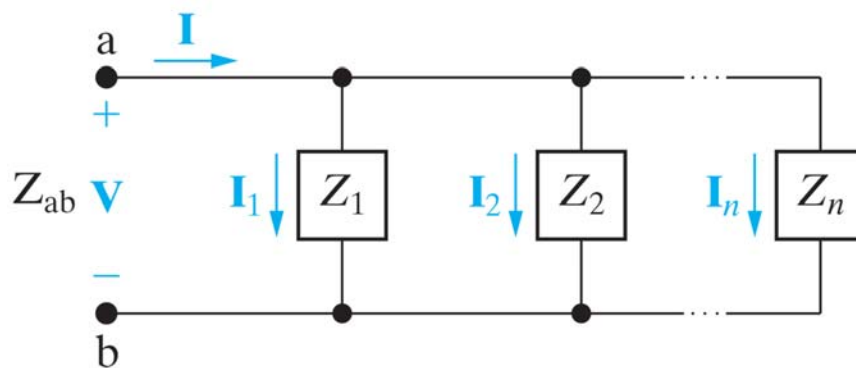

Copyright ©2015 Pearson Education, All Rights Reserved


Example

$$i_s = 8 \cos 200,000t$$

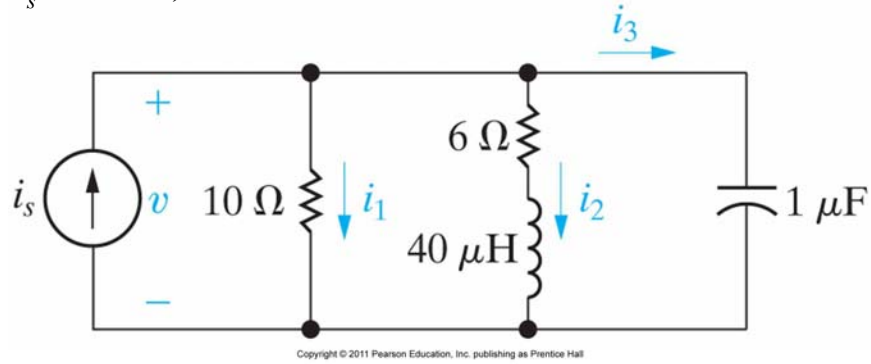


Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Example

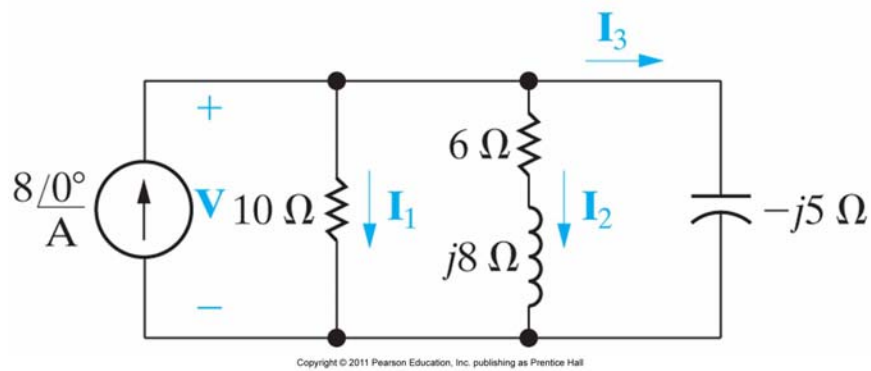


Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Figure 9.20 The delta-to-wye transformation.

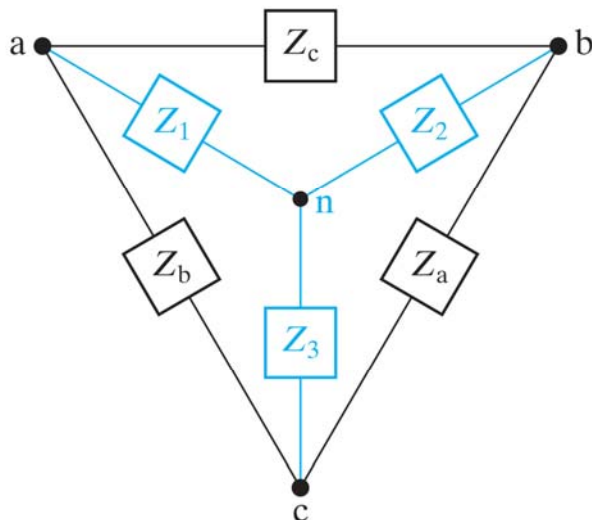


Copyright ©2015 Pearson Education, All Rights Reserved

Figure 9.21 The circuit for Example 9.8.

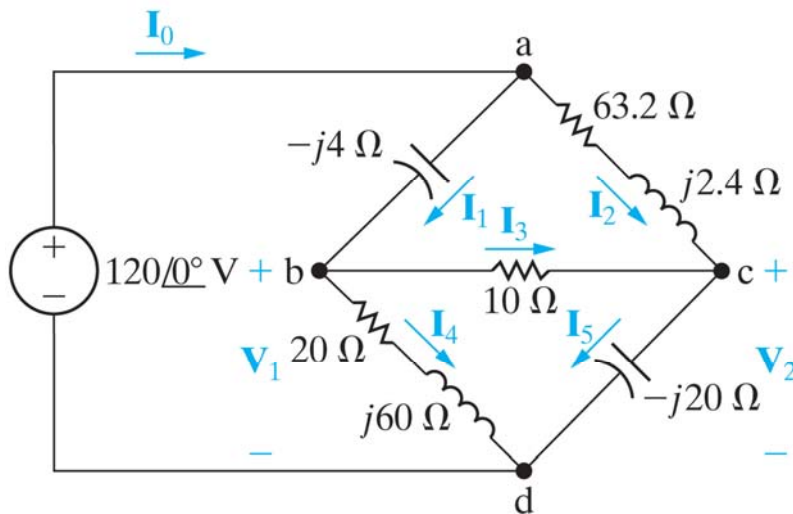


Copyright ©2015 Pearson Education, All Rights Reserved

Figure 9.22 The circuit shown in Fig. 9.21, with the lower delta replaced by its equivalent wye.

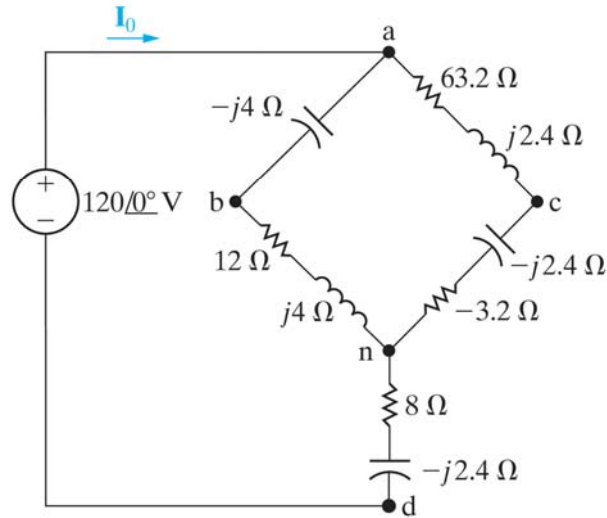

Copyright ©2015 Pearson Education, All Rights Reserved

Figure 9.23 A simplified version of the circuit shown in Fig. 9.22.

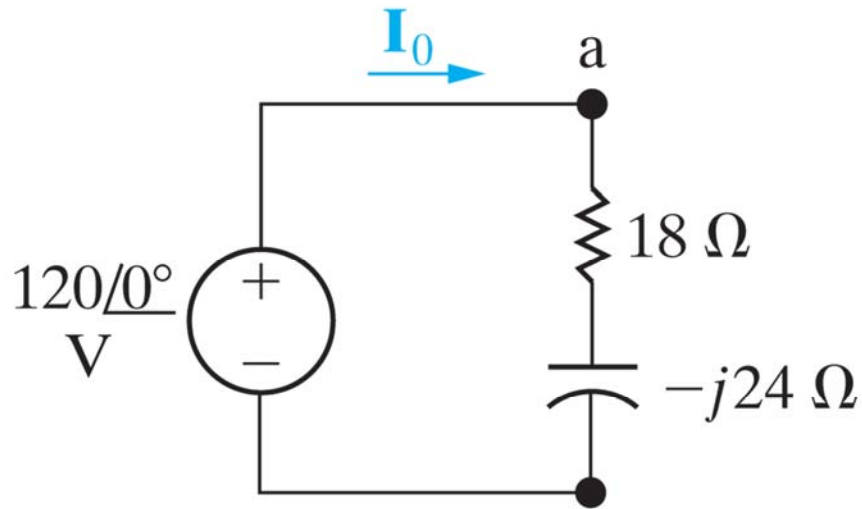

Copyright ©2015 Pearson Education, All Rights Reserved

Figure 9.24 A source transformation in the frequency domain.

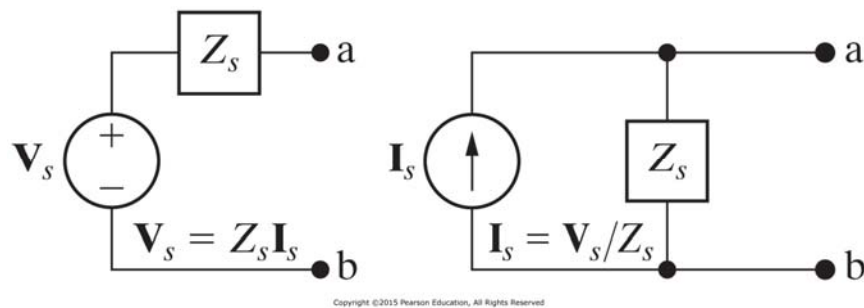


Figure 9.25 The frequency-domain version of a Thévenin equivalent circuit.



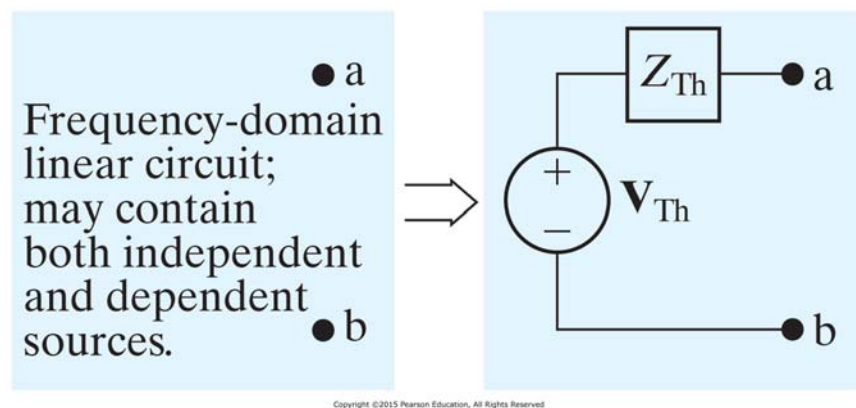


Figure 9.26 The frequency-domain version of a Norton equivalent circuit.

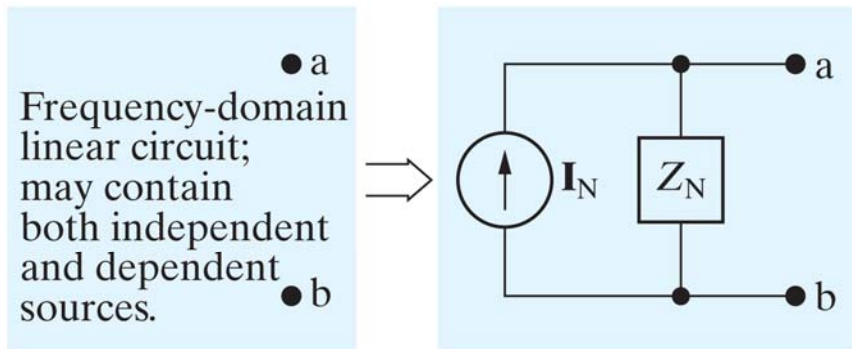


Copyright ©2015 Pearson Education, All Rights Reserved

Figure 9.30 The circuit for Example 9.10.

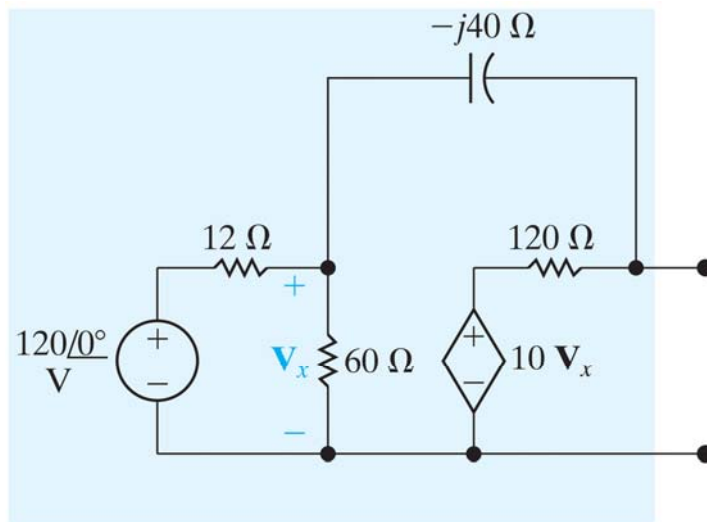


Copyright ©2015 Pearson Education, All Rights Reserved

Figure 9.31 A simplified version of the circuit shown in Fig. 9.30.

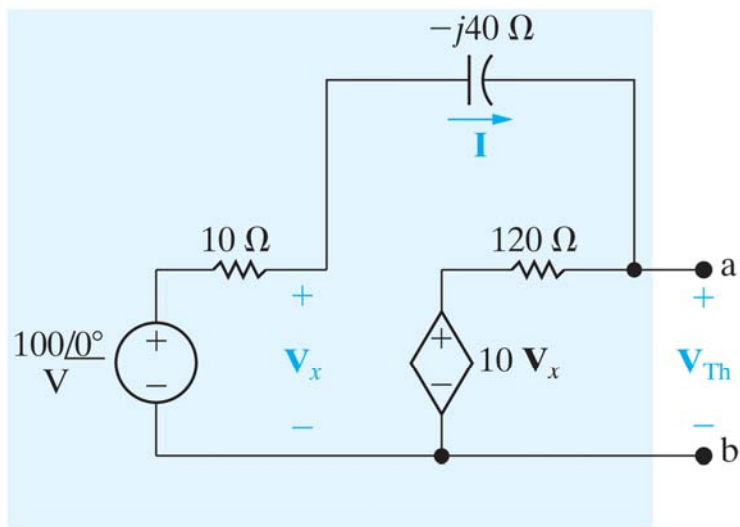


Copyright ©2015 Pearson Education, All Rights Reserved

Figure 9.32 A circuit for calculating the Thévenin equivalent impedance.

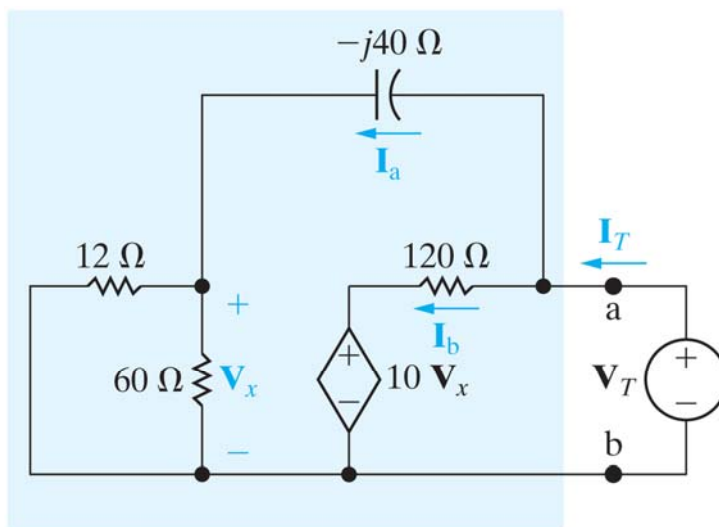


Copyright ©2015 Pearson Education, All Rights Reserved

Figure 9.33 The Thévenin equivalent for the circuit shown in Fig. 9.30.

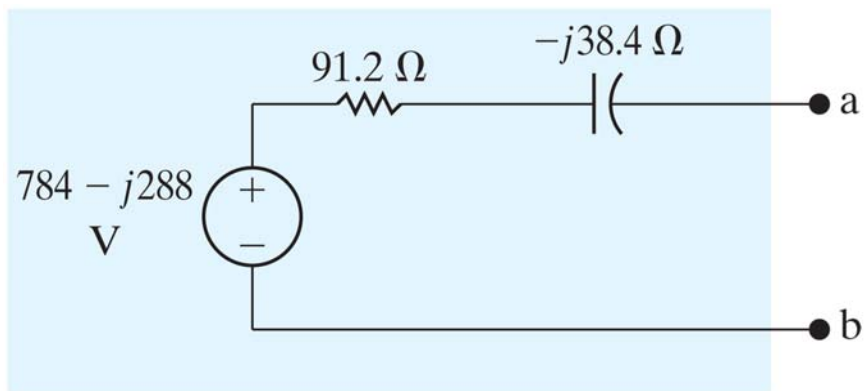


Copyright ©2015 Pearson Education, All Rights Reserved

Figure 9.38 The frequency domain circuit model for a transformer used to connect a load to a source.

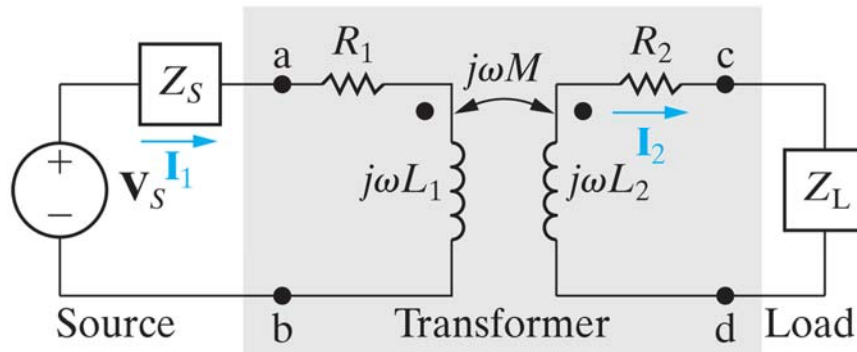

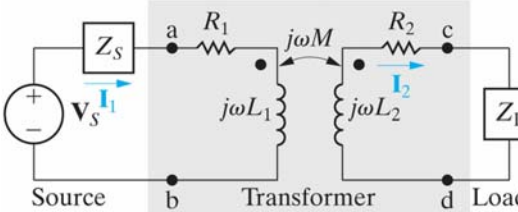Copyright ©2015 Pearson Education, All Rights Reserved



Copyright © 2011 Pearson Education, Inc. publishing as Pearson Hall

$V_s = I_1(Z_s + R_1 + j\omega L_1) - I_2 j\omega M$
 $0 = -j\omega M I_1 + I_2(R_2 + j\omega L_2 + Z_L)$

$j\omega M I_1 = I_2(R_2 + j\omega L_2 + Z_L)$

$I_2 = \frac{j\omega M I_1}{(R_2 + j\omega L_2 + Z_L)}$

$Z_{11} = Z_s + R_1 + j\omega L_1$
 $Z_{22} = Z_L + R_2 + j\omega L_2$


$I_1 = \frac{Z_{22}}{Z_{11} Z_{22} + \omega^2 M^2} V_s$

$\frac{V_2}{I_1} = Z_{total} = Z_{11} + \frac{\omega^2 M^2}{Z_{22}}$

Impedance in the primary loop Reflected impedance

ALWAYS LEARNING *Electronic Circuits, Tenth Edition*
 James W. Nilsson | Susan A. Riedel

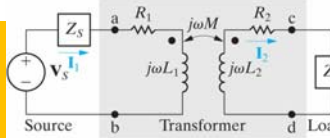Copyright © 2015, 2008, 2005 by Pearson Education, Inc. All rights reserved. **PEARSON**



Copyright © 2011 Pearson Education, Inc. publishing as Pearson Hall

$Z_{reflected} = \frac{\omega^2 M^2}{Z_{22}}$

$Z_{reflected} = \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L}$

$Z_{reflected} = \frac{\omega^2 M^2}{R_2 + j\omega L_2 + R_L + j\omega X_L}$

$Z_{reflected} = \frac{\omega^2 M^2}{(R_2 + R_L) + j\omega(L_2 + X_L)}$

$Z_{reflected} = \frac{\omega^2 M^2}{|Z_{22}|^2} [(R_2 + R_L) - j\omega(L_2 + X_L)]$

ALWAYS LEARNING *Electronic Circuits, Tenth Edition*
 James W. Nilsson | Susan A. Riedel

Copyright © 2015, 2008, 2005 by Pearson Education, Inc. All rights reserved. **PEARSON**

Figure 9.39 The frequency-domain equivalent circuit for Example 9.13.

