

ENG2200

Electric Circuits

Chapter 4


Techniques for Circuit Analysis

Objectives


- Understand and being able to use node-voltage and mesh-current methods to solve a circuit.
- Understand source transformation and being able to use it to solve a circuit.
- Understand the concept of Thevenin and Norton equivalent circuits and being able to construct them for any circuit.
- Know the condition for maximum power transfer to a resistive load, and being able to calculate the value of the load resistor that achieves that.

Terminology



- **Node:** A point that connects two or more circuit elements.
- **Essential node:** A node where 3 or more circuit elements join.
- **Path:** A trace of adjoining basic elements with no element included twice.
- **Branch:** A path that connects two nodes.
- **Essential path:** A path which connects two essential nodes without passing through an essential node.
- **Loop:** A path whose last node is the same as the first
- **Mesh:** A loop that does not enclose any other loops
- **Planar circuit:** A circuit that could be drawn on a plane with no crossing branches.

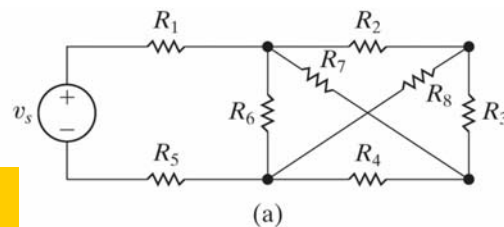

Planar Circuit (same circuit).

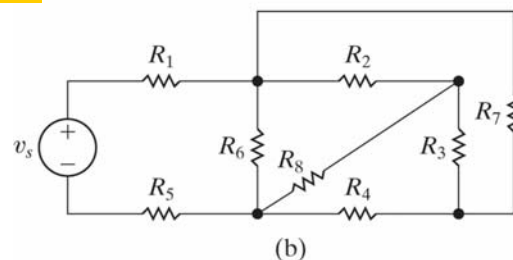


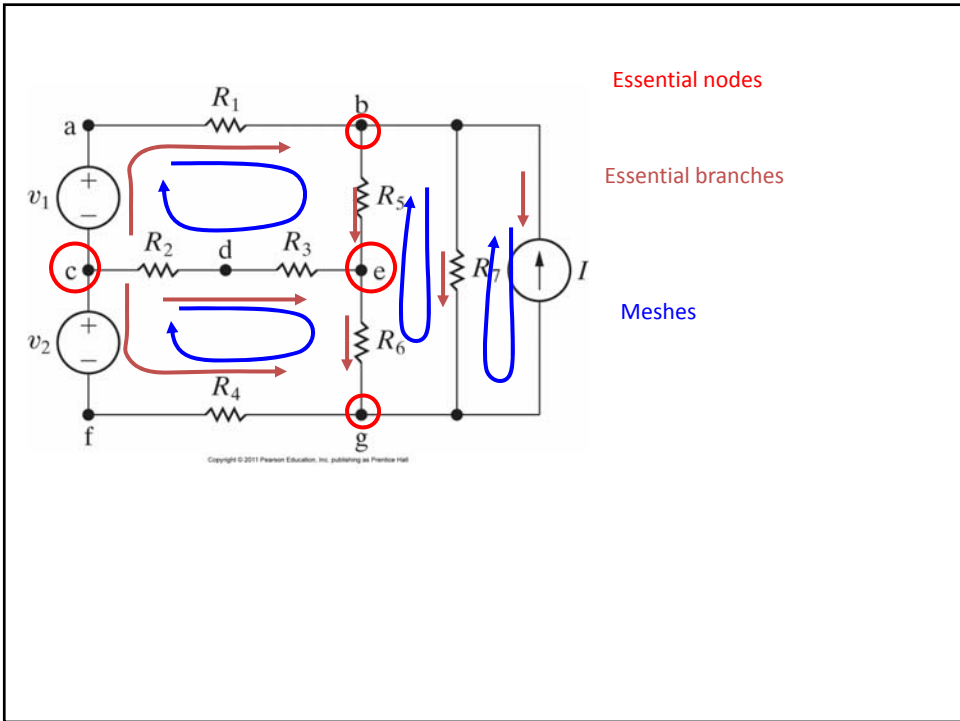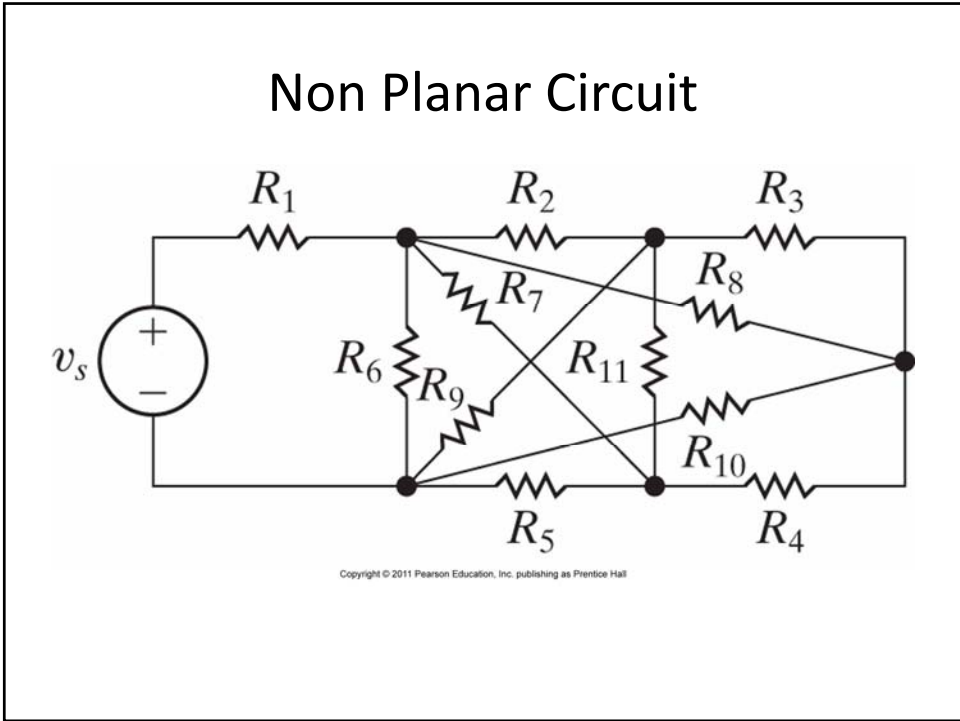Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall




Simultaneous Equations

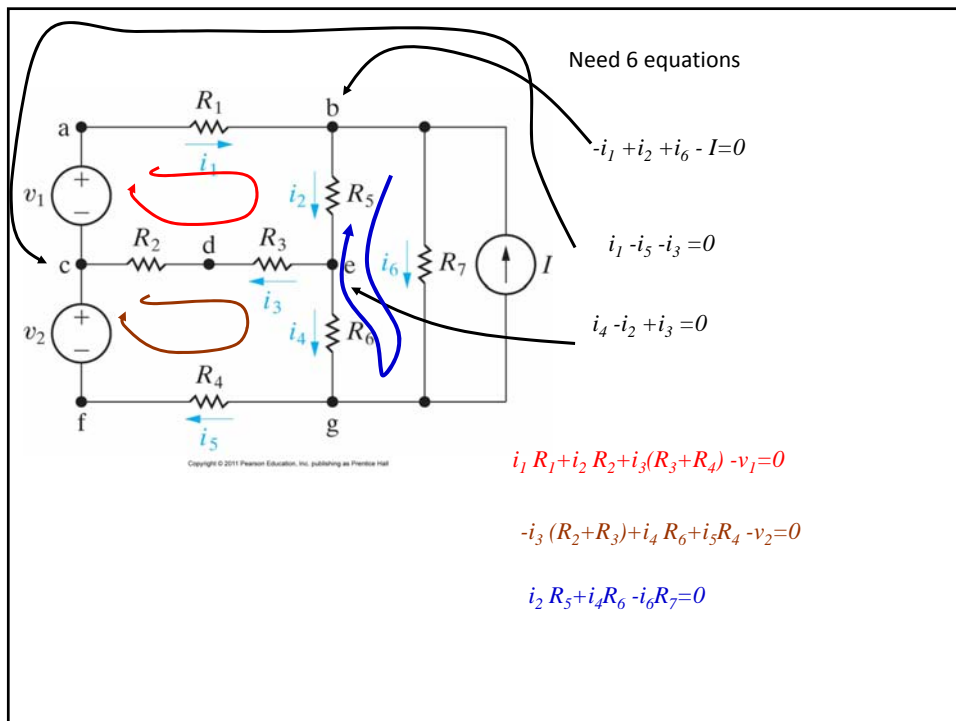- In a circuit with b essential branches, and n essential nodes
- Get $n-1$ equations by applying KCL at $n-1$ nodes (**why not n ?**)
- Still need $b-n+1$ equations to solve for the currents in each essential branch.
- Use KVL on loops or meshes to get the remaining $b-n+1$ equations
- Solve them.




Node-Voltage Method

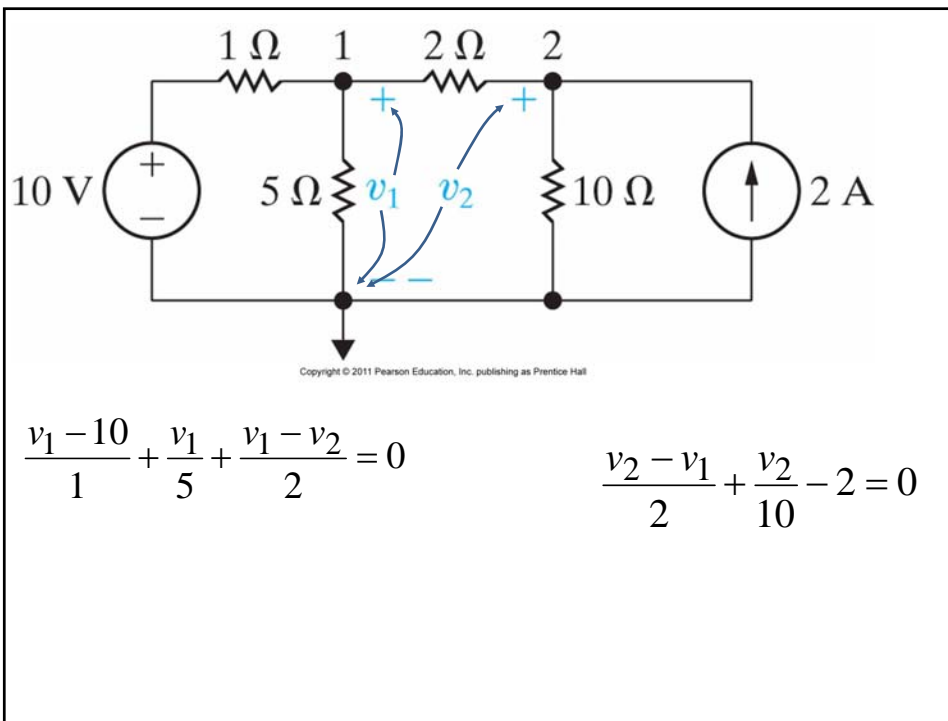- Draw the circuit in a neat way
- If the circuit has n essential nodes, we need $n-1$ equations.
- Select one of the n nodes as a reference node (usually the one with the most branches).
- Define the node voltages for the $n-1$ nodes (voltage rise from reference to the node).
- Write KCL for the $n-1$ nodes as a function of the node voltage.




Example

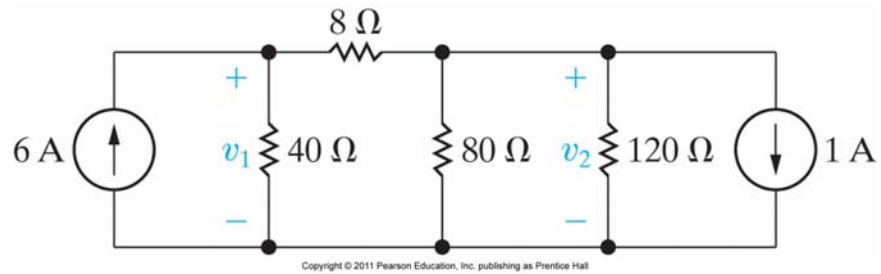

Node-Voltage and Dependent Sources.

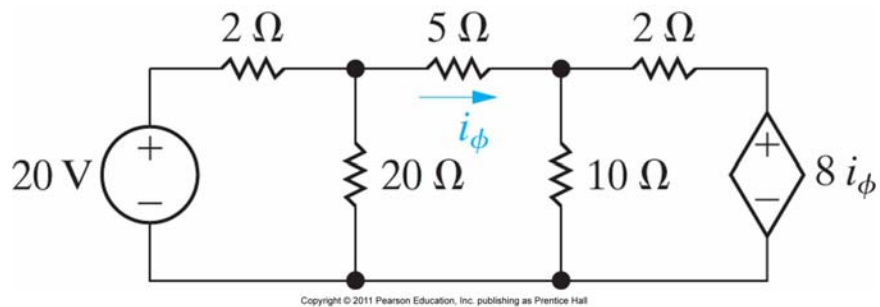- Another constraint is added by the dependent source



Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

$$\frac{v_2 - 20}{2} + \frac{v_1 - v_2}{5} + \frac{v_1}{20} = 0 \qquad \frac{v_2 - 8i_\phi}{2} + \frac{v_2 - v_1}{5} + \frac{v_2}{10} = 0$$

$$i_\phi = \frac{v_1 - v_2}{5}$$

Special cases

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

$$i + \frac{v_2 - 50}{5} + \frac{v_2}{50} = 0$$

© Pearson Education, Inc. publishing as Prentice Hall
 Add these 2 equations. To get rid of i

$$\frac{v_3}{100} - 4 - i = 0$$

$$\frac{v_2 - 50}{5} + \frac{v_2}{50} + \frac{v_3}{100} - 4 = 0$$

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

When we have a voltage source between 2 nodes, we can use the concept of a supernode to derive the previous equation

$$\frac{v_2 - 50}{5} + \frac{v_2}{50} + \frac{v_3}{100} - 4 = 0$$

Need one more equation in v_2 and v_3 to be able to solve the circuit

$$v_3 = 10i_\phi + v_2$$

Using the concept of a super node

$$\frac{v_b - V_{CC}}{R_1} + \frac{v_b}{R_2} + \frac{v_c}{R_E} - \beta i_B = 0$$

Need 2 more equation to get rid of v_c and i_B

$$v_c = v_b - V_0$$

$$v_c = (i_B + \beta i_B) R_E$$

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Example

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Concept of reference node

2 different reference nodes

What is the voltages at a, b, c are they the same?



What about voltage differences?

Mesh-Current Method


- For planar circuit
- A mesh current is a current that exists only in the perimeter in the mesh
- Mesh current may or may not be an actual current in a circuit element (i_1 and i_2)



7 branches vs. 4 meshes (the number of equations you need to solve the circuit)

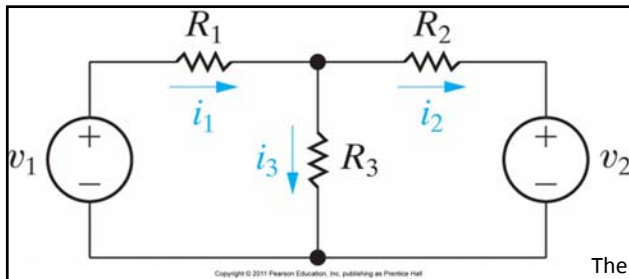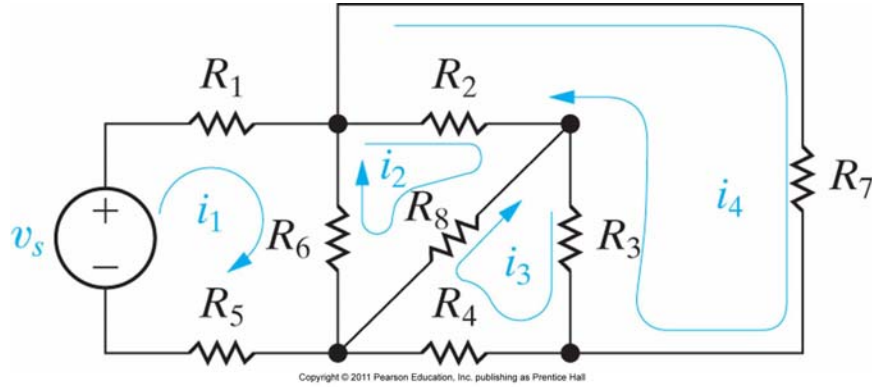Is i_7 an actual current in a circuit element? What about i_2 ?





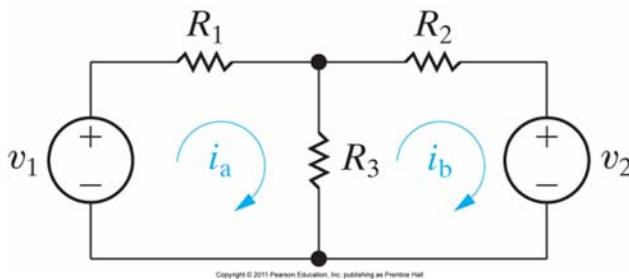The relation between mesh currents and currents in a circuit element.



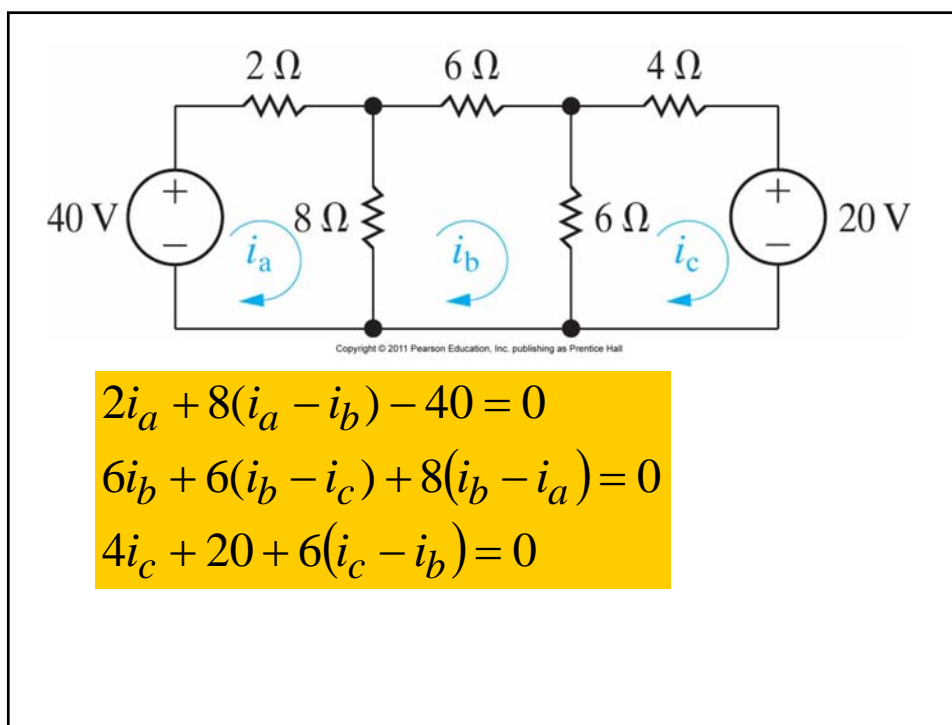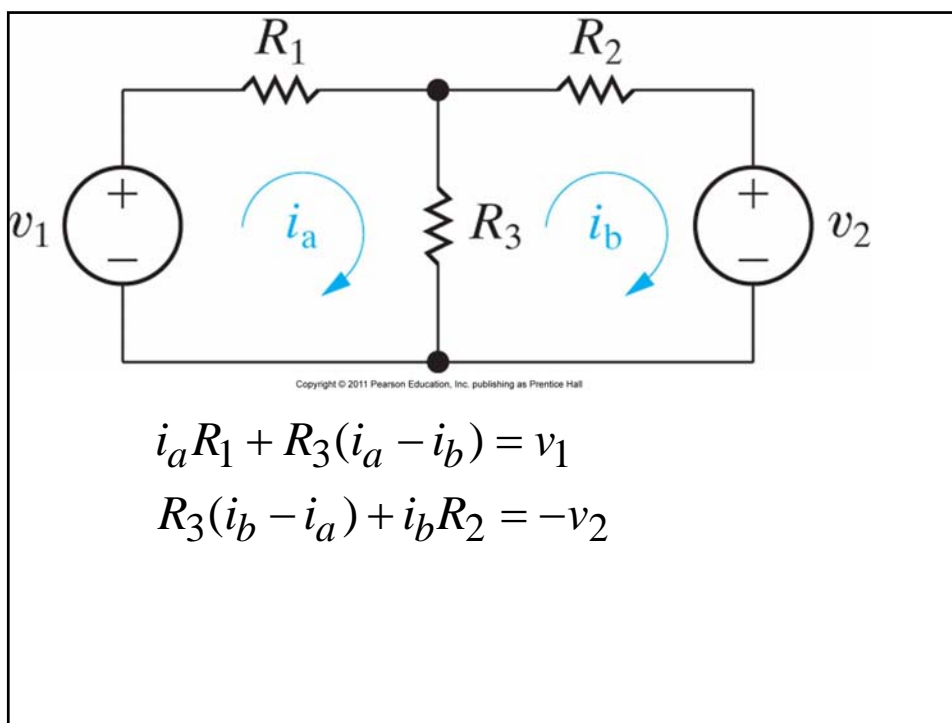

Mesh-Current with Dependent Sources

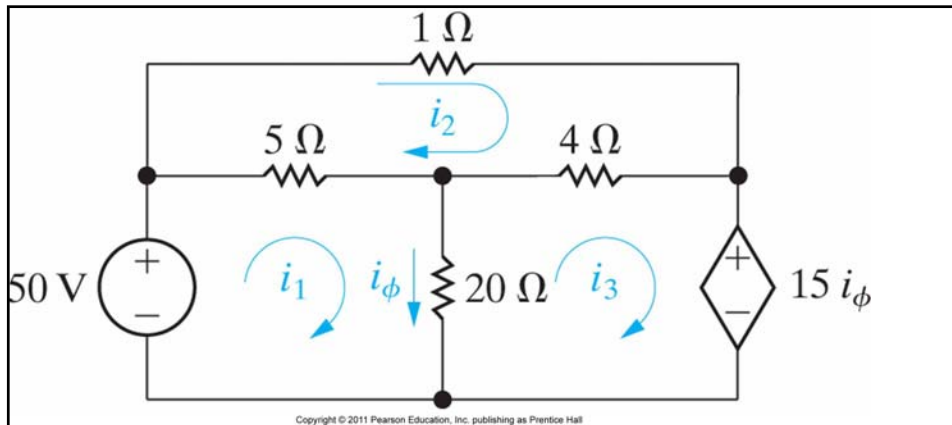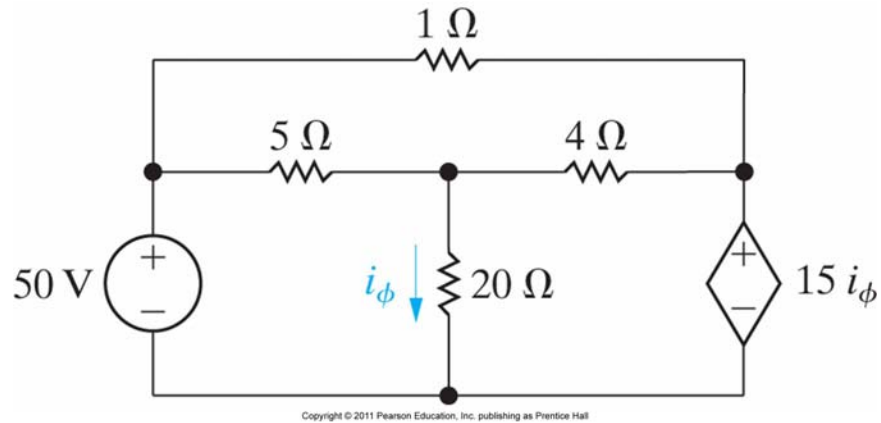


You can easily write 3 mesh-current equations. But what about i_ϕ

$$i_\phi = i_1 - i_2$$


Current Source between two nodes

We do not know v
Can NOT use KVL

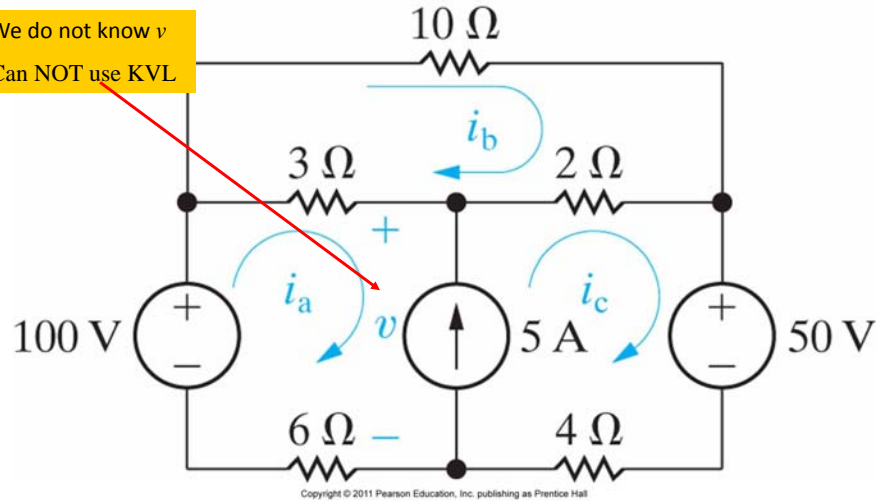


2 equations in 3 unknown


$$i_c - i_a = 5$$

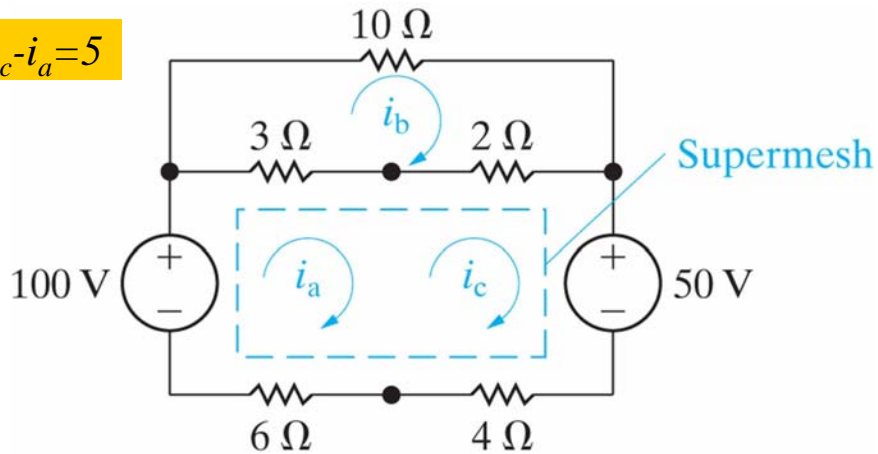

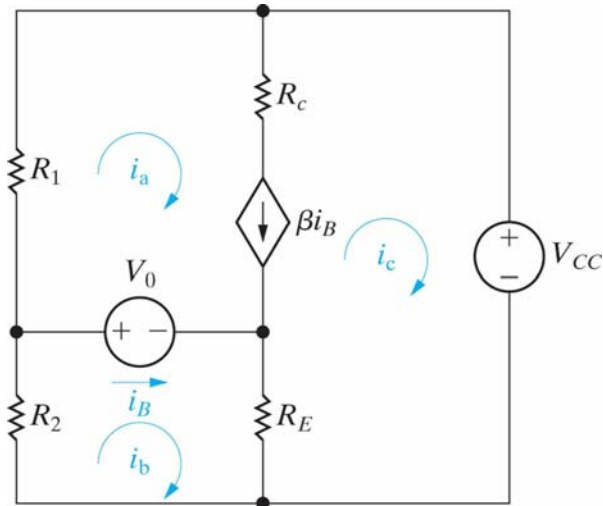We do not know the voltage drop across the current source.
 Can not write KVL for mesh a and c without introducing another variable



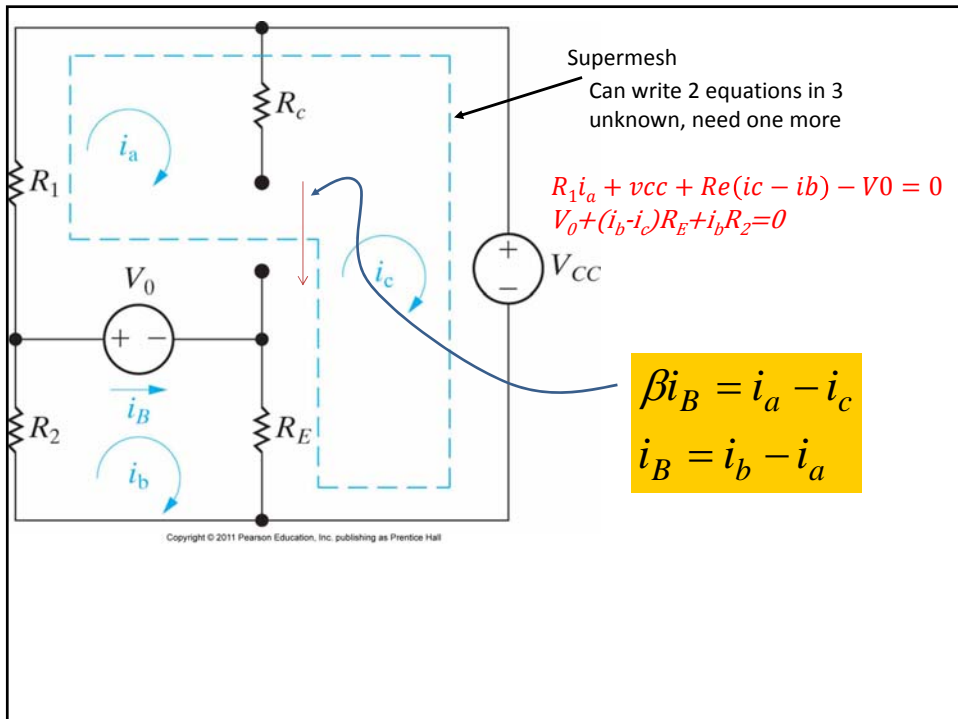
Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall



Node-Voltage vs. Mesh Current


- Which is better (less equations)
- Depends
 - Number of equations formed for each
 - Any supernode (node voltage)
 - Supermesh? (mesh-current)
 - Do we have to solve for the entire circuit?

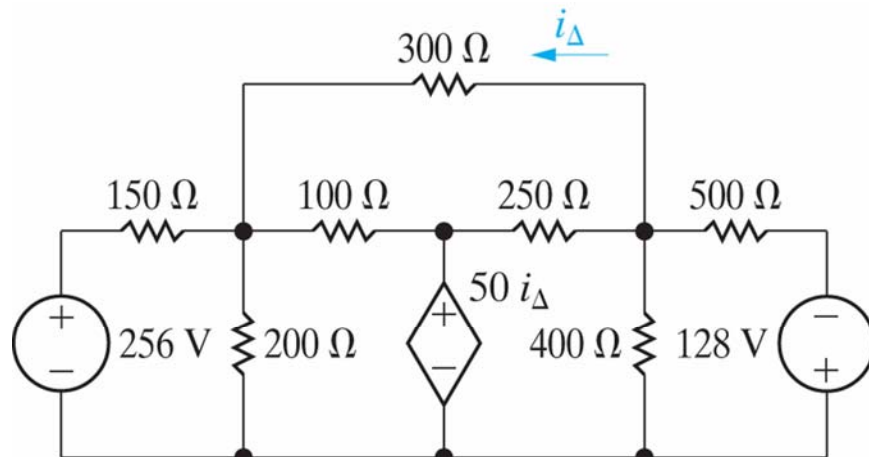Find power in the 300 ohm R,
which is better




Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

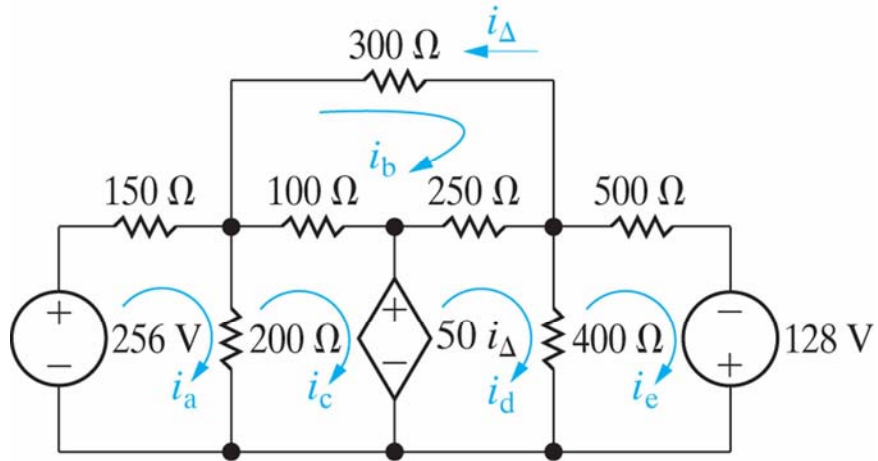Mesh current: 5 equations (note that $i_A = -i_b$)



Node voltages: 4 nodes, need only 3 equations

Which node to choose a reference node?

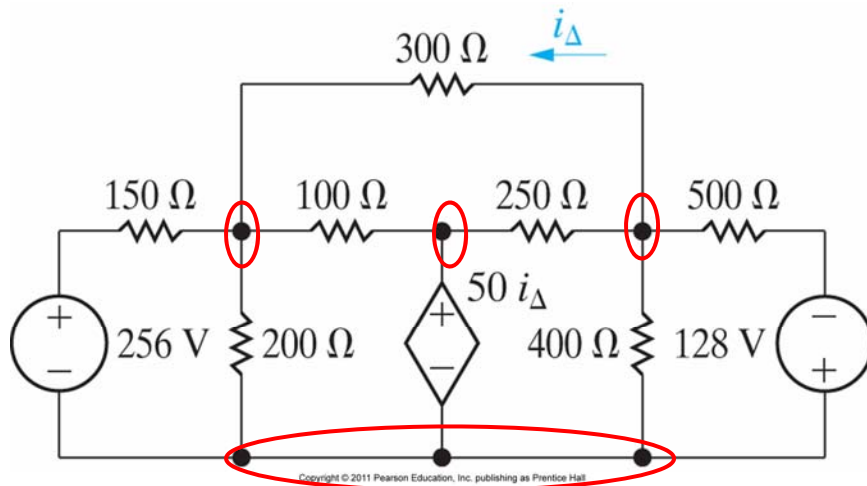

reference

Can not write KCL at v1 or v3 WHY?

$$\frac{v_1}{100} + \frac{v_3}{200} + \frac{v_3 + 256}{150} + \frac{v_1 - v_2}{250} + \frac{v_3 - v_2}{400} + \frac{v_3 - 128 - v_2}{500} = 0$$

$$\frac{v_2 - v_1}{250} + \frac{v_2 + 128 - v_3}{500} + \frac{v_2 - v_3}{400} + \frac{v_2}{300} = 0 \quad \text{At node 2}$$

$$v_1 - v_3 = 50i_\Delta = 50 \frac{v_2}{300} \quad \text{Constraint at supernode}$$

$$\frac{v_a}{200} + \frac{v_a - 256}{150} + \frac{v_a - v_b}{100} + \frac{v_a - v_c}{300} = 0 \quad \text{Node a}$$



$$\frac{v_c - v_b}{250} + \frac{v_c}{400} + \frac{v_c + 128}{500} + \frac{v_c - v_a}{300} = 0 \quad \text{Node c}$$

$$v_b = 50i_\Delta = 50 \frac{v_c - v_b}{300} \quad \text{Constraint at supernode}$$



Source Transformation

- Some times it helps in reducing the circuit complexity

Why? $i_s = \frac{v_s}{R}$

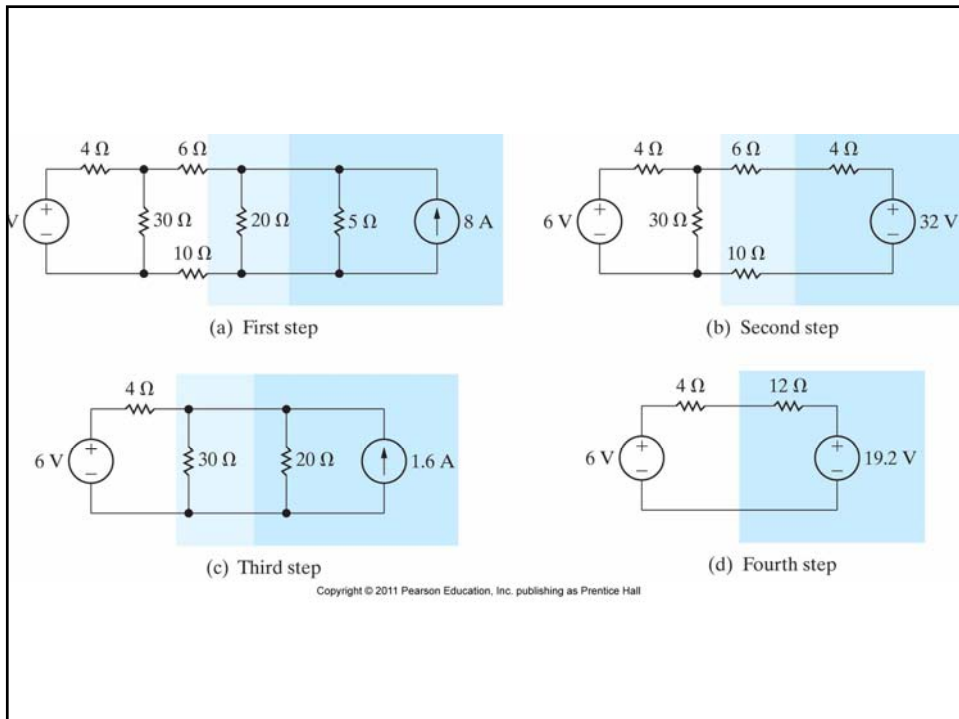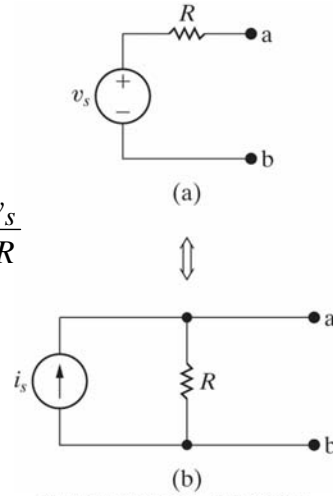


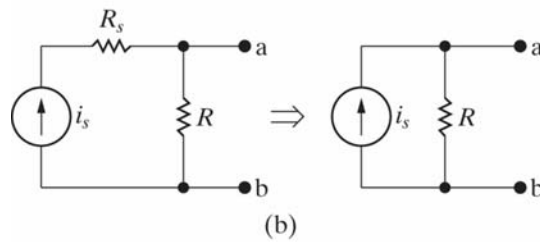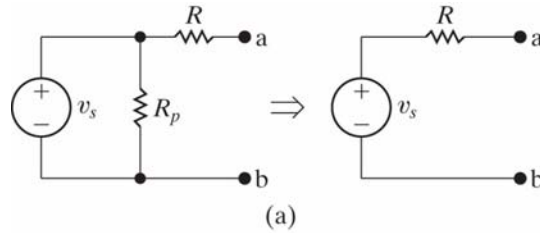Are these 2 circuits equivalent? Power lost in R_p ?



Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Thevenin Equivalent Circuit

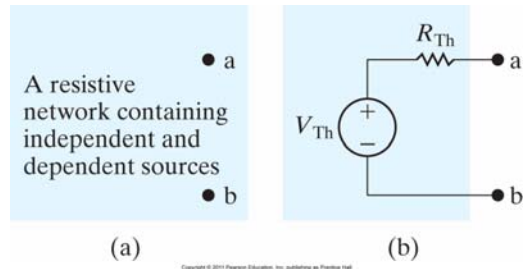


Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Especially useful when we are interested in the behavior of the circuit between two terminals.

Any resistive network with dependent or independent sources could be represented as a dependent voltage source V_{TH} in series with a resistance R_{TH} .


Thevenin equivalent Circuit

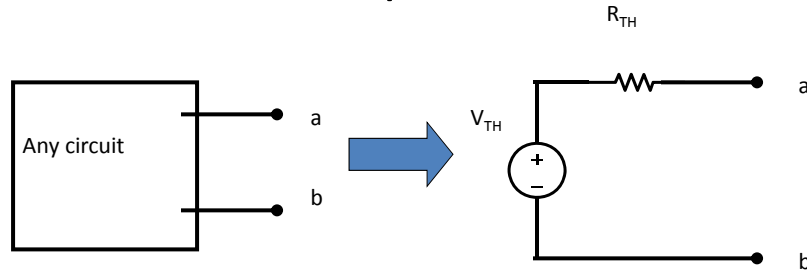

V_{TH} = the open circuit voltage between a and b


$R_{TH} = V_{TH}/I_{sc}$ where I_{sc} is the short circuit current from a to b

EXCEPT for an ideal current source

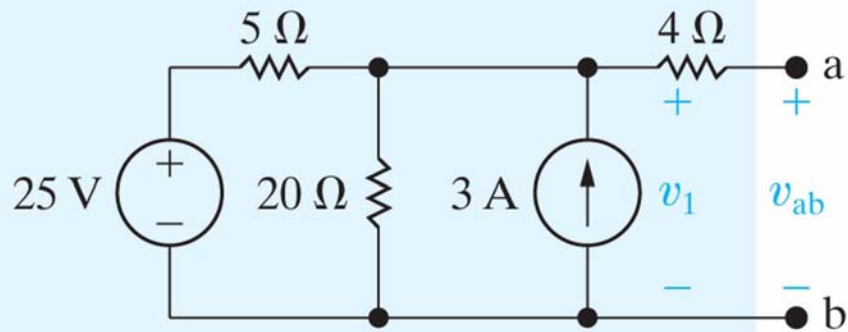


Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Find Thevenin equivalent

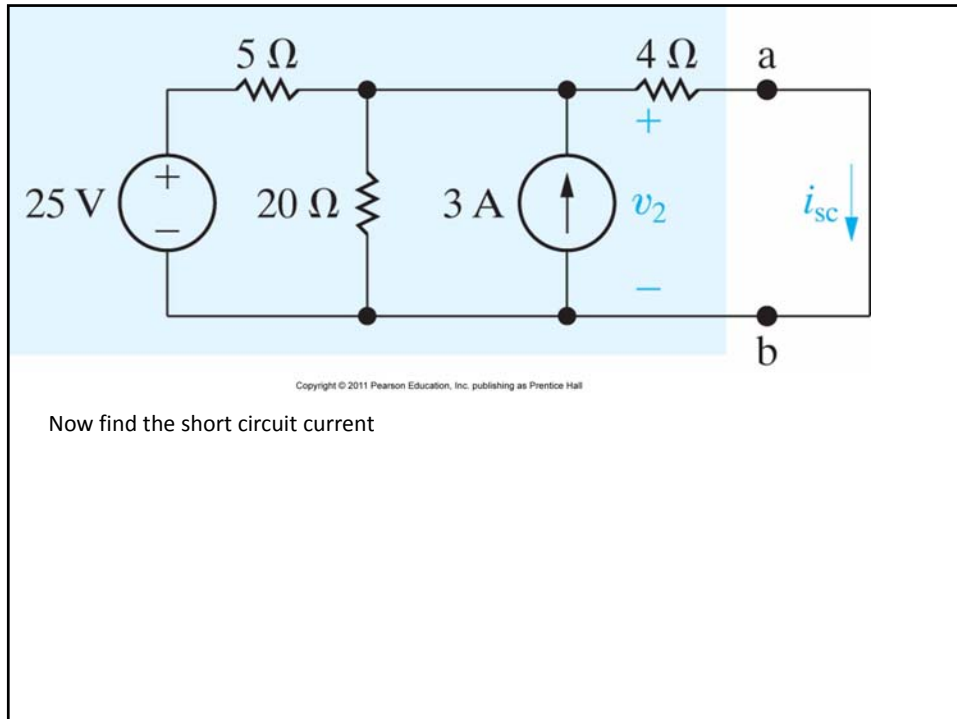



Norton Equivalent Circuit

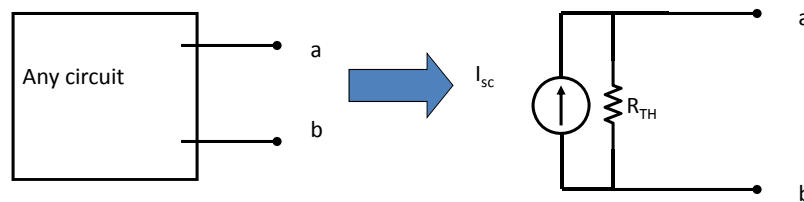



I_{sc} = the short circuit current between a and b



$R_{TH} = V_{TH}/I_{sc}$ where I_{sc} is the short circuit current from a to b


EXCEPT for an ideal voltage source

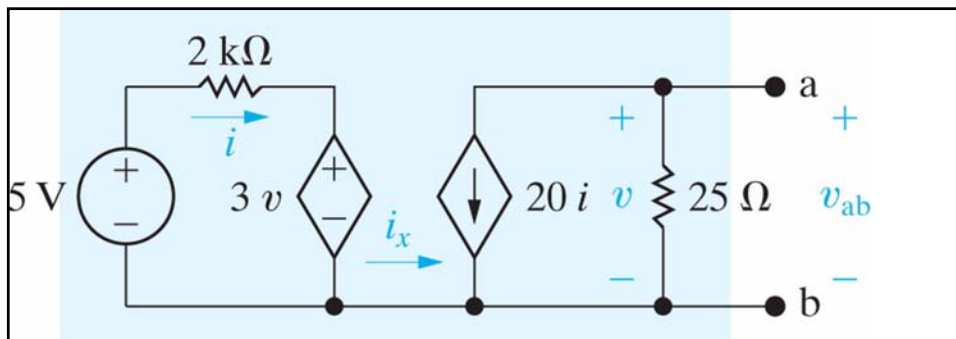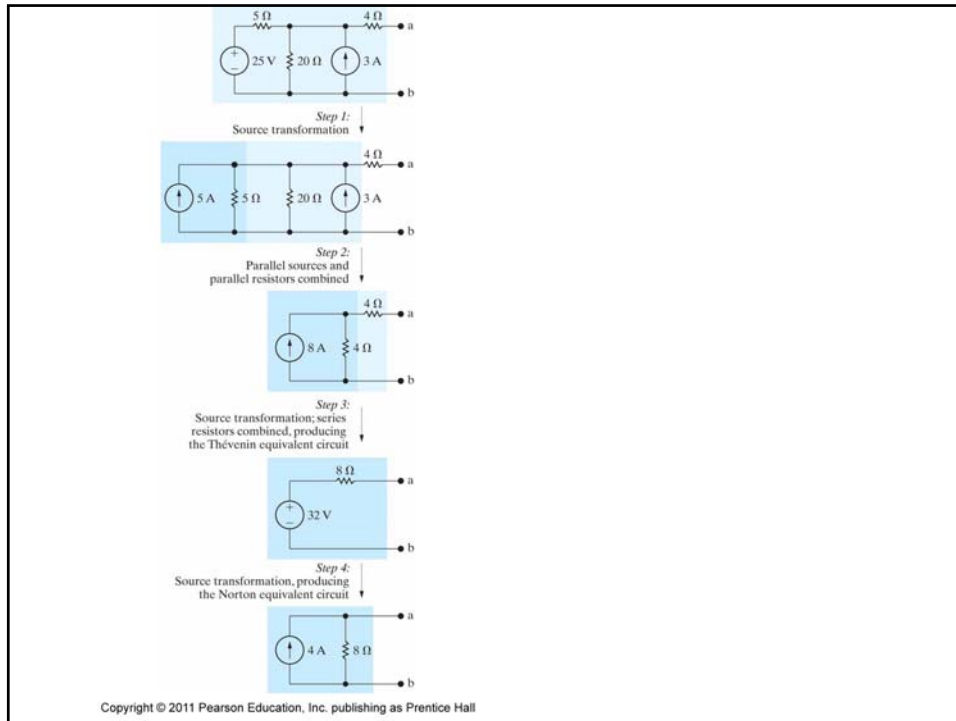

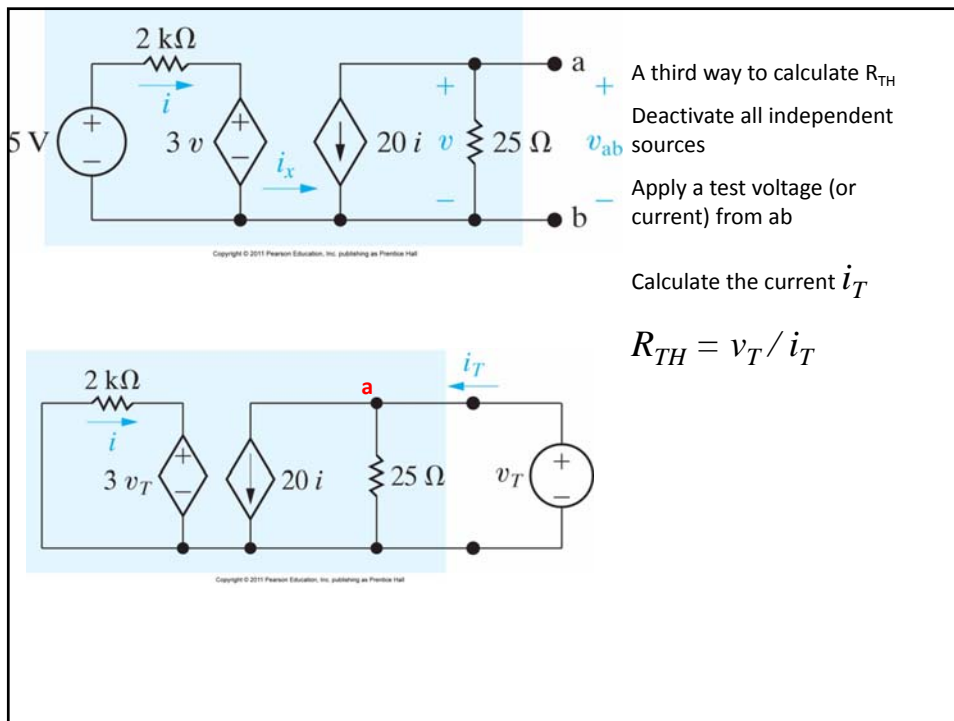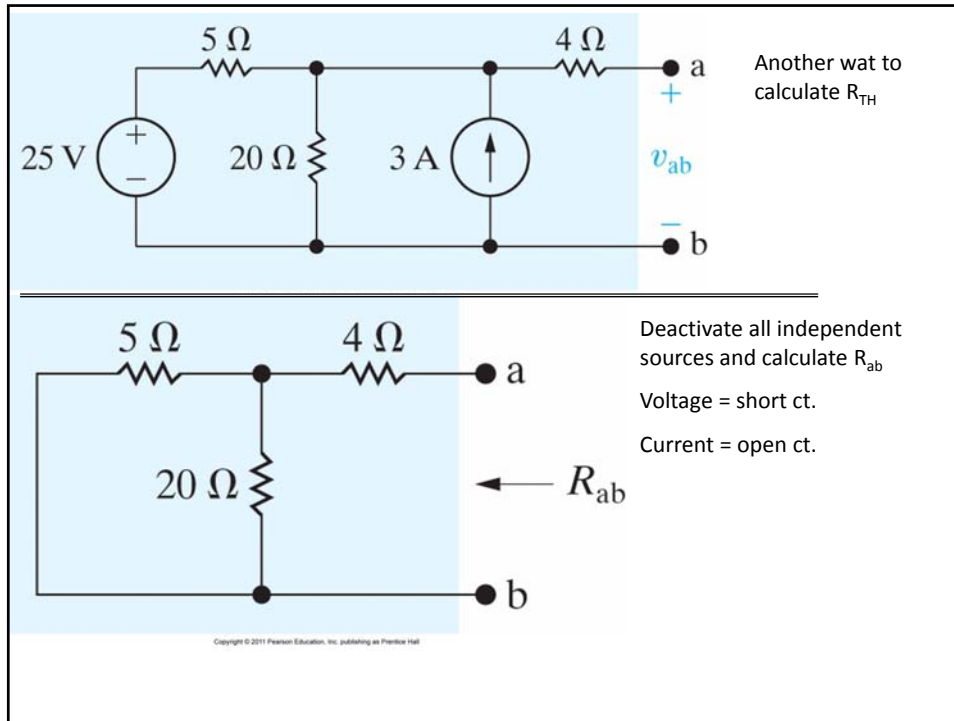1. Note that $i_x = 0$ (why?)
2. KCL at node a
3. KVL at the loop to the left get $v_{ab} = V_{th}$
4. Short circuit a and b
5. $I_{sc} = -20i$, find i from KVL o the left



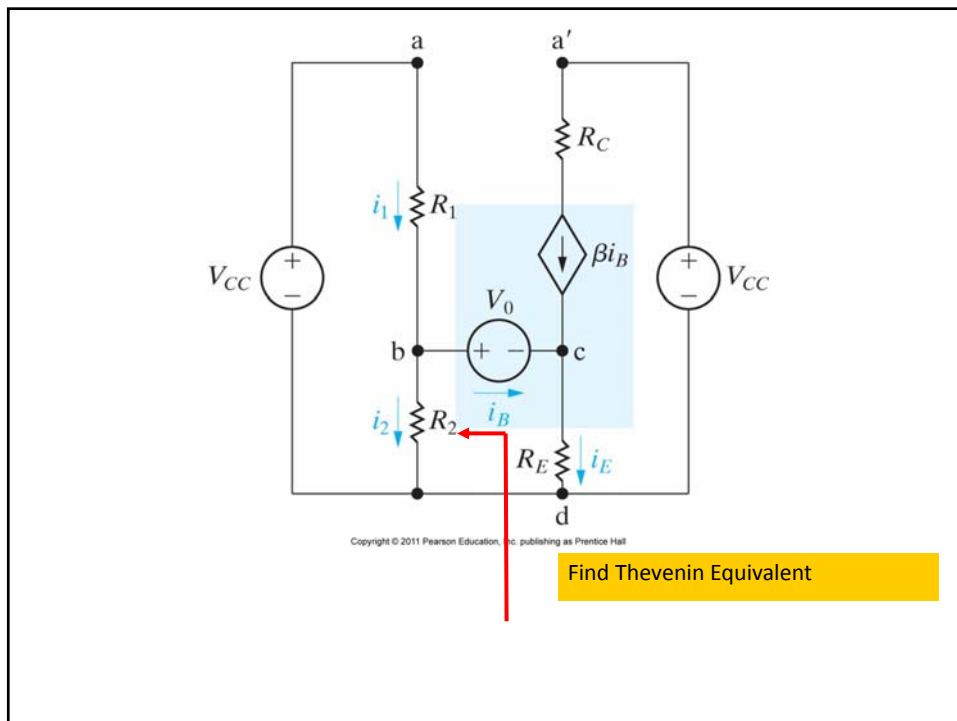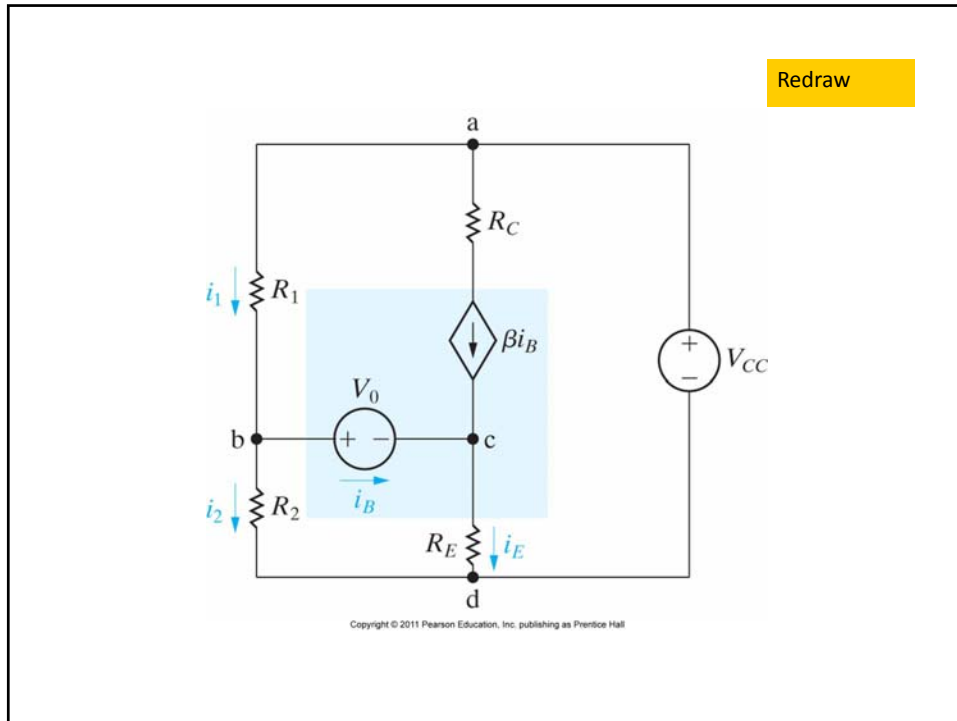

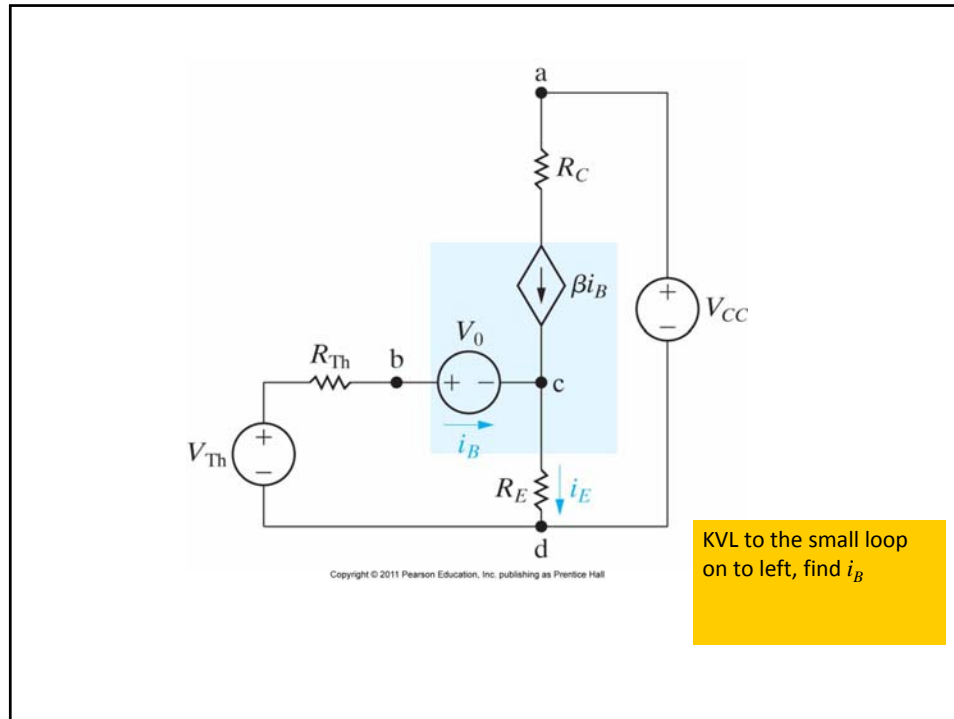


Maximum Power Transfer



- Assume a voltage source, V with internal resistance R_0 is driving a load R_L
- What is the maximum power R_L can get?
- Calculate $p(R_L, R_0)$ and differentiate $=0$
- What if it is not a simple source with an internal resistance?
- Thevenin equivalent

Superposition

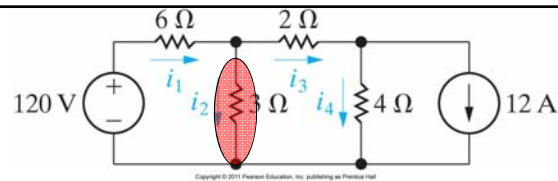- When a linear system is excited by more than one independent source, the total response is the sum of the individual responses where each response is the result of one of the independent sources acting alone.



Find the current here

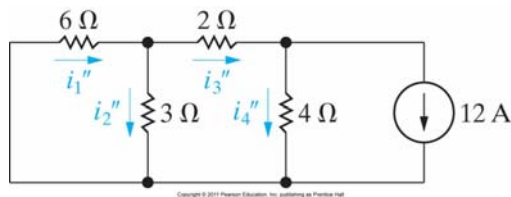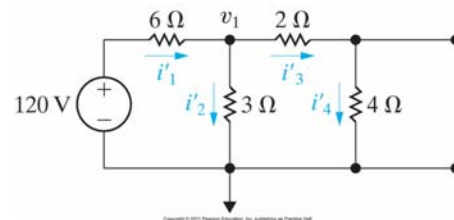

Find v_o using superposition

