


ENG2200 Electric Circuits

Chapter 10
Sinusoidal Steady Power Calculation

Objectives

- Understanding the difference between instantaneous power, average power reactive power, complex power and how to calculate them.
- Understanding power factor and how to calculate it.
- Understand the condition for a maximum real power delivered to the load.

Figure 10.1 The black box representation of a circuit used for calculating power.

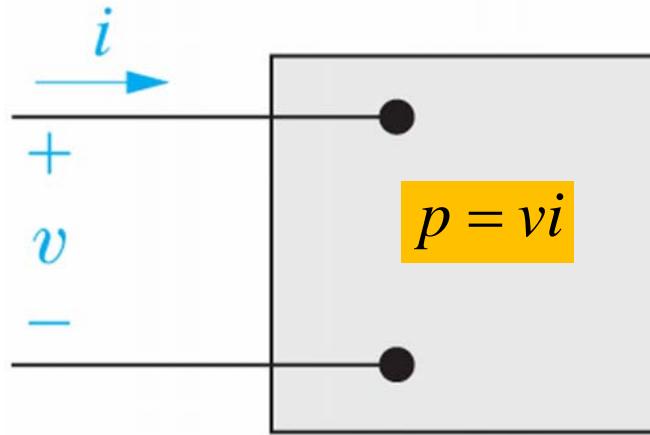

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Instantaneous Power

- $v = V_m \cos(\omega t + \theta_v)$ $i = I_m \cos(\omega t + \theta_i)$

$$v = V_m \cos(\omega t + \theta_v - \theta_i)$$

$$i = I_m \cos(\omega t)$$


$$p = I_m V_m \cos(\omega t + \theta_v - \theta_i) \cos(\omega t)$$

$$p = \frac{1}{2} I_m V_m \{ \cos(\theta_v - \theta_i) + \cos(2\omega t + \theta_v - \theta_i) \}$$

$$p = \frac{I_m V_m}{2} \cos(\theta_v - \theta_i) + \frac{I_m V_m}{2} \cos(2\omega t + \theta_v - \theta_i)$$

$$p = \frac{I_m V_m}{2} \cos(\theta_v - \theta_i) + \frac{I_m V_m}{2} \cos(\theta_v - \theta_i) \cos 2\omega t - \frac{I_m V_m}{2} \sin(\theta_v - \theta_i) \sin 2\omega t$$
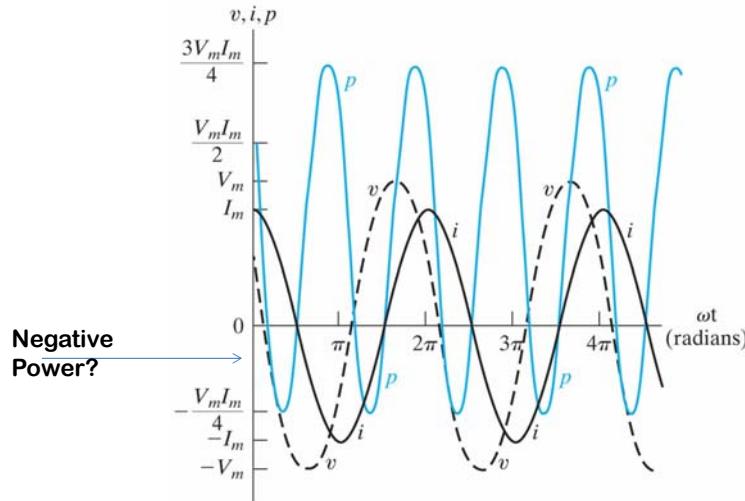
$$p = \frac{I_m V_m}{2} \cos(\theta_v - \theta_i) + \frac{I_m V_m}{2} \cos(\theta_v - \theta_i) \cos 2\omega t - \frac{I_m V_m}{2} \sin(\theta_v - \theta_i) \sin 2\omega t$$



Average and Reactive Power


$$p = \frac{I_m V_m}{2} \cos(\theta_v - \theta_i) + \frac{I_m V_m}{2} \cos(\theta_v - \theta_i) \cos 2\omega t - \frac{I_m V_m}{2} \sin(\theta_v - \theta_i) \sin 2\omega t$$

$$p = P + P \cos 2\omega t - Q \sin 2\omega t$$

- P is the average power (real power) the power transferred from electric to non-electric (the consumer made use of it)
- Q is the reactive power

Purely Resistive Circuits $\theta_i = \theta_v$

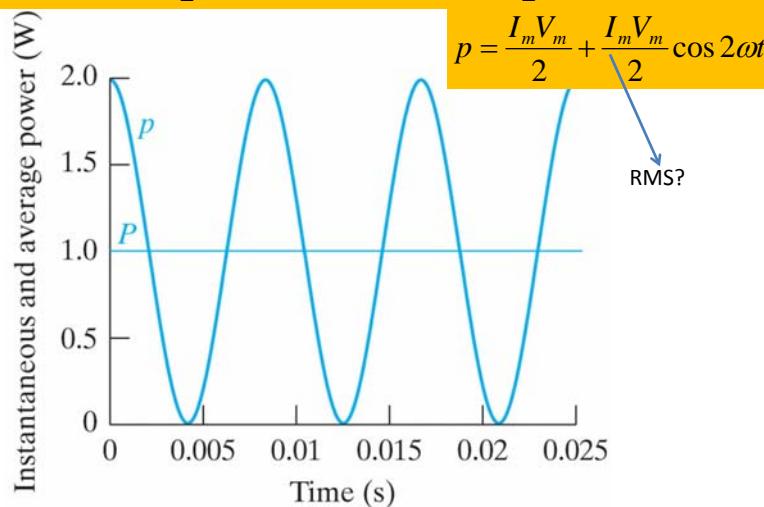
$$p = \frac{I_m V_m}{2} \cos(\theta_v - \theta_i) + \frac{I_m V_m}{2} \cos(\theta_v - \theta_i) \cos 2\omega t - \frac{I_m V_m}{2} \sin(\theta_v - \theta_i) \sin 2\omega t$$



Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Purely Inductive $\theta_i = \theta_v - 90^\circ$

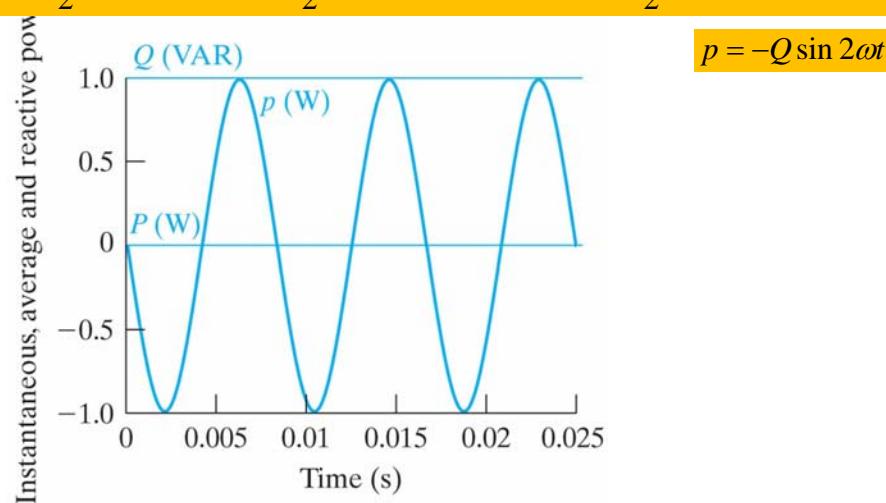
$$p = \frac{I_m V_m}{2} \cos(\theta_v - \theta_i) + \frac{I_m V_m}{2} \cos(\theta_v - \theta_i) \cos 2\omega t - \frac{I_m V_m}{2} \sin(\theta_v - \theta_i) \sin 2\omega t$$



Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Purely Capacitive Circuits $\theta_i = \theta_v + 90^\circ$
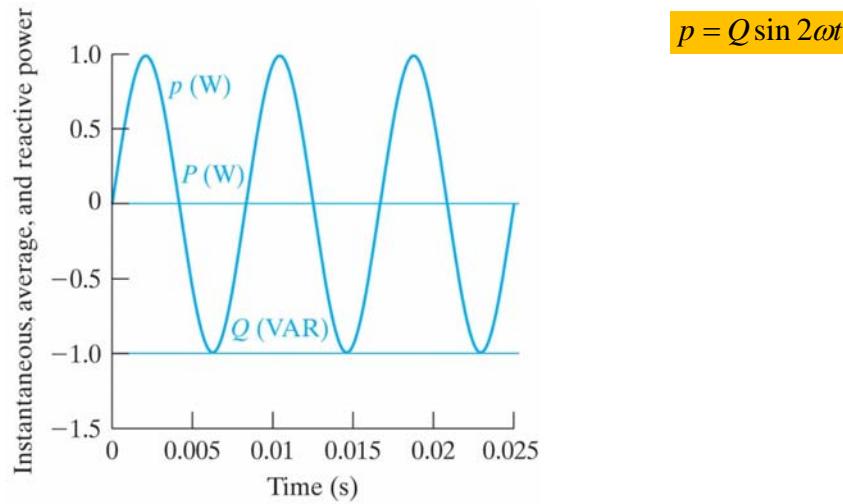
$$p = \frac{I_m V_m}{2} \cos(\theta_v - \theta_i) + \frac{I_m V_m}{2} \cos(\theta_v - \theta_i) \cos 2\omega t - \frac{I_m V_m}{2} \sin(\theta_v - \theta_i) \sin 2\omega t$$



Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Power Factor


- The units for p is Watt (W)
- The units for Q is VAR (Volt Ampere Reactive)
- $\theta_i - \theta_v$ power factor angle
- $PF = \cos(\theta_i - \theta_v)$
- Note that $\cos(\theta_i - \theta_v) = \cos(\theta_v - \theta_i)$
- PF is defined as lagging (current lags voltage – inductive) or leading (current leads voltage – capacitive)

Example

$$v = 100 \cos(\omega t + 15^\circ) \text{ V}$$

$$i = \sin(\omega t - 15^\circ) \text{ A}$$
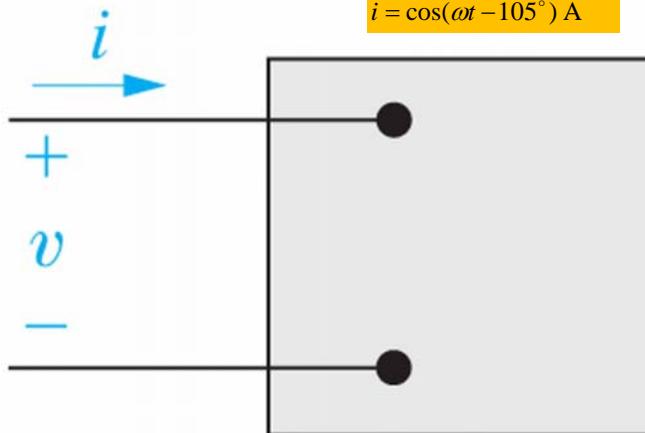
$$i = \cos(\omega t - 105^\circ) \text{ A}$$



Calculate the average power, reactive power

TABLE 10.1 Annual Energy Requirements of Electric Household Appliances

Appliance	Average Wattage	Est. kWh Consumed Annually ^a	Appliance	Average Wattage	Est. kWh Consumed Annually ^a
Food preparation					
Coffeemaker	1,200	140	Health and beauty		
Dishwasher	1,201	165	Hair dryer	600	25
Egg cooker	516	14	Shaver	15	0.5
Frying pan	1,196	100	Sunlamp	279	16
Mixer	127	2			
Oven, microwave (only)	1,450	190	Home entertainment		
Range, with oven	12,200	596	Radio	71	86
Toaster	1,146	39	Television, color, tube type	240	528
Laundry			Solid-state type	145	320
Clothes dryer	4,856	993			
Washing machine, automatic	512	103	Housewares		
Water heater	2,475	4,219	Clock	2	17
Quick recovery type	4,474	4,811	Vacuum cleaner	630	46
Comfort conditioning					
Air conditioner (room)	860	860 ^b			
Dehumidifier	257	377			
Fan (circulating)	88	43			
Heater (portable)	1,322	176			

a) Based on normal usage. When using these figures for projections, such factors as the size of the specific appliance, the geographical area of use, and individual usage should be taken into consideration. Note that the wattages are not additive, since all units are normally not in operation at the same time.

b) Based on 1000 hours of operation per year. This figure will vary widely depending on the area and the specific size of the unit. See EEI-Pub #76-2, "Air Conditioning Usage Study," for an estimate for your location.

Source: Edison Electric Institute.

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall



Figure 10.7 A sinusoidal voltage applied to the terminals of a resistor.

$$P = \frac{1}{T} \int_{t_0}^{t_0+T} \frac{V_m^2 \cos^2(\omega t + \theta_v)}{R} dt$$

$$P = \frac{1}{R} \left[\frac{1}{T} \int_{t_0}^{t_0+T} V_m^2 \cos^2(\omega t + \theta_v) dt \right]$$

$$P = \frac{V_{RMS}^2}{R}$$

$$P = I_{RMS}^2 R$$

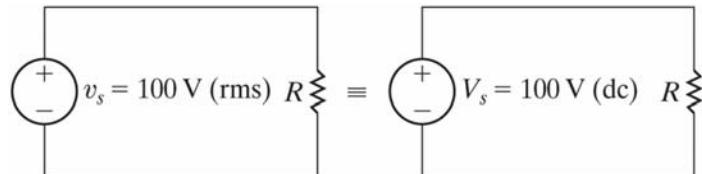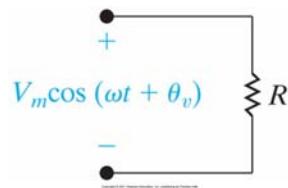


Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Complex Power

- Complex power $S = P + JQ$

$$\frac{Q}{P} = \frac{(V_m I_m / 2) \sin(\theta_v - \theta_i)}{(V_m I_m / 2) \cos(\theta_v - \theta_i)} = \tan(\theta_v - \theta_i)$$

- Apparent Power $|S|$

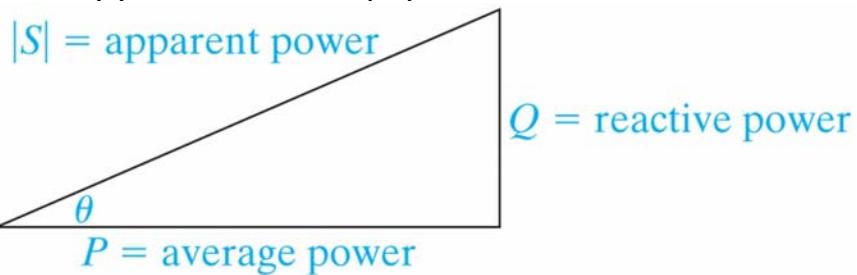

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Example

- An electrical motor operates at 240 V rms. The average power is 8 kW at a lagging power factor of 0.8

Power calculation

$$\begin{aligned}
 S &= (V_m I_m / 2) \cos(\theta_v - \theta_i) + j(V_m I_m / 2) \sin(\theta_v - \theta_i) \\
 S &= \frac{V_m I_m}{2} [\cos(\theta_v - \theta_i) + j \sin(\theta_v - \theta_i)] \\
 S &= \frac{V_m I_m}{2} e^{j(\theta_v - \theta_i)} = \frac{V_m I_m}{2} \angle(\theta_v - \theta_i) \\
 S &= V_{rms} \angle \theta_v \times I_{rms} \angle -\theta_i \\
 S &= V_{rms} I_{rms}^* = \frac{1}{2} V I^*
 \end{aligned}$$

Power calculation

$$S = V_{rms} I_{rms}^*$$

$$V_{rms} = I_{rms} Z$$

$$S = I_{rms} I_{rms} Z$$


$$S = |I_{rms}|^2 Z$$

$$S = |I_{rms}|^2 (R + jX)$$

$$S = |I_{rms}|^2 R + j|I_{rms}|^2 X$$

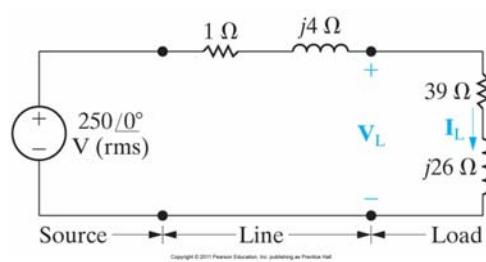
Example

- Find I_L and V_L
- Calculate S supplied by the source
- Calculate S delivered to the load
- Calculate S delivered to the line



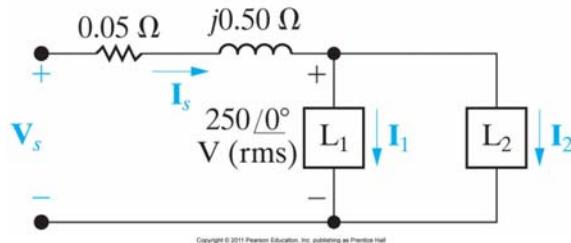
Example

Load 1
8 KW leading pf 0.8
Load 2
20 kVA at lagging pf 0.6



Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

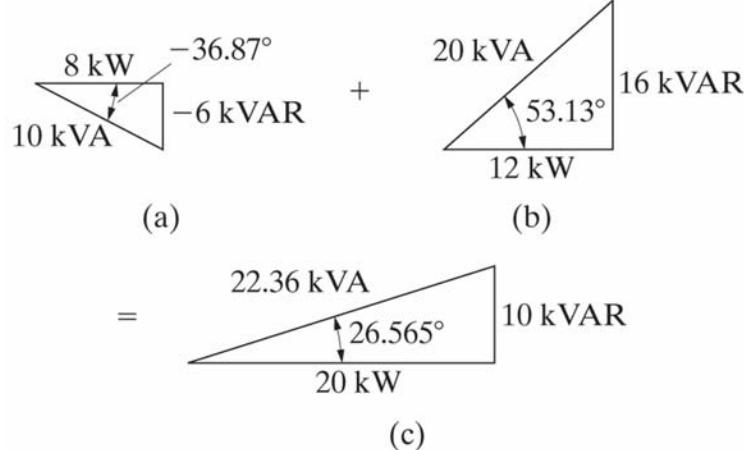- Find the pf of the 2 loads in parallel
- Find I_s and the apparent power to supply the load
- Assuming 60 Hz, what is the capacitor required to correct the power factor



Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall


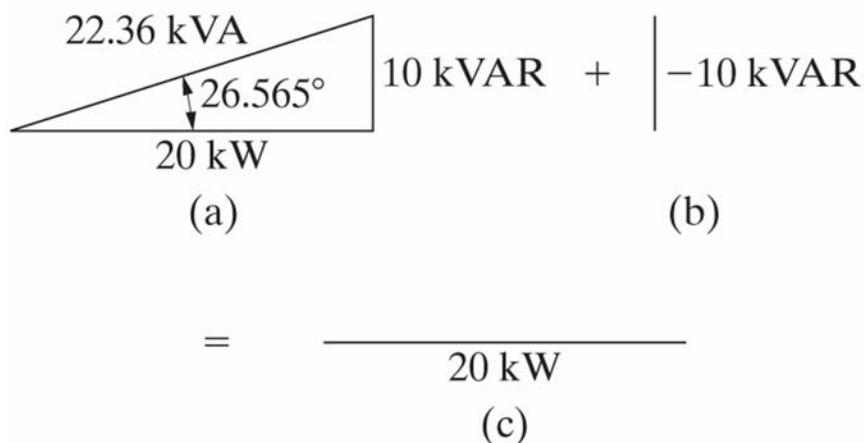


Figure 10.17 The circuit, with solution, for Example 10.7.

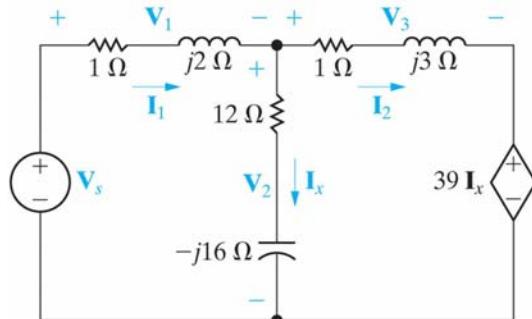

$$\mathbf{V}_s = 150 \angle 0^\circ \text{ V}$$

$$\mathbf{V}_1 = (78 - j104) \text{ V} \quad \mathbf{I}_1 = (-26 - j52) \text{ A}$$

$$\mathbf{V}_2 = (72 + j104) \text{ V} \quad \mathbf{I}_r = (-2 + j6) \text{ A}$$

$$\mathbf{V}_3 = (150 - j130) \text{ V} \quad \mathbf{I}_2 = (-24 - j58) \text{ A}$$