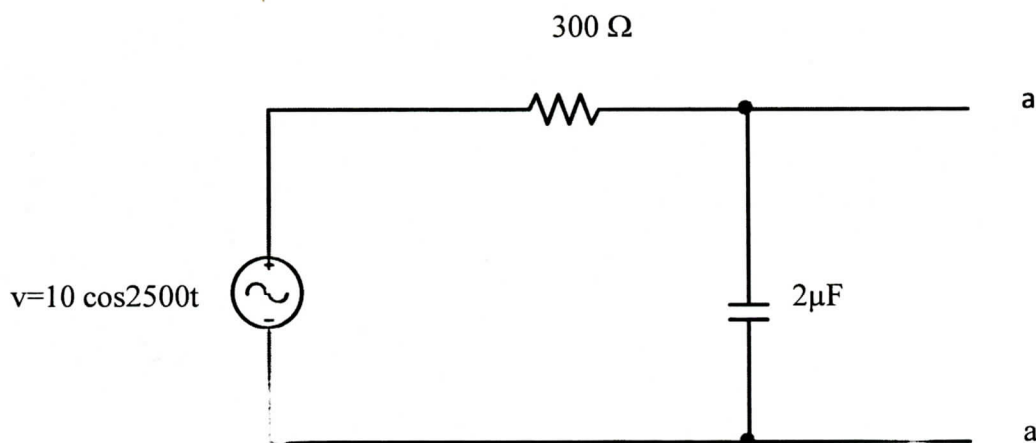


## Dept. of Electrical Engineering and Computer Science

EECS2200  
Electric Circuits  
Quiz 3 – 25 minutes  
Dec. 4 2014

### Question 1 – 5 points

Find the Norton equivalent circuit between points a and b



$$X_C = \frac{1}{j\omega C} = \frac{1}{j \times 2500 \times 2 \times 10^{-6}} = -j200$$

$I_N$ : Short circuit current, short a & a

$$= \frac{10 \angle 0}{300 \angle 0} = 0.0333 \angle 0 \text{ A}$$

$$Z_N = Z_{Th} = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

$$= \frac{-j200 \times 300}{300 - j200}$$

$$= 92.3 - j138.5$$

$$= 166 \angle -56$$