



EECS 3201: Digital Logic Design Lecture 13

Ihab Amer, PhD, SMIEEE, P.Eng.



Verilog HDL for Synthesis

- Verilog HDL was originally designed as a logic circuit *description* and *simulation* language, and was later adopted to *synthesis*
- Thus, the language has several features and constructs that cannot be synthesized
- Even if synthesizable code is used, it should be taken care that the style of the written code can have a big impact on the quality of synthesized circuits

Using **always** Blocks for Combinational Logic

```
always @(a or b) begin
  if (a== 1'b0 && b==1'b0)
    f =1'b0;
  else
    f =1'b1;
end
```

*Synthesis**

  

**Produced using XST (synthesis tool of Xilinx ISE 10.1). Target Device: XC3S500E-4FG320. Same applies for rest of examples.*

Rules to Infer Combinational Logic

- All inputs to the circuit should be included in the sensitivity list
- No other signals should be included in the sensitivity list
- None of the statements within the **always** block can be sensitive to rising or falling edges of any signals

Examples' Template

```

// DEFINITIONS
`define VEC_SIZE 2

// MODULE DECLARATION
module seq1 (vec1, c, d, e, f, g, clk, a, b);

    output [`VEC_SIZE-1:0] vec1;           // bit vector output
    output c, d, e, f, g;                 // single bit outputs output
    input clk;                             // clock signal
    input a, b;                             // data inputs

// SIGNAL DECLARATIONS
    reg c, d, e, f, g;                     // connects to the outputs
    reg [`VEC_SIZE-1:0] vec1;             // bit vector output
    reg [`VEC_SIZE-1:0] vec2;             // other bit vectors
    wire [`VEC_SIZE-1:0] vec3;

// ** MODULE UNDER SYNTHESIS TEST GOES HERE

endmodule


```

Example 1


```

always @(a or b) begin
  if (b)
    c = a;
end
  
```

Synthesis

 

Inferred latch. Typically, unintended

 

Workaround

```

always @(a or b) begin
  if (b)
    c = a;
  else
    c = 1'bx;
end

```


OR

```


always @(a or b) begin
  c = 1'bx;
  if (b)
    c = a;
end

```

Synthesis

 

 Pure combinational logic.
Inferred latch disappeared!




Synthesis

Example 2


```

always @(a or b) begin
  if (a)
    d = ~b;
  else
    e = b;
end
  
```

Synthesis

 

Two inferred latches!

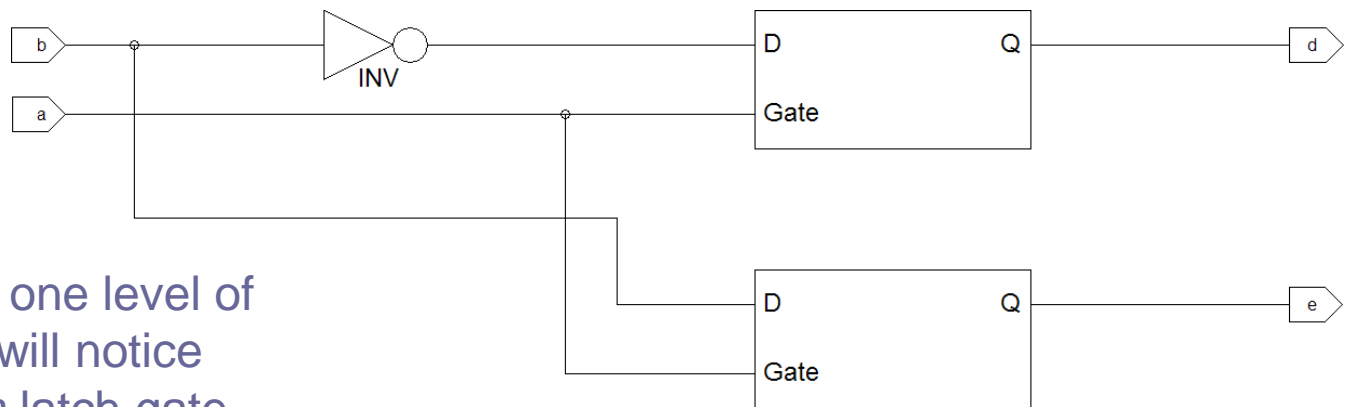

If you go down one level of hierarchy, you will notice that the *bottom-latch* gate port is inverted. Why?

Workaround

```

always @(a or b) begin
  if (a)
    begin
      d = ~b;
      e = 1'bx;
    end
  else
    begin
      e = b;
      d = 1'bx;
    end
  end


```

OR

```

always @(a or b) begin
  d = 1'bx;
  e = 1'bx;
  if (a)
    d = ~b;
  else
    e = b;
  end

```

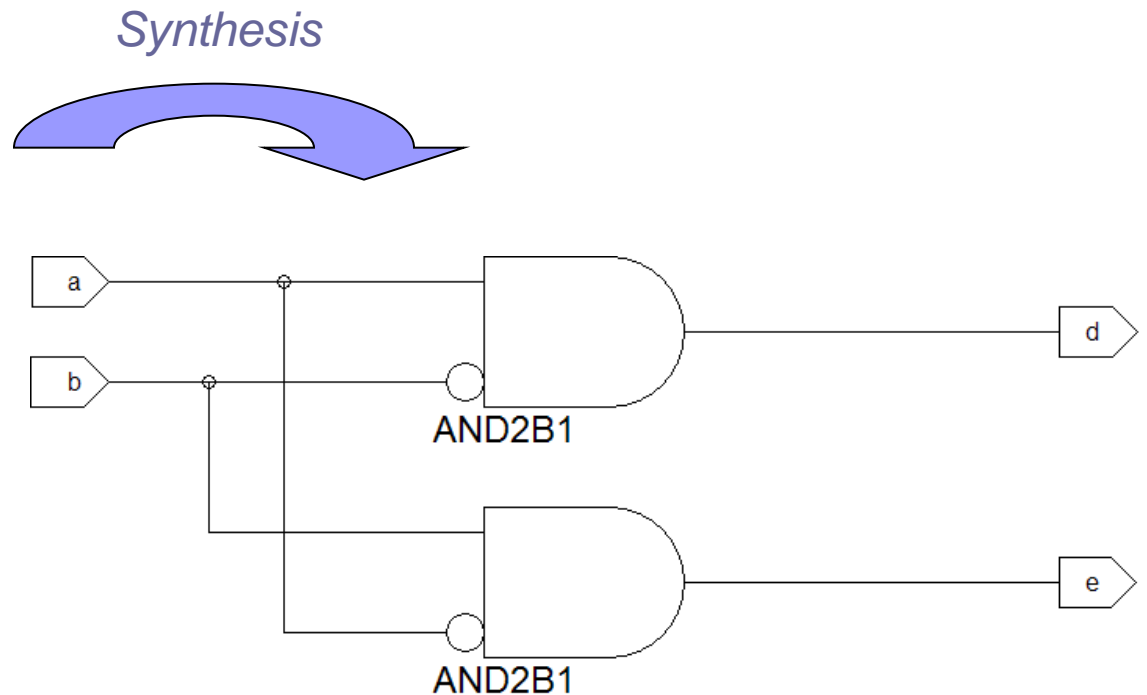

Moral



- Latches are created by **if-else** statements with no **else** clause. Such latches are typically unintended
- Workaround – Two possible solutions:
 - Every **if** statement should have an **else** clause. Every variable that is assigned a value in one **if** or **else** clause, should also be assigned a value in every other clause (even if we do not care about this value)
 - Unconditionally assign default values to variables at the beginning of the **always** block

Example 3

```

always @(a or b)
case ({a,b})
    2'b00: c = 1'b0;
    2'b01: c = 1'b1;
    2'b10: c = 1'b0;
endcase
    
```

Synthesis

  

Inferred latch!
If you go down one level of hierarchy, you will notice that the latch gate port is inverted. Why?

Workaround

```

always @(a or b)
case ({a,b})
  2'b00: c = 1'b0;
  2'b01: c = 1'b1;
  2'b10: c = 1'b0;
  2'b11: c = 1'bx;
endcase
  
```

OR

```



always @(a or b)
case ({a,b})
  2'b00: c = 1'b0;
  2'b01: c = 1'b1;
  2'b10: c = 1'b0;
  default: c = 1'bx;
endcase
  
```

OR


```

always @(a or b) begin
  c = 1'bx;
  case ({a,b})
    2'b00: c = 1'b0;
    2'b01: c = 1'b1;
    2'b10: c = 1'b0;
  endcase
end
  
```

Synthesis

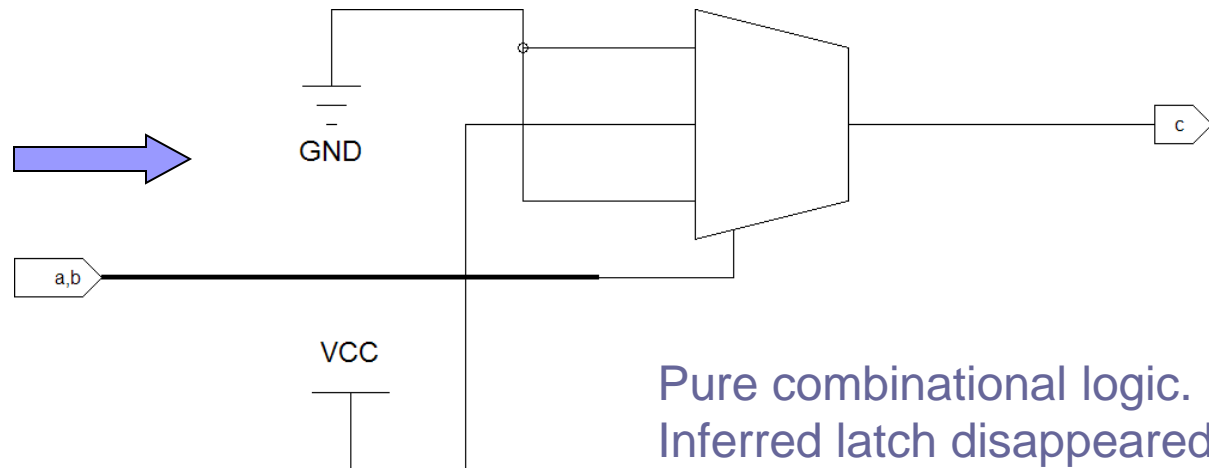 

Synthesis

 


Moral

- Latches are created by **case** statements that miss the code for an outcome of some input combinations. Such latches are typically unintended
- Workaround – Three possible solutions:
 - Every **case** statement should be a “*full*” **case** (covering all input combinations). Every variable that is assigned a value in one **case**, should also be assigned a value in every other **case** (even if we do not care about this value)
 - Unconditionally assign default values to variables. This can be done at the beginning of the **always** block or using the **default** statement
 - Using default values is a good coding practice, even though the **case** choices are *all-inclusive*. It accounts for ‘x’ and ‘z’ values at the inputs (especially for simulation)

Example 4

```
always @(a) begin
  if (~a)
    vec2 = ~vec3;
end
```

Synthesis

 

Nothing!
Why?!

The output `vec2` is an internal signal value that is not used to generate any output signal – thus, this section of code is redundant, and is optimized out by the synthesis tools


Moral

- Any logic that is deemed to be redundant may be optimized out by the synthesis tool
- Even a structural Verilog description may not result in the same structural connections once it is synthesized
- If the designer would like to retain a specific structure, then synthesis options must be used to disable “flattening” of the hierarchy. Submodules must be created (in order to create an artificial hierarchy), and “Don’t Touch” options must be checked for those submodules that must not be optimized

Example 5

```
always @(posedge clk) begin  
    f <= a;                // using nonblocking assignment  
    vec1 <= vec1 + 1;      // counter  
    vec2 <= vec2 + 1;      // This part will be optimized out  
    case (a)  
        1'b0: g <= b;  
        //default: g <= 1'bx; // What happens if this is uncommented?  
    endcase                // note that case 1'b1 is not covered  
end
```


Example 5 – Synthesis Results

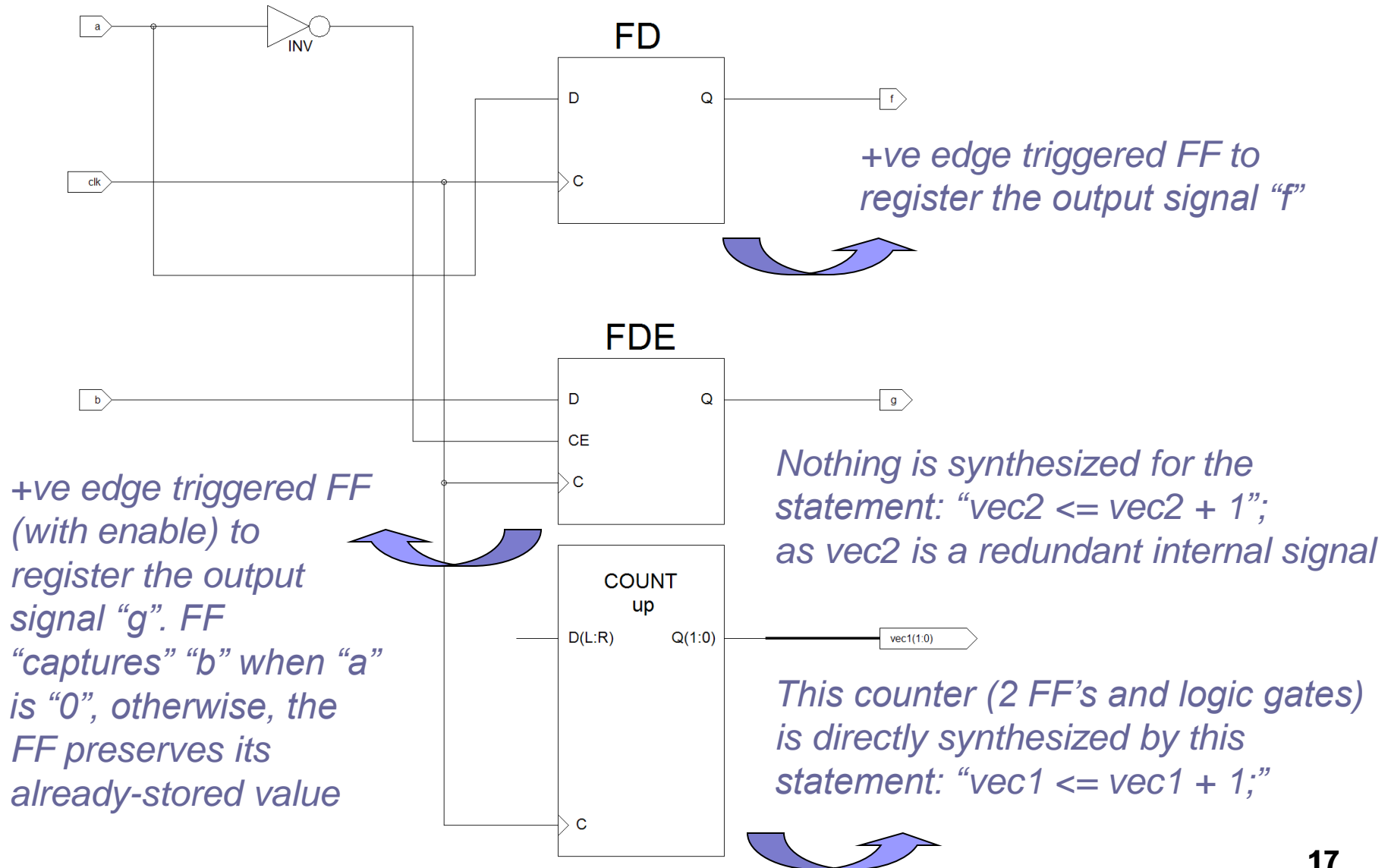

Example 6*

Multi-level nested if-else statement


```

always @(a or b or inp) begin
    if (a==1'b0)
        if (b==1'b0)
            if (inp==1'b0)
                f = 1'b0;
            else
                f = 1'b1;
        else
            if (inp==1'b0)
                f = 1'b1;
            else
                f = 1'b0;
    else
        if (b==1'b0)
            if (inp==1'b0)
                f = 1'b1;
            else
                f = 1'b1;
        else
            if (inp==1'b0)
                f = 1'b0;
            else
                f = 1'b0;
end

```

**An input port (inp) is added to the module template for this specific example*

Example 6 – Synthesis Results

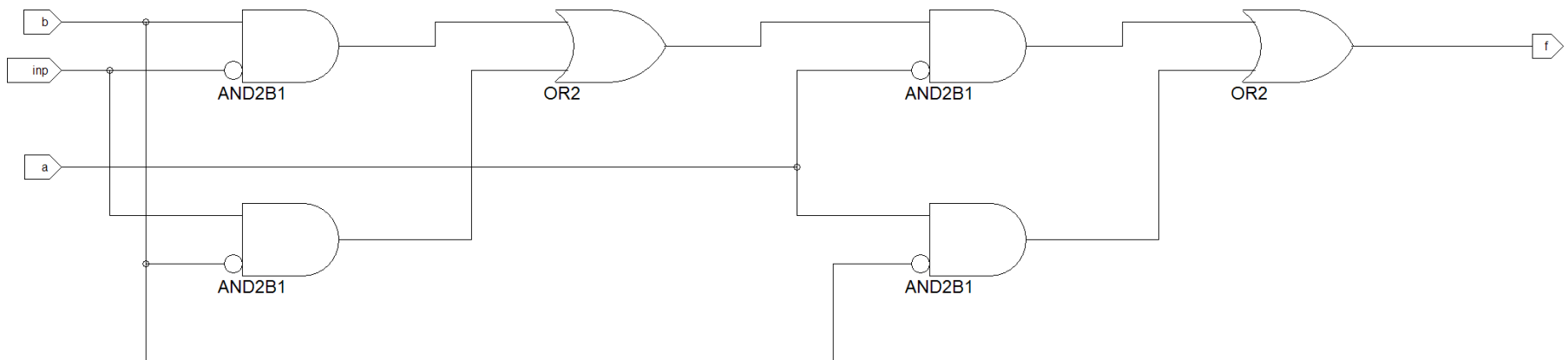

-Completely Serial Circuit


-Long Critical Path (4 “gate-levels”)

Example 6 – Workaround I

*Parallel if-else
statement*

```
always @(a or b or inp) begin  
    if (a==1'b0 && b==1'b0 && inp==1'b0)  
        f = 1'b0;  
    else if (a==1'b0 && b==1'b0 && inp==1'b1)  
        f = 1'b1;  
    else if (a==1'b0 && b==1'b1 && inp==1'b0)  
        f = 1'b1;  
    else if (a==1'b0 && b==1'b1 && inp==1'b1)  
        f = 1'b0;  
    else if (a==1'b1 && b==1'b0 && inp==1'b0)  
        f = 1'b1;  
    else if (a==1'b1 && b==1'b0 && inp==1'b1)  
        f = 1'b1;  
    else if (a==1'b1 && b==1'b1 && inp==1'b0)  
        f = 1'b0;  
  
    else  
        f = 1'b0;  
  
end
```

Workaround I – Synthesis Results

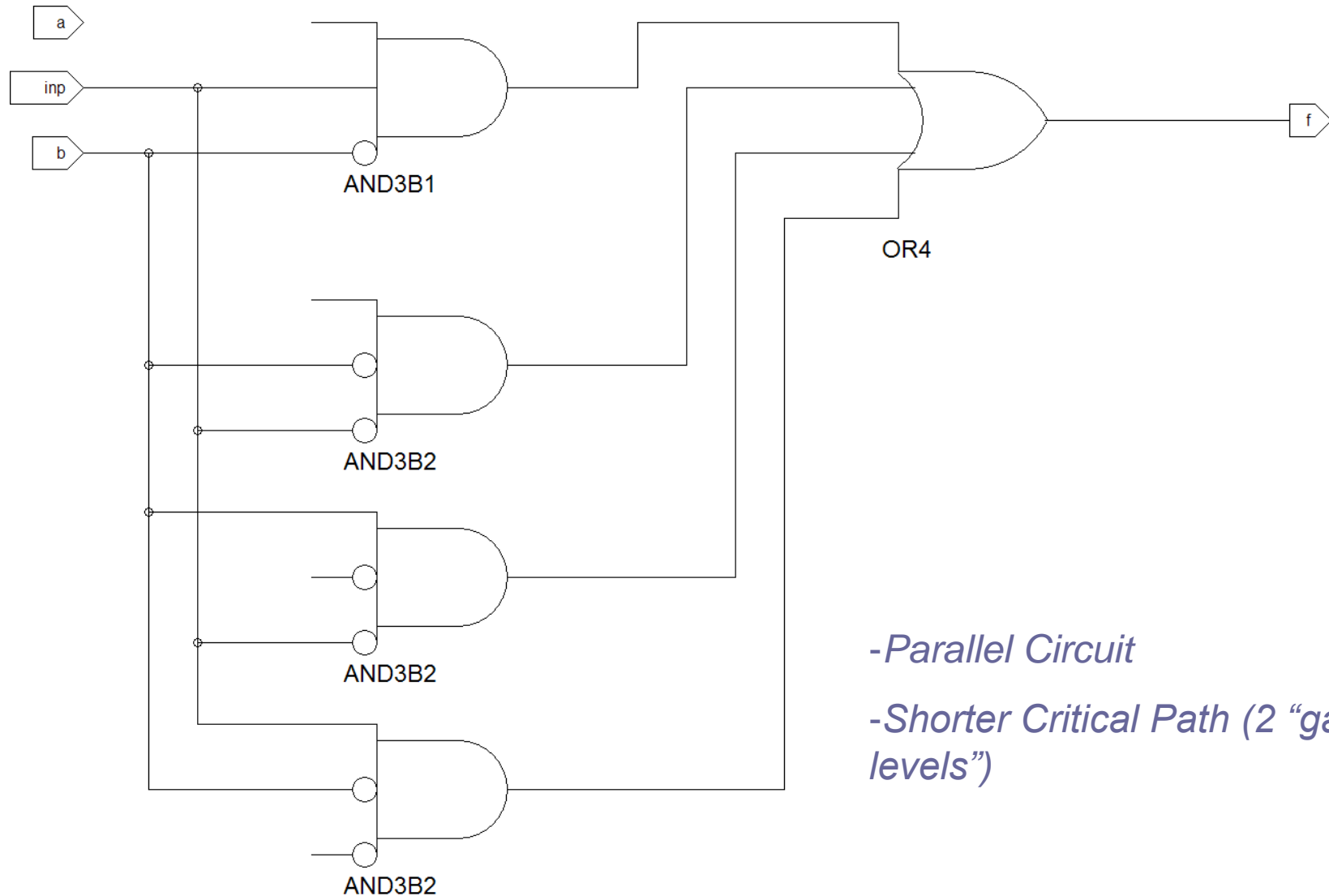

-Parallel Circuit


-Shorter Critical Path (2 “gate-levels”)

Example 6 – Workaround II

*Parallel case
statement*

```
always @(a or b or inp)
    case ({a,b,inp})
        3'b000: f = 1'b0;
        3'b001: f = 1'b1;
        3'b010: f = 1'b1;
        3'b011: f = 1'b0;
        3'b100: f = 1'b1;
        3'b101: f = 1'b1;
        3'b110: f = 1'b0;
        default: f = 1'b0;
    endcase
```

Workaround II – Synthesis Results

 

- Optimized ROM (or MUX) circuit
- 2 “gate-levels”



Moral

- “Serial” control structures (like nested **if-else** statements) can result in corresponding serial chain of logic gates to test conditions
- It is often better to use a **case** statement, especially if the conditions are *mutually exclusive* (so can be evaluated in parallel). This is strongly valid for situations with two or more cases

Non-blocking Assignment

```

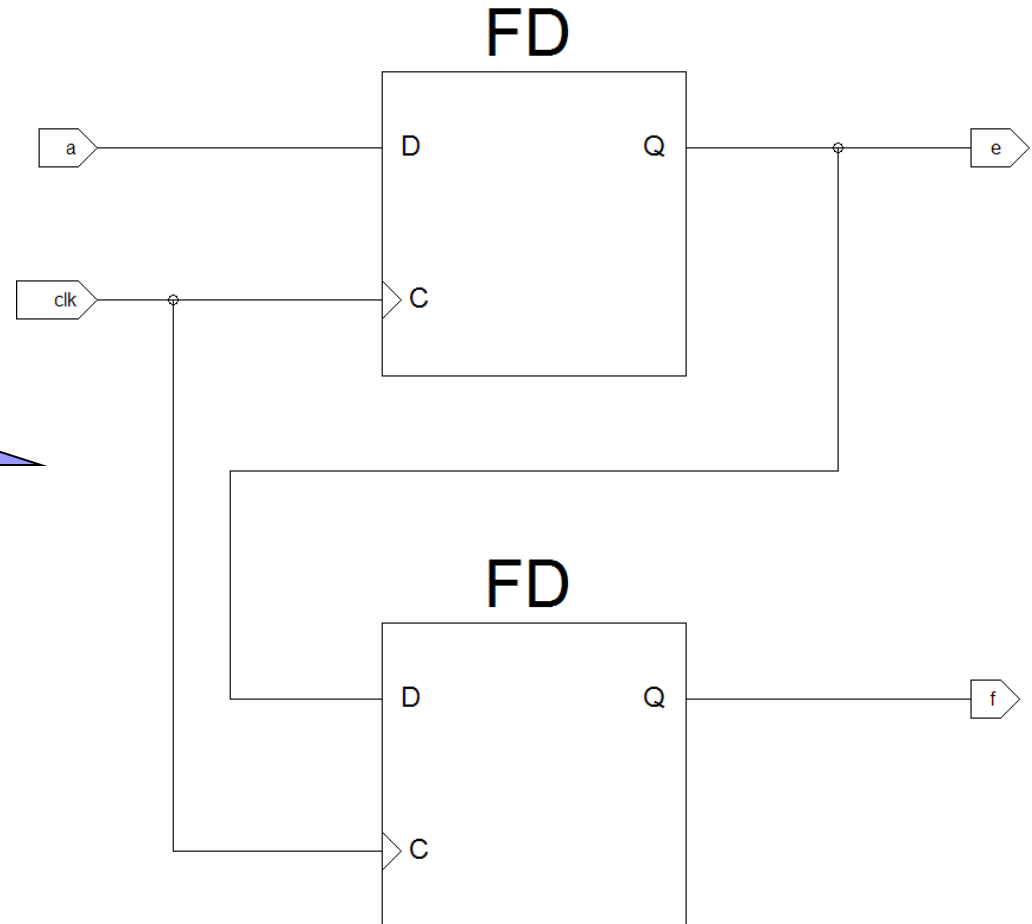 always @(posedge clk) begin
    e <= a;
    f <= e;
end
    
```





Blocking Assignment

```

always @(posedge clk) begin
    e = a;
    f = e;
end
    
```

Synthesis

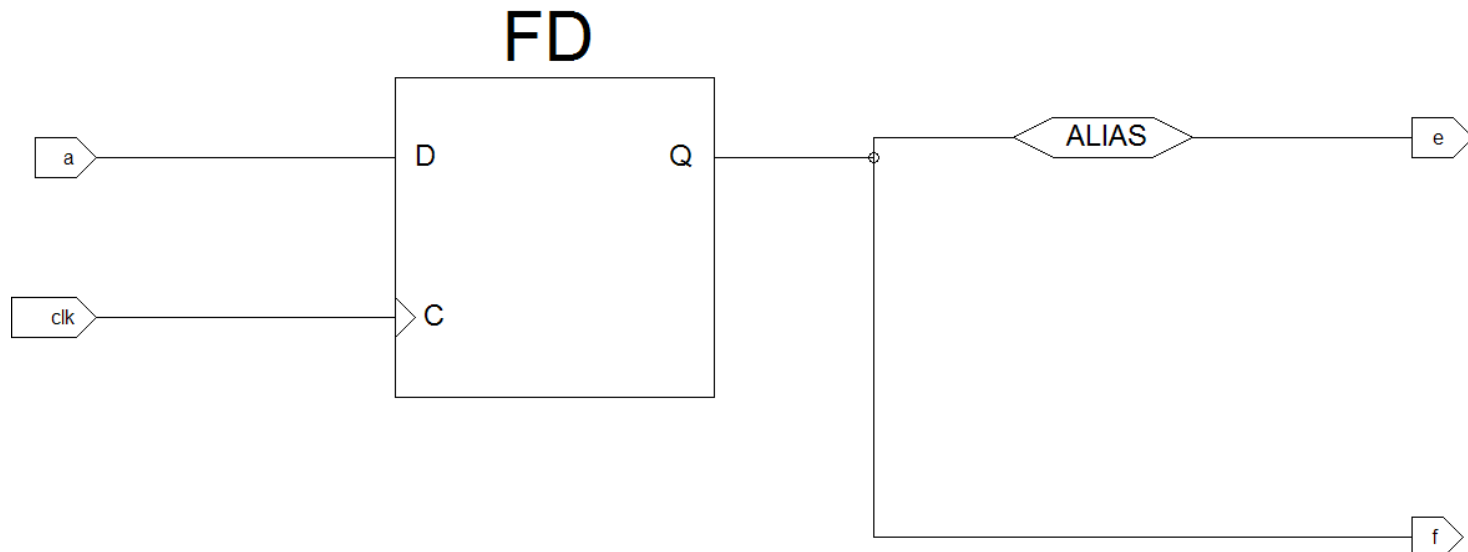 

Examples of Non-synthesizable Verilog HDL Features

- The “delay” statements “#”
- The “**initial**” blocks
- Usage of sensitivity lists that contain data inputs beside the clock-edge (other than the RST)
- **Always** blocks that are sensitive to both the *rising* and the *falling* edges of the same signal
- Such statements still can be useful in:
 - Testbenches (as they are not synthesized; they are generally used to test the behavior of the circuit)
 - Early-stage models of the circuit to perform early verification of its behavior

Concept of Simulation

- Pretends to simulate concurrent statements using event lists and sensitivity matrix, based on all the individual sensitivity lists
- Each concurrent statement gives rise to at least one SW process in the simulator
- At every *simulation cycle*, the “concurrent” processes are executed one after the other
- After a simulation cycle completes, the event list is scanned for the signal(s) that change at the earliest time on the list, and the simulation time advances to this time
- All the processes that are sensitive to a signal that just changed are scheduled for execution in the next simulation cycle, which now begins

Further Recommended Coding Practices

- Look at the synthesis options, and choose the ones that suits your needs
- Inspect the synthesized circuit whenever possible
- Loops generally create multiple copies of combinational logic. If you prefer re-using one copy of combinational logic, then use an FSM-controlled sequential circuit
- Avoid using **always** blocks with empty sensitivity list

Practice Assignment

- Redo all examples of this lecture using Quartus II RTL Viewer
- Analyze the difference(s) if any, and consult your professor if you fail to explain it

References

- Digital Design, 4th Edition, John Wakerly
- Advanced Digital Logic Design, Sunggu Lee
- www.ece.cmu.edu/~thomas/VSLIDES.pdf