



EECS 3201: Digital Logic Design Lecture 14

Ihab Amer, PhD, SMIEEE, P.Eng.

Modular Approach

- A digital system is a sequential logic system constructed with flip-flops and gates
- Number of states in actual digital systems is typically high
- This makes it difficult to represent large digital systems with state tables
- Hence, digital systems are typically designed using a modular approach
- A system is partitioned into modular subsystems, each of which performs some functional task
- Examples of subsystems are registers, decoders, multiplexers, arithmetic elements, and control logic
- Modules are interconnected with common data and control paths

Register Transfer Level (RTL)

- A digital system is represented at the RTL level by the following three components:
 - The set of registers in the system
 - Operations performed on data stored in registers (e.g. transfer, arithmetic, logic, and shift)
 - Control that supervises the sequence of operations in the system

Examples of RTL Statements

- $R2 \leftarrow R1$
- If($T1 = 1$) then ($R2 \leftarrow R1$)
- If($T3 = 1$) then ($R2 \leftarrow R1, R1 \leftarrow R2$)
- $R1 \leftarrow R1 + R2$ (Add contents of R2 to R1)
- $R3 \leftarrow R3 + 1$ (Increment R3 by 1)
- $R4 \leftarrow \text{shr } R4$ (Shift right R4)
- $R5 \leftarrow 0$ (Reset R5 to 0)

RTL in HDL

assign S = A + B;

Combinational Logic

always @ (A or B)

S = A + B;

Sequential Logic

always @ (posedge clock)

begin

RA = RA + RB;

RD = RA

end

always @ (negedge clock)

begin

RA <= RA + RB;

RD <= RA

end

Accurately models synchronous sequential circuits

Looping Statements


```
//description of 2x4 decoder
//using for-loop statement
module decoder (IN, Y);
    input [1:0] IN; //Two binary inputs
    output [3:0] Y; //Four binary outputs
    reg [3:0] Y;
    integer I; //control variable for loop
    always @ (IN)
        for (I = 0; I <= 3; I = I + 1)
            if (IN == I) Y[I] = 1;
            else Y[I] = 0;
endmodule
```

Looping statements (e.g. *repeat*, *forever*, *while*, and *for*) must appear inside an **initial** or **always** block

Refer to Mano textbook for examples of other types of loops

```
if (IN == 00) Y[0] = 1; else Y[0] = 0;
if (IN == 01) Y[1] = 1; else Y[1] = 0;
if (IN == 10) Y[2] = 1; else Y[2] = 0;
if (IN == 11) Y[3] = 1; else Y[3] = 0;
```

Structure of a Typical Digital System

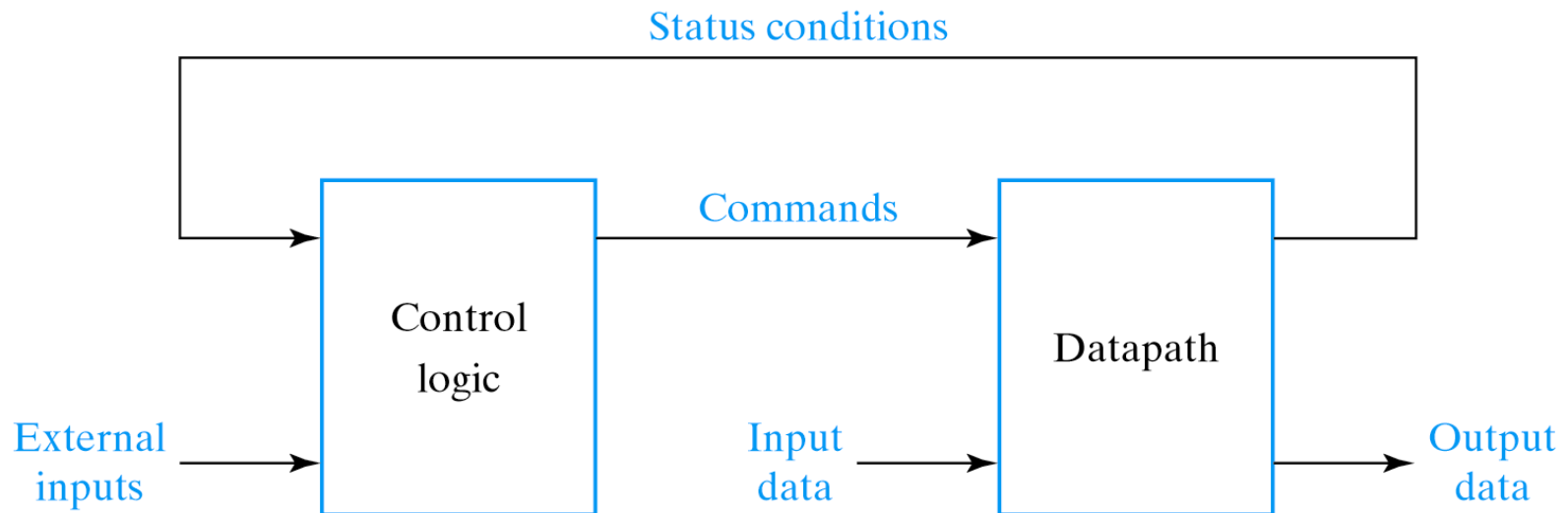

Control and Datapath Interaction

Control Unit (Control)

- Controls Data Movements in the Execution Unit by Switching Multiplexers and Enabling or Disabling Resources
- Follows Some 'Program' or Schedule
- Often Implemented as Finite State Machine or collection of Finite State Machines

Execution Unit (Datapath)


- Provides All Necessary Resources and Interconnects Among Them to Perform Specified Task
- Examples of Resources
 - Adders, Multipliers, Registers, Memories, etc.

Algorithmic State Machine (ASM)


- Representation of a Finite State Machine that is suitable for digital systems with a larger number of inputs, outputs, and states compared to FSMs that are expressed using state diagrams and state tables

Elements Used in ASM Charts

(1/2)

 


(a) General description

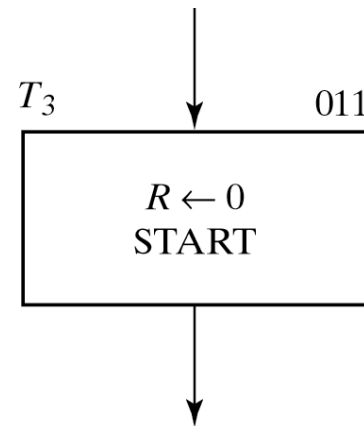


(b) Specific example

State Box

 

Decision Box

 


Elements Used in ASM Charts


(2/2)

Conditional Box

From exit path of decision box

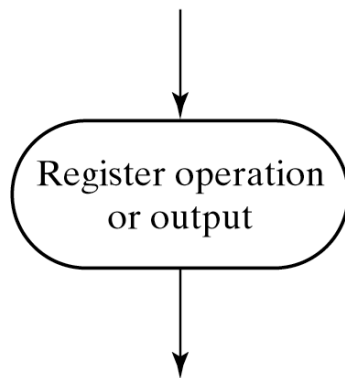


(a) General description

 


(b) Example with conditional box

ASM Block

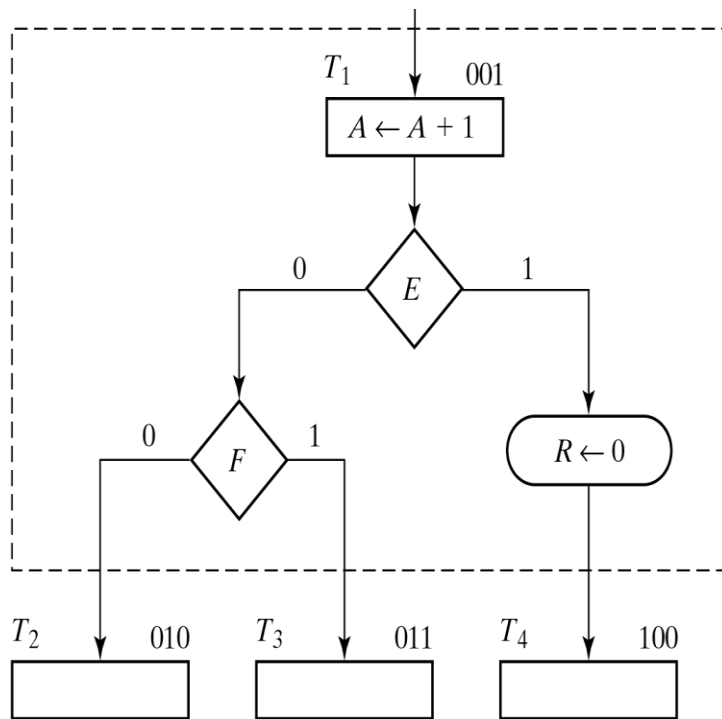

ASM Block

 


State Diagram Equivalent to the ASM Chart

Timing Considerations

- In the previous ASM block, the following operations occur in synchronism during the clock edge transition (simultaneously):

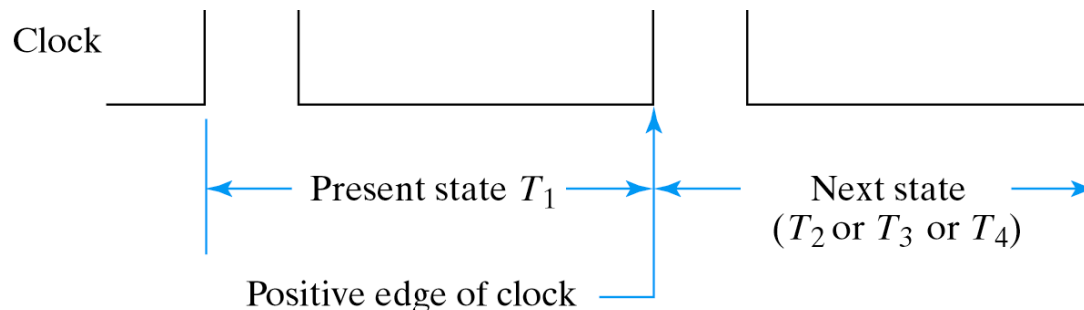
- Register A is incremented
 - If $E = 1$, register R is cleared
 - Control transfers to the next state
- Operations in datapath*
- Change in control logic*



Design Example

- Design a digital system with two flip-flops, E & F, and one 4-bit binary counter A ($A_4A_3A_2A_1$). A start signal S initiates system operation by clearing the counter A and flip-flop F. The counter is then incremented by one starting from the next clock pulse and continues to increment until the operations stop. Bits A_3 and A_4 determine the sequence of operations as follows:
 - If $A_3 = 0$, E is cleared and count continues
 - If $A_3 = 1$, E is set to 1; then if $A_4 = 0$, count continues, but if $A_4 = 1$, F is set to 1 on the next clock pulse and the system heads to initial state the clock pulse after
 - Then if $S = 0$, the system remains in the initial state, but if $S = 1$, the operation cycle repeats

ASM Chart

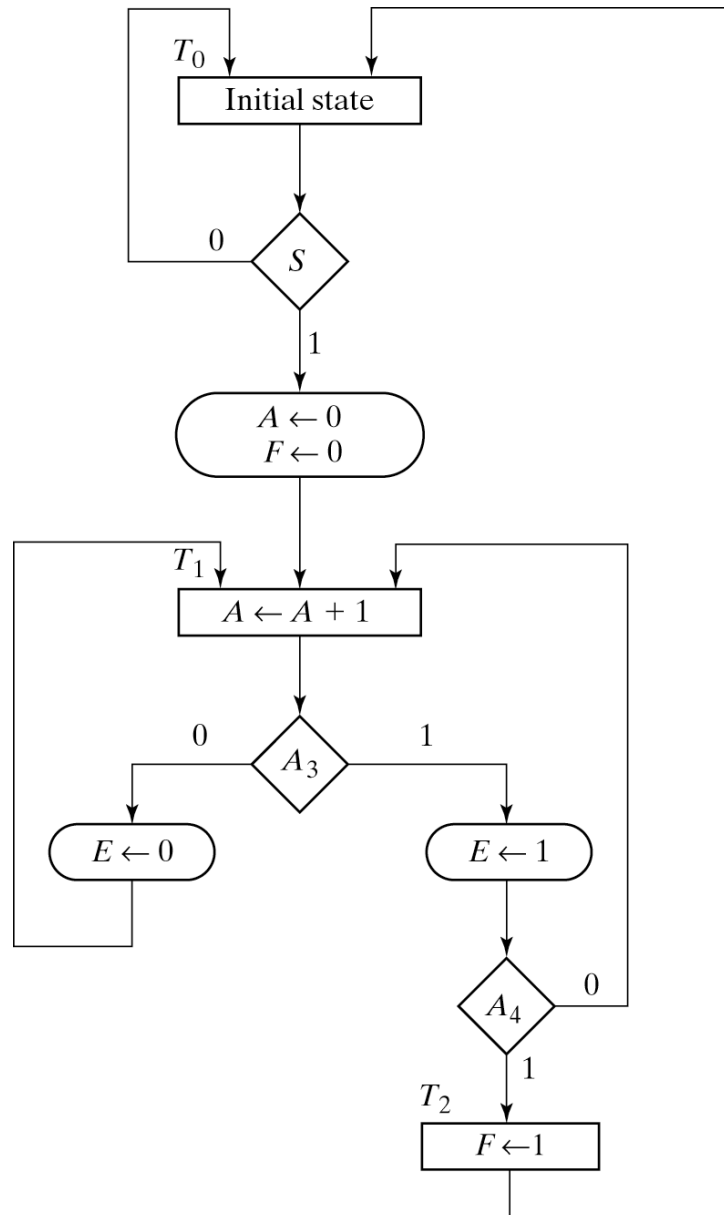


Sequence of Operations


Counter

Flip-Flops


A_4	A_3	A_2	A_1	E	F	Conditions	State
0	0	0	0	1	0	$A_3 = 0, A_4 = 0$	T_1
0	0	0	1	0	0		
0	0	1	0	0	0		
0	0	1	1	0	0		
0	1	0	0	0	0	$A_3 = 1, A_4 = 0$	
0	1	0	1	1	0		
0	1	1	0	1	0		
0	1	1	1	1	0		
1	0	0	0	1	0	$A_3 = 0, A_4 = 1$	
1	0	0	1	0	0		
1	0	1	0	0	0		
1	0	1	1	0	0		
1	1	0	0	0	0	$A_3 = 1, A_4 = 1$	
1	1	0	0	1	0		T_2
1	1	0	0	1	1		T_0

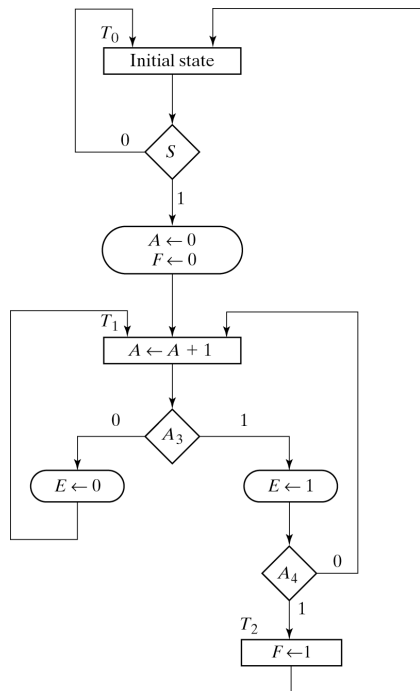

Datapath of Design

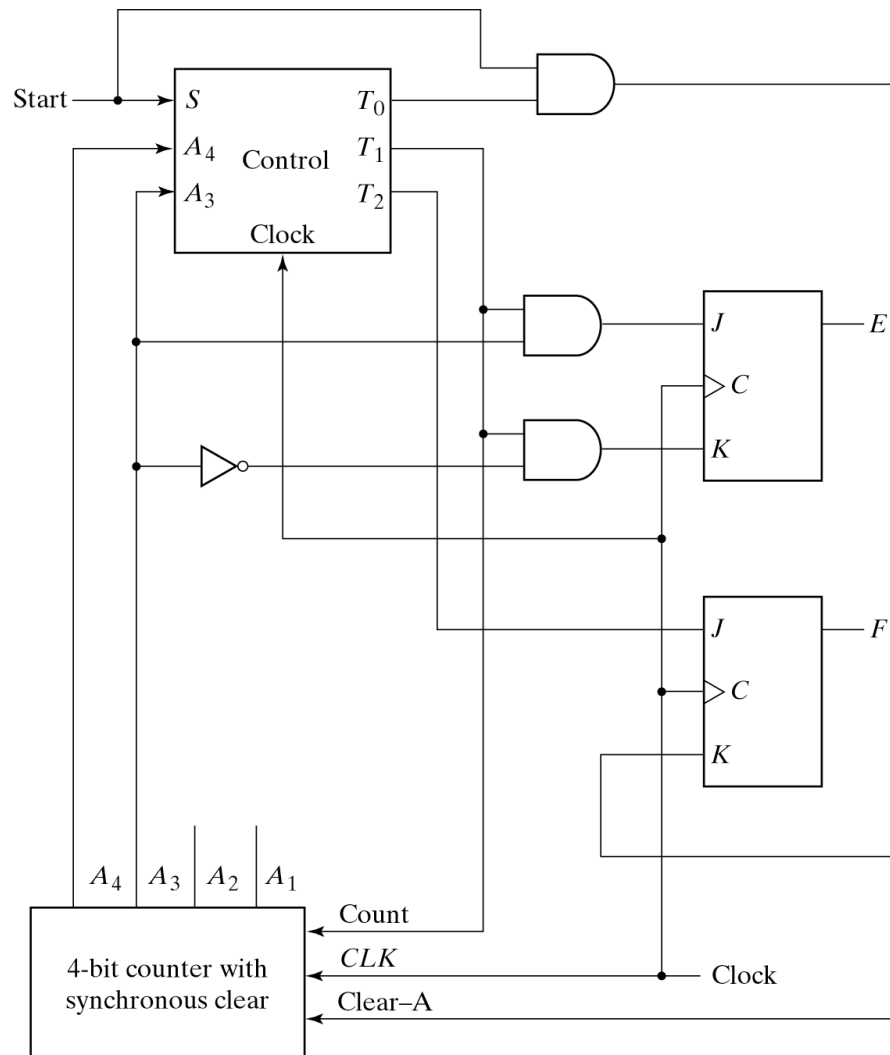

RTL Description

 

(a) State diagram for control

T_0 : if ($S = 1$) then $A \leftarrow 0, F \leftarrow 0$

T_1 : $A \leftarrow A + 1$

if ($A_3 = 1$) then $E \leftarrow 1$

if ($A_3 = 0$) then $E \leftarrow 0$


T_2 : $F \leftarrow 1$

(a) Register transfer operations

State Table for Control

Present -State Symbol	Present State		Inputs			Next State		Outputs		
	G_1	G_0	S	A_3	A_4	G_1	G_0	T_0	T_1	T_2
T_0	0	0	0	X	X	0	0	1	0	0
T_0	0	0	1	X	X	0	1	1	0	0
T_1	0	1	X	0	X	0	1	0	1	0
T_1	0	1	X	1	0	0	1	0	1	0
T_1	0	1	X	1	1	1	1	0	1	0
T_2	1	1	X	X	X	0	0	0	0	1

Control Logic

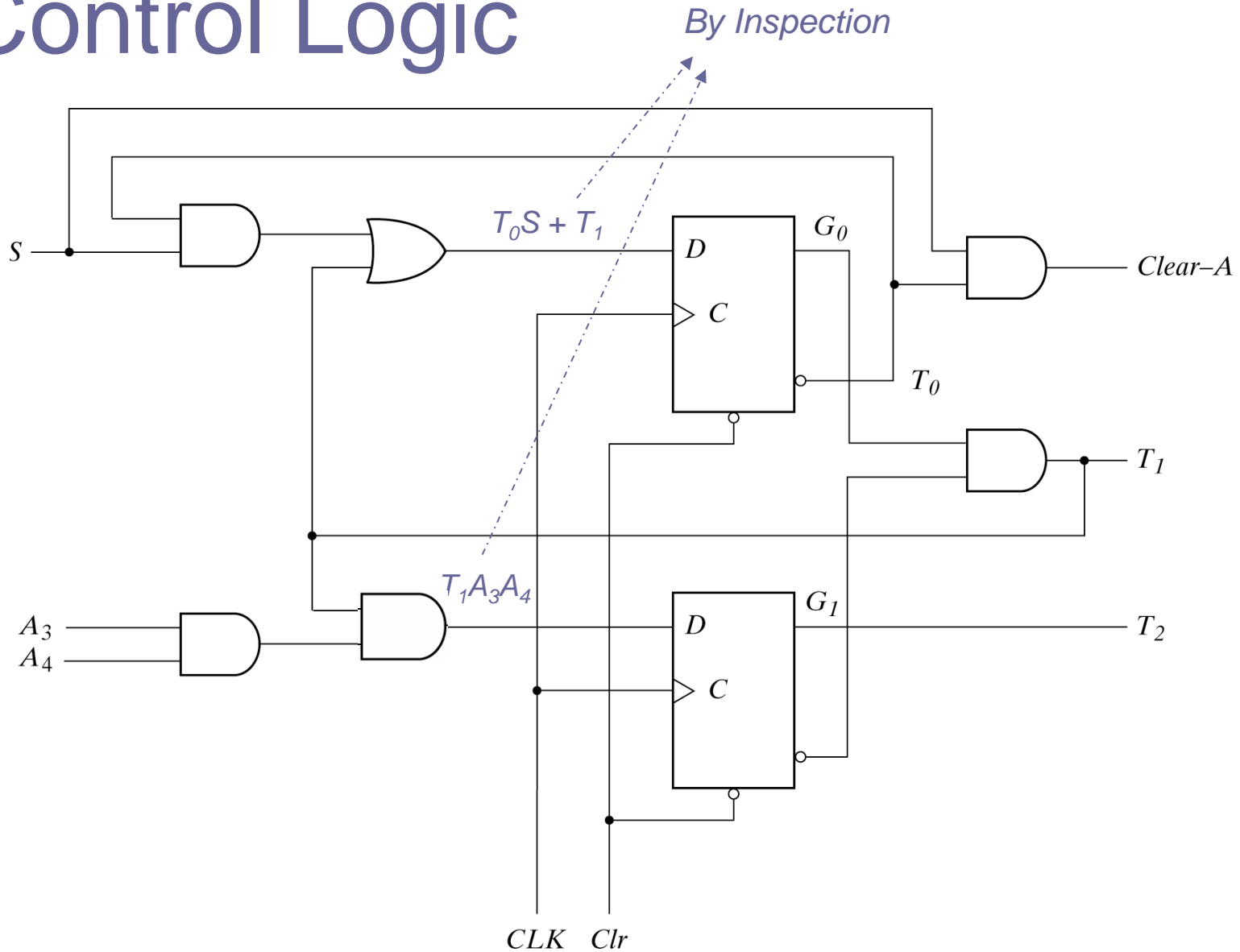

References

- Digital Design, M. Morris, Mano