



EECS 3201: Digital Logic Design Lecture 16

Ihab Amer, PhD, SMIEEE, P.Eng.

Forget EECS 3201 – Lets try to solve a “real problem” 😊

INPUT:
dirty laundry



OUTPUT:
6 more weeks



Device: Washer

Function: Fill, Agitate, Spin

Washer_{PD} = 30 mins




Device: Dryer

Function: Heat, Spin

Dryer_{PD} = 60 mins

One Load at a Time

*Non-Engineers
would do that*

 


$$\begin{aligned} \text{Total} &= \text{Washer}_{PD} + \text{Dryer}_{PD} \\ &= \underline{\quad 90 \quad} \text{ mins} \end{aligned}$$

Not a smart idea!

Doing N Loads of Laundry

 
*Still with the non-engineers
“combinational” way*



$$\begin{aligned} \text{Total} &= N * (\text{Washer}_{PD} + \text{Dryer}_{PD}) \\ &= \underline{\quad N * 90 \quad} \text{ mins} \end{aligned}$$

This is how engineers would do it

 *So, engineering sense,
sometimes, makes sense!*



Actually, it's more like $N \cdot 60 + 30$ if we account for the startup transient correctly. When doing pipeline analysis, we're mostly interested in the "steady state" where we assume we have an infinite supply of inputs.

$$\begin{aligned} \text{Total} &= N * \text{Max}(\text{Washer}_{PD}, \text{Dryer}_{PD}) \\ &= \underline{\quad N \cdot 60 \quad} \text{ mins} \end{aligned}$$

Some Definitions (1/2)

Latency

The *delay* from when an input is established until the output associated with that input becomes valid

Non-Engineers' Laundry = 90 mins

Engineers' Laundry = 120 mins

At steady state

Throughput

The *rate* of which inputs or outputs are processed

Non-Engineers' Laundry = 1/90 outputs/mins


Engineers' Laundry = 1/60 outputs/mins

Some Definitions (2/2)

Pipelining

Break task into stages, each stage outputs data for next stage, all stages operate concurrently (if they have data)

Ok... Back to Digital Logic ☹️

 


For combinational logic:

$$\text{latency} = t_{PD}$$

$$\text{throughput} = 1/t_{PD}$$

 
We can't get the answer faster, but are we making effective use of our hardware at all times?



F & G are "idle", just holding their outputs stable while H performs its computation

Pipelined Circuits — Use registers to hold

H's input stable

 


Now F & G can be working on input X_{i+1} while H is performing its computation on X_i . We've created a 2-stage *pipeline*: if we have a valid input X during clock cycle j, P(X) is valid during clock j+2.

Suppose F, G, H have propagation delays of 15, 20, 25 ns and we are using ideal zero-delay registers:

	<u>latency</u>	<u>throughput</u>
unpipelined	45	1/45
2-stage pipeline	<u>50</u>	<u>1/25</u>
	worse	better

Pipeline Diagrams

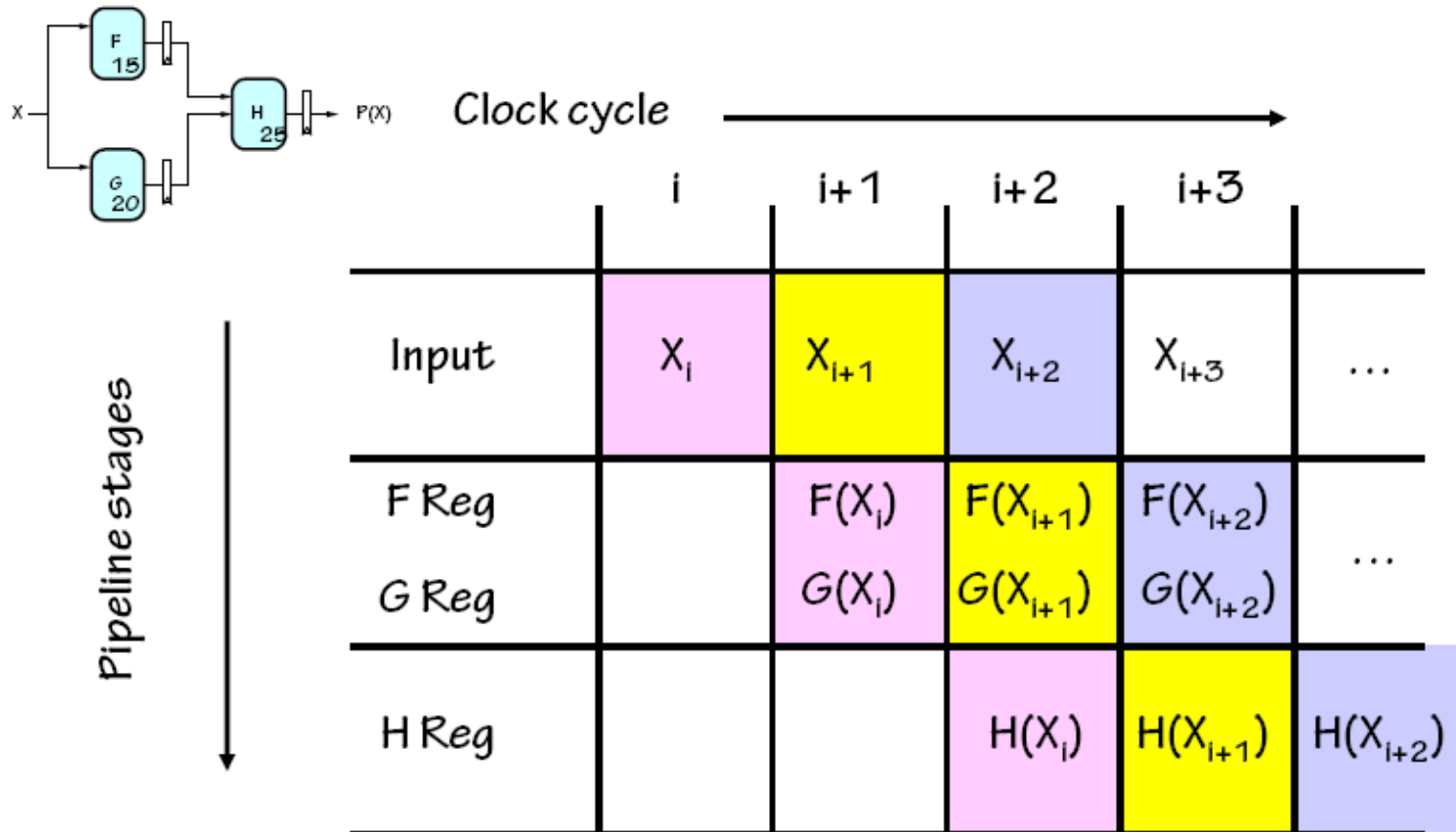

The results associated with a particular set of input data moves *diagonally* through the diagram, progressing through one pipeline stage each clock cycle.

Pipeline Conventions

DEFINITION:

a *K-Stage Pipeline* (“K-pipeline”) is an acyclic circuit having exactly K registers on every path from an input to an output.

a COMBINATIONAL CIRCUIT is thus an 0-stage pipeline.

CONVENTION:

Every pipeline stage, hence every K-Stage pipeline, has a register on its *OUTPUT* (not on its input).



ALWAYS:

The CLOCK common to all registers must have a period sufficient to cover propagation over combinational paths PLUS (input) register t_{PD} PLUS (output) register t_{SETUP} .


The LATENCY of a K-pipeline is K times the period of the clock common to all registers.

The THROUGHPUT of a K-pipeline is the frequency of the clock.

Pipelining Example (1/5)

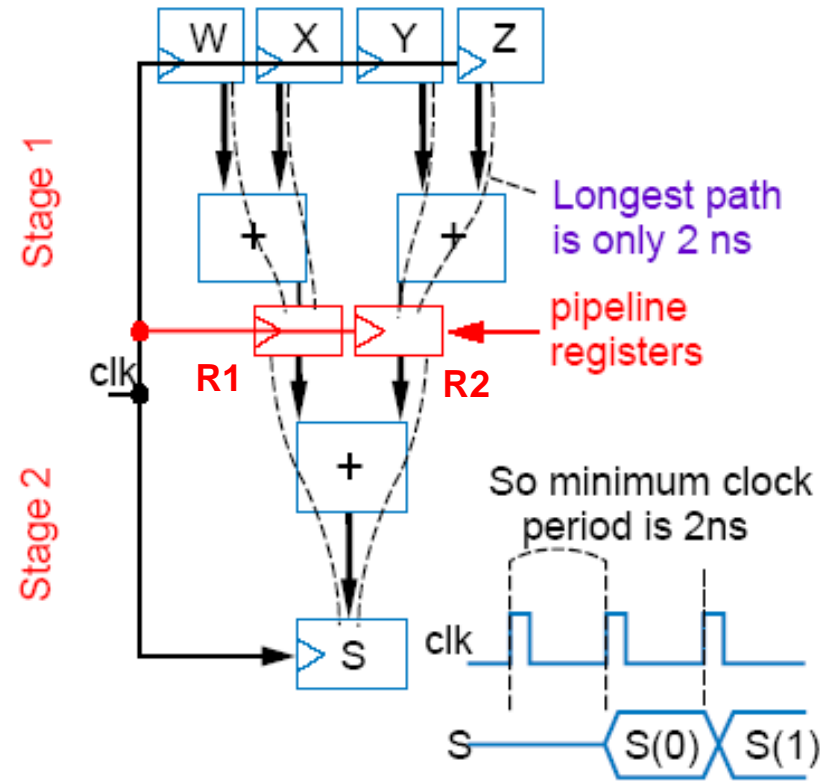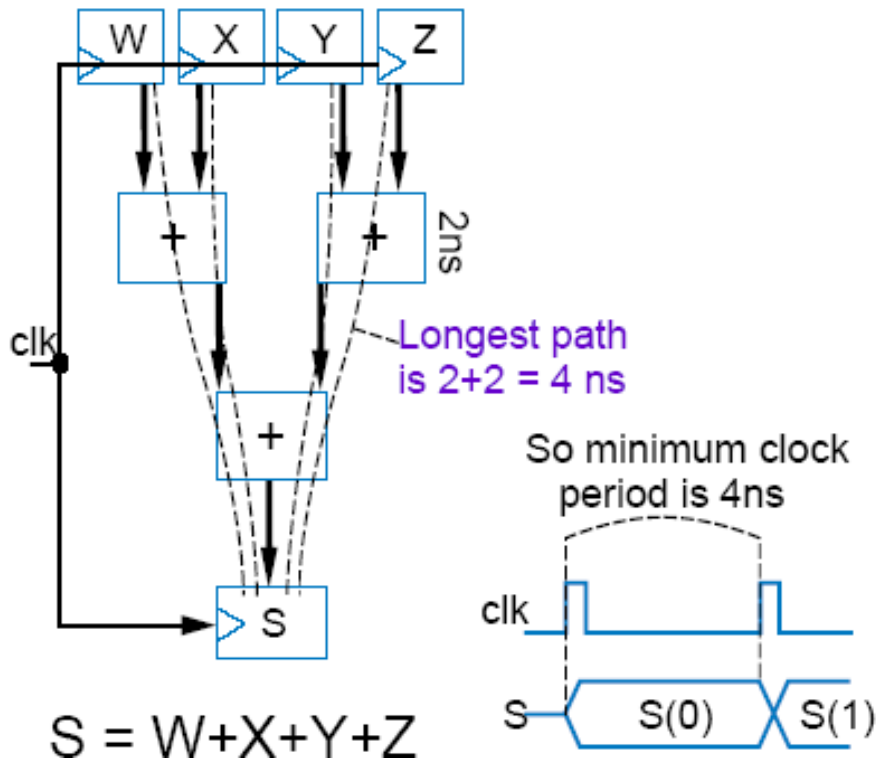

Pipelining Example (2/5)

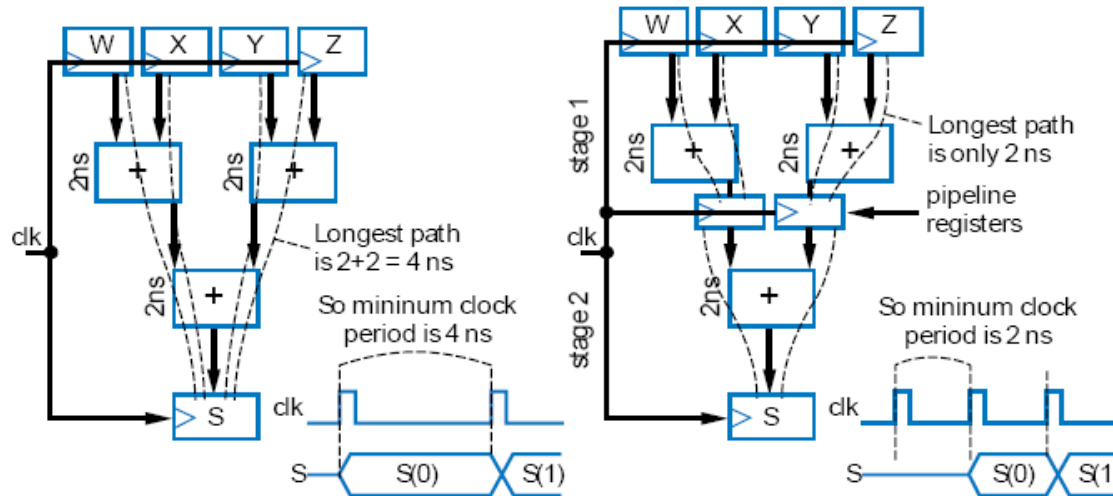


- Datapath on left has *critical path* of **4 ns**, so shortest clock period is **4 ns**
 - Can read new data, add, and write data to S, every **4 ns**
- Datapath on right has *critical path* of only **2 ns**
 - So can read new data every **2 ns** – sort of doubled performance
- So Pipelining the above system
 - Doubled the *throughput*, from 1 item / 4 ns, to 1 item / 2 ns
 - Latency stayed the same: **4 ns** (sometimes it may increase)

Pipelining Example (3/5)


```
module pipeline(W, X, Y, Z, CLK, Clr, S);  
  input CLK, Clr;  
  input [3:0] W; input [3:0] X; input [3:0] Y; input [3:0] Z;  
  output [5:0] S;  
  reg [5:0] S;  
  reg [4:0] R1;  
  reg [4:0] R2;  
  always @ (posedge CLK or negedge Clr)  
    if (~Clr) S <= 6'b000000;  
    else  
      begin  
        R1 <= W + X;  
        R2 <= Y + Z;  
        S <= R1 + R2;  
      end  
endmodule
```

Pipelining Example (4/5)

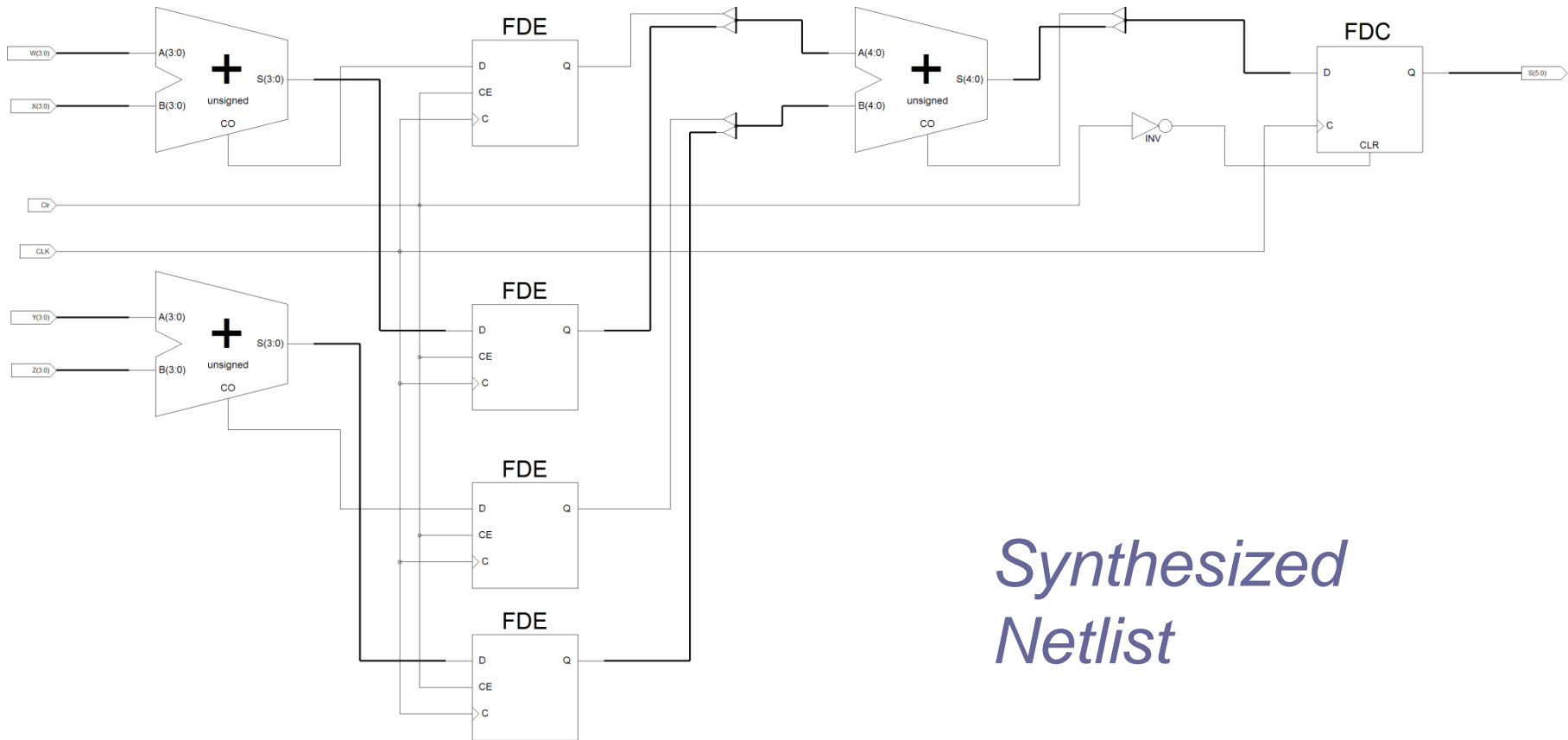

*Synthesized
Netlist*

Pipelining Example (5/5)

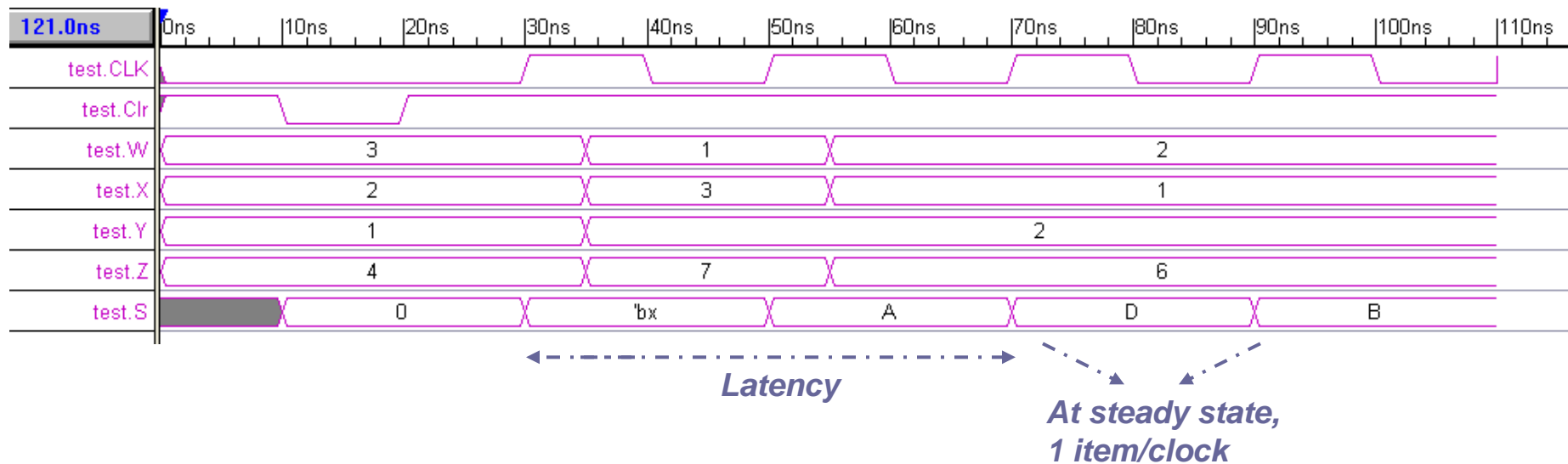

Simulation

Pipelining Summary

■ Advantages:

- Allows us to increase throughput, by breaking up long combinational paths and (hence) increasing clock frequency

■ Disadvantages:

- May increase latency
- Only as good as the weakest link: slowest step constraints system throughput

References

- MIT Lecture Notes on:
<http://www.ece.concordia.ca/~asim>
- <http://www.ics.uci.edu/~harris/ics151/>