



EECS 3201: Digital Logic Design Lecture 4

Ihab Amer, PhD, SMIEEE, P.Eng.

What is a HDL?

- A high-level computer language that can describe digital systems in textual form
- Two applications of HDL processing:
 - Logic Simulation
 - Logic Synthesis

HDL Applications

□ Logic Simulation

- A simulator translates the HDL description to a readable output such as *timing diagram*
- It predicts how the hardware will work before it is actually fabricated
- Functional errors can be corrected before actual fabrication
- Stimulus that tests the design is called *test-bench* (also written in HDL)

□ Logic Synthesis

- Deriving the *gate-level netlist* from the HDL
- Typically accompanied with optimization, and automated with computer software
- Restrictions on coding style for RTL model
- The outcome (netlist) is tool dependent

IEEE-Supported HDL's

EECS 3201

VHDL

- VHSIC HDL
- Based on Ada
- Department of defense (DARPA) mandated language
- Generally, considered more difficult to learn



- Verify Logic
- Based on C
- Started as a Gateway Design proprietary language then later bought by Cadence
- Generally, considered easier to learn

Example (Simple Circuit)

Module name *Ports names* *Punctuation*

```
module smpl_ct (A, B, C, x, y);
```



Ports *modes* *Internal connection*

```
input A, B, C;
output x, y;
wire e;
```

Primitive gates *Gate output* *Gate inputs*

```
and g1(e, A, B);
not g2(y, C);
or g3(x, e, y);
```

endmodule *Optional gate-name*

  

Gate Delays

```
module ct_with_delay (A, B, C, x, y);
```

```
    input A, B, C;
```

```
    output x, y;
```

```
    wire e; → Gate delay in (ns)
```


```
    and #(30) g1(e, A, B);
```

```
    or #(20) g3(x, e, y);
```

```
    not #(10) g2(y, C);
```


```
endmodule
```

Time (ns)	Input A B C	Output y e x
–	0 0 0	1 0 1
–	1 1 1	1 0 1
10	1 1 1	0 0 1
20	1 1 1	0 0 1
30	1 1 1	0 1 0
40	1 1 1	0 1 0
50	1 1 1	0 1 1

 

Simulation Output

Timing Diagram

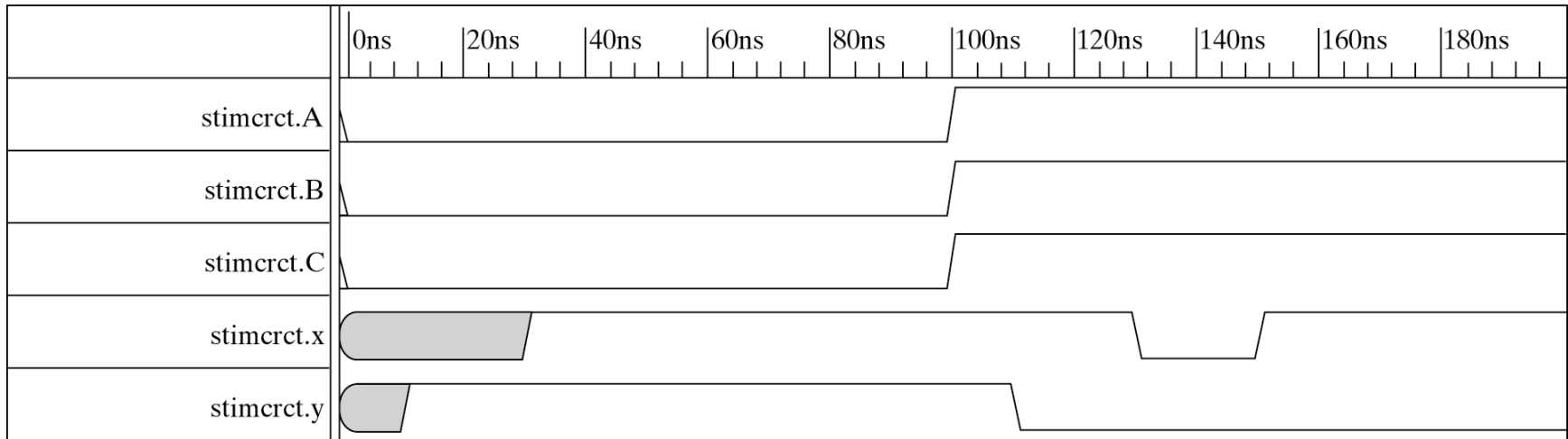

Boolean Expression



```
module ct_bln (A, B, C, x, y);
```

```
  input A, B, C;
```

```
  output x, y;
```

```
  assign x = (A & B) | ~C;
```

```
endmodule
```

  


Verilog HDL Operators


- Refer to table 4-10 of Mano textbook for a list of Verilog HDL Operators

Three-State Gates


Tri-state buffer

 

if1 vs. if0 tri-state buffers

 


bufif1

 


bufif0

if1 vs. if0 tri-state inverters

 

notif1

 

notif0

Four-Valued Logic

■ Verilog Logic Values

- The underlying data representation allows for any bit to have one of four values:
- 0, 1, z (high impedance), and x (unknown)

No Question!

- *A possible output from tri-state gates*
- *It is a real electric effect*

- *Not a real value*
- *Maybe 0, 1, z, or in the state of change*
- *Simulator cannot determine the value, and perhaps you should worry!*

Truth Tables for Primitive Gates


and	0	1	x	z
0	0	0	0	0
1	0	1	x	x
x	0	x	x	x
z	0	x	x	x

or	0	1	x	z
0	0	1	x	x
1	1	1	1	1
x	x	1	x	x
z	x	1	x	x


xor	0	1	x	z
0	0	1	x	x
1	1	0	x	x
x	x	x	x	x
z	x	x	x	x

not	input	output
	0	1
	1	0
	x	x
	z	x

Verilog Design Styles

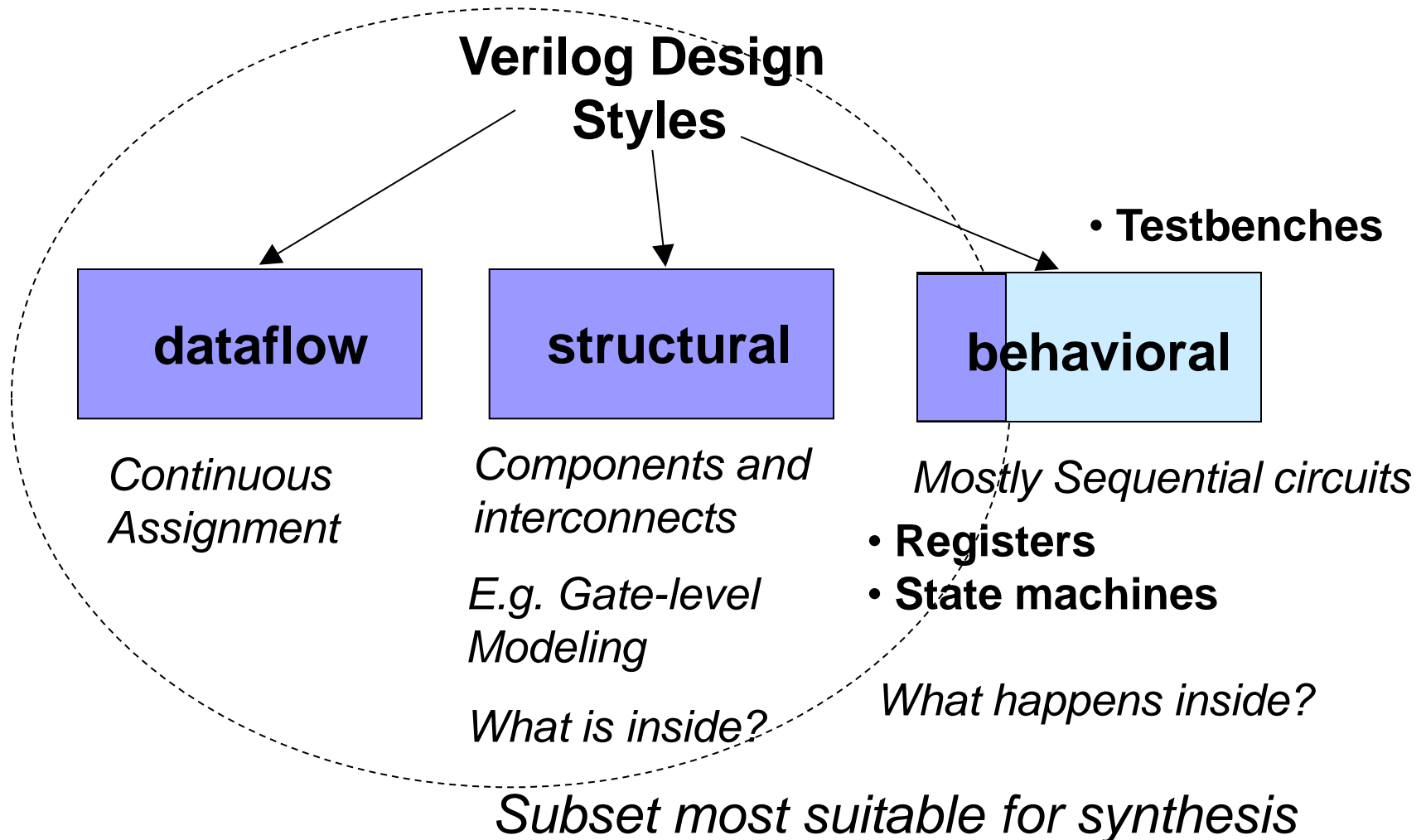

Example – 2:1 MUX

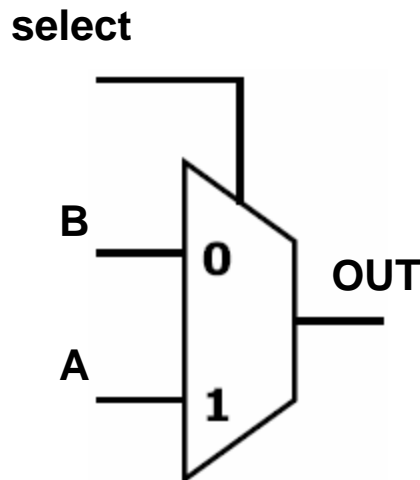

select	OUT
0	B
1	A

$$\text{OUT} = (A \cdot \text{select}) + (B \cdot \text{select}')$$

Gate-Level Model

```


module mux2x1_gl (A, B, select, OUT);

    input A, B, select;
    output OUT;
    wire s_comp, c, d;

    not g1(s_comp, select);
    and g2(c,select,A);
    and g3(d,s_comp,B);
    or g4(OUT,c,d);

endmodule
    
```

Components
and
Interconnects

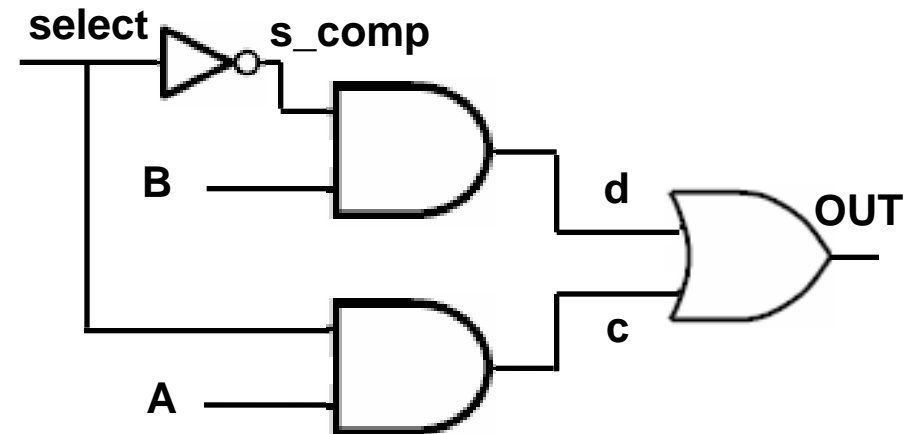

Dataflow Model

```

module mux2x1_df1 (A, B, select, OUT);
    input A, B, select;
    output OUT;
    assign OUT = (A & select) | (B & ~select);
endmodule
    
```

**Continuous
Assignment**

```

module mux2x1_df2 (A, B, select, OUT);
    input A, B, select;
    output OUT;
    assign OUT = select ? A : B;
endmodule
    
```

**Another
Dataflow Model**

Behavioral Model

Mostly used
with sequential
circuits

```
module mux2x1_bh (A, B, select, OUT);
```

*Retains its
value until
a new
value is
assigned*

```
input A, B, select;  
output OUT;  
reg OUT;
```

Sensitivity List

```
always @ (select or A or B)
```

*Executes every time
there is a change in
any of the variables
in the sensitivity list*

```
if (select == 1) OUT = A;
```

```
else OUT = B;
```

*Equality Symbol
Can be written as:
if (select) ...*

```
endmodule
```

*Procedural
Assignment*

Structural Design – Recap

- Structural design is the simplest to understand. This style is the closest to schematic capture and utilizes simple building blocks to compose logic functions
- Components are interconnected in a hierarchical manner
- Structural descriptions may connect simple gates (gate-level) or complex, abstract components
- Useful when expressing a design that is naturally composed of sub-blocks

Data-Flow Design – Recap

- Describes how data moves through the system and the various processing steps
- Data Flow uses series of continuous assignment statements
- Data Flow is most useful style when series of Boolean equations can represent a logic

Behavioral Design – Recap

- It accurately models what happens on the inputs and outputs of the black box (no matter what is inside and how it works)
- This style uses *always* statements in *Verilog*
- Procedural statements in an *always* block executes sequentially. However, the *always* block itself executes concurrently with other concurrent statements in the same module (instances, continuous assignments, and other *always* statements)
- Typically used for test-benches or high-level implementations to drive logic synthesis tools

Nets, Variables, Parameters, and Directives

- **Net:** Physical wire between modules
 - A *wire* is the most commonly-used net
- **Variable:** Stores a value during a Verilog program's execution, and needs not have physical significance in a circuit
 - A *reg* is the most commonly-used variable
- **Parameter:** A facility provided by Verilog for defining named constants within a module, to improve readability and maintainability
 - E.g. `parameter ESC = 7'b0011011;`
- **Directive:** To control the compilation process
 - `'include` and `'define` are the most commonly-used directives

Logical Vs Bitwise Operators

- Examples of Ambiguities:
 - $(2'b01 \ \&\& \ 2'b10) \ \underline{Vs} \ (2'b01 \ \& \ 2'b10)$
 - $!(5) \ \underline{Vs} \ \sim(5)$


Ok... Design is done...

How should I test it?


- Same as what you would do to test a SW program:
 - Give it some inputs, and see if it does what you expect
 - After testing, do you guarantee that the program is bug free? NO!
 - But, to the extent possible, you have determined that the program does what you want it to do
- Same happens in HW design, you simulate the system's behavior with some input stimulus

Test Bench

Stimulus Module

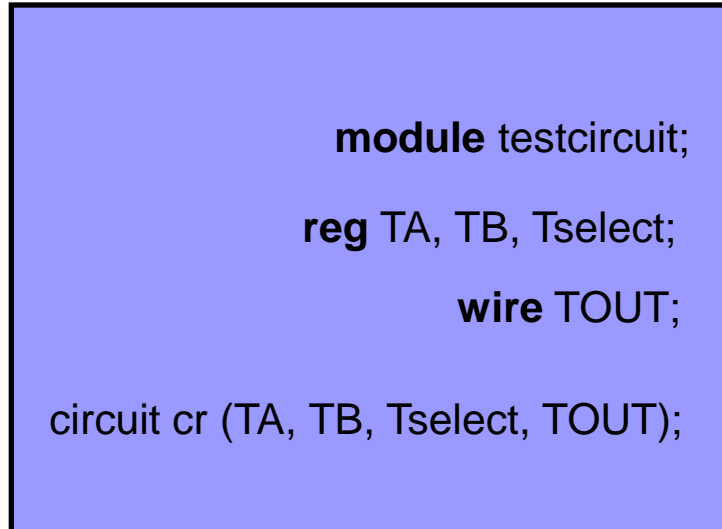

Design Module

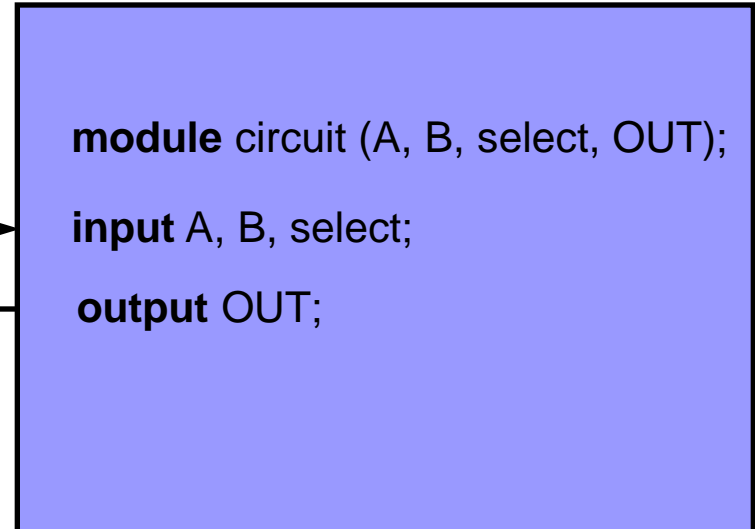

I am sick of this MUX!!

```

module stimcrct;
    reg A, B, select;
    wire OUT;
    mux2x1_df2 mux (A, B, select, OUT);
    initial
        begin
            A = 1'b0; B = 1'b1; select = 1'b0;
            #100
            A = 1'b0; B = 1'b1; select = 1'b1;
            #100    $finish;
        end
    endmodule

```

Executes only once at t = 0

Instance of design module

Procedural Assignment – used with “reg”

Terminates simulation

Stimulus Module

```

module mux2x1_df2 (A, B, select, OUT);
    input A, B, select;
    output OUT;
    assign OUT = select ? A : B;
endmodule

```

Design Module

Simulation Output



Examples of Stimulus Generation

```

initial
  begin
    A = 0; B = 0;
    #10 A = 1;
    #20 A = 0; B = 1;
  end

```

```

initial
  begin
    D = 3'b000;
    repeat (7)
      #10 D = D + 3'b001;
  end

```

3-bits Truth Table

References

- Lecture Notes of Dr. Sebastian Magierowski – Fall 2013
- Digital Design, 3rd Edition, M. Morris, Mano
- Digital Design, 4th Edition, John Wakerly
- cpk.auc.dk/education/SSU-2007/mm10/ssu_mm10.pdf
- www.ece.cmu.edu/~thomas/VSLIDES.pdf
- <http://ece.gmu.edu/coursewebpages/ECE/ECE448/S10/>