
 


# EECS 3201: Digital Logic Design Lecture 5

Ihab Amer, PhD, SMIEEE, P.Eng.

# Hierarchical Design

 

# 4-bit Adder – GL (Hierarchical)

```
module halfadder (S,C,x,y);
  input x,y;
  output S,C;
  //Instantiate primitive gates
  xor (S,x,y);
  and (C,x,y);
endmodule
```

```
module fulladder (S,C,x,y,z);
  input x,y,z;
  output S,C;
  wire S1,D1,D2; //Outputs of
  //first XOR and two AND gates
  //Instantiate the halfadder
  halfadder HA1 (S1,D1,x,y),
             HA2 (S,D2,S1,z);
  or g1(C,D2,D1);
endmodule
```


```
module _4bit_adder (S,C4,A,B,C0);
  input [3:0] A,B;
  input C0;
  output [3:0] S;
  output C4;
  wire C1,C2,C3; //Intermediate carries
  //Instantiate the fulladder
  fulladder FA0 (S[0],C1,A[0],B[0],C0),
             FA1 (S[1],C2,A[1],B[1],C1),
             FA2 (S[2],C3,A[2],B[2],C2),
             FA3 (S[3],C4,A[3],B[3],C3);
endmodule
```

*A vector of 4 bits*

# 4-bit Adder – DF


```
module binary_adder (A, B, Cin, SUM, Cout);  
  
    input [3:0] A, B;  
    input Cin;  
    output [3:0] SUM;  
    output Cout;  
  
    assign {Cout, SUM} = A + B + Cin;  
  
endmodule
```

# Muxtri – GL

 

```
module muxtri (A,B,select,OUT);
  input A,B,select;
  output OUT;
  tri OUT;
  bufif1(OUT,A,select);
  bufif0(OUT,B,select);
endmodule
```

# 4:1 MUX – BH

 

$s_1$	$s_0$	$f$
0	0	$w_0$
0	1	$w_1$
1	0	$w_2$
1	1	$w_3$

```

module mux4x1_bh (i0,i1,i2,i3,select,y);
  input i0,i1,i2,i3;
  input [1:0] select;
  output y;
  reg y;
  always @ (i0 or i1 or i2 or i3 or select)
    case (select)
      2'b00: y = i0;
      2'b01: y = i1;
      2'b10: y = i2;
      2'b11: y = i3;
    endcase
endmodule

```

$$f = s_1's_0'w_0 + s_1's_0w_1 + s_1s_0'w_2 + s_1s_0w_3$$

# Agenda

- Boolean Axioms and Theorems
- Basic application to Boolean equations
- A simple synthesis example
- Basic definition
- Sum-of-Products
- Product-of-Sums
- Other gates (more transistor stuff)
- Bubble pushing

# Boolean Algebra

- **Boolean Equations:** Expressions relating variables that are true or false
  - perfect for describing digital logic circuits
  - should be able to write directly from truth table
    - but this could lead to pretty complex looking expressions
    - can we simplify?
- **Boolean Algebra:** A bunch of rules to manipulate and simplify Boolean equations (i.e. stuff describing our circuits) to make it easier to realize complex functions with simple logic gates

# Axioms

Axiom		Dual		Name
A1	$B = 0$ if $B \neq 1$	A1'	$B = 1$ if $B \neq 0$	Binary field
A2	$\overline{0} = 1$	A2'	$\overline{1} = 0$	NOT
A3	$0 \bullet 0 = 0$	A3'	$1 + 1 = 1$	AND/OR
A4	$1 \bullet 1 = 1$	A4'	$0 + 0 = 0$	AND/OR
A5	$0 \bullet 1 = 1 \bullet 0 = 0$	A5'	$1 + 0 = 0 + 1 = 1$	AND/OR

- Duality in axioms (and theorems):
  - ANDs and ORs, 0's and 1's interchanged

# Theorems

- From axioms
- Rules for dealing with single variables

Theorem		Dual	Name
T1	$B \bullet 1 = B$	T1'	$B + 0 = B$
T2	$B \bullet 0 = 0$	T2'	$B + 1 = 1$
T3	$B \bullet B = B$	T3'	$B + B = B$
T4		$\bar{\bar{B}} = B$	Involution
T5	$B \bullet \bar{B} = 0$	T5'	$B + \bar{B} = 1$
			Complements

# Theorems of Several Variables

Theorem	Dual	Name
T6 $B \bullet C = C \bullet B$	T6' $B + C = C + B$	Commutativity
T7 $(B \bullet C) \bullet D = B \bullet (C \bullet D)$	T7' $(B + C) + D = B + (C + D)$	Associativity
T8 $(B \bullet C) + B \bullet D = B \bullet (C + D)$	T8' $(B + C) \bullet (B + D) = B + (C \bullet D)$	Distributivity
T9 $B \bullet (B + C) = B$	T9' $B + (B \bullet C) = B$	Covering
T10 $(B \bullet C) + (B \bullet \bar{C}) = B$	T10' $(B + C) \bullet (B + \bar{C}) = B$	Combining
T11 $(B \bullet C) + (\bar{B} \bullet D) + (C \bullet D)$ $= B \bullet C + \bar{B} \bullet D$	T11' $(B + C) \bullet (\bar{B} + D) \bullet (C + D)$ $= (B + C) \bullet (\bar{B} + D)$	Consensus
T12 $\overline{B_0 \bullet B_1 \bullet B_2 \dots}$ $= (\overline{B_0} + \overline{B_1} + \overline{B_2} \dots)$	T12' $\overline{B_0 + B_1 + B_2 \dots}$ $= (\overline{B_0} \bullet \overline{B_1} \bullet \overline{B_2})$	De Morgan's Theorem

# Simplifying Boolean Equations

- Example 1
- $Y = AB + \overline{A}B$

- Example 2
- $Y = A(AB + ABC)$

# Synthesis Example

$x_1$	$x_2$	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

# Some Definition

- **Complement**: variable with a bar over it  
 $\bar{A}, \bar{B}, \bar{C}$
- **Literal**: variable or its complement  
 $A, \bar{A}, B, \bar{B}, C, \bar{C}$
- **Implicant**: product of literals  
 $ABC, \bar{A}C, BC$
- **Minterm**: product that includes all input variables  
 $ABC, \bar{A}\bar{B}\bar{C}, ABC$
- **Maxterm**: sum that includes all input variables  
 $(A+\bar{B}+C), (\bar{A}+B+\bar{C}), (\bar{A}+\bar{B}+C)$

# Sum-of-Products (SOP) Form

- All equations can be written in SOP form
- Each row has a **minterm**
- A minterm is a product (AND) of literals
- Each minterm is TRUE for that row (and only that row)
- Form function by ORing minterms where the output is TRUE
- Thus, a sum (OR) of products (AND terms)

<b>A</b>	<b>B</b>	<b>Y</b>	<b>minterm</b>	<b>minterm name</b>
0	0	0	$\overline{A} \overline{B}$	$m_0$
0	1	1	$\overline{A} B$	$m_1$
1	0	0	$A \overline{B}$	$m_2$
1	1	1	$A B$	$m_3$

$$Y = F(A, B) =$$

# Product-of-Sums (POS) Form

- All Boolean equations can be written in POS form
- Each row has a maxterm
- A maxterm is a sum (OR) of literals
- Each maxterm is FALSE for that row (and only that row)
- Form function by ANDing the maxterms for which the output is FALSE
- Thus, a product (AND) of sums (OR terms)

<b>A</b>	<b>B</b>	<b>Y</b>	<b>maxterm</b>	<b>name</b>
0	0	0	$A + B$	$M_0$
0	1	1	$A + \bar{B}$	$M_1$
1	0	0	$\bar{A} + B$	$M_2$
1	1	1	$\bar{A} + \bar{B}$	$M_3$

$$Y = F(A, B) = (A + B)(A + \bar{B}) = \Pi(0, 2)$$


# Boolean Equations Example

- You are going to the cafeteria for lunch
  - You won't eat lunch ( $\overline{E}$ )
  - If it's not open ( $\overline{O}$ ) or
  - If they only serve corndogs ( $C$ )
- Write a truth table for determining if you will eat lunch ( $E$ )

$O$	$C$	$E$
0	0	0
0	1	1
1	0	0
1	1	1

# Basic Synthesis Example

- Synthesize

 

# Other Circuits

- We have more basic logic functions to synthesize with

**XOR**



$$Y = A \oplus B$$

**NAND**



$$Y = \overline{AB}$$

**NOR**



$$Y = \overline{A + B}$$

**XNOR**



$$Y = \overline{A \oplus B}$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0


A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1
 
# DeMorgan's Theorem

- $Y = \overline{AB} = \overline{A} + \overline{B}$





 - $Y = \overline{A + B} = \overline{A} \cdot \overline{B}$




  
# Bubble Pushing

- Backward:
  - Body changes
  - Adds bubbles to inputs




  - Forward:
  - Body changes
  - Adds bubble to output



 
# Bubble Pushing and SOP

- What is the Boolean expression for this circuit?



 
# Bubble Pushing and POS

- What is the Boolean expression for this circuit?


 
# Bubble Pushing Rules

- Begin at output, then work toward inputs
- Push bubbles on final output back
- Draw gates in a form so bubbles cancel



# References

- Lecture Notes of Dr. Sebastian Magierowski – Fall 2013