

CSE 2021 Computer Organization

Appendix Part 1

The Basics of Logic Design




Outline

- Fundamental Boolean operations
- Deriving logic expressions from truth tables
- Boolean Identities
- Simplifying logic expressions using Boolean identities
- Combinational and sequential circuits

Boolean Algebra

- Boolean algebra is the basic math used in digital circuits and computers.
- A Boolean variable takes on only 2 values: $\{0, 1\}$, $\{T, F\}$, $\{Yes, No\}$, etc.
- There are 3 fundamental Boolean operations:
 - AND, OR, NOT

Fundamental Boolean Operations

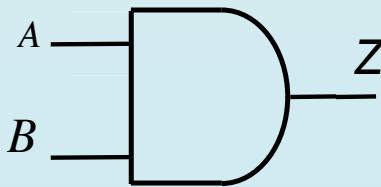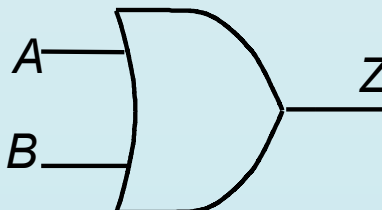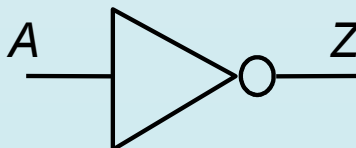AND	OR	NOT																																				
																																						
$Z=A*B \text{ (AB)}$	$Z=A+B$	$Z=\bar{A}$																																				
Truth Table	Truth Table	Truth Table																																				
<table><tr><th>A</th><th>B</th><th>Z</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	Z	0	0	0	0	1	0	1	0	0	1	1	1	<table><tr><th>A</th><th>B</th><th>Z</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	Z	0	0	0	0	1	1	1	0	1	1	1	1	<table><tr><th>A</th><th>Z</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	A	Z	0	1	1	0
A	B	Z																																				
0	0	0																																				
0	1	0																																				
1	0	0																																				
1	1	1																																				
A	B	Z																																				
0	0	0																																				
0	1	1																																				
1	0	1																																				
1	1	1																																				
A	Z																																					
0	1																																					
1	0																																					


Boolean Algebra

- A *truth table* specifies output signal logic values for every possible combination of input signal logic values
- In evaluating Boolean expressions, the *Operation Hierarchy* is: 1) NOT 2) AND 3) OR. Order can be superseded using (...)
- *Example:* $A = T, B = F, C = T, D = T$
- What is the value of $Z = (\bar{A} + B) \cdot (C + \bar{B} \cdot D)$?

$$\begin{aligned} Z &= (\bar{T} + F) \cdot (C + \bar{B} \cdot D) = (F + F) \cdot (C + \bar{B} \cdot D) \\ &= F \cdot (C + \bar{B} \cdot D) = F \end{aligned}$$

Deriving Logic Expressions From Truth Tables

 Light must be ON when both switches A and B are OFF, or when both of them are ON.



Truth Table:

A	B	Z
0	0	1
0	1	0
1	0	0
1	1	1

- *What is the Boolean expression for Z?*

Minterms and Maxterms

- Minterms
 - AND term of all input variables.
 - For variables with value 0, apply complements
- Maxterms
 - OR factor with all input variables
 - For variables with value 1, apply complements

A	B	Z	Minterms	Maxterms
0	0	1	$\bar{A} \cdot \bar{B}$	$A + B$
0	1	0	$\bar{A} \cdot B$	$A + \bar{B}$
1	0	0	$A \cdot \bar{B}$	$\bar{A} + B$
1	1	1	AB	$\bar{A} + \bar{B}$

Minterms and Maxterms

- A function with n variables has 2^n minterms (and Maxterms) – exactly equal to the number of rows in truth table
- Each minterm is true for exactly one combination of inputs
- Each Maxterm is false for exactly one combination of inputs

A	B	Z	Minterms	Maxterms
0	0	1	$\bar{A} \cdot \bar{B}$	$A + B$
0	1	0	$\bar{A} \cdot B$	$A + \bar{B}$
1	0	0	$A \cdot \bar{B}$	$\bar{A} + B$
1	1	1	AB	$\bar{A} + \bar{B}$

Equivalent Logic Expressions

- Two equivalent logic expressions can be derived from Truth Tables:
 1. *Sum-of-Products* (SOP) expressions:
 - Several AND terms OR'd together, e.g.

$$\overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C}$$

2. *Product-of-Sum* (POS) expressions:
 - Several OR terms AND'd together, e.g.

$$(\overline{A} + \overline{B} + C)(A + B + \overline{C})$$

Rules for Deriving SOP Expressions

1. Find each row in TT for which output is 1 (rows 1 & 4)
2. For those rows write a **minterm** of all input variables.
3. OR together all **minterms** found in (2):
Such an expression is called a *Canonical SOP*

A	B	Z	Minterms	Maxterms
0	0	1	$\bar{A} \cdot \bar{B}$	$A + B$
0	1	0	$\bar{A} \cdot B$	$A + \bar{B}$
1	0	0	$A \cdot \bar{B}$	$\bar{A} + B$
1	1	1	AB	$\bar{A} + \bar{B}$

$$Z = \bar{A} \bar{B} + AB$$

Rules for Deriving POS Expressions

1. Find each row in TT for which output is 0 (rows 2 & 3)
2. For those rows write a **maxterm**
3. AND together all **maxterm** found in (2):
Such an expression is called a *Canonical POS*.

A	B	Z	Minterms	Maxterms
0	0	1	$\bar{A}.\bar{B}$	$A + B$
0	1	0	$\bar{A}.B$	$A + \bar{B}$
1	0	0	$A.\bar{B}$	$\bar{A} + B$
1	1	1	AB	$\bar{A} + \bar{B}$

$$Z = (A + \bar{B})(\bar{A} + B)$$

CSOP and CPOS

- Canonical SOP: $Z = \bar{A} \bar{B} + AB$
- Canonical POS: $Z = (A + \bar{B})(\bar{A} + B)$
- Since they represent the same truth table, they should be identical

Verify that

$$Z = \bar{A} \bar{B} + AB \equiv (A + \bar{B})(\bar{A} + B)$$

- *CPOS and CSOP expressions for the same TT are logically equivalent. Both represent the same information.*

Activity 1

Derive SOP and POS expressions for the following TT.

A	B	Carry
0	0	0
0	1	0
1	0	0
1	1	1

Activity 1

Derive SOP and POS expressions for the following TT.

A	B	Carry	Minterms	Maxterms
0	0	0	$A'B'$	$A+B$
0	1	0	$A'B$	$A+B'$
1	0	0	AB'	$A'+B$
1	1	1	AB	$A'+B'$

SOP: $\text{Carry} = AB$

POS: $\text{Carry} = (A+B)(A+B')(A'+B)$



Boolean Identities

Boolean Identities

- Useful for simplifying logic equations.

	(a)	(b)
1	$\overline{\overline{A}} = A$	$\overline{\overline{A}} = A$
2	$A + \text{false} = A \quad (A + 0 = A)$	$A \cdot \text{true} = A \quad (A \cdot 1 = A)$
3	$A + \text{true} = \text{true} \quad (A + 1 = 1)$	$A \cdot \text{false} = \text{false} \quad (A \cdot 0 = 0)$
4	$A + A = A$	$A \cdot A = A$
5	$A + \overline{A} = \text{true} \quad (A + \overline{A} = 1)$	$A \cdot \overline{A} = \text{false} \quad (A \cdot \overline{A} = 0)$
6	$A + B = B + A$	$A \cdot B = B \cdot A$
7	$A + B + C = (A + B) + C = A + (B + C)$	$A \cdot B \cdot C = (A \cdot B) \cdot C = A \cdot (B \cdot C)$
8	$A \cdot (B + C) = A \cdot B + A \cdot C$	$A + B \cdot C = (A + B)(A + C)$
9	$\overline{A + B} = \overline{A} \cdot \overline{B}$	$\overline{A \cdot B} = \overline{A} + \overline{B}$
10	$A \cdot B + A \cdot \overline{B} = A$	$(A + B)(A + \overline{B}) = A$
11	$A + A \cdot B = A$	$A(A + B) = A$
12	$A(\overline{A} + B) = A \cdot B$	$A + \overline{A} \cdot B = A + B$
13	$A \cdot B + \overline{A} \cdot C + B \cdot C = A \cdot B + \overline{A} \cdot C$	$(A + B)(\overline{A} + C)(B + C) = (A + B)(\overline{A} + C)$

Duals

Boolean Identities

Identities	Property
1-5	Single variable, foundations of Boolean manipulation
6	Commutative
7	Associative
8	Distributive
9	De Morgan's
10	Combining
11	Absorption
13	Consensus

Boolean Identities

- The right side is the dual of the left side

1. Duals formed by replacing

AND \rightarrow OR

OR \rightarrow AND

0 \rightarrow 1


1 \rightarrow 0

2. The dual of any true statement in Boolean algebra is also a true statement.


Boolean Identities

- DeMorgan's laws very useful: 9a and 9b

 
$$\overline{A+B} = \overline{A}.\overline{B}$$




≡

 
 
$$\overline{AB} = \overline{A} + \overline{B}$$



≡

 

Activity 2

Proofs of some Identities:

$$12b: \quad A + \overline{A}B = A + B$$

$$13a: \quad AB + \overline{A}C + BC = AB + \overline{A}C$$

Activity 2

Proofs of some Identities:

$$A + \overline{A}B = A + B$$

$$\begin{aligned} 12b: \quad A + \overline{A}B &= A + AB + \overline{A}B \quad (A + AB = A(B + 1) = A) \quad (\text{Using 11}) \\ &= A + B \end{aligned}$$


$$AB + \overline{A}C + BC = AB + \overline{A}C$$

$$\begin{aligned} 13a: \quad &= AB + \overline{A}C + (A + \overline{A})BC \\ &= AB + \overline{A}C + ABC + \overline{A}BC \\ &= AB(C + 1) + \overline{A}C(B + 1) \\ &= AB + \overline{A}C \end{aligned}$$




Simplifying Logic Expressions Using Boolean Identities

Simplifying Logic Equations – Why?

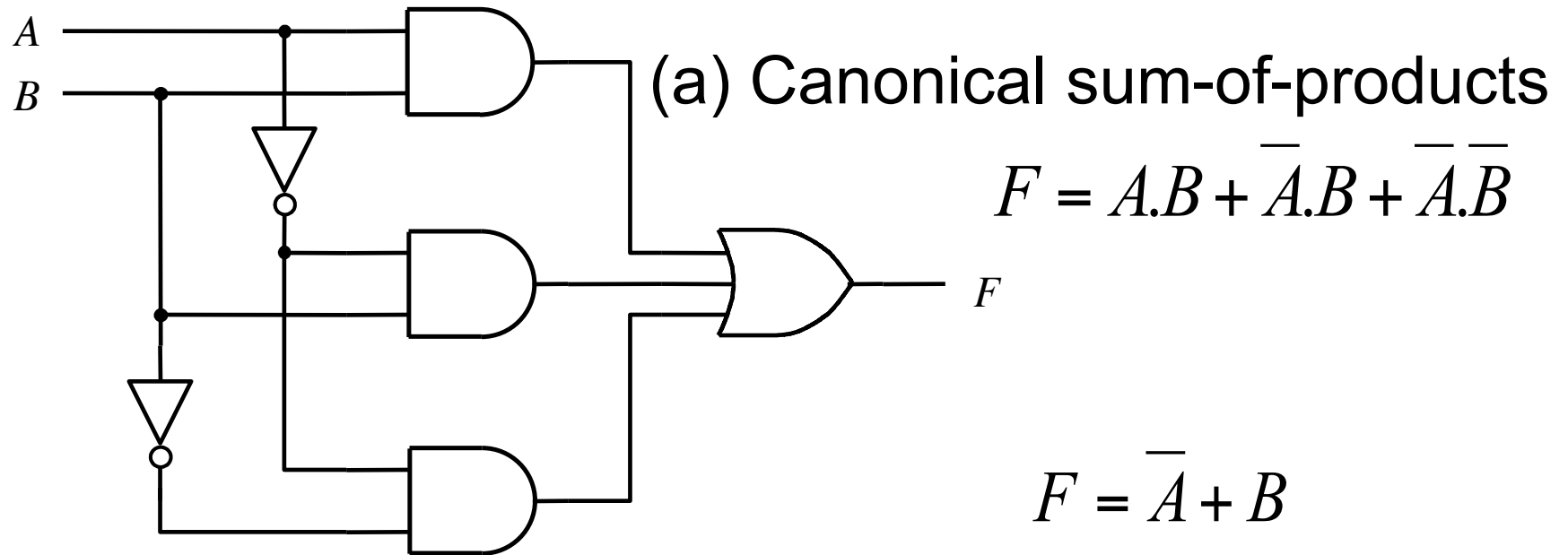

$$F = \bar{A} + B$$

 

(b) Minimal-cost realization

Simplifying Logic Equations

- Simplifying logic expressions can lead to using smaller number of gates (parts) to implement the logic expression
- Can be done using
 - Boolean Identities (algebraic)
 - Karnaugh Maps (graphical)
- A *minimum SOP* (MSOP) expression is one that has no more AND terms or variables than any other equivalent SOP expression.
- A *minimum POS* (MPOS) expression is one that has no more OR factors or variables than any other equivalent POS expression.
- There may be several MSOPs of an expression

Example of Using Boolean Identities

- Find an MSOP for

$$F = \overline{X}W + Y + \overline{Z}(Y + \overline{X}W)$$

$$= \overline{X}W + Y + \overline{Z}Y + \overline{Z}\overline{X}W$$

$$= \overline{X}W(1 + \overline{Z}) + Y(1 + \overline{Z})$$

$$= \overline{X}W + Y$$

Activity 3

- Find an MSOP for

$$F = V\overline{W}XY + VWYZ + V\overline{X}YZ$$

Activity 3

- Find an MSOP for

$$F = V\overline{W}XY + VWYZ + V\overline{X}YZ$$

$$= VY(\overline{W}X + WZ + \overline{X}Z)$$

$$= VY(\overline{W}X + Z(W + \overline{X})) \quad [W + \overline{X} = \overline{\overline{W}X}]$$

$$= VY(\overline{W}X + Z\overline{\overline{W}X}) \quad [A + \overline{A}B = A + B]$$

$$= VY(\overline{W}X + Z)$$

$$= VY\overline{W}X + VYZ$$

Combinational and Sequential Circuits


Digital Circuit Classification

- Combinational circuits
 - Output depends only solely on the current combination of circuit inputs
 - Same set of input will always produce the same outputs
 - Consists of AND, OR, NOR, NAND, and NOT gates
- Sequential circuits
 - Output depends on the current inputs and state of the circuit (or past sequence of inputs)
 - Memory elements such as flip-flops and registers are required to store the “state”
 - Same set of input can produce completely different outputs

Combinational Circuits


Multiplexer

 - A multiplexer (MUX) selects data from one of N inputs and directs it to a single output, just like a railyard switch
 - 4-input Mux needs 2 select lines to indicate which input to route through
 - N -input Mux needs $\log_2(N)$ selection lines



Multiplexer (2)

- An example of 4-input Mux

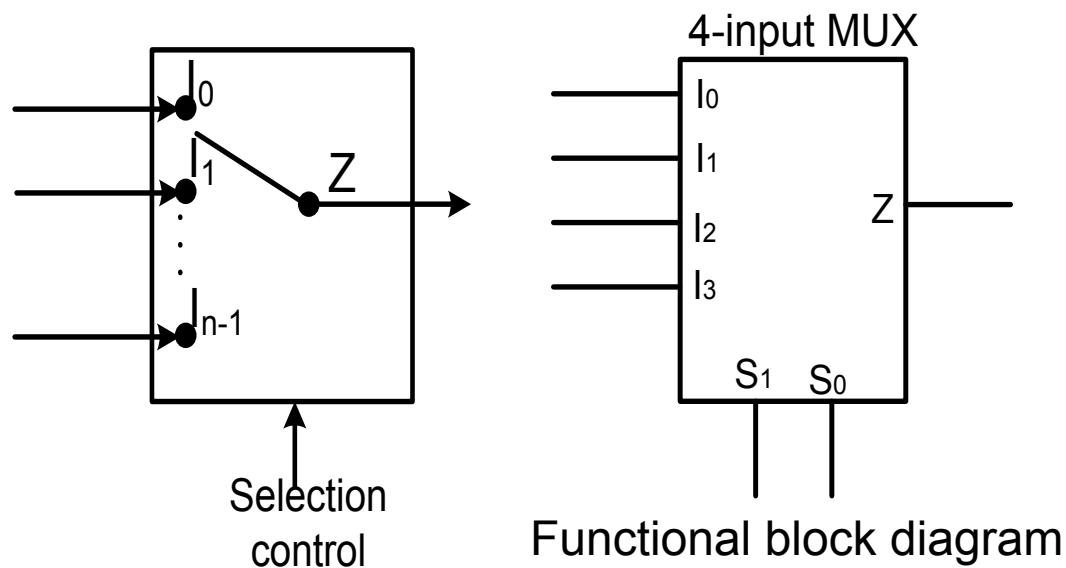


Actual truth table would have 2^6 rows corresponding to I_0 , I_1 , I_2 , I_3 , S_0 and S_1

S_1	S_0	Z
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

Condensed truth table

Decoder

 - A decoder is a circuit element that will decode an N -bit code.
- It activates an appropriate output line as a function of the applied N -bit input code



Functional block diagram

Truth Table


A_2	A_1	A_0	Z_0	Z_1	Z_2	Z_3	Z_4	Z_5	Z_6	Z_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Sequential Circuits

Why Bit Storage ?

 
3.2

- Flight attendant call button
 - Press call: light turns on
 - **Stays on** after button released
 - Press cancel: light turns off
 - Logic gate circuit to implement this?




Doesn't work. $Q=1$ when $Call=1$, but doesn't stay 1 when $Call$ returns to 0

 
Need some form of "memory" in the circuit



1. Call button pressed – light turns on

 

 
2. Call button released – light **stays on**



 3. Cancel button pressed – light turns off

Bit Storage Using SR Latch


- Simplest memory elements are Latch and Flip-Flops
- SR (set-reset) latch is an ***un-clocked*** latch
 - Output $Q=1$ when $S=1$, $R=0$ (set condition)
 - Output $Q=0$ when $S=0$, $R=1$ (reset condition)
 - Problem - Q is undefined if $S=1$ and $R=1$



Clocks


- **Clock period:** time interval between pulses
 - example: period = 20 ns
- **Clock frequency:** $1/\text{period}$
 - example: frequency = $1 / 20 \text{ ns} = 50 \text{ MHz}$
- **Edge-triggered clocking:** all state changes occur on a clock edge.

Freq	Period
100 GHz	0.01 ns
10 GHz	0.1 ns
1 GHz	1 ns
100 MHz	10 ns
10 MHz	100 ns

 


Clock and Change of State

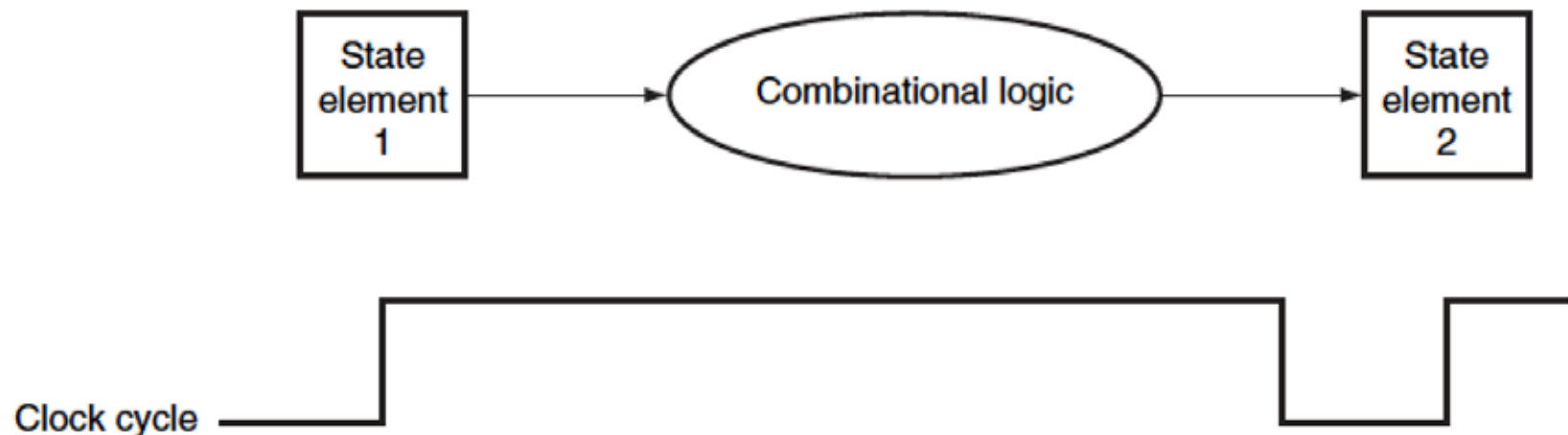- Clock controls when the state of a memory element changes
- ***Edge-triggered clocking***: all state changes occur on a clock edge.




Clock Edge Triggered Bit Storage

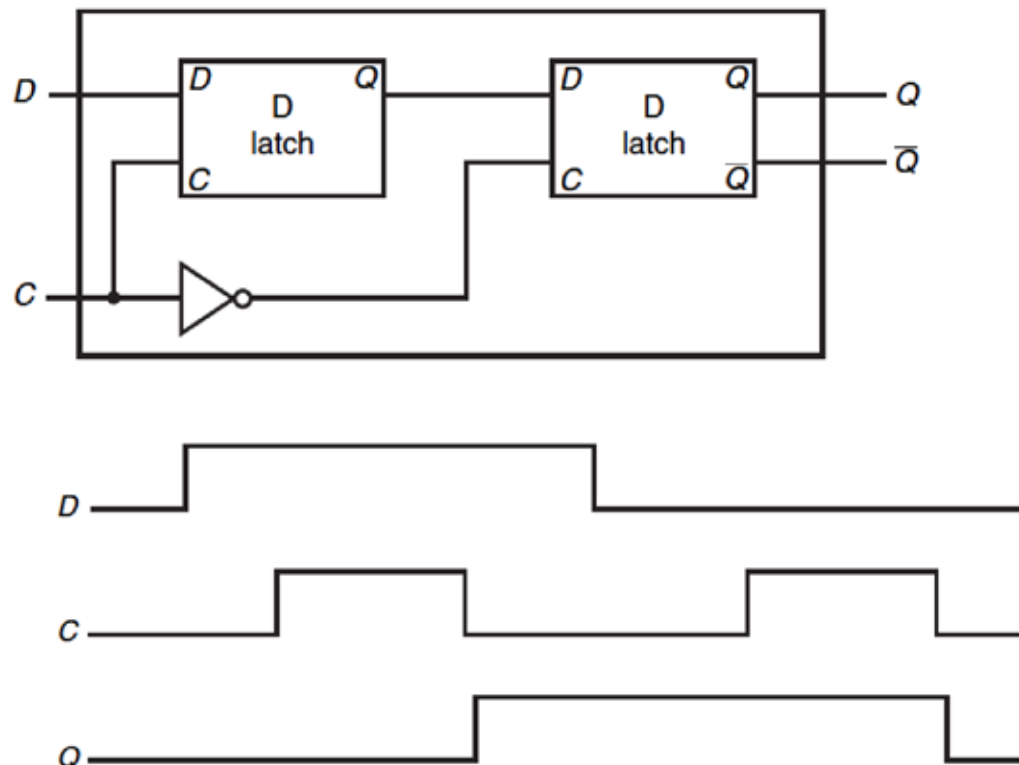- **Flip-flop** - Bit storage that stores on clock edge, not level
- D Flip-flop
 - Two latches, master and slave latches.
 - Output of the first goes to input of second, slave latch has inverted clock signal (falling-edge trigger)



Setup and Hold Time

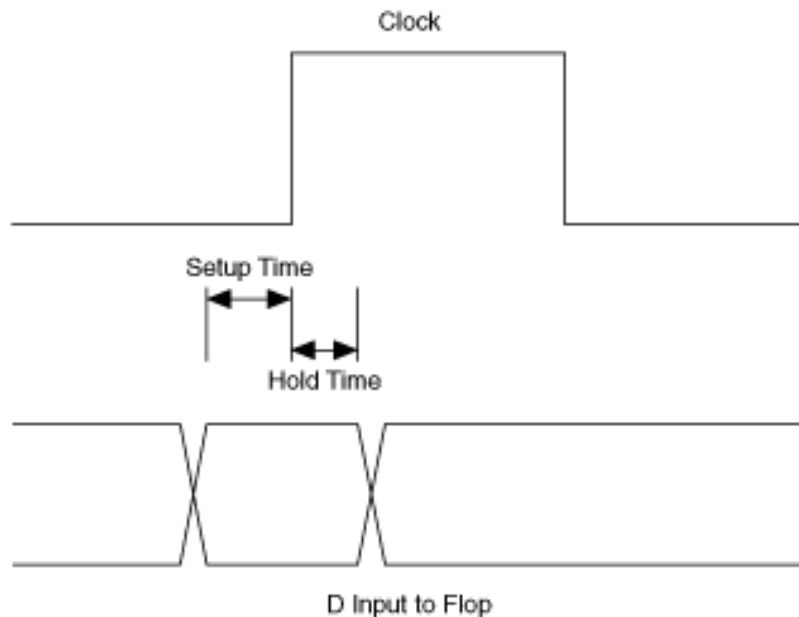- Setup time
 - The minimum amount of time the data signal should be held steady before the clock edge arrives.
- Hold time
 - The minimum amount of time the data signal should be held steady after the clock edge.



N-Bit Register

- Cascade N number of D flip-flops to form a N -bit register
- An example of 8-bit register formed by 8 edge-triggered D flip-flops

