

6.28 large β $I_c \approx I_E$

$$V_E = I_E = \frac{10.7 - 0.7}{10k} = 1mA \approx I_c$$

$$V_2 = -10.7 + 1mA \times 10k = -0.7V$$


c)

$$I_c = \frac{0 - (-10)}{10} = 1mA$$

$$I_5 = 1mA$$

$$I_B = 0$$

$$V_4 = 1V$$

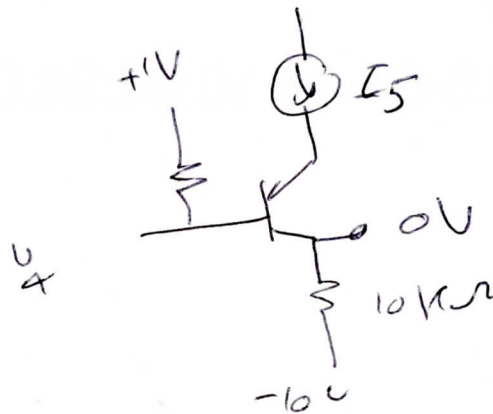

6.33



6.49

(a) Active

$$I_C = \frac{5 - 1}{1k} = 4mA \quad I_B = \frac{4}{50} = 0.08mA$$

$$V_{BB} = 0.7 + 20 \times 0.08 = 2.3V$$

(b) $V_C = 0.3$ & Repeat $I_C = \frac{5 - 0.3}{1k} \dots$

(c) Sat $V_C = 0.2V$

6.55 Normal Condition $V_B = 0$

$$V_E = -0.7V$$

$$I_E = 1 \frac{-0.7}{1k\Omega} = 0.3mA \approx I_C$$

$$V_C = (5 - 0.3) \times 1k\Omega = 4.7V$$

At cutoff $V_{BE} = 0.5V$

$$V_E = -1 \times 1.1V \quad (\text{all current is through } R_E, \text{ no } I_E)$$

6.55 (cont. (b))

$$V_B = -1 + 0.5 = -0.5 \text{ V}$$

$$I_C = I_E = 0$$

Sat.

$$V_{CE} = 0.2 \text{ V}$$

$$V_C = V_E + 0.2$$

$$I_C = \frac{5 - V_C}{1}$$

$$I_E = \frac{V_E}{1} + 1 \quad I_E = I_C$$

$$\frac{5 - V_C}{1} = V_E + 1 \rightarrow \frac{5 - (V_E + 0.2)}{1} = V_E + 1$$

$$V_E = 2.1 \text{ V}$$

$$V_B = 2.1 + 0.7 = 2.8$$

$$V_C = V_E + 0.2 = 2.3 \text{ V}$$


6.71

$$V_o = 0.3 \text{ V @ sat}$$

$$\Delta V_o = -0.7 \text{ V}$$

$$I_C = \frac{V_{CC} - V_o}{R_C}$$


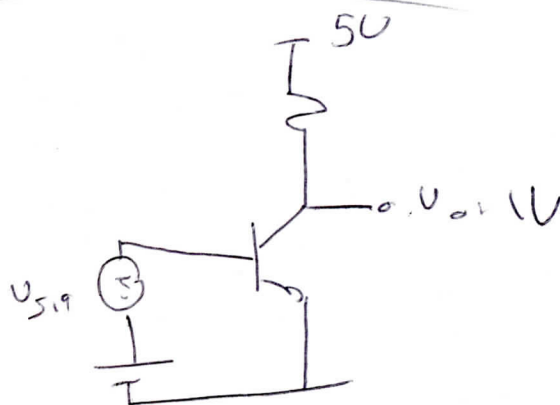
$$\frac{I_{C1}}{I_{C2}} = \frac{4}{4.7} \rightarrow \frac{4.7}{4} = e^{\frac{\Delta V_{BE}}{V_T}}$$



6.71 Cont.

$$\Delta V_{BE} = 4.03 \text{ mV}$$

6.77

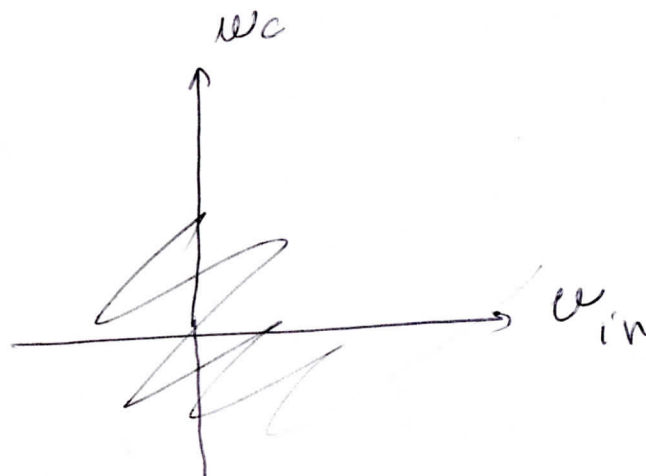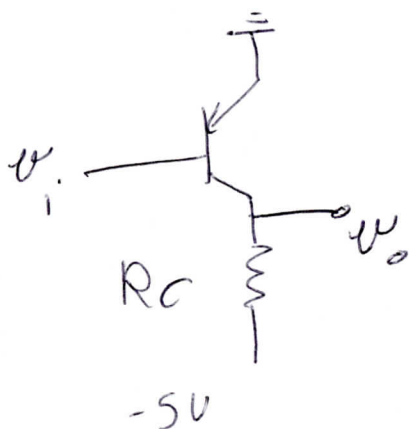

v_i down to -0.5V cutoff $v_o = -5\text{V}$

v_i $> -5\text{V}$ ON current flows v_o rises

⑦ Sat $v_o = V_{CE\text{sat}} = 0.2\text{V}$

