

# Solution to Assignment 2 (Diodes)


---

4.4

The best way is to draw the transfer function, for example

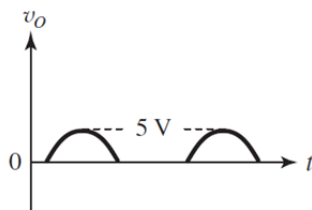(a) In this circuit, when D is on ( $V_i > 0$ )  $V_o = V_i$  otherwise it is 0


The output looks like with  $V_{p+} = +5\text{V}$ ,  $V_{p-} = -5\text{V}$  and  $f = 1\text{KHz}$



In (c) neither diode is conducting, output = 0 all the time  $V_{p+} = V_{p-} = 0$   $f = 0$

In (i) when  $V_i > 0$   $V_o = V_i$

When  $V_i < 0$  D is On and  $V_o = 0.5V_i$

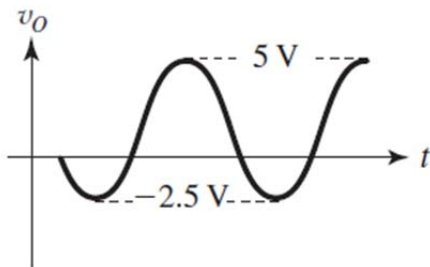

Problem 4.6

A	B	X	Y
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

#### Problem 4.9

Assume D1 and D2 ON,  $V=0$ ,  $I(D2) = (0 - (-3)) / 6 = 0.5A$

$$I(D1) = (3 - 0) / 12 = 0.25A$$

$I=0.25A$  up, can not be, wrong assumption.

D1=OFF, D2=ON

$V=-1V$   $I=0$  (to get  $V$  a voltage divider between  $+3, -3$  with  $12, 6K\Omega$ )

4.10

Use thevenin to change the  $2\ 10K$  resistor and  $5V$  source to  $2.5V$  and  $5K$  resistor and solve the circuit

4.20

$I = I_S \cdot \exp(V_D / V_T)$  substitute and solve

4.38

$$V_D = 0.7 \rightarrow i_{D1} = (v - 0.7) / R$$

$$V_D = 0.6 \rightarrow i_{D1} = (v - 0.6) / R \text{ for the difference to be } 1\%$$

$$v - 0.6 = 1.01(v - 0.7)$$

$$v = 10.7V$$

substitute with  $V=3V$  and  $R=1k$ , the difference is  $4\%$

4.51

The current in each diode is  $I/2$ ,  $r_d = V_T/(I/2) = 0.05/I$

Draw the equivalent circuit, and calculate  $V_o/v_i$

$$I=0 \rightarrow V_o=0$$

$$I=1\text{e-}6 \text{ rd} = 50\text{k} \text{ vo/vi}=0.167$$

$$I=10\text{e-}6 \text{ rd} = 5\text{k} \text{ vo/vi}=0.667$$

4.63

4.72