

## CHAPTER 7

# Transistor Amplifiers


## BJT

**Disclaimer:** Most of the slides are skeletons that will be filled/modified in the lecture. Please do not assume that you can know the material just by reading the slides.

Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press

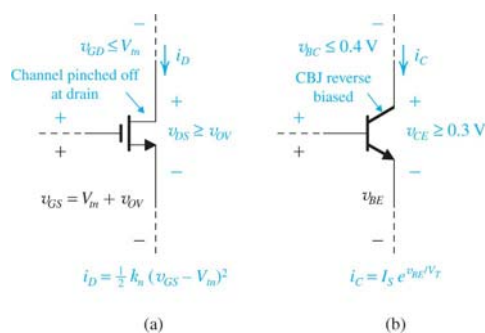


**Figure 7.1** Operating (a) an NMOS transistor and (b) a npn transistor in the active mode. Note that  $v_{GS} = V_m + v_{OV}$  and  $v_{DS} \geq v_{OV}$ ; thus  $v_{GD} \leq V_m$ , which ensures channel pinch-off at the drain end. Similarly,  $v_{BE} \simeq 0.7$  V, and  $v_{CE} \geq 0.3$  V results in  $v_{BC} \leq 0.4$  V, which is sufficient to keep the CBJ from conducting.

Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press

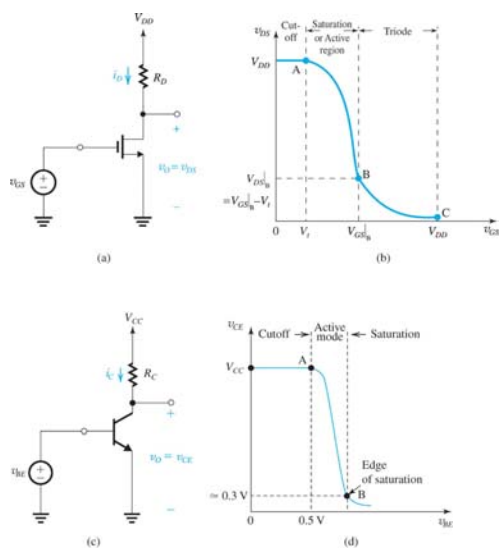


**Figure 7.2** (a) An NMOS amplifier and (b) its VTC; and (c) a *npn* amplifier and (d) its VTC.

Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press

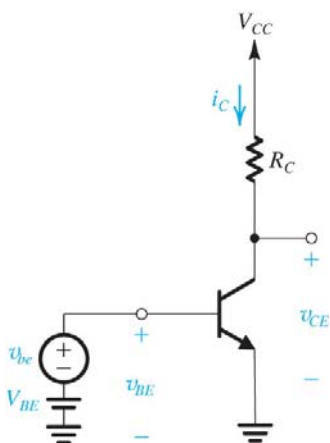


**Figure 7.6** BJT amplifier biased at a point Q, with a small voltage signal  $v_{be}$  superimposed on the dc bias voltage  $V_{BE}$ . The resulting output signal  $v_{ce}$  appears superimposed on the dc collector voltage  $V_{CE}$ . The amplitude of  $v_{ce}$  is larger than that of  $v_{be}$  by the voltage gain  $A_v$ .

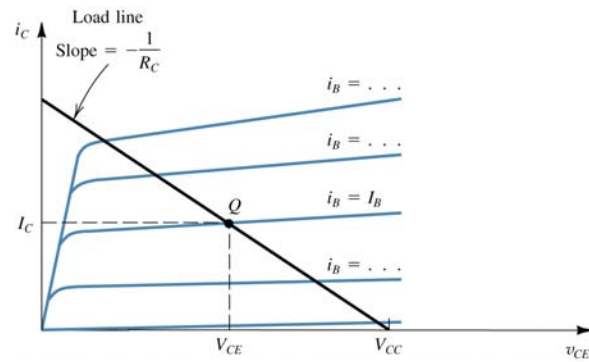Microelectronic Circuits, Seventh Edition

Sedra/Smith


Copyright © 2015 by Oxford University Press



Microelectronic Circuits, Seventh Edition

Sedra/Smith

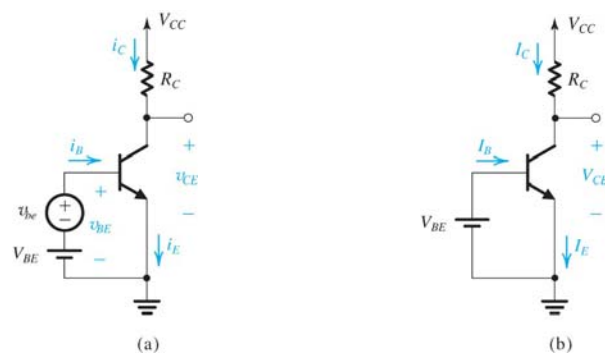Copyright © 2015 by Oxford University Press


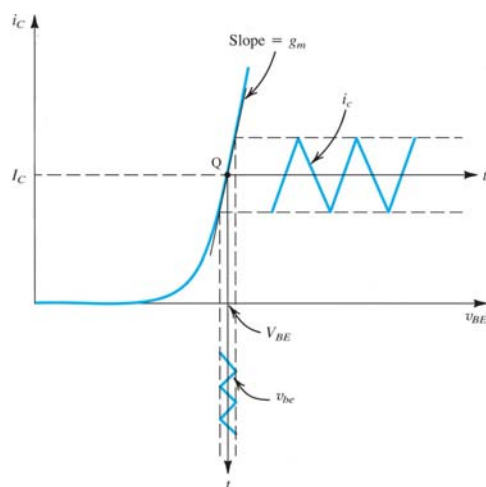


**Figure 7.20** (a) Conceptual circuit to illustrate the operation of the transistor as an amplifier. (b) The circuit of (a) with the signal source  $v_{be}$  eliminated for dc (bias) analysis.



Microelectronic Circuits, Seventh Edition



Sedra/Smith

Copyright © 2015 by Oxford University Press

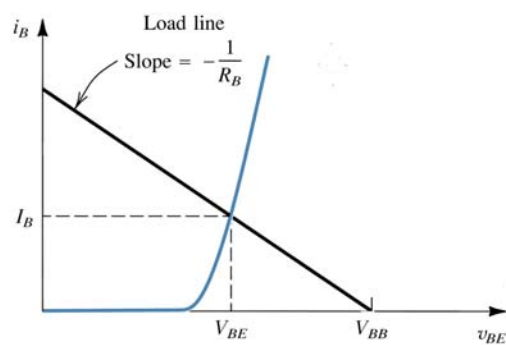

**Figure 7.21** Linear operation of the transistor under the small-signal condition: A small-signal  $v_{be}$  with a triangular waveform is superimposed on the dc voltage  $V_{BE}$ . It gives rise to a collector-signal current  $i_c$ , also of triangular waveform, superimposed on the dc current  $I_C$ . Here,  $i_c = g_m v_{be}$ , where  $g_m$  is the slope of the  $i_C$ - $v_{BE}$  curve at the bias point  $Q$ .

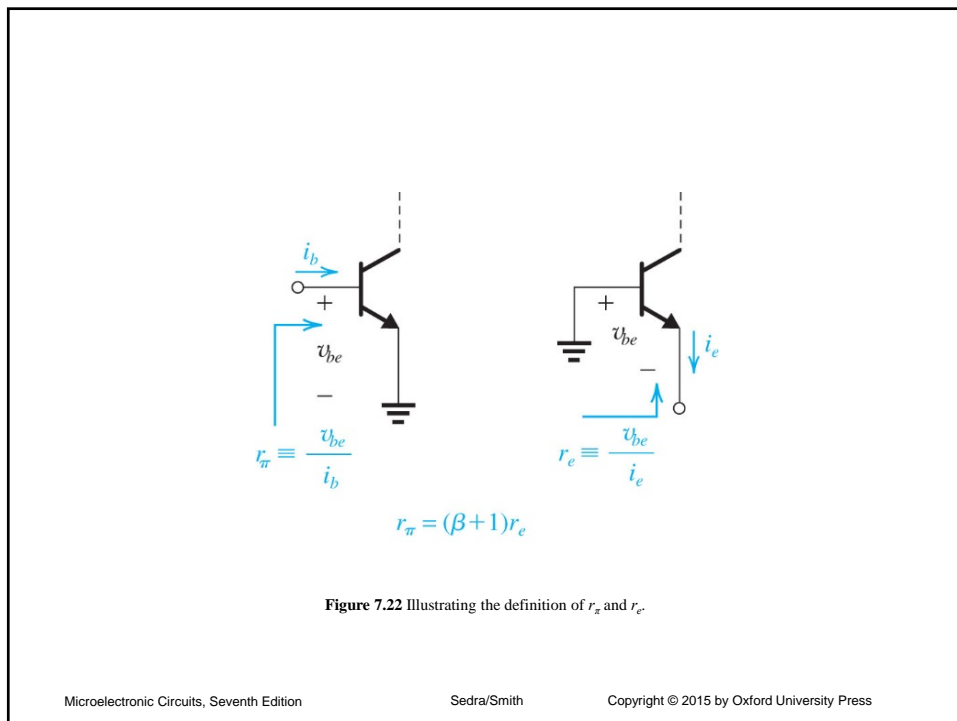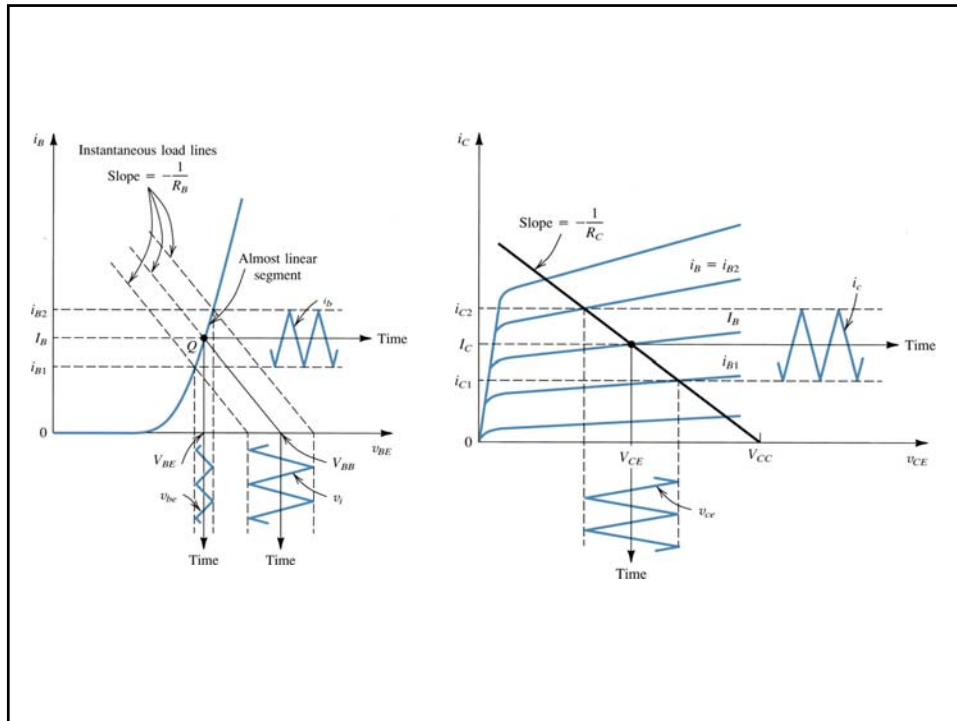


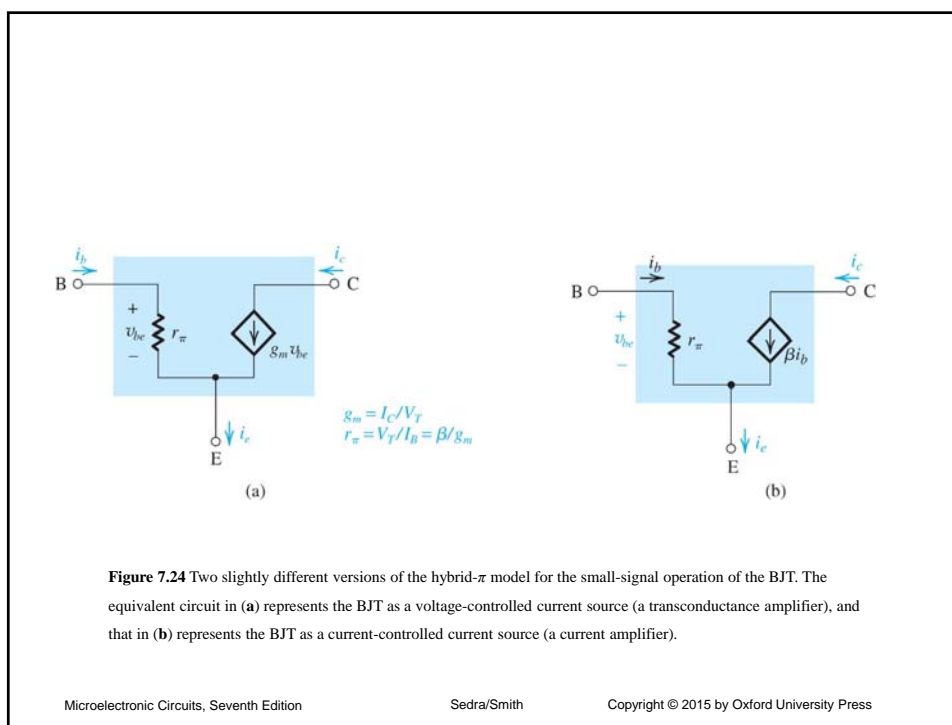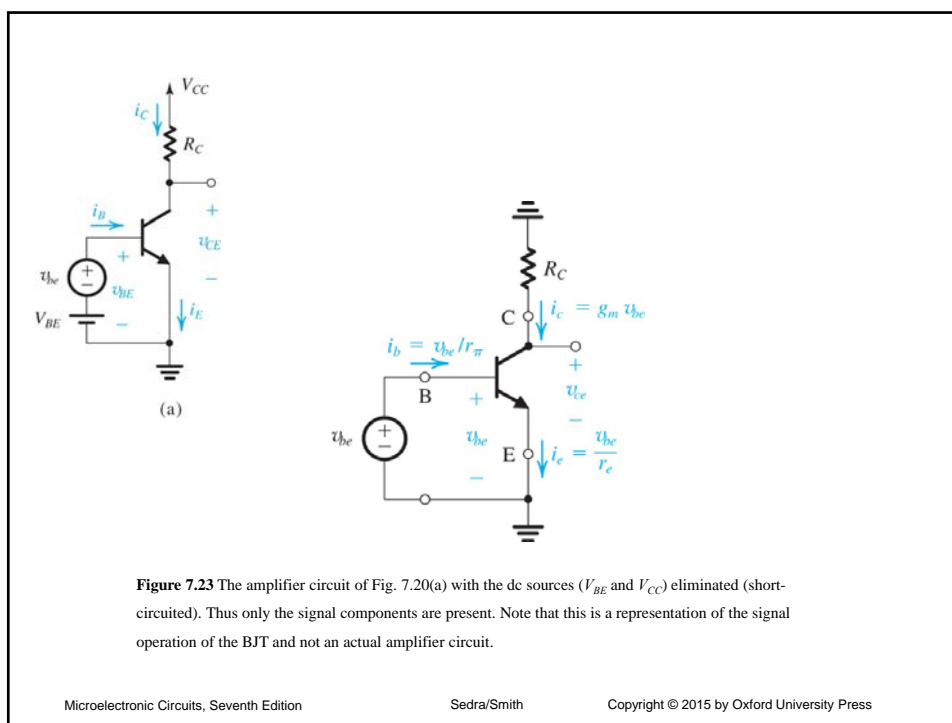

$$g_m = I_C / V_T$$

$$r_\pi = V_T / I_B = \beta / g_m$$

$$r_o = V_A / I_C$$

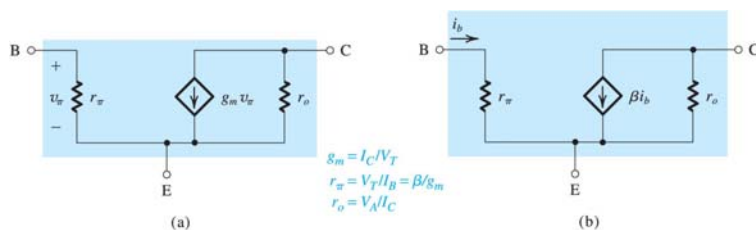

**Figure 7.25** The hybrid- $\pi$  small-signal model, in its two versions, with the resistance  $r_o$  included.


Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press

$$g_m = I_C / V_T$$

$$r_e = V_T / I_E = \alpha / g_m$$

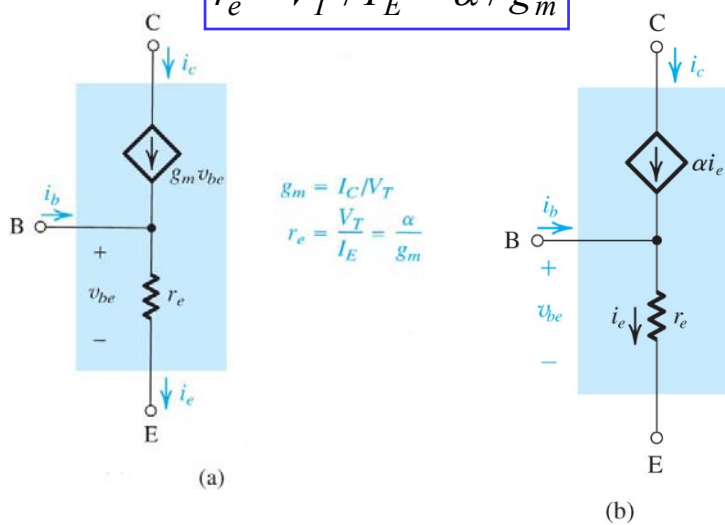

Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press

$$g_m = I_C / V_T$$

$$r_e = V_T / I_E = \alpha / g_m$$

$$r_o = V_A / I_C$$


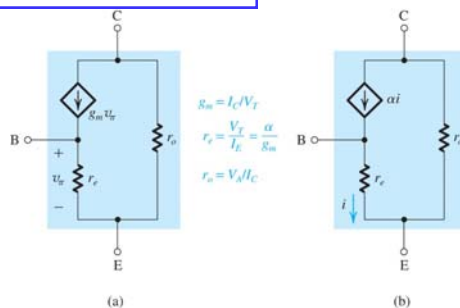


Figure 7.27 The T models of the BJT.

Microelectronic Circuits, Seventh Edition

Sedra/Smith

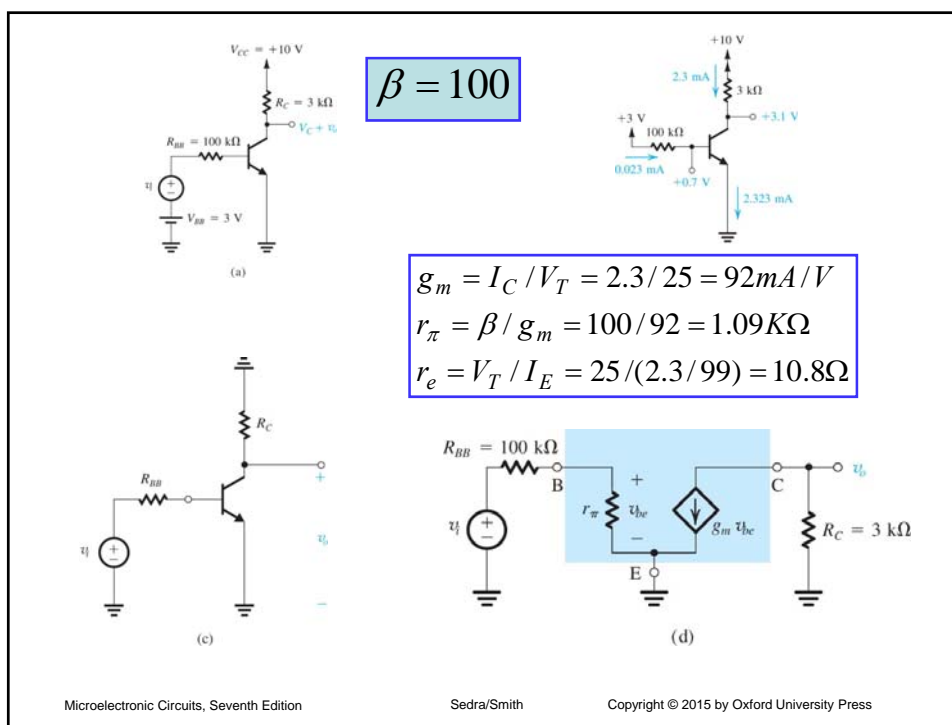Copyright © 2015 by Oxford University Press







Microelectronic Circuits, Seventh Edition

Sedra/Smith

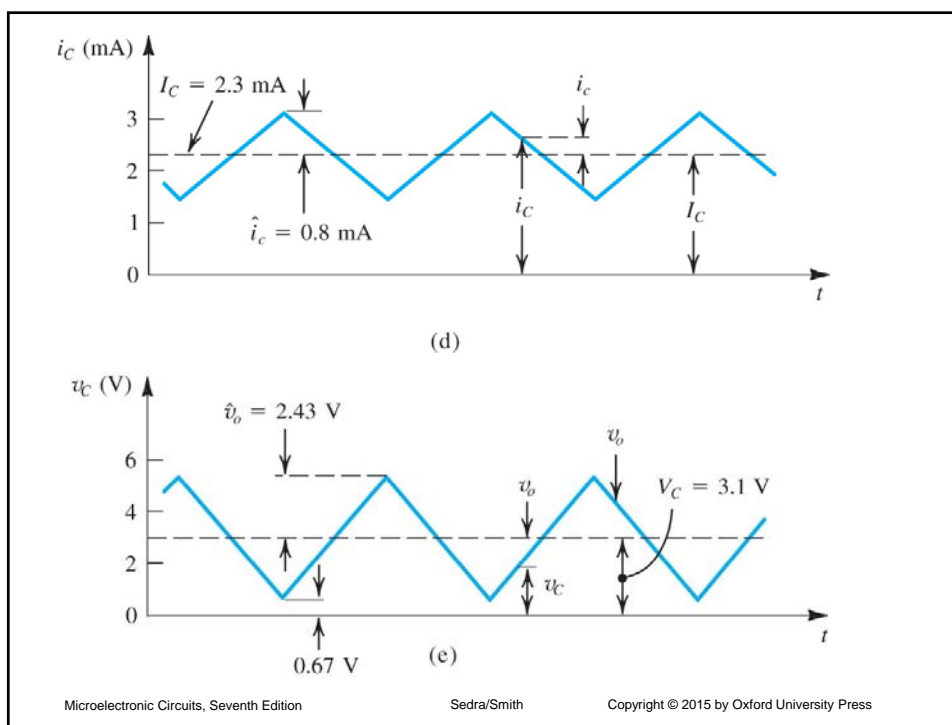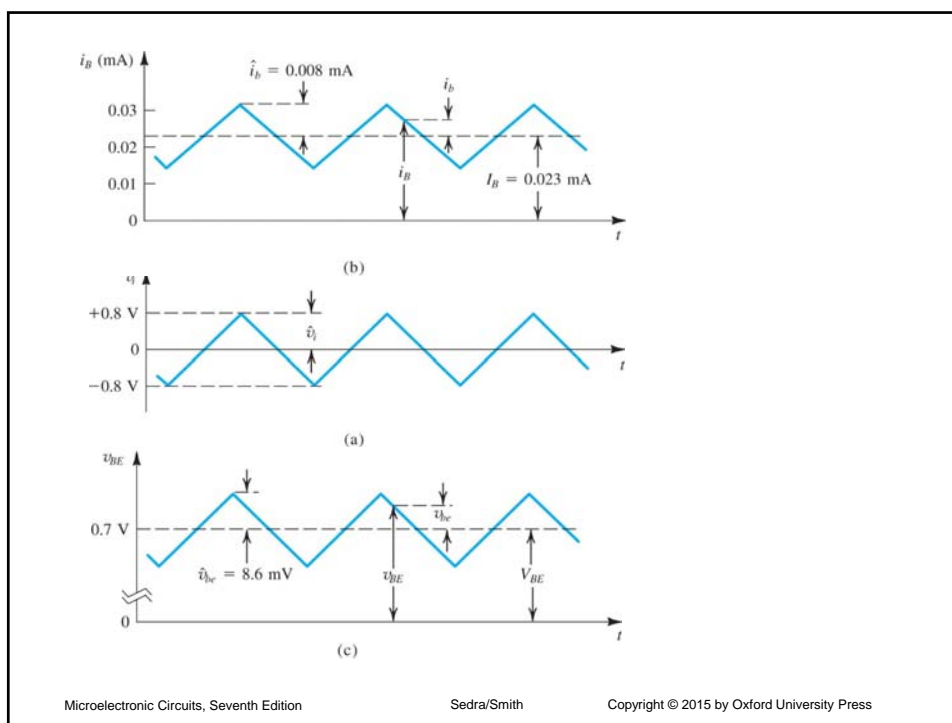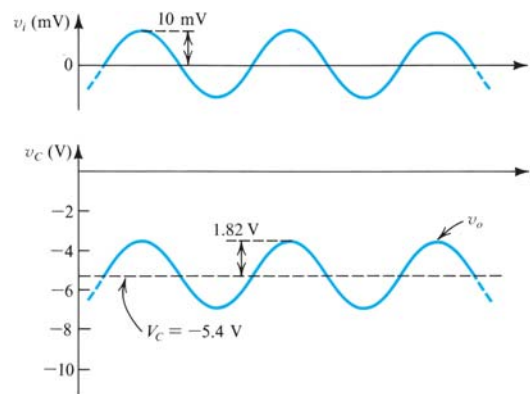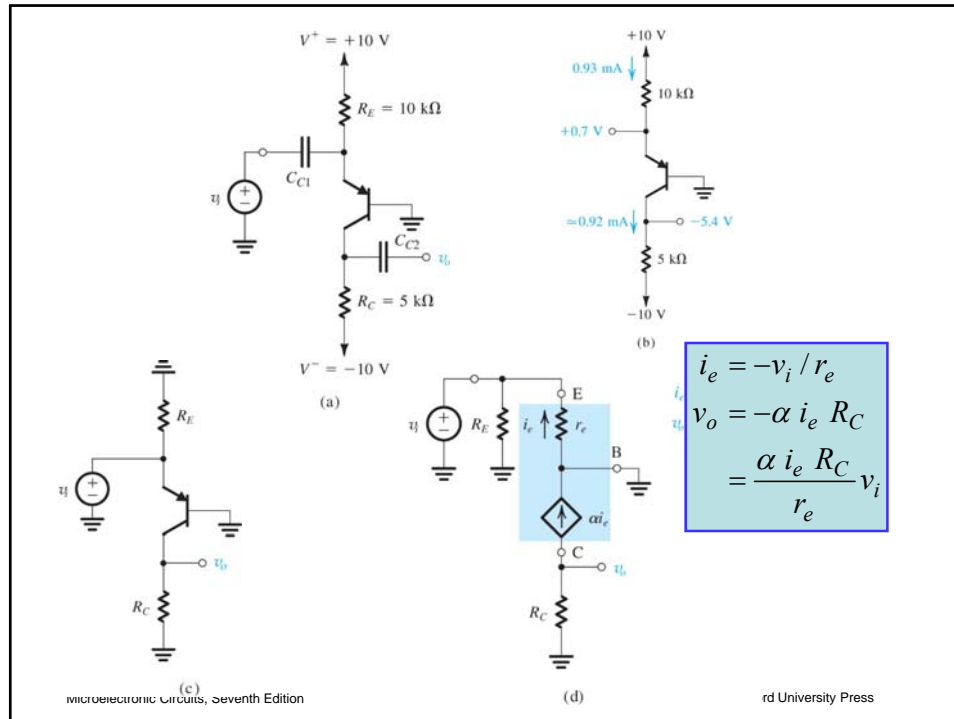Copyright © 2015 by Oxford University Press

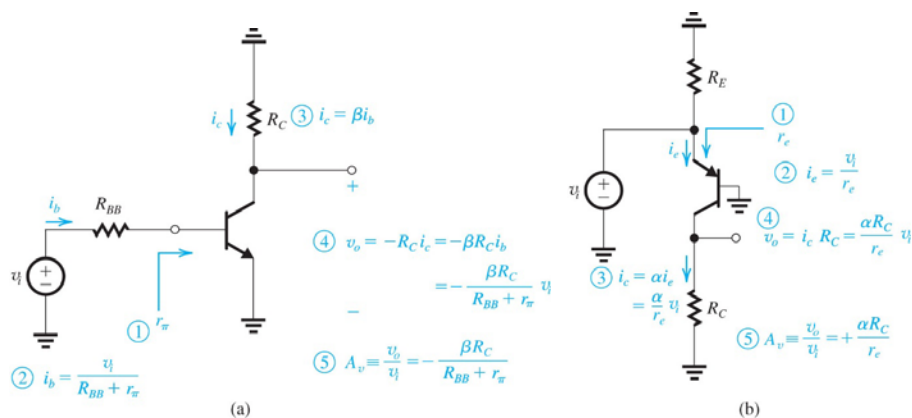






**Figure 7.31** Input and output waveforms for the circuit of Fig. 7.30. Observe that this amplifier is noninverting, a property of the grounded-base configuration.

## Performing Small Signal Analysis Directly on the Circuit



Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press

 $\beta=100$   $V_A=100V$ 

- Find  $V_A$ ,  $V_B$ , and  $V_C$  ignoring Early Effect
- Find  $g_m$ ,  $r_\pi$ ,  $r_o$
- $Z$  is grounded and  $v_{sig}$  is connected to  $X$  (with 2K internal R, and 8K load resistance connected to  $Y$  find  $A_v$  with or without the Early effect

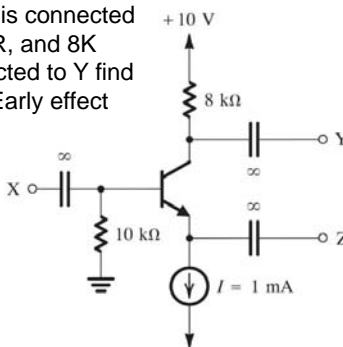


Figure E7.20

Microelectronic Circuits, Seventh Edition

Sedra/Smith


Copyright © 2015 by Oxford University Press

**Table 7.1** Systematic Procedure for the Analysis of Transistor Amplifier Circuits


1. Eliminate the signal source and determine the dc operating point of the transistor.
2. Calculate the values of the parameters of the small-signal model.
3. Eliminate the dc sources by replacing each dc voltage source by a short circuit and each dc current source by an open circuit.
4. Replace the transistor with one of its small-signal, equivalent-circuit models. Although any of the models can be used, one might be more convenient than the others for the particular circuit being analyzed. This point will be made clearer in the next section.
5. Analyze the resulting circuit to determine the required quantities (e.g., voltage gain, input resistance).

**Table 7.3** Small-Signal Models of the BJT

Hybrid- $\pi$ Model			
■ ( $g_m, r_o$ ) Version	■ ( $\beta i_b$ ) Version		
T Model			
■ ( $g_m, v_{be}$ ) Version	■ ( $\alpha i_e$ ) Version		
Model Parameters in Terms of DC Bias Currents			
$g_m = \frac{I_C}{V_T}$	$r_e = \frac{V_T}{I_E} = \frac{V_T}{\alpha I_C}$	$r_e = \frac{V_T}{I_E} = \frac{V_T}{\beta I_C}$	$r_o = \frac{ V_A }{I_C}$
In Terms of $g_m$			
$r_e = \frac{\alpha}{g_m}$	$r_e = \frac{\beta}{g_m}$		
In Terms of $r_e$			
$g_m = \frac{\alpha}{r_e}$	$r_o = (\beta + 1)r_e$	$g_m + \frac{1}{r_o} = \frac{1}{r_e}$	
Relationships between $\alpha$ and $\beta$			
$\beta = \frac{\alpha}{1 - \alpha}$	$\alpha = \frac{\beta}{\beta + 1}$	$\beta + 1 = \frac{1}{1 - \alpha}$	

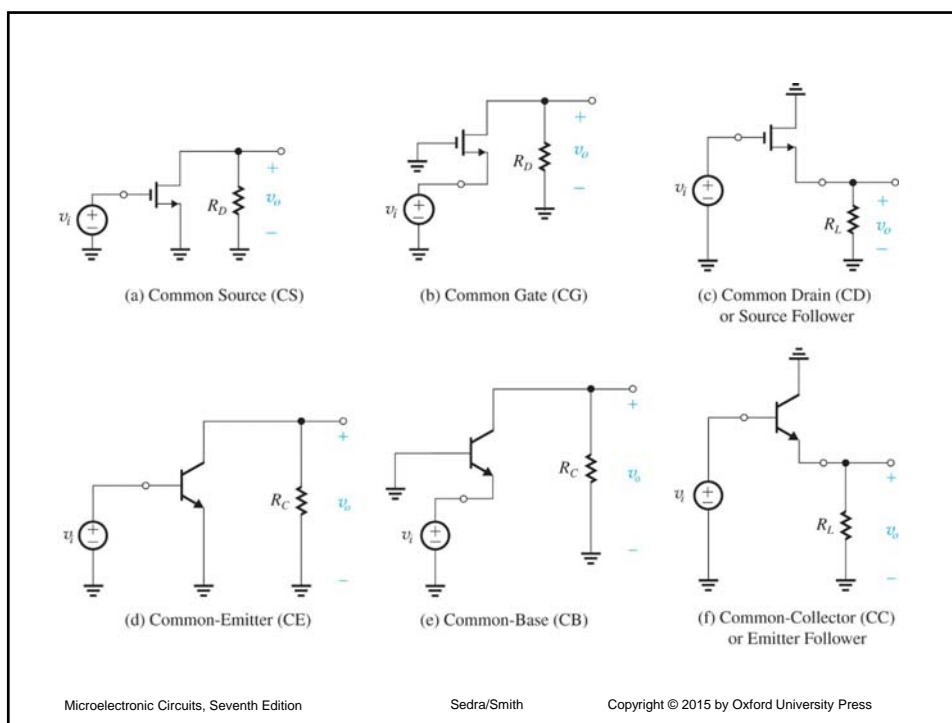

## Amplifiers

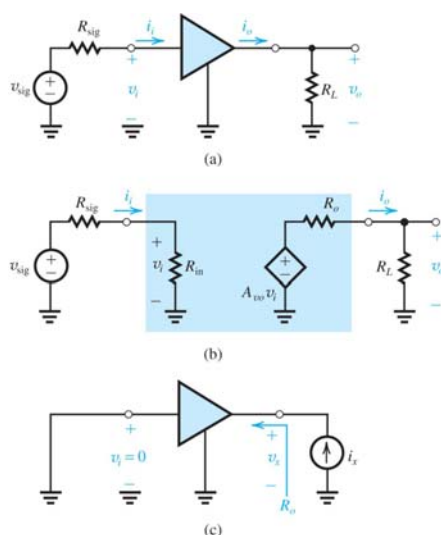


Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press


# Common Emitter

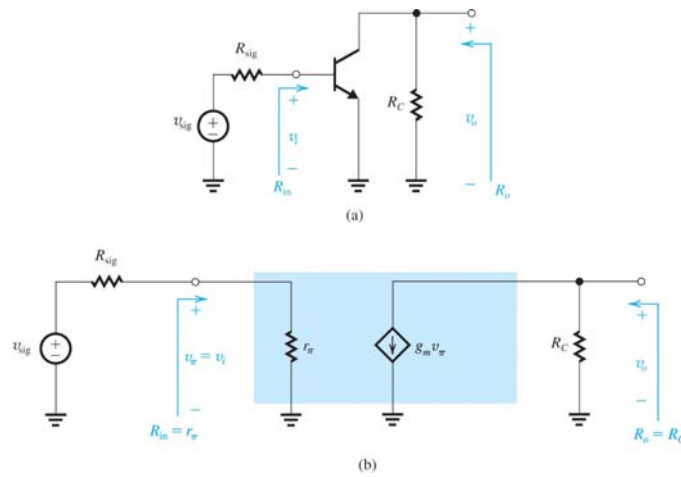

Microelectronic Circuits, Seventh Edition

Sedra/Smith

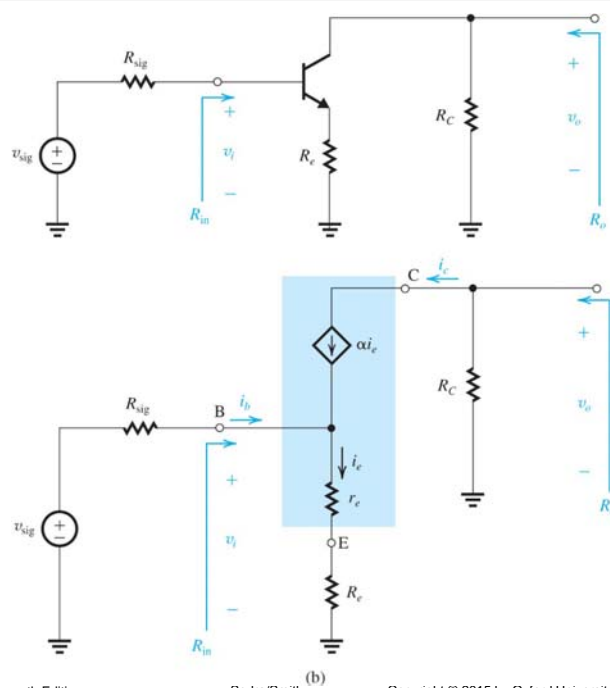Copyright © 2015 by Oxford University Press




Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press

## Common Base

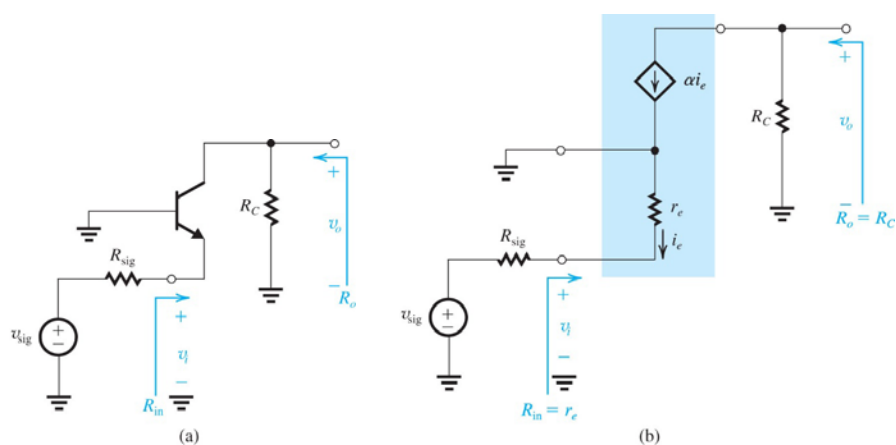


Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press

## Common Collector – Emitter Follower

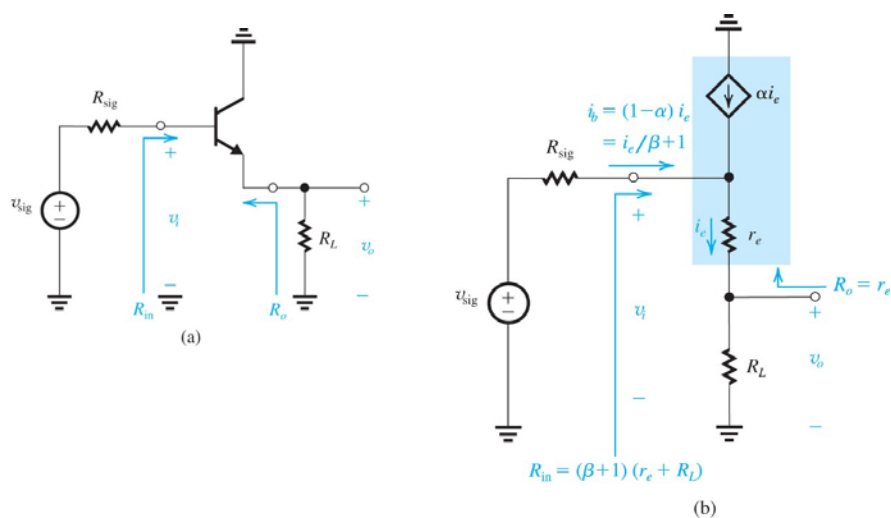

Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press