

CHAPTER 6

Bipolar Junction Transistors (BJTs)

Disclaimer: Most of the slides are skeletons that will be filled/modified in the lecture. Please do not assume that you can know the material just by reading the slides.

Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press

Chapter Objectives

- Learn the physical structure of bipolar transistors and how it works.
- Learn how to analyze and design circuits that contain BJT.
- How the voltage between two terminals control the current that flows through the third terminal.
- How to use BJT to make amplifiers.
- How to obtain linear amplification from nonlinear BJT's

Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press

Bipolar Junction Transistors

BJT


- Developed at Bell Labs in 1948. The vast majority of IC's now are MOSFET.
- BJT's are more reliable (Automotive applications) and have wider frequency response (RF systems).
- BJT are current driven (input current controls output current). For MOSFET (gate voltage controls drain current).
- BJT depends on the flow of both electrons and holes (only one carrier in MOSFET).
- BiCMOS

Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press

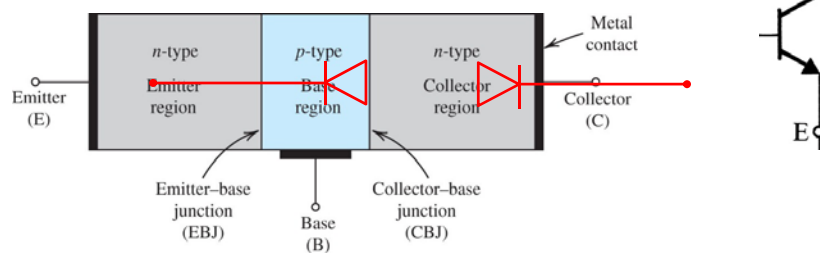
- 3 terminals (Emitter, Base, Collector)
- Two coupled p-n junctions
- The base is shared between the 2 junctions





Microelectronic Circuits, Seventh Edition


Sedra/Smith

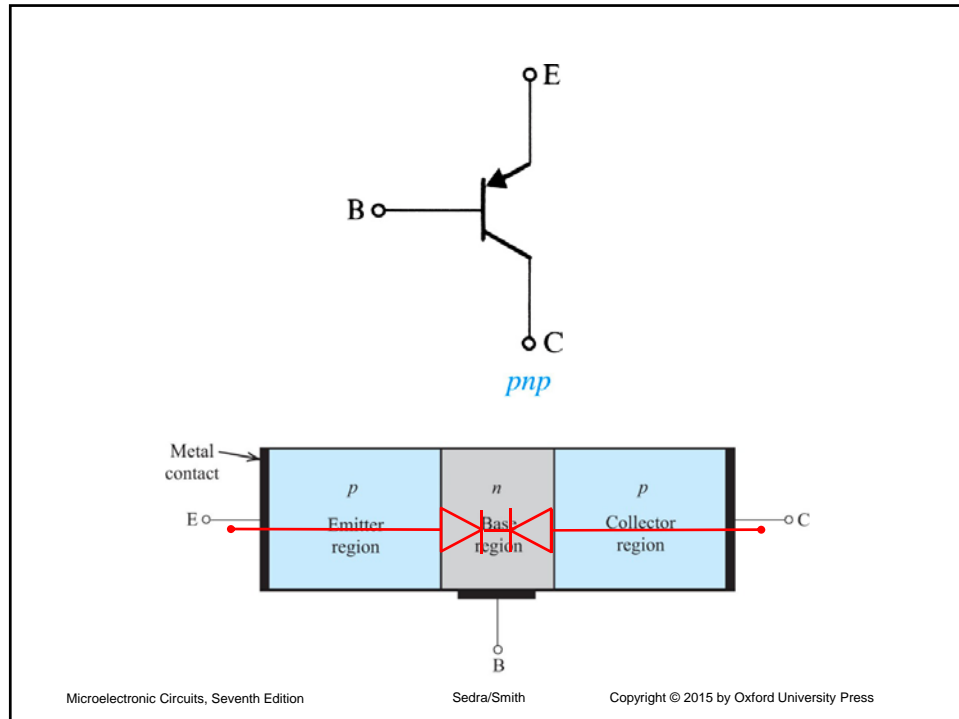Copyright © 2015 by Oxford University Press



Mode	EBJ	CBJ
Cutoff	Reverse	Reverse
Active	Forward	Reverse
Saturation	Forward	Forward

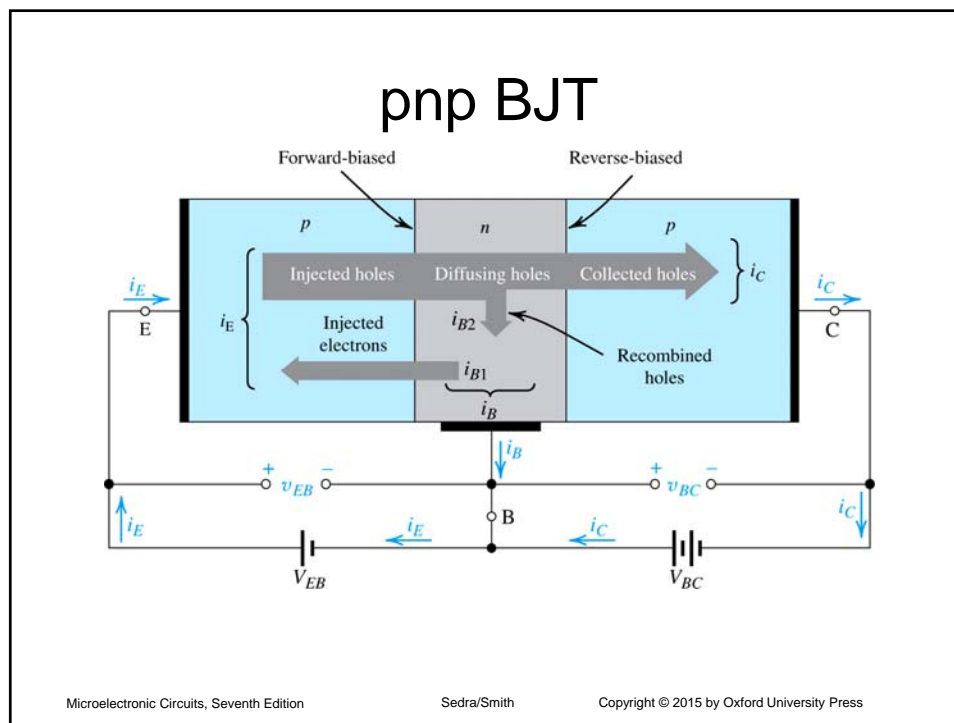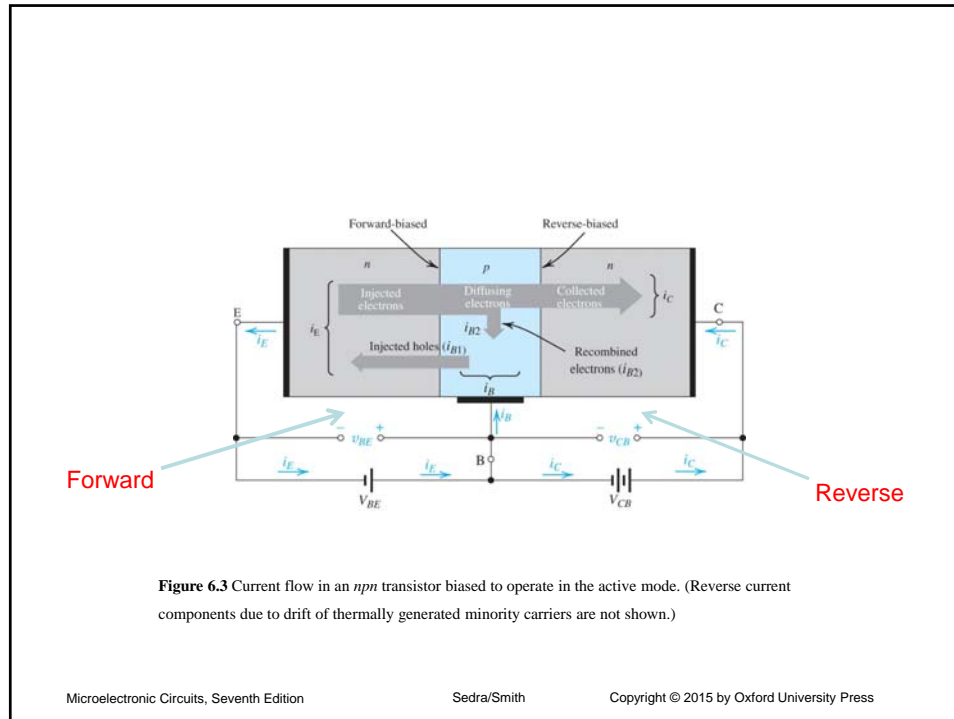

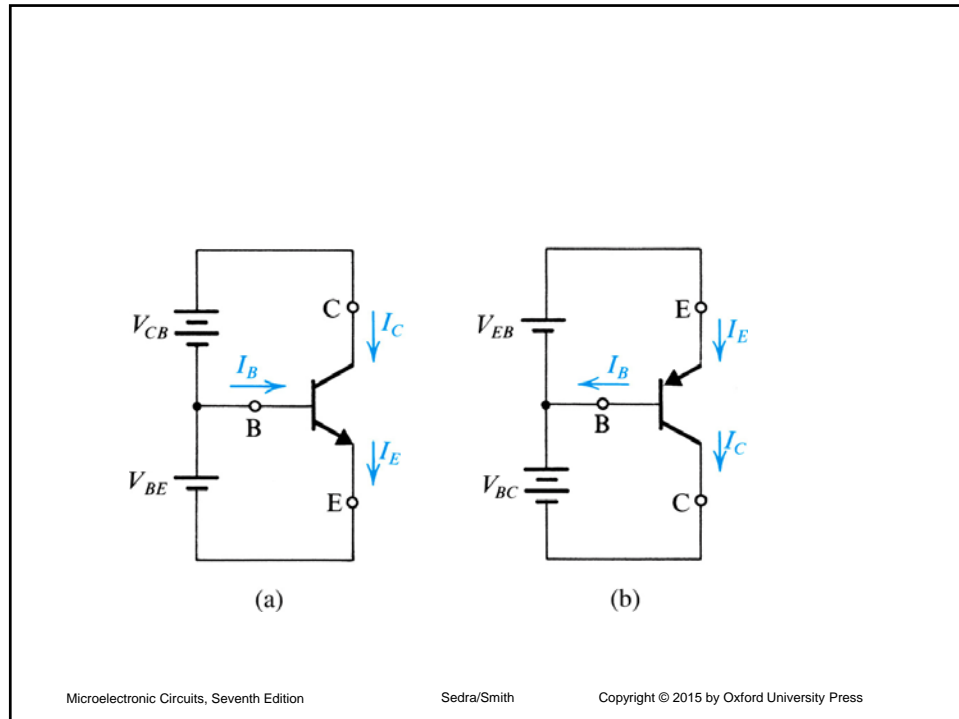

Currents in BJT

- $i_E = i_C + i_B$
- In BJT, base current controls collector current
- $i_C = I_S e^{V_{BE}/V_T}$

$$i_C = \beta_F i_B$$

Common emitter current gain

$$i_C = \alpha_F i_E$$

Common base current gain

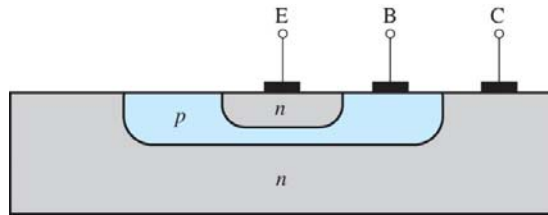


Figure 6.7 Cross section of an *n**p**n* BJT.

Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press


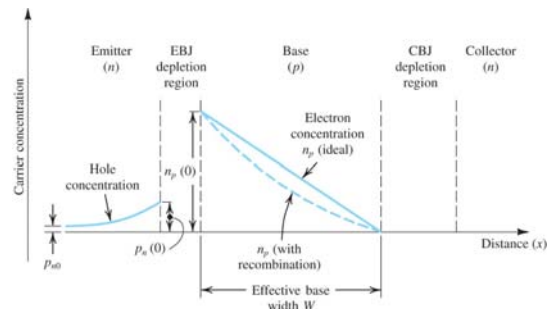
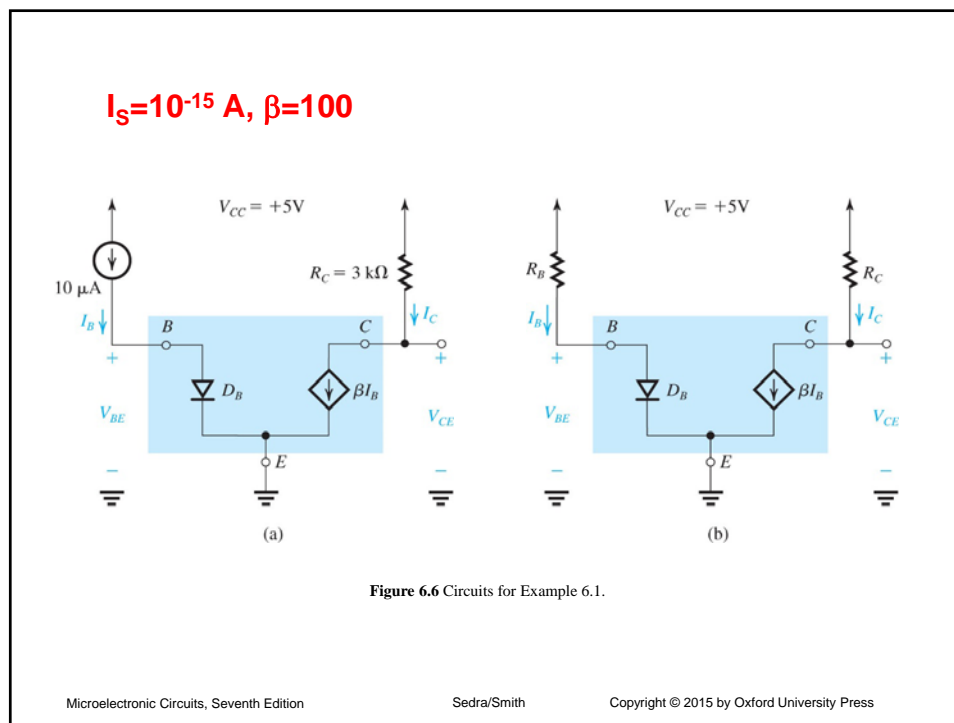


Figure 6.4 Profiles of minority-carrier concentrations in the base and in the emitter of an *n**p**n* transistor operating in the active mode: $v_{BE} > 0$ and $v_{CB} \geq 0$.

Microelectronic Circuits, Seventh Edition

Sedra/Smith

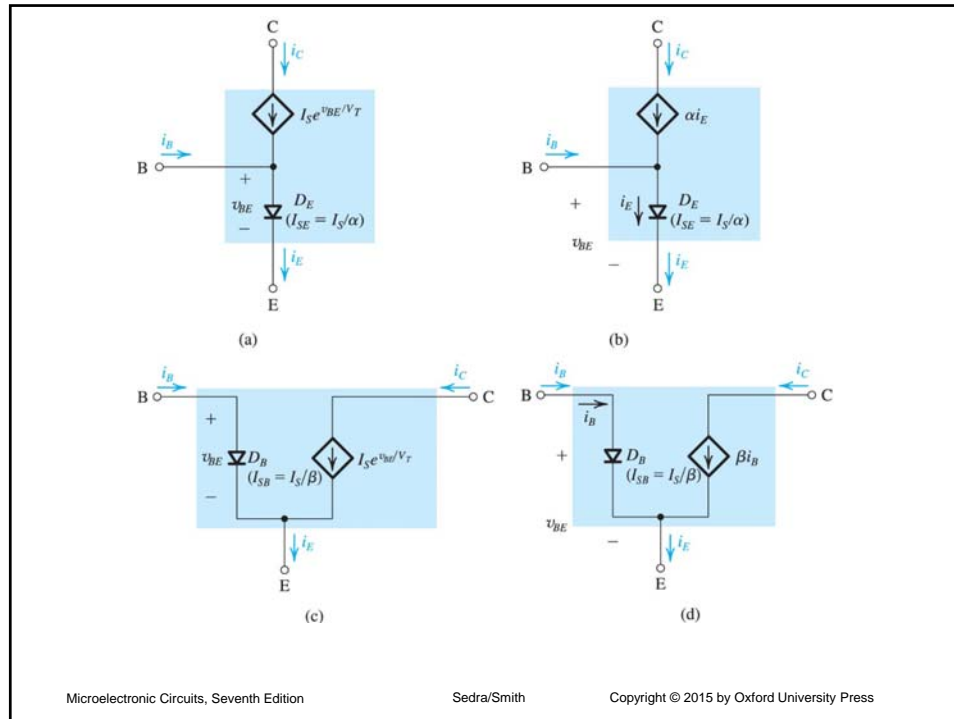Copyright © 2015 by Oxford University Press



Exercise

6.5 -- A transistor with $I_S=10^{-16}\text{A}$, $\beta=100$ with $I_C=1\text{mA}$ find v_{BE} , I_{SE} , and I_{SB}


Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press

Operation in Saturation Mode

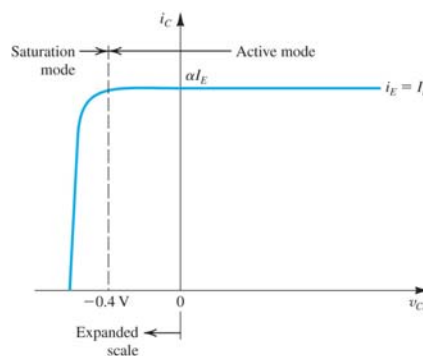- For Forward active region, the CB junction must be reverse biased.
- THE CB junction will not be ON till at least 0.4V forward biased
- Before that, the collector current is constant
- After CB junction is foreword biased, the collector current decreases, why?



Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press

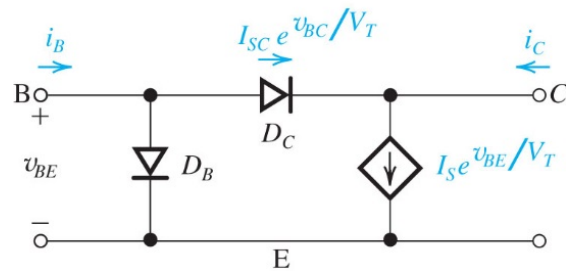


Figure 6.9 Modeling the operation of an *nnp* transistor in saturation by augmenting the model of Fig. 6.5(c) with a forward-conducting diode D_C . Note that the current through D_C increases i_B and reduces i_C .

Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press

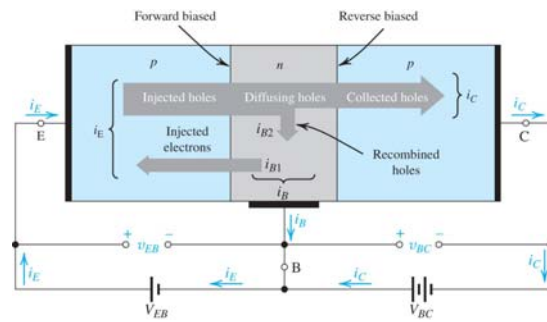


Figure 6.10 Current flow in a *pnp* transistor biased to operate in the active mode.

Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press

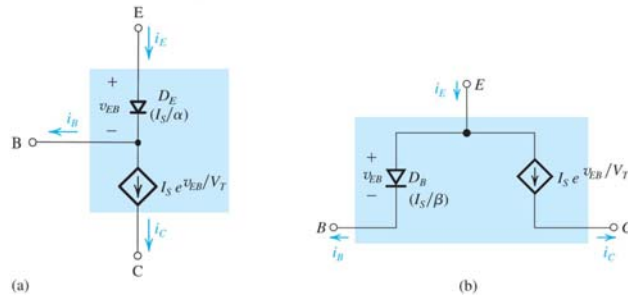


Figure 6.11 Two large-signal models for the *pnp* transistor operating in the active mode.

Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press

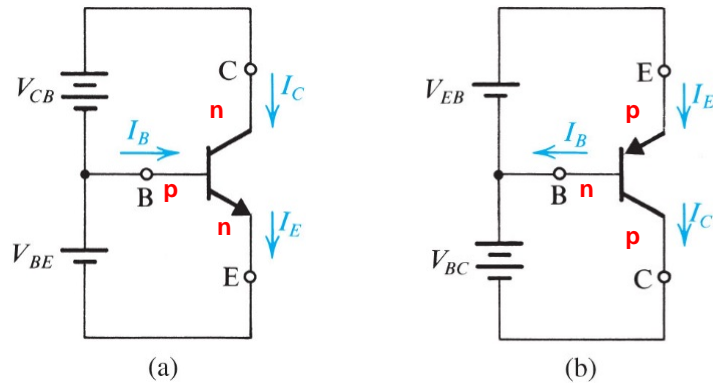


Figure 6.13 Voltage polarities and current flow in transistors operating in the active mode.

Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press

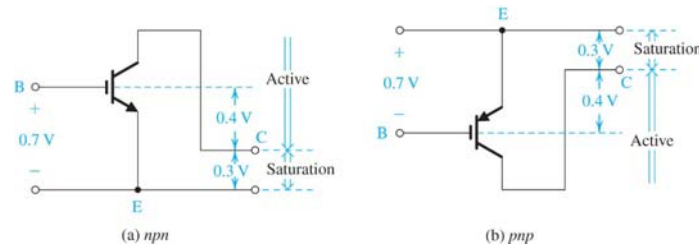


Figure 6.14 Graphical representation of the conditions for operating the BJT in the active mode and in the saturation mode.

Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press

Table 6.2 Summary of the BJT Current–Voltage Relationships in the Active Mode

$$i_C = I_S e^{v_{BE}/V_T}$$

$$i_B = \frac{i_C}{\beta} = \left(\frac{I_S}{\beta} \right) e^{v_{BE}/V_T}$$

$$i_E = \frac{i_C}{\alpha} = \left(\frac{I_S}{\alpha} \right) e^{v_{BE}/V_T}$$

Note: For the *pnp* transistor, replace v_{BE} with v_{EB} .

$$i_C = \alpha i_E \quad i_B = (1 - \alpha) i_E = \frac{i_E}{\beta + 1}$$

$$i_C = \beta i_B \quad i_E = (\beta + 1) i_B$$

$$\beta = \frac{\alpha}{1 - \alpha} \quad \alpha = \frac{\beta}{\beta + 1}$$

$$V_T = \text{thermal voltage} = \frac{kT}{q} \simeq 25 \text{ mV at room temperature}$$

Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press