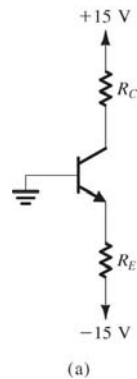


$\beta=100$ , and  $v_{BE} = 0.7 \text{ V}$  at  $i_c = 1 \text{ mA}$   
 Design the circuit to have  $i_c=2 \text{ mA}$  and collector voltage =  $5 \text{ V}$

$$V_{BE1} = V_{BE2} + V_T \ln\left(\frac{i_{C1}}{i_{C2}}\right)$$



Microelectronic Circuits, Seventh Edition

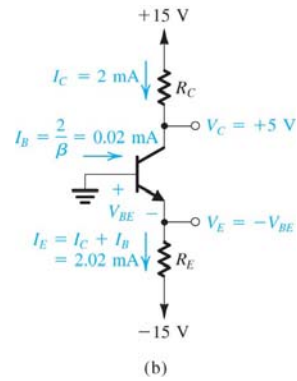


Figure 6.15 Circuit for Example 6.2.

Sedra/Smith

Copyright © 2015 by Oxford University Press

$V_E = -0.7 \text{ V}$ ,  $\beta = 50$   
 Find  $I_E, I_B, I_C, V_C$

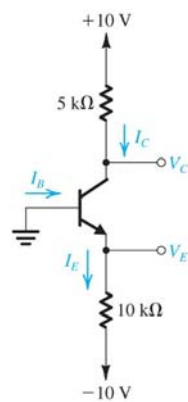


Figure E6.13

Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press

Measurements:  $V_B = 1.0\text{V}$ ,  
 $V_E = 1.7\text{V}$  find  $\alpha$ ,  $\beta$  and  $V_C$

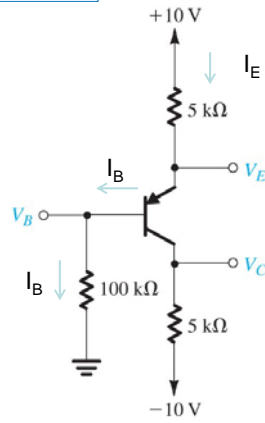




Figure E6.14

Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press

$$i_C = I_s e^{v_{BE}/V_T}$$

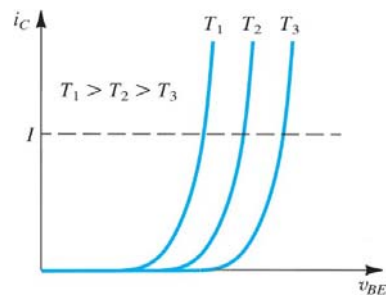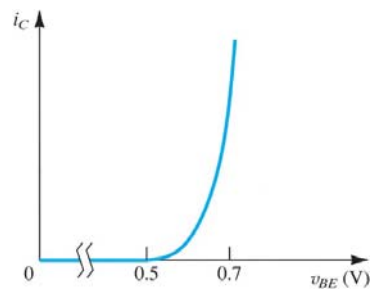

Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press


## The Early Effect

- In our analysis, we assume  $v_{BE}$  will be the only factor to determine  $i_C$  and  $i_B$ .
- Practical BJT s show some dependence of the collector current on the collector voltage (J. M. Early)
- The real  $i$ - $v$  characteristics as shown on the next slide

Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press

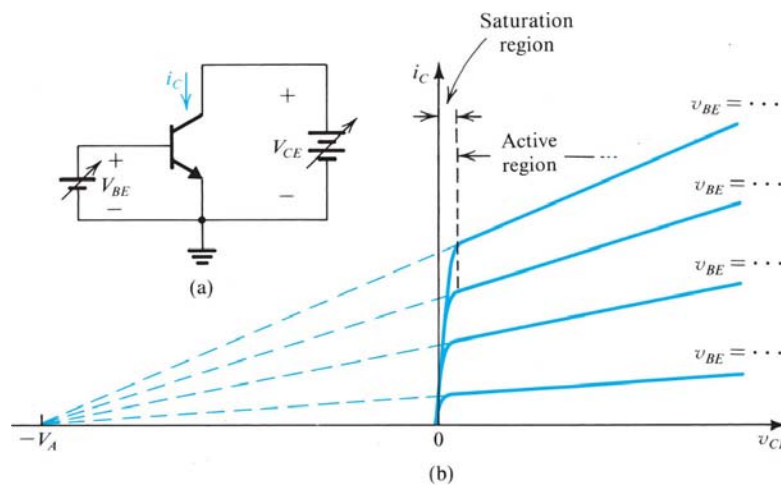


**Figure 6.18** (a) Conceptual circuit for measuring the  $i_C$ - $v_{CE}$  characteristics of the BJT. (b) The  $i_C$ - $v_{CE}$  characteristics of a practical BJT.

Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press

### Large signal model including $r_o$

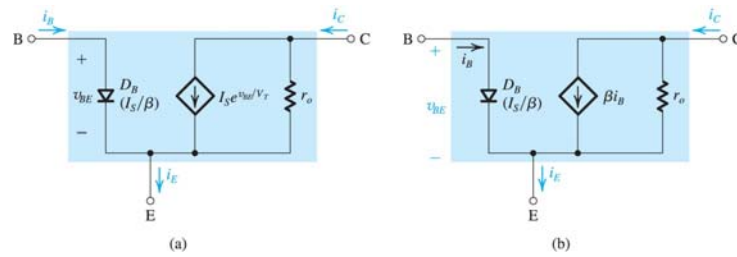

**Figure 6.19** Large-signal, equivalent-circuit models of an npn BJT operating in the active mode in the common-emitter configuration with the output resistance  $r_o$  included.


Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press
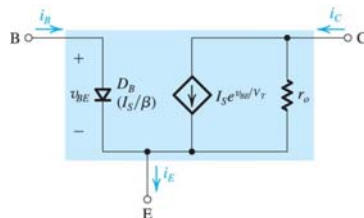
## Example

- Use this model to express  $i_C$  in terms of  $v_{BE}$  and  $v_{CE}$



Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press


## Common Emitter C/C (alt. form)

- $i_B$  is used as a parameter
- **Common Emitter Current Gain  $\beta$** : Another way to measure  $\beta$  (incremental  $\beta$ )
- $\Delta i_C / \Delta i_B$
- Saturation voltage and saturation resistance ( $\beta_{\text{forced}} < \beta$ )

Microelectronic Circuits, Seventh Edition

Sedra/Smith

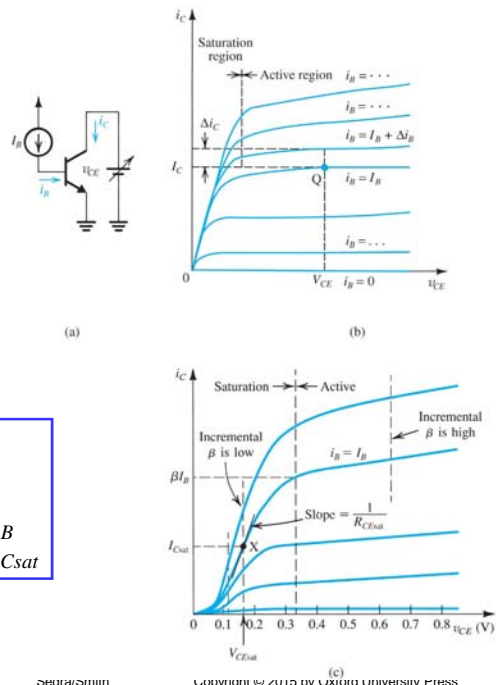
Copyright © 2015 by Oxford University Press



Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press

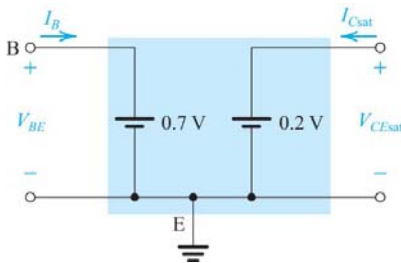

**Figure 6.21** A simplified equivalent-circuit model of the saturated transistor.


Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press

$R_C = 10\text{ k}\Omega$ , what should be  $V_{BB}$  for

- Active  $V_{CE} = 5\text{ V}$ ,  $\beta = 50$
- Edge of saturation
- Deep sat with  $\beta = 10$

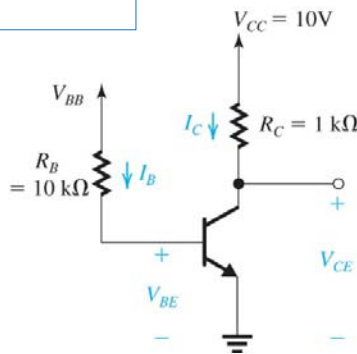

**Figure 6.22** Circuit for Example 6.3.

Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press

Find  $V_{CE}$  for  $V_{BB} = 0V$

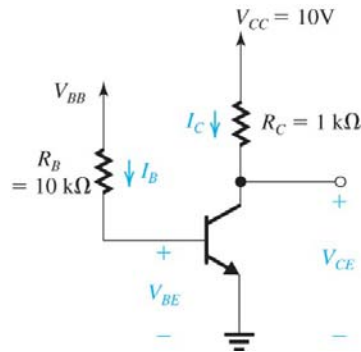


Figure 6.22 Circuit for Example 6.3.

Table 6.3 Simplified Models for the Operation of the BJT in DC Circuits

	npn	npn	npn	npn
Active				
EBJ:				
Forward				
Biased				
CBJ:				
Reverse				
Biased				
Saturation				
EBJ:				
Forward				
Biased				
CBJ:				
Forward				
Biased				