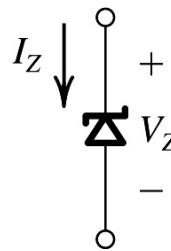



Zener Diode

- Diodes that are designed to operate in the reverse breakdown region.
- Used for low current regulators (although regulators chips are widely used now).




Zener diodes

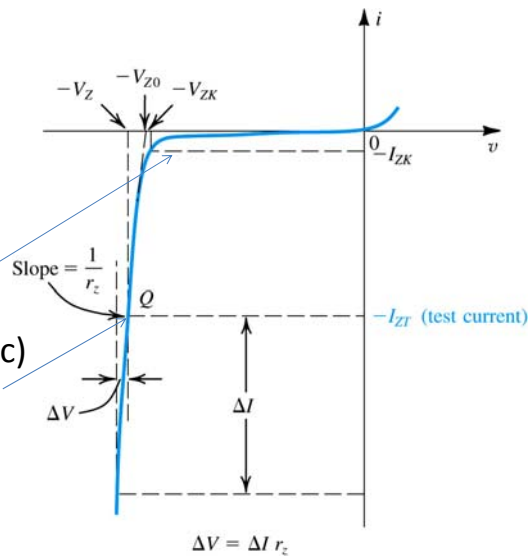- Characterized by
 - V_Z at a specified test current I_{ZT}
 - Maximum power
 - Knee current I_{KZ}
 - Incremental (dynamic) resistance $r_z = \Delta V / \Delta I$



Zener Diodes

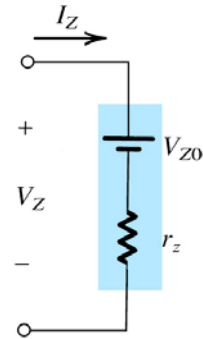- Equivalent circuit
- V_{Z0} in practice is the same as the knee voltage




Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.

Assume a 6.8-V Zener diode with $V_Z = 6.8$ at $I_Z = 5\text{mA}$, $r_z = 20\ \Omega$, $I_{ZK} = 0.2\text{mA}$, $V^+ = 10\text{V} \pm 1\text{V}$

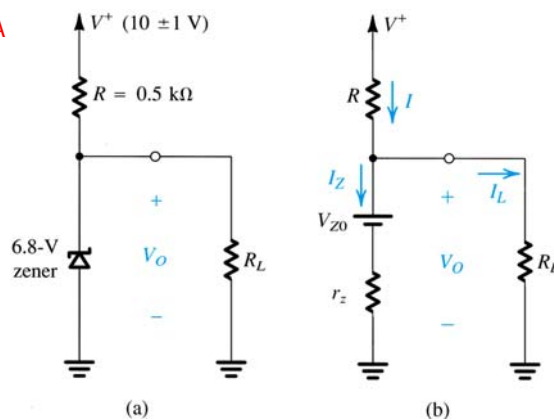- Find V_O and the line regulation at no load
- Find the load regulation when the load current is 1mA
- Find V_O for $R = 2\text{K}\Omega$, $0.5\text{K}\Omega$
- Find the minimum load for the diode to operate in the breakdown region



Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.

Changing amplitude and Electrical isolation

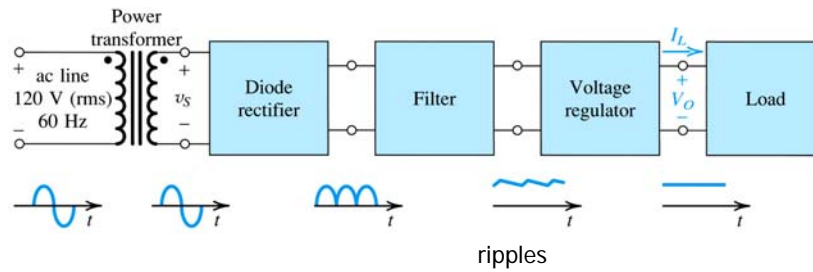


Figure 4.20 Block diagram of a dc power supply.


Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.

Half-Wave Rectifier

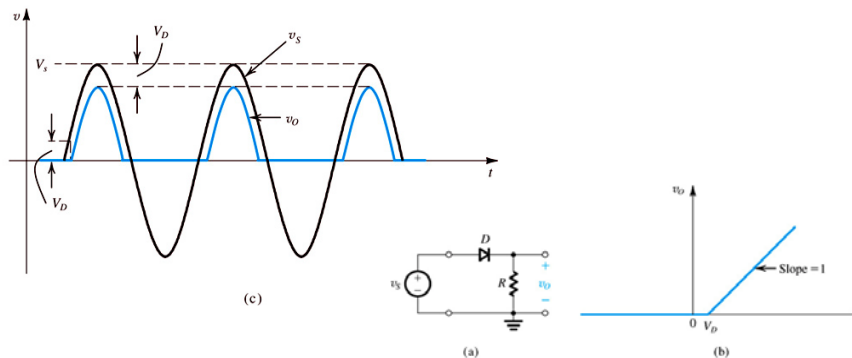- Removes the negative voltage half cycle
- Peak inverse voltage < breakdown voltage





Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.

Full-Wave Rectifier

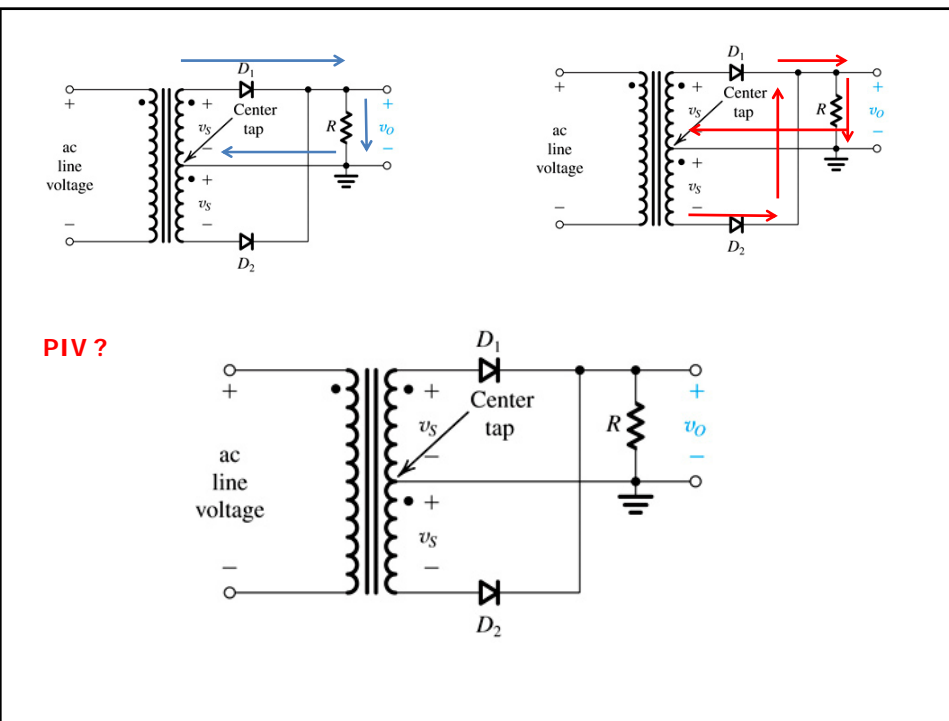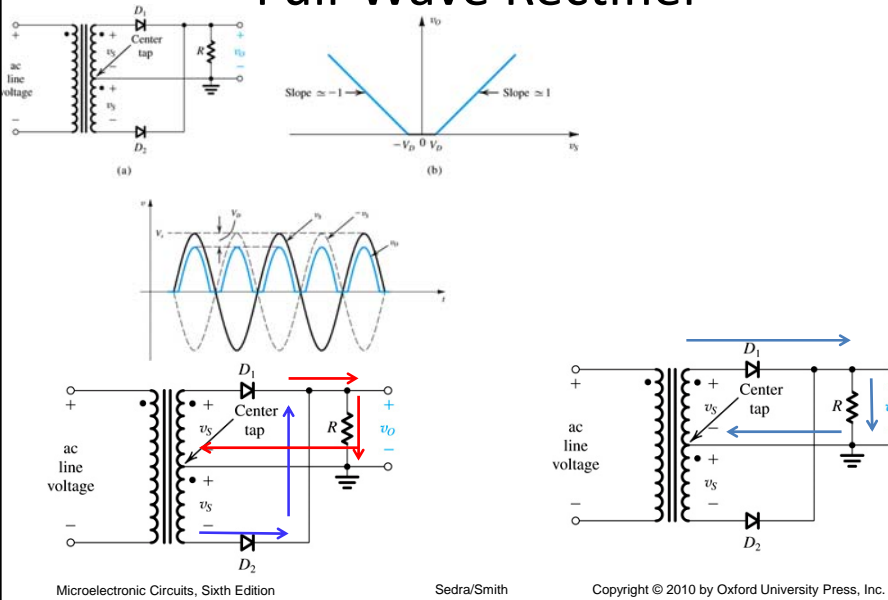

Bridge Rectifier

PIV ?

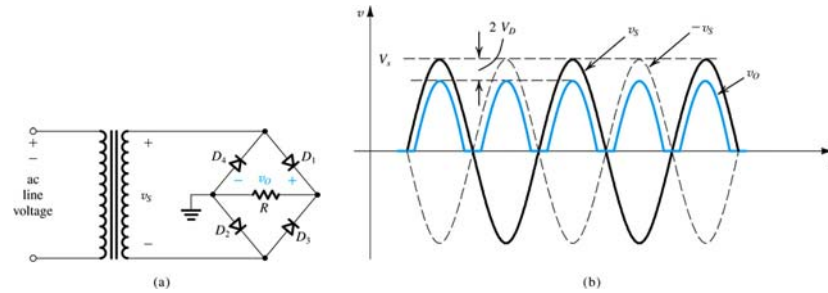


Figure 4.23 The bridge rectifier: (a) circuit; (b) input and output waveforms.

Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.


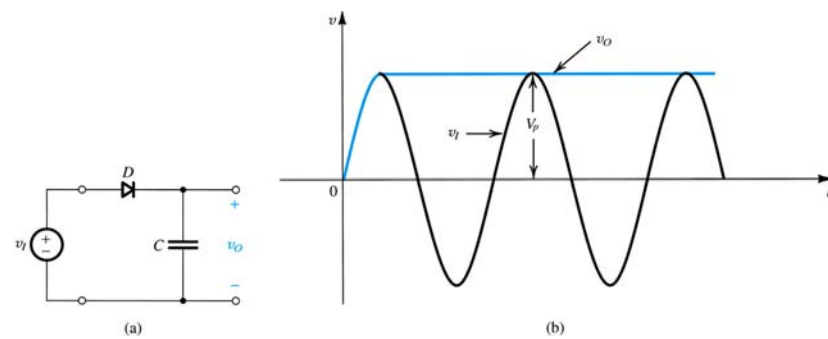
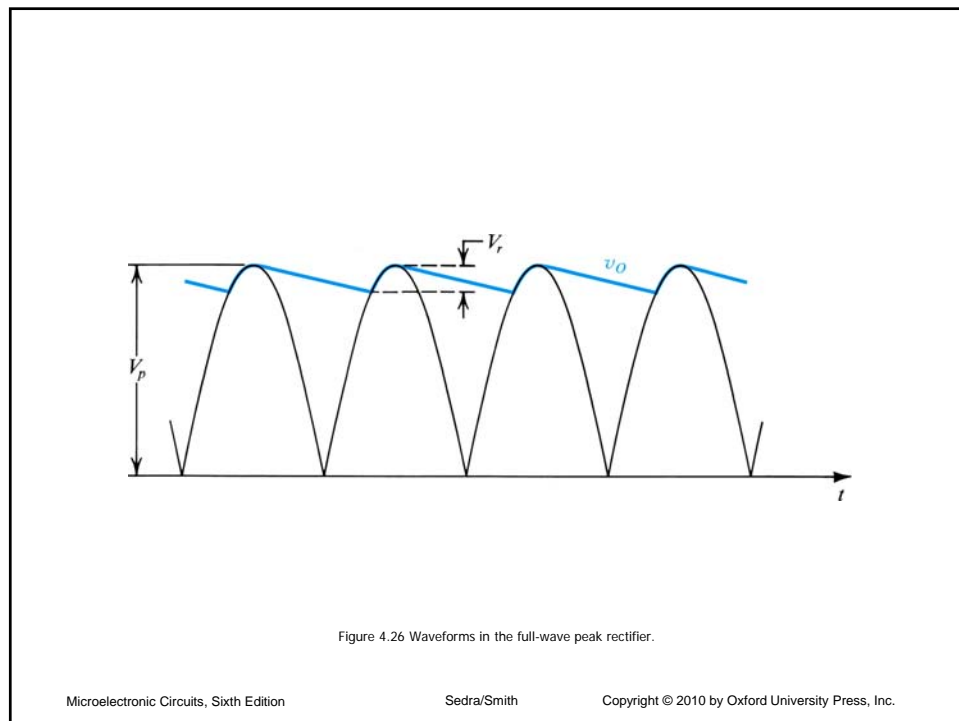


Figure 4.24 (a) A simple circuit used to illustrate the effect of a filter capacitor. (b) Input and output waveforms assuming an ideal diode. Note that the circuit provides a dc voltage equal to the peak of the input sine wave. The circuit is therefore known as a *peak rectifier* or a *peak detector*.

Microelectronic Circuits, Sixth Edition

Sedra/Smith

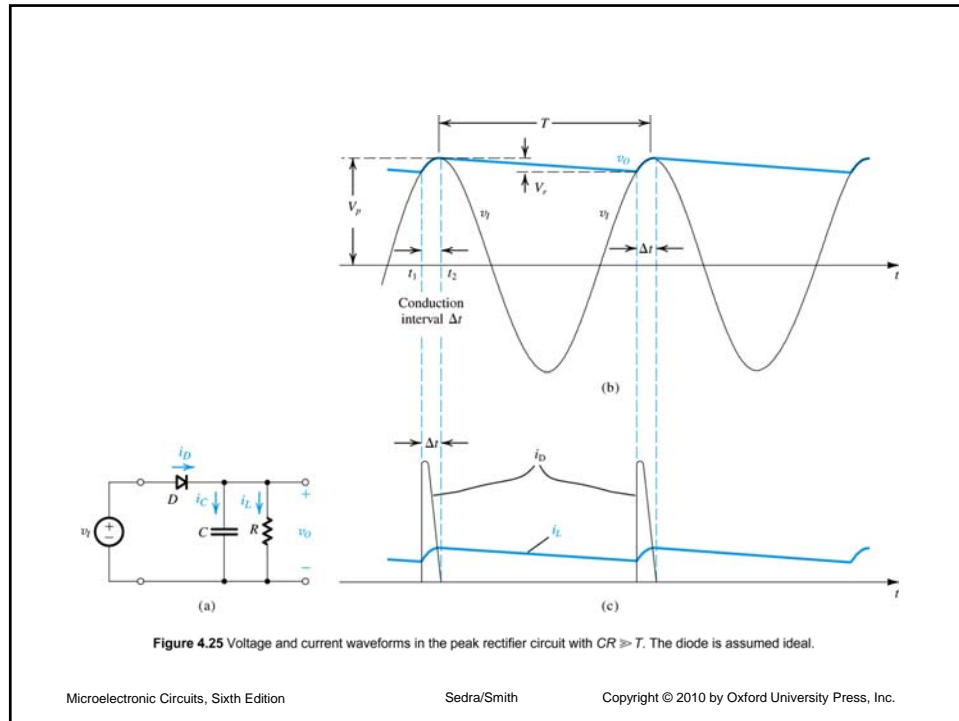Copyright © 2010 by Oxford University Press, Inc.




Superdiode

- There is one or 2 diode voltage drops in the rectifier circuits we studied.
- That is O.K. when we are designing a DC power supply.
- Can not be used to rectify a small voltage signal (100 mV).

Superdiode

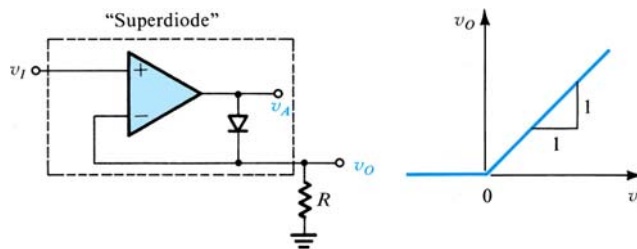- When v_I is positive, v_A is positive, the diode conducts providing the $-ve$ feed back and $v_O = v_I$
- When v_I is $-ve$ v_A is negative diode is reverse biased, no current in R no drop on R, $v_O = 0$



Microele

(a)

(b)


ord University Press, Inc.

Diode Circuits


- Limiter circuits
- Clamped capacitor or DC restorer
- Voltage doubler

Limiter Circuits

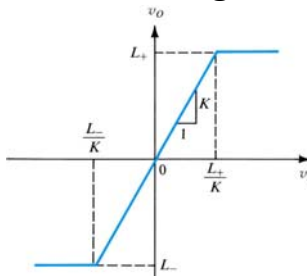- K could be > 1 , but we concentrate on $K \leq 1$ (passive limiter)
- Also known as clippers
- Soft limiting vs. hard limiting



Microelectronic Circuits, Sixth Edition

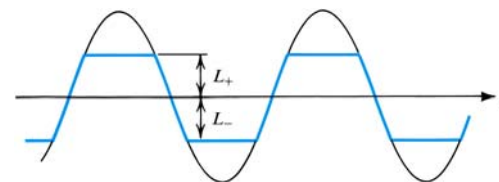

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.

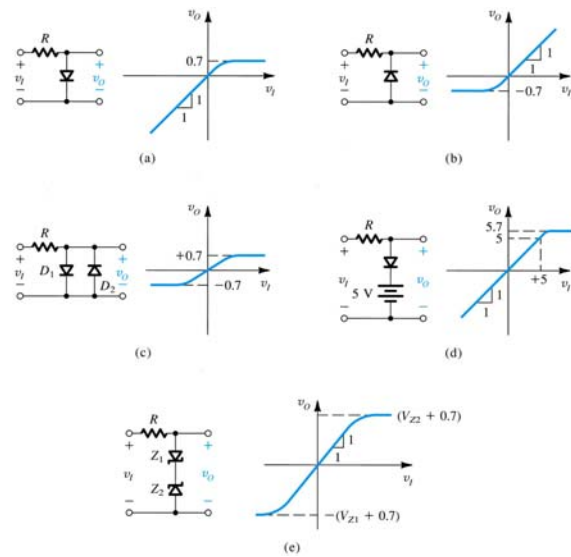


Figure 4.31 A variety of basic limiting circuits.

Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.

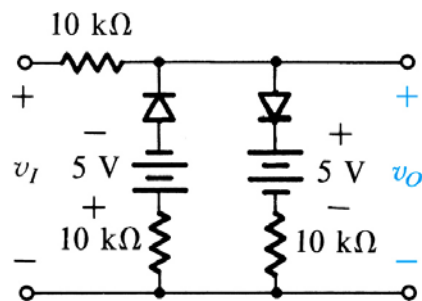


Figure E4.26


Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.

Clamped Capacitor (DC restorer)

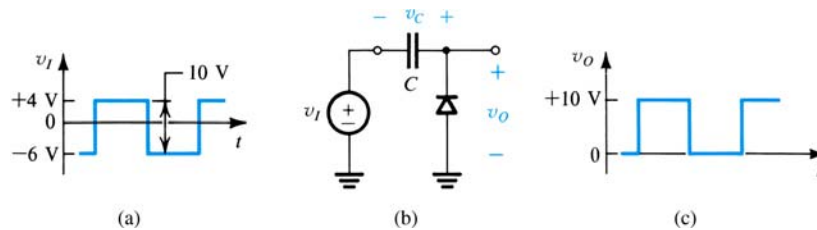- Shifts the input signal by a specific amount
- When v_I is -6, $v_C = 6$ V as shown
- When v_I is +4, diode is off and capacitor does not discharge
- $v_O = v_I + v_C$




Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.

Clamped Capacitor with a Load

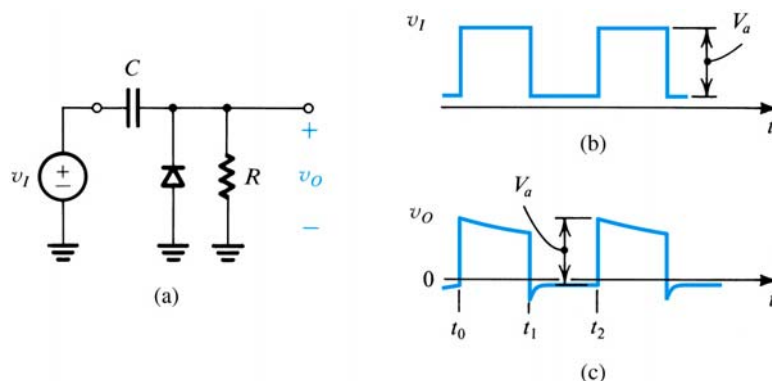Figure 4.33 The clamped capacitor with a load resistance R .

Microelectronic Circuits, Sixth Edition

Sedra/Smith

Copyright © 2010 by Oxford University Press, Inc.

Voltage Doubler

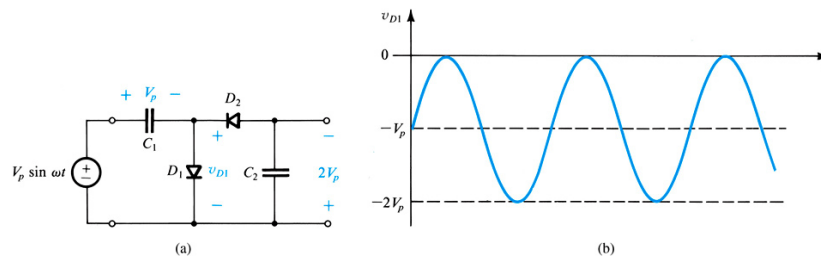


Figure 4.34 Voltage doubler: (a) circuit; (b) waveform of the voltage across D_1 .