

## CHAPTER 7

# Transistor Amplifiers

Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press

- After completing this chapter you will learn
  1. How to use MOSFET as amplifier
  2. How to model the linear operation of the transistor around the Q point using an equivalent circuit (small signal model)
  3. The three basic amplifier configuration

Microelectronic Circuits, Seventh Edition

Sedra/Smith

Copyright © 2015 by Oxford University Press

- In saturation, the MOSFET acts as a voltage controlled current source

$$i_D = \frac{1}{2} k_n' \left( \frac{W}{L} \right) V_{ov}^2 (1 + \lambda v_{DS})$$

- Non-linear
- If the current ( $i_D$ ) flows in a resistive load, output voltage is proportional to  $i_D$ .

Microelectronic Circuits, Seventh Edition


Sedra/Smith



Copyright © 2015 by Oxford University Press



MOSFET as an amplifier

$$v_o = v_{DS} = V_{DD} - i_D R_D$$

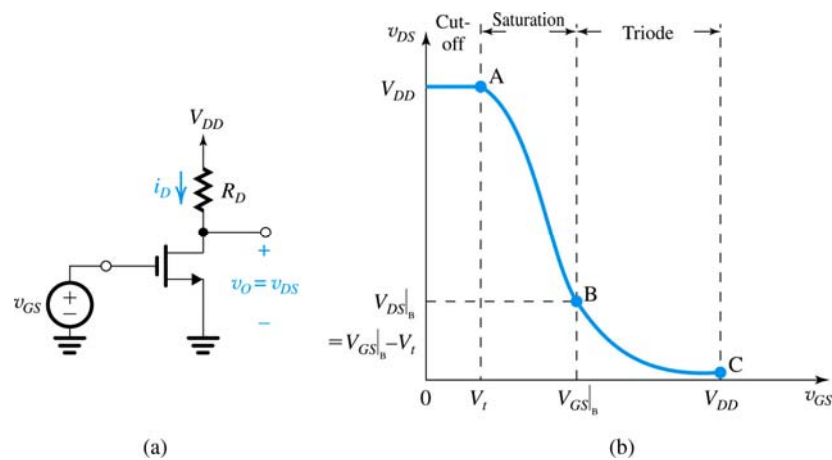Later, we will discuss small signal equivalent circuit





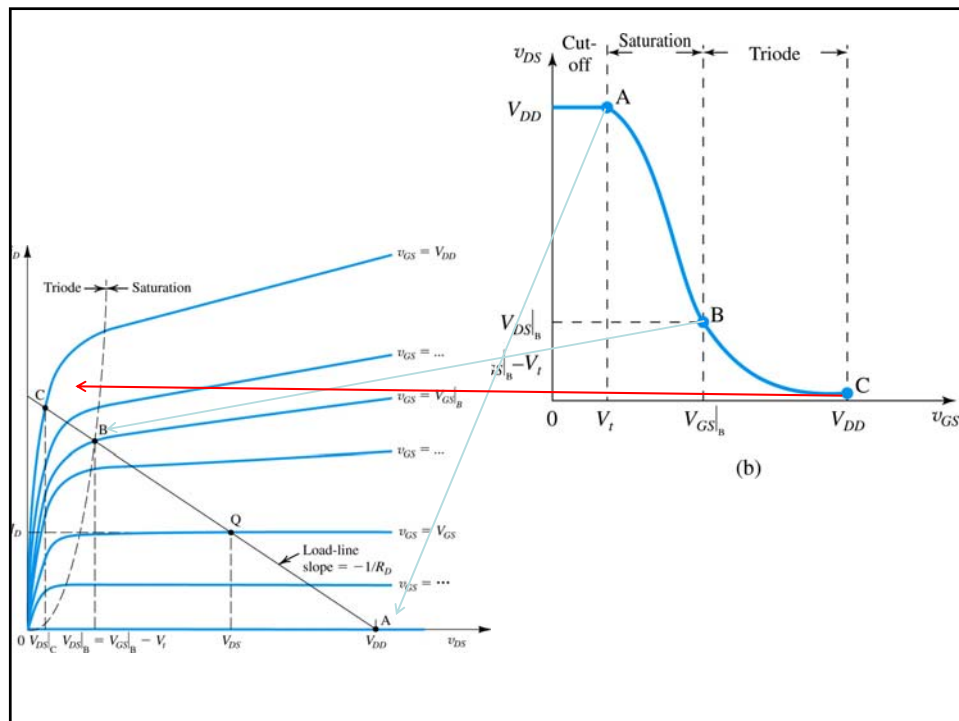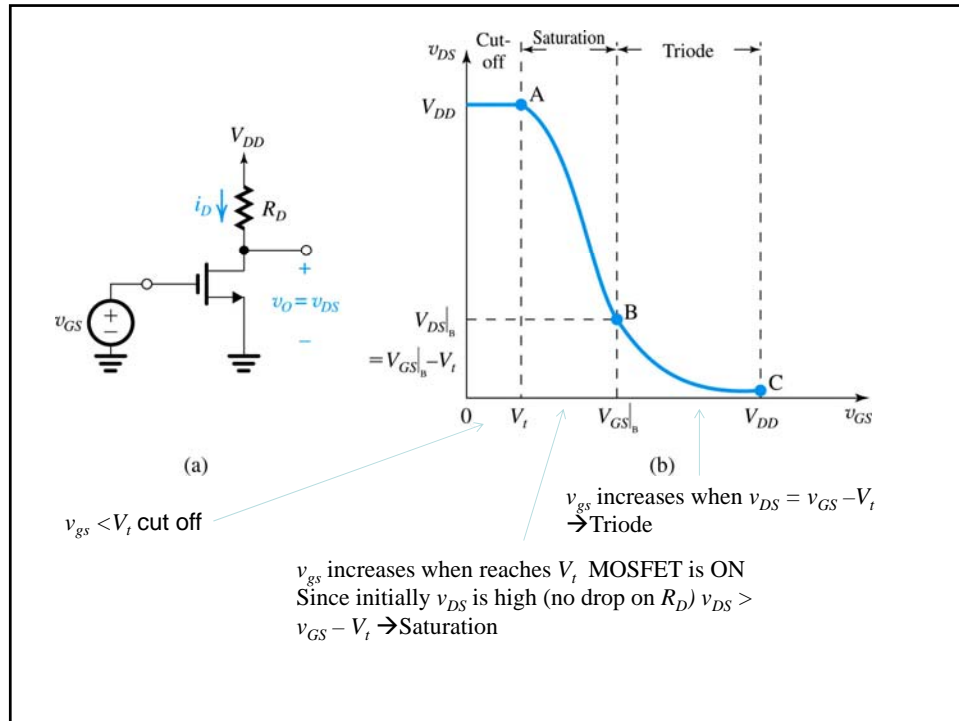

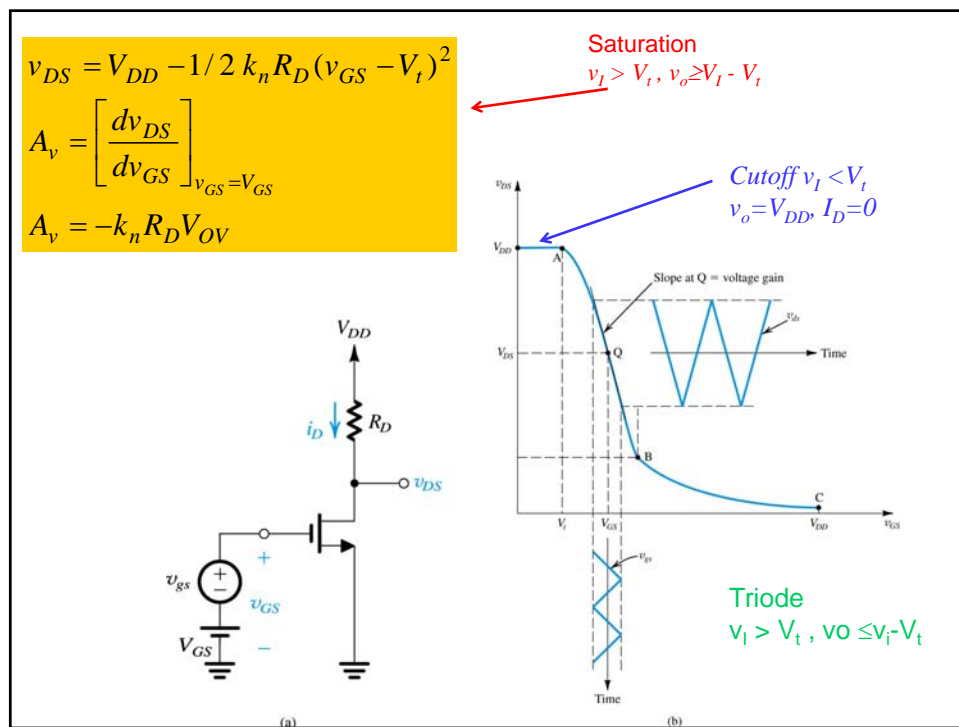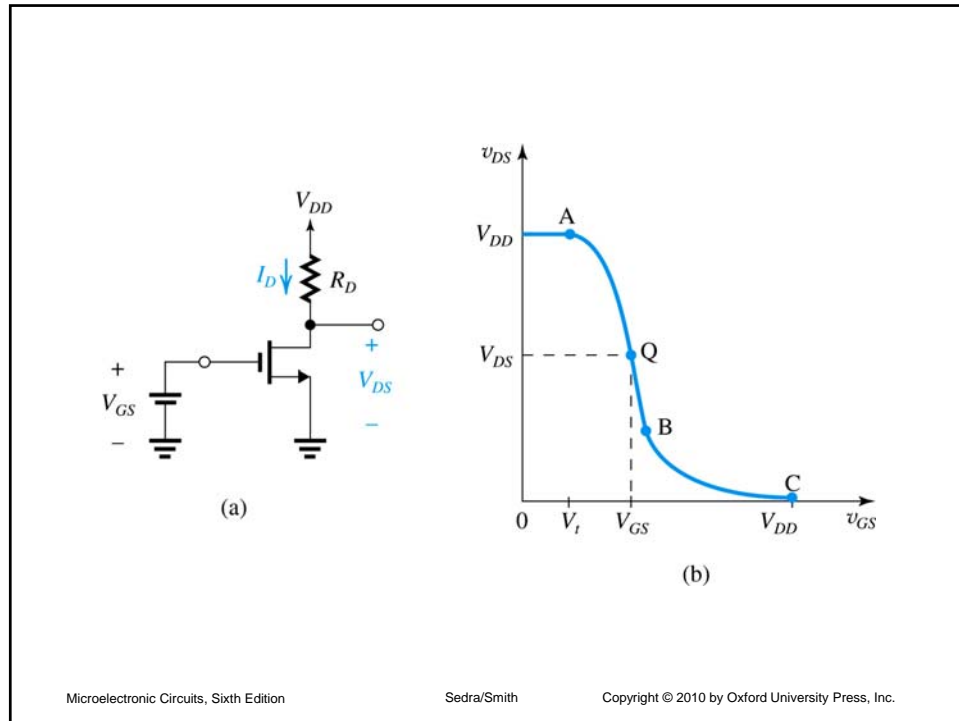

$$V_{DS} = V_{DD} - 1/2 k_n R_D (v_{GS} - V_t)^2$$


$$v_{GS}(t) = V_{GS} + v_{gs}(t)$$

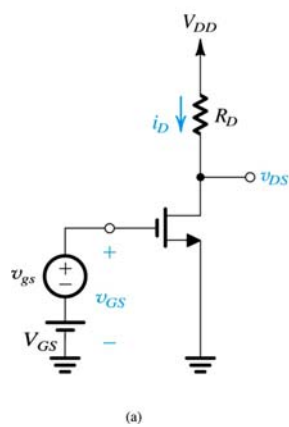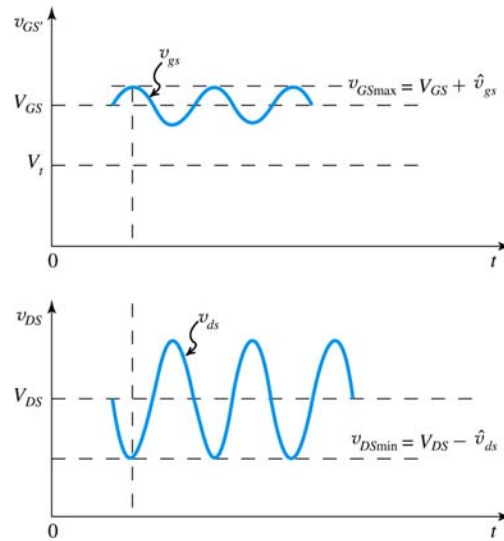

2 Designs for a gain of 10

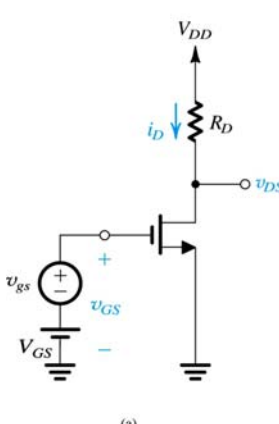1. Changing  $R_D$  while keeping  $V_{OV}$  constant
2. Changing  $V_{OV}$  while keeping  $R_D$  constant

$V_t=0.4V$ ,  $V_{DD}=1.8V$ ,  $V_{GS}=0.6V$ ,  $K_n'=0.4mA/V^2$ ,  
 $W/L=10$ ,  $R_D = 17.5K\Omega$



a) For  $v_{gs}=0$  find  $V_{ov}$ ,  $I_D$ , and  $A_v$   
 b) What is the max symmetrical signal swing allowed at the drain, and  $v_{gs}$



$V_t=0.4V$ ,  $V_{DD}=1.8V$ ,  $V_{GS}=0.6V$ ,  $K_n'=0.4mA/V^2$ ,  
 $W/L=10$ ,  $R_D = 17.5K\Omega$

(a)

Microelectronic Circuits, Seventh Edition      Sedra/Smith      Copyright © 2015 by Oxford University Press

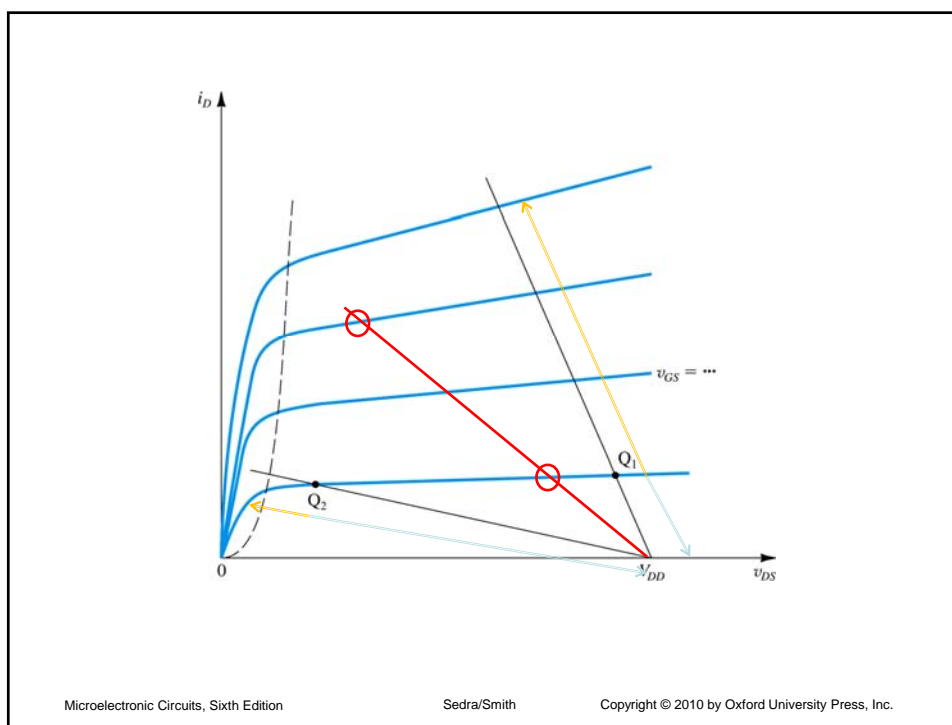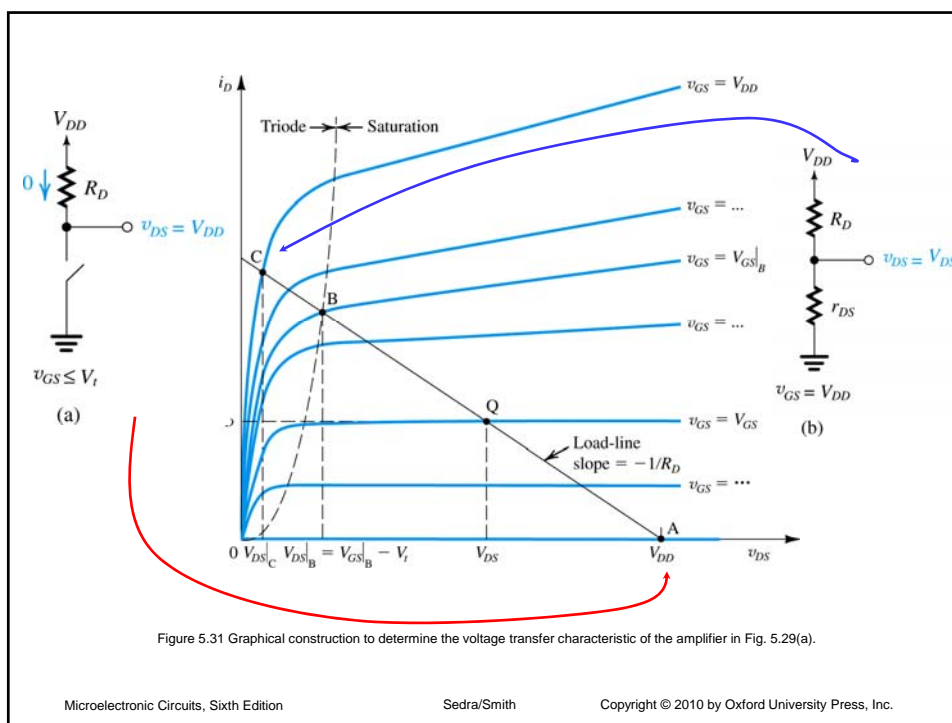
## VTC by Graphical Analysis

- Not used in circuit analysis, used only to illustrate for gaining a greater insight into circuit operation.
- From elementary circuit theory we have
- $V_{DD} = i_D R_D + v_{DS}$
- That represents a line with a slope of  $-1/R_D$
- The transistor operates on a point along that line.


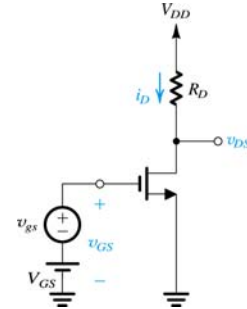
## Small Signal Operations

- The signal  $v_{gs}$  is superimposed on  $V_{GS}$
- $v_{GS} = V_{GS} + v_{gs}$
- $I_D = \frac{1}{2} k_n V_{OV}^2$
- $i_D = \frac{1}{2} k_n (V_{OV} + v_{gs})^2$



$$i_D = \underbrace{\frac{1}{2} k_n V_{OV}^2}_{I_D} + \underbrace{k_n V_{OV} v_{gs}}_{i_D} + \underbrace{\frac{1}{2} k_n v_{gs}^2}_{i_D}$$

## Small Signal Operation

- To minimize the nonlinear part

$$\frac{1}{2} k_n v_{gs}^2 \ll k_n V_{OV} v_{gs}$$

$$v_{gs} \ll 2V_{OV}$$

- $i_D \approx I_D + i_d$

$$v_{DS} = V_{DD} - i_D R_D$$

$$v_{DS} = V_{DD} - (I_D + i_D) R_D$$

$$v_{DS} = V_{DS} - i_d R_D$$



## Small Signal Operation

$$i_D = \frac{1}{2}k_n V_{OV}^2 + k_n V_{OV} v_{gs} + \frac{1}{2}k_n v_{gs}^2$$

Assuming small

$$i_d = k_n V_{OV} v_{gs}$$

$$g_m = \frac{i_d}{v_{gs}} = k_n V_{OV}$$


$$g_m = \left. \frac{\partial i_D}{\partial v_{GS}} \right|_{v_{GS}=V_{GS}}$$

$$A_V = -g_m R_D$$


- Transconductance: relates  $i_d$  and  $v_{ds}$
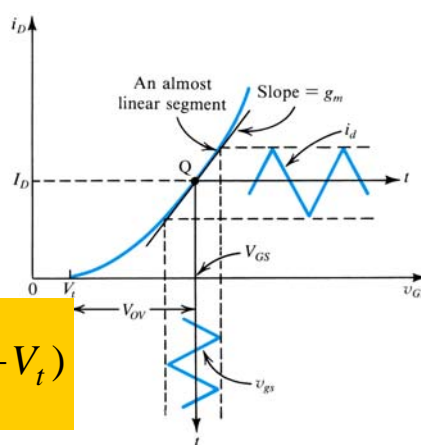
## Transconductance

- The slope of the  $i_{DS}-v_{GS}$  characteristics at the Q point (DC bias point)
- As shown, almost linear.


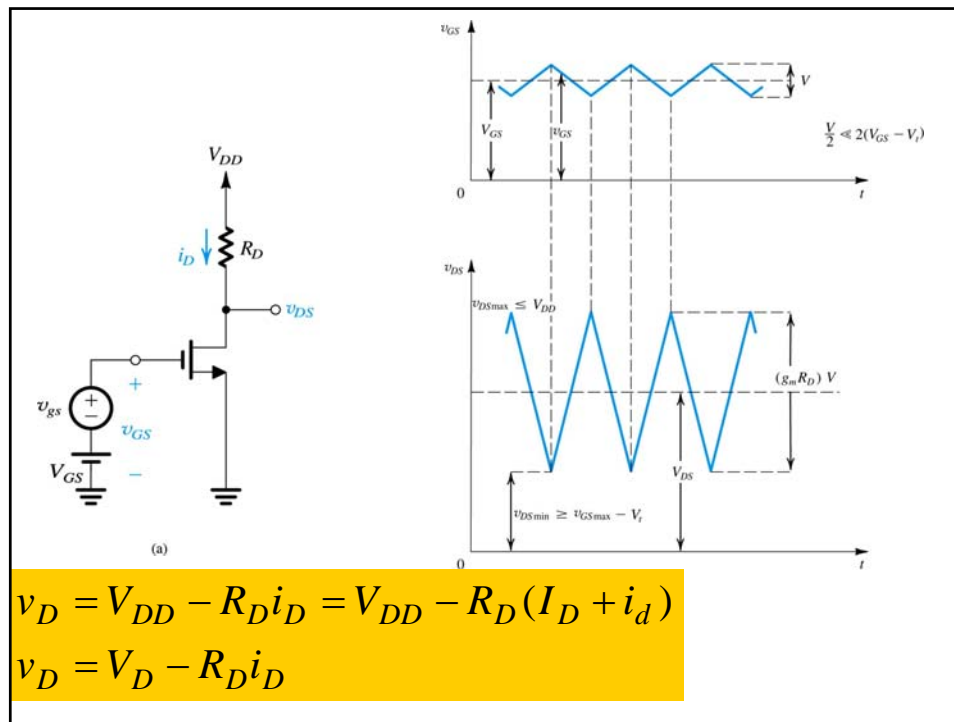
$$g_m = \frac{i_D}{v_{GS}} = k_n' \left( \frac{W}{L} \right) (V_{GS} - V_t)$$




## Separating DC Analysis and Signal Analysis

- Signal quantities are superimposed on DC quantities.
- We can separate DC and AC Analysis.
- The DC Analysis determine the Q Point
- (Bypass) Capacitors are added to prevent disturbing the DC bias (Q point). **WHY?**
- Draw the circuit from the signal point of view
  - DC voltages (current) are short (open)
  - Capacitors are short
  - MOSFET replaced by **small signal equivalent Circuit**


## Why Capacitors

- Adding the load

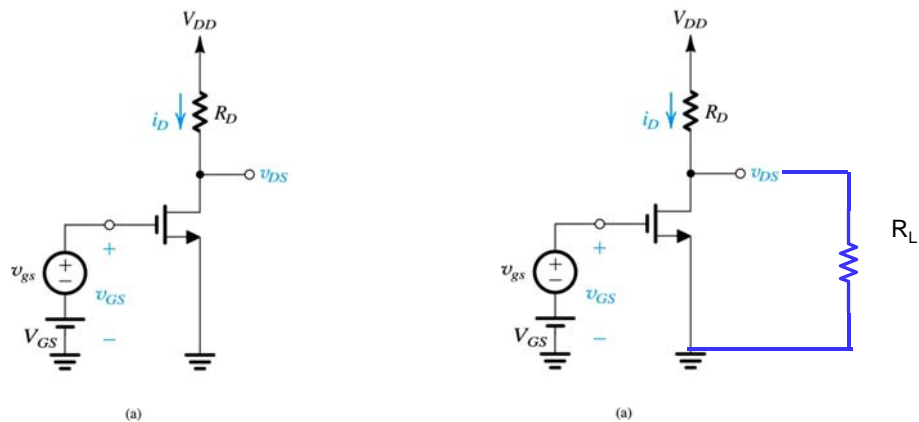

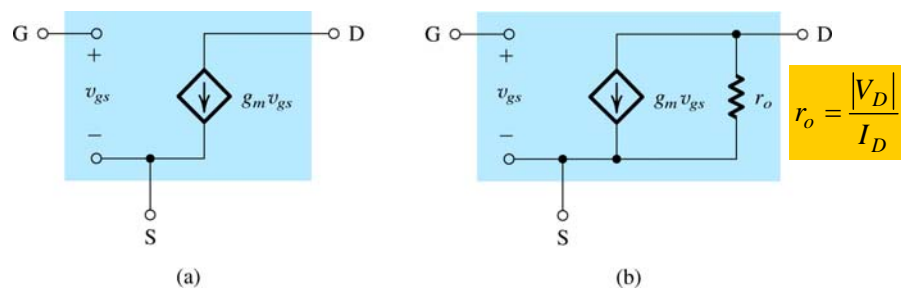
## Small Signal Equivalent Circuit

- Represents only time varying component (DC only determine the bias point)
- What is the difference between (a) and (b).



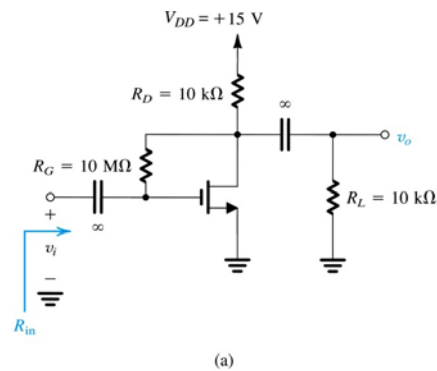
## Example



- Find the small signal voltage gain, input resistance, and the largest allowable input signal.  $V_t = 1.5\text{V}$ ,  $k'_n = 0.25\text{mA/V}^2$ ,  $V_A = 50\text{V}$ .




## Example cont.

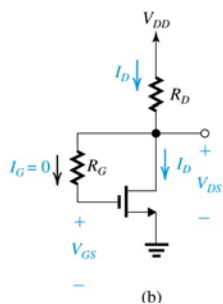


## Example cont.

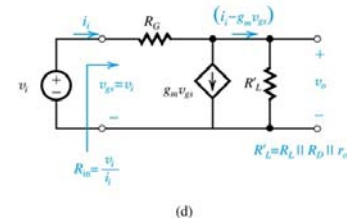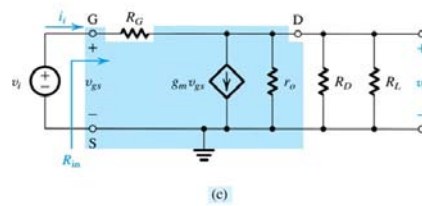

## T-Equivalent-Circuit Model

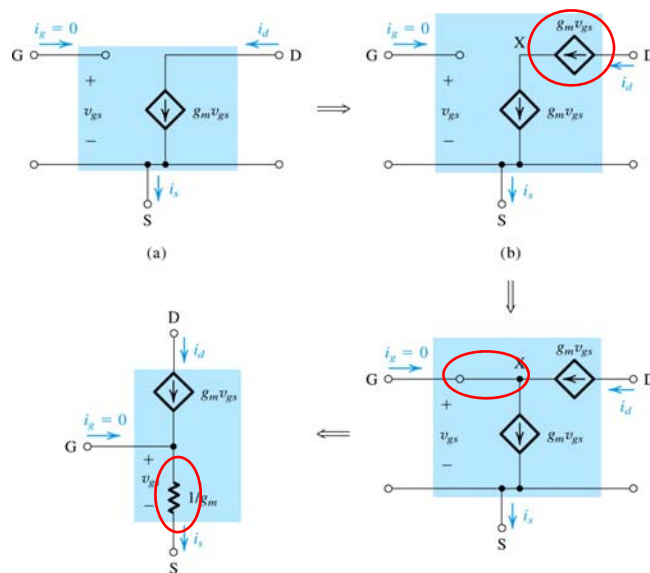

## Incorporating $r_o$

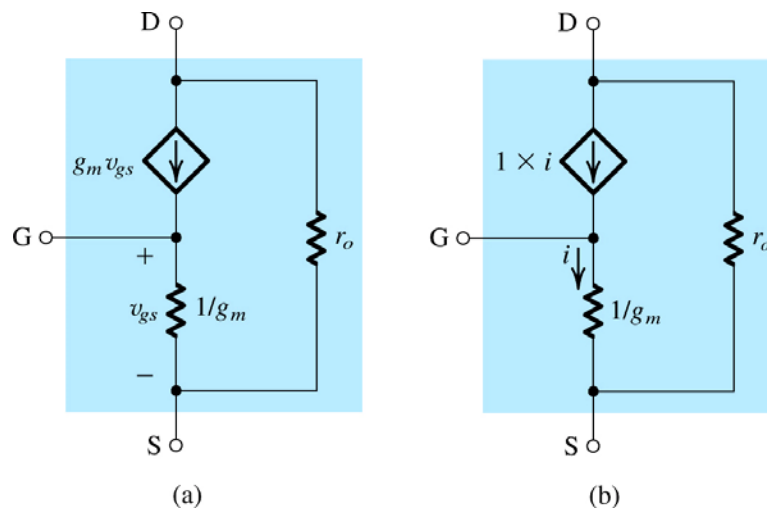

## Example

- Assume saturation, find gain and input

