

Exercise 1. (a) Sample period T_{sample} of the given DFG is

$$T_{sample} = 4T \quad (3.1)$$

So the maximum achievable sample rate is

$$f_{sample} = \frac{1}{T_{sample}} = \frac{1}{4T} \quad (3.2)$$

(b) The pipelining levels are shown by the dashed lines in Figure 3.1. 9 registers are required.

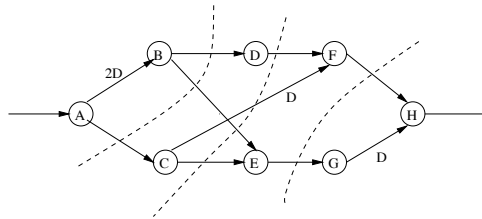


Fig. 3.1 Pipelining levels for Exercise 1(b)

Exercise 3. Let:

$$y_1(n) = a_1x_1(n) + a_2x_1(n-1) + a_3x_1(n-2) + a_4x_1(n-3) + a_5x_1(n-4) \quad (3.3)$$

$$y_2(n) = b_1x_2(n) + b_2x_2(n-1) + b_3x_2(n-2) + b_4x_2(n-3) + b_5x_2(n-4) \quad (3.4)$$

$$y(n) = y_1(n) + y_2(n) \quad (3.5)$$

Then transpose operation can be applied to $y_1(n)$ and $y_2(n)$ separately. The equivalent data-broadcast implementation is shown in Figure 3.3.

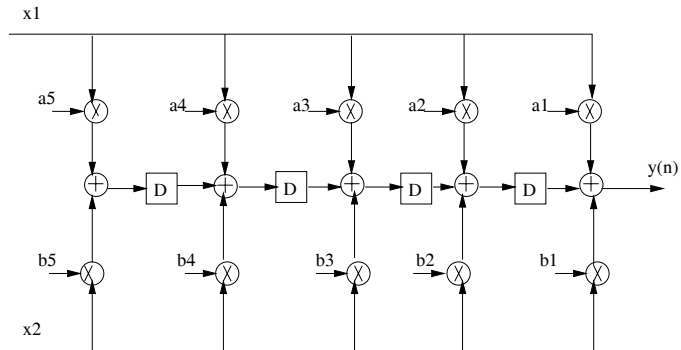


Fig. 3.3 Equivalent data-broadcast structure for Exercise 3

- Exercise 7. (a). The critical path of one multiply-add time can be achieved by using the transpose FIR filter structure as shown in Figure 3.7(a).
- (b). The block filter with block size 3 can be described by

$$\begin{aligned}y(3k) &= ax(3k) + bx(3k - 4) + cx(3k - 6) \\y(3k + 1) &= ax(3k + 1) + bx(3k - 3) + cx(3k - 5) \\y(3k + 2) &= ax(3k + 2) + bx(3k - 2) + cx(3k - 4).\end{aligned}\tag{3.7}$$

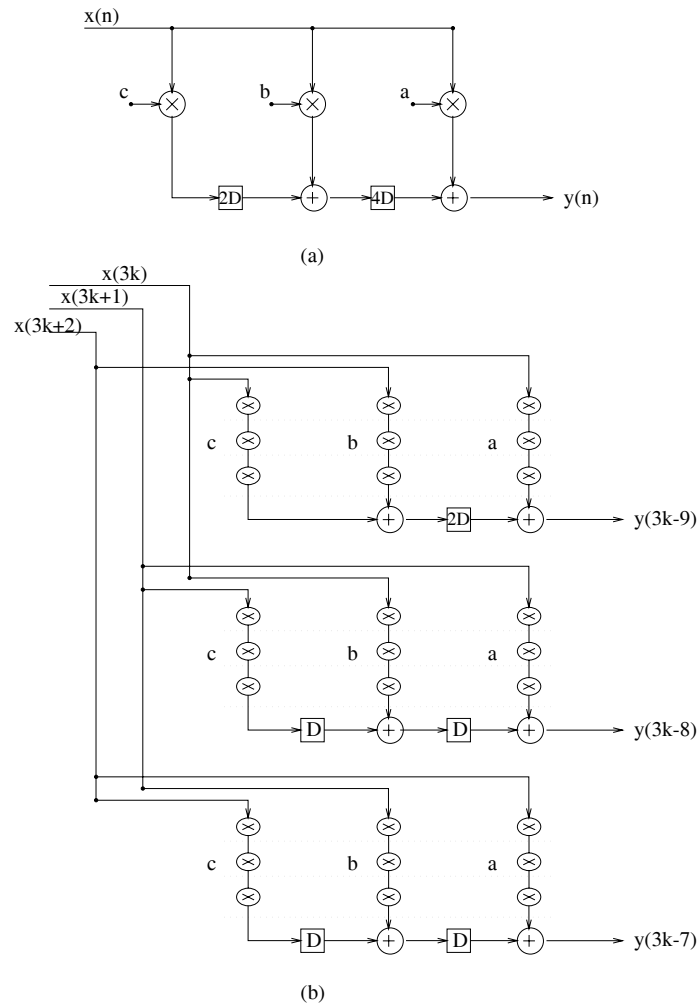


Fig. 3.7 (a):Transpose FIR filter for Exercise 7; (b):Pipelined Block Filter for Exercise

Exercise 9. Suppose M level pipelining is needed. Let β be the supply voltage reduction factor, i.e., the supply voltage can be reduced to βV_0 for the pipelined system. From text, the power reduction factor is β^2 . Therefore, we have

$$\beta^2 \leq \frac{1}{5}. \quad (3.8)$$

Suppose that the pipelined system and the original system have the same sample rate, we have

$$M = \frac{\beta(V_0 - V_t)^2}{(\beta V_0 - V_t)^2}. \quad (3.9)$$

Take $\beta = \sqrt[2]{0.2} = 0.447$, then

$$M = \lceil \frac{0.447(5 - 0.4)^2}{(0.447 \times 5 - 0.4)^2} \rceil = \lceil 2.8 \rceil = 3. \quad (3.10)$$

Therefore, the system should be pipelined at 3 level. Substitute $M = 3$ into (3.9) and solve for $\beta = 0.427$. The supply voltage for pipelined system is $\beta V_0 = 2.14$ Volts. ■

Exercise 12. Since pipelining level $M=4$ and block size $L=4$, we have

$$16(\beta V_0 - V_t)^2 = \beta(V_0 - V_t)^2 \quad (3.15)$$

Substitute $V_0=5$ Volts and $V_t=0.4$ Volts in to (3.15), we have

$$\beta^2 - 0.2129\beta + 0.0064 = 0. \quad (3.16)$$

Solving for β , we get

$$\beta = 0.176675, \text{ or } \beta = 0.03622. \quad (3.17)$$

$\beta = 0.03622$ is disgarded since $0.03622V_0 = 0.181$ Volts, which is less than the threshold voltage. Therefore, the supply voltage for the parallel pipelined system is $\beta V_0 = 0.883$ Volts. The power ratio is

$$Ratio = \beta^2 = 3.12\%. \blacksquare \quad (3.18)$$