

Chapter 3


Arithmetic Circuits

Instructor: Prof. Peter Lian
Department of Electrical
Engineering & Computer Science
Lassonde School of Engineering
York University

Adders


Ripple-Carry Adder
Carry-Bypass Adder
Carry-Select Adder
Carry-Lookahead Adder

Full-Adder

 

A	B	C_i	S	C_o	<i>Carry status</i>
0	0	0	0	0	delete
0	0	1	1	0	delete
0	1	0	1	0	propagate
0	1	1	0	1	propagate
1	0	0	1	0	propagate
1	0	1	0	1	propagate
1	1	0	0	1	generate
1	1	1	1	1	generate

The Binary Adder

 

$$\begin{aligned}
 S &= A \oplus B \oplus C_i \\
 &= A\bar{B}\bar{C}_i + \bar{A}B\bar{C}_i + \bar{A}\bar{B}C_i + ABC_i \\
 C_o &= AB + BC_i + AC_i
 \end{aligned}$$

Generate, Propagate, and Delete

Define 3 new variable which ONLY depend on A, B

$$\text{Generate (G)} = AB$$

$$\text{Propagate (P)} = A \oplus B$$

$$\text{Delete} = A B$$

$$C_o(G, P) = G + PC_i$$


$$S(G, P) = P \oplus C_i$$

Can also derive expressions for S and C_o based on D and P

Note that we will be sometimes using an alternate definition for

$$\text{Propagate (P)} = A + B$$

The Ripple-Carry Adder

 


Worst case delay linear with the number of bits

$$t_d = O(N)$$


$$t_{adder} = (N-1)t_{carry} + t_{sum}$$

Goal: Make the fastest possible carry path circuit

Complimentary Static CMOS Full Adder

 


Inversion Property

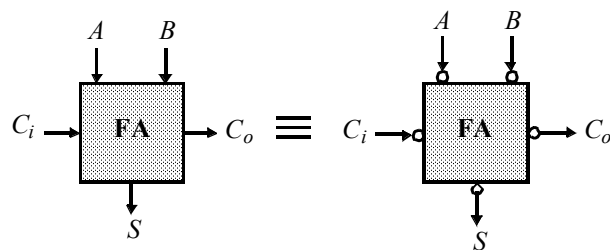

$$\bar{S}(A, B, C_i) = S(\bar{A}, \bar{B}, \bar{C}_i)$$


$$\bar{C}_o(A, B, C_i) = C_o(\bar{A}, \bar{B}, \bar{C}_i)$$

 Minimize Critical Path by Reducing Inverting Stages



Exploit Inversion Property

A Better Structure: The Mirror Adder

 


24 transistors


Notes on the Mirror Adder

- The NMOS and PMOS chains are **completely symmetrical**. A maximum of two series transistors can be observed in the carry-generation circuitry.
- When laying out the cell, the most critical issue is the minimization of the capacitance at node C_o . The reduction of the diffusion capacitances is particularly important.
- The capacitance at node C_o is composed of four diffusion capacitances, two internal gate capacitances, and six gate capacitances in the connecting adder cell.
- The transistors connected to C_i are placed closest to the output.
- Only the transistors in the carry stage have to be optimized for optimal speed.

Full Adder Implementation

 


Transmission Gate Full Adder

 


Manchester Carry Chain

Static

 


Dynamic

 


Manchester Carry Chain

 - Implement P with pass-transistors
- Implement G with pull-up, delete with pull-down
- Use dynamic logic to reduce the complexity and speed up




Carry-Bypass Adder

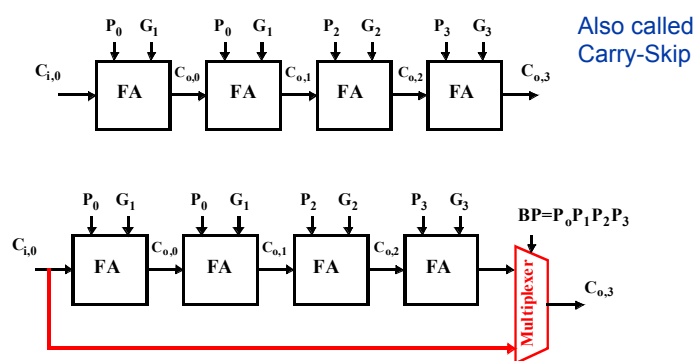


Idea: If (P_0 and P_1 and P_2 and $P_3 = 1$)
then $C_{o3} = C_0$, else “kill” or “generate”.

Carry-Bypass Adder

 


$$t_{adder} = t_{setup} + M t_{carry} + (N/M - 1) t_{bypass} + (M - 1) t_{carry} + t_{sum}$$

Carry-Bypass Adder

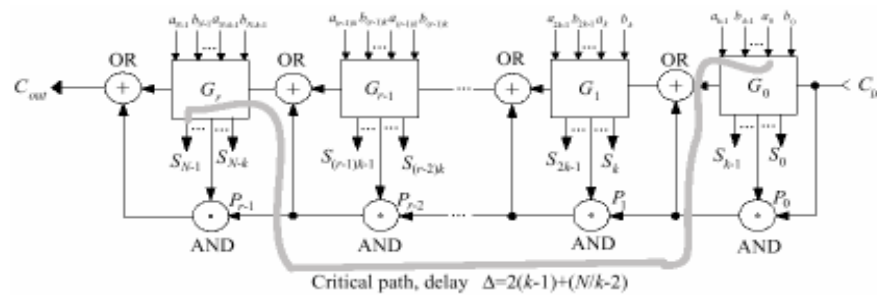


Carry Ripple vs. Carry-Bypass

 

Carry-Bypass Adder

Variable Group Length

 


$$x_1 = x_4 = 4, \quad x_2 = x_7 = 7, \quad x_3 = x_6 = 10, \quad x_5 = x_8 = 11.$$


$$t_d = c_1 + \sqrt{c_2 N + c_3}$$

Oklobdzija, Barnes, Arith'85


Carry-Bypass Adder

 


Carry-Select Adder

 

CSA: Critical Path

 


Linear Carry Select

 


$$t_{add} = t_{setup} + \left(\frac{N}{M}\right)t_{carry} + Mt_{mux} + t_{sum}$$

Square Root Carry Select

 

$$t_{add} = t_{setup} + P \cdot t_{carry} + (\sqrt{2N})t_{mux} + t_{sum}$$


Adder Delays - Comparison

 

Carry-Lookahead Adders

- Carry-Lookahead Adder – CLA
- Adder trees
 - Radix of a tree
 - Minimum depth trees
 - Sparse trees
- Logic manipulation
 - Conventional vs. Ling
 - Stack height limiting

LookAhead - Basic Idea

 

$$C_{\alpha, k} = f(A_k, B_k, C_{\alpha, k-1}) = G_k + P_k C_{\alpha, k-1}$$

Generate and Propagate

Define 3 new variable which ONLY depend on A, B

$$\text{Generate (G)} = AB$$

$$\text{Propagate (P)} = A \oplus B$$

$$\text{Delete} = A B$$

$$C_o(G, P) = G + PC_i$$

$$S(G, P) = P \oplus C_i$$

Can also derive expressions for S and C_o based on D and P

Note that we will be sometimes using an alternate definition for

$$\text{Propagate (P)} = A + B$$

Lookahead Adder

Lookahead Equations

Position i : $c_i = g_i + p_i c_{i-1}$

Position $i+1$: $c_{i+1} = g_{i+1} + p_{i+1} c_i$

$$= g_{i+1} + p_{i+1} (g_i + p_i c_{i-1})$$

$$= g_{i+1} + p_{i+1} g_i + p_{i+1} p_i c_{i-1}$$

Carry exists if:

- Generated in stage $i+1$
- Generated in stage i and propagated through $i+1$
- Propagated through both i and $i+1$

Block Lookahead

- Example for 4th bit carry:

$$c_{i+4} = g_{i+3} + p_{i+3}g_{i+2} + p_{i+3}p_{i+2}g_{i+1} + p_{i+3}p_{i+2}p_{i+1}g_i \\ + p_{i+3}p_{i+2}p_{i+1}p_i c_{i-1}$$

- Block generate and block propagate:

$$G_{i,i+3} = g_{i+3} + p_{i+3}g_{i+2} + p_{i+3}p_{i+2}g_{i+1} + p_{i+3}p_{i+2}p_{i+1}g_i$$

$$P_{i,i+3} = p_{i+3}p_{i+2}p_{i+1}p_i$$

$$c_{i+4} = G_{i,i+3} + P_{i,i+3}c_{i-1}$$

Look-Ahead: Topology


Expanding Lookahead equations:

$$C_{o,k} = G_k + P_k(G_{k-1} + P_{k-1}C_{o,k-2})$$


All the way:

$$C_{o,k} = G_k + P_k(G_{k-1} + P_{k-1}(\dots + P_1(G_0 + P_0C_{i,0})))$$

Mirror implementation

 

Logarithmic Look-Ahead Adder

 

Carry Lookahead Trees

$$\begin{aligned}
 C_{0,0} &= G_0 + P_0 C_{i,0} \\
 C_{0,1} &= G_1 + P_1 G_0 + P_1 P_0 C_{i,0} \\
 C_{0,2} &= G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_{i,0} \\
 &= (G_2 + P_2 G_1) + (P_2 P_1)(G_0 + P_0 C_{i,0}) = G_{2:1} + P_{2:1} C_{0,0}
 \end{aligned}$$

Can continue building the tree hierarchically.

Tree Adders

$$P_G = p_m \cdot p_l \quad m: \text{more significant bit}$$


$$G_G = g_m + p_m \cdot g_l \quad l: \text{less significant bit}$$

- Start from the input P, G and continue up the tree.

$$\begin{aligned} (g, p) &= (g_m, p_m) \bullet (g_l, p_l) \\ &= (g_m + p_m \cdot g_l, p_m \cdot p_l) \end{aligned}$$


- Kogge, Stone, Trans on Comp. 1973

Tree Adders: Radix 2

 


16-bit radix-2 Kogge-Stone tree

Tree Adders: Radix 4

 


16-bit radix-4 Kogge-Stone Tree

Tree Adders: Sparse Trees

 


16-bit radix-2 sparse tree with sparseness of 2

Tree Adders: Brent-Kung Tree

 


Brent-Kung Tree

Tree Adders: Ladner-Fischer

 

Full versus Sparse Trees

 - Sparse trees have less transistors, wires – less power
- Less input loading
- Recovering missing carries – ripple or precompute
 - Complex precomputer can get into the critical path



Ling Adder

- Variation of CLA

Conventional

Ling's equations

$$p_i = a_i \oplus b_i$$

$$t_i = a_i + b_i$$

$$g_i = a_i \cdot b_i$$

$$g_i = a_i \cdot b_i$$

$$G_i = g_i + p_i \cdot G_{i-1}$$

$$H_i = g_i + t_{i-1} \cdot H_{i-1}$$

$$S_i = p_i \oplus G_{i-1}$$

$$S_i = t_i \oplus H_i + g_i t_{i-1} H_{i-1}$$

Ling, IBM J. Res. Dev., 5, 1981

Ling Adder

- Conventional radix-4


$$G_3 = g_3 + t_3 g_2 + t_3 t_2 g_1 + t_3 t_2 t_1 g_0$$

- Ling radix-4

$$\begin{aligned} H_3 &= g_3 + t_2 g_2 + t_2 t_1 g_1 + t_2 t_1 t_0 g_0 \\ &= g_3 + g_2 + t_2 g_1 + t_2 t_1 g_0 \end{aligned}$$

- Reduces the stack height (or width)
- Reduces input loading

Ling versus CLA

 


R. Zlatanovici and B. Nikolic, ESSCIRC 2003

Stack Height Limiting


$$G4_i = G_i + P_i \cdot G_{i+1} + P_i \cdot P_{i+1} \cdot G_{i+2} + P_i \cdot P_{i+1} \cdot P_{i+2} \cdot G_{i+3}$$
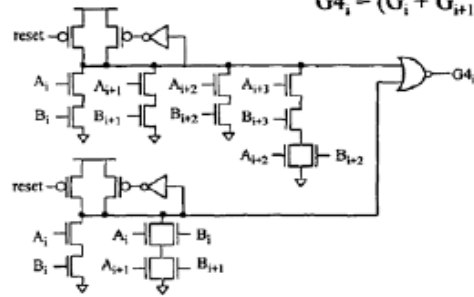
$$G4_i = (G_i + G_{i+1} + G_{i+2} + P_{i+2} \cdot G_{i+3}) \cdot (G_i + P_i \cdot P_{i+1})$$




Park, VLSI Circ'00

Example: Domino Adder

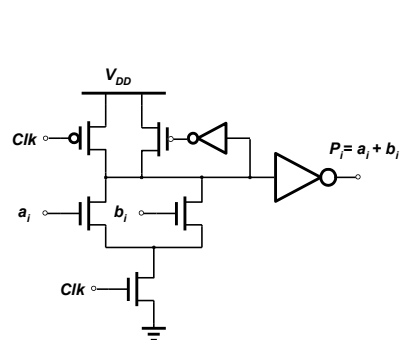


Propagate

 


Generate

Example: Domino Adder

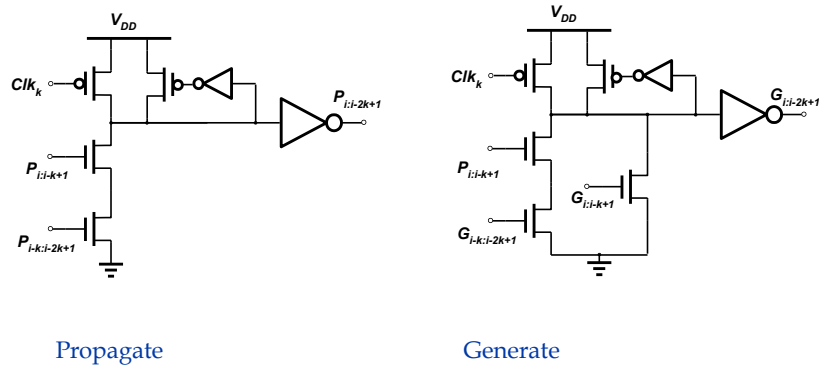

Example: Domino Sum

 

Multipliers

The Binary Multiplication

$$\begin{aligned}Z &= \vec{X} \times Y = \sum_{k=0}^{M+N-1} Z_k 2^k \\&= \left(\sum_{i=0}^{M-1} X_i 2^i \right) \left(\sum_{j=0}^{N-1} Y_j 2^j \right) \\&= \sum_{i=0}^{M-1} \left(\sum_{j=0}^{N-1} X_i Y_j 2^{i+j} \right)\end{aligned}$$

with

$$\begin{aligned}X &= \sum_{i=0}^{M-1} X_i 2^i \\Y &= \sum_{j=0}^{N-1} Y_j 2^j\end{aligned}$$

The Binary Multiplication


				1	0	1	0	1	0			Multiplicand: N bits
x						1	0	1	1			Multiplier: M bits
				1	0	1	0	1	0			
			1	0	1	0	1	0				
		0	0	0	0	0	0					
+		1	0	1	0	1	0					
		1	1	1	0	0	1	1	1	0		Result: N+M bits

AND operation
 Partial products


Shift-and-Add Multiplier

- Standard adder and shift-in the multiplicand
- Shift the result as well and add
- N cycles
- Parallel adders and more hardware (adders) instead.

The Array Multiplier

 


The MxN Array Multiplier— Critical Path

 

$$t_{mult} \sim [(M-1) + (N-2)]t_{carry} + (N-1)t_{sum} + (N-1)t_{and}$$


Carry-Save Multiplier

 

Vector Merging Adder

$$t_{mult} = (N-1)t_{carry} + (N-1)t_{and} + t_{merge}$$


Multiplier Floorplan

 


Multipliers

- Partial product generation
- Partial product accumulation
- Final summation


Wallace-Tree Multiplier

 

Wallace-Tree Multiplier

 

Wallace-Tree Multiplier

 

Multipliers —Summary

- Optimization Goals Different Vs Binary Adder
- Once Again: Identify Critical Path
- Other possible techniques
 - Logarithmic versus Linear (Wallace Tree Mult)
 - Data encoding (Booth)
 - Pipelining

FIRST GLIMPSE AT SYSTEM LEVEL OPTIMIZATION

Acknowledgement

- The materials are adopted from “Digital Integrated Circuits: A Design Perspective” by Jan M. Rabaey, Anantha Chandrakasan, and Borivoje Nikolic, 2nd Edition, 2003, Pearson.