

Chapter 7


Retiming

Instructor: Prof. Peter Lian
Department of Electrical
Engineering & Computer Science
Lassonde School of Engineering
York University

Introduction

- Retiming is a transformation technique that is used to change the locations of delay elements in a circuit without changing its functionality.
- Could be considered as a generalization of the pipelining technique studies in Chapter 6
 - Pipelining is equivalent to introduce many delays at the input followed by retiming
- Applications
 - Reduce the number of registers in the circuit
 - Reduce the critical path of the system
 - Reduce the power consumption of the circuit
 - Logic synthesis

IIR Filter Example

 

Retiming


- Mapping G to G_r (retimed)
- U and V are nodes, e is an edge
- $r(U)$ is a retiming value
- $w(e)$ is the weight of edge e from node $U \rightarrow V$ in graph G
- $w_r(e)$ is the weight of edge e in from node $U \rightarrow V$ in retimed graph G_r

$$w_r(e) = w(e) + r(V) - r(U)$$
- A solution is feasible if all $w_r(e) \geq 0$

Retiming Value $r(U)$


- Movement of register from input to output or vice versa does not affect the functionality
- Retiming value of node U

Retime by -1 , $r(u)=-1$

 


Retime by 1 , $r(u)=1$

- Example


 


Feasible Solution

- A solution is feasible if all $w_r(e) \geq 0$
- $w_r(e) = w(e) + r(V) - r(U)$ for edge $e = (U, V)$
 - If $r(U) < 0$, $r(V) > 0$, $w_r(e) > 0$
 - If $r(U) > 0$, $r(V) < 0$, $w_r(e) > 0$ if $|r(U) + r(V)| < w(e)$
 - If $r(U) > 0$, $r(V) > 0$, $w_r(e) > 0$ if $r(V) > r(U)$
 - If $r(U) < 0$, $r(V) < 0$, $w_r(e) > 0$ if $|r(U)| > |r(V)|$

 

IIR Filter Example

  

$$r(1) = r(3) = r(4) = 0 \quad r(2) = 1$$

$$w_r(3 \xrightarrow{e} 2) = w(3 \xrightarrow{e} 2) + r(2) - r(3) = 0 + 1 - 0 = 1$$

$$w_r(4 \xrightarrow{e} 2) = w(4 \xrightarrow{e} 2) + r(2) - r(4) = 0 + 1 - 0 = 1$$

Property I

- The weight of a retimed Path is given by:

$$w_r(p) = w(p) + r(k) - r(0)$$

$$p = V_0 \xrightarrow{e_0} V_1 \xrightarrow{e_1} V_2 \cdots V_{k-1} \xrightarrow{e_{k-1}} V_k$$

$$w_r(p) = w_r(e_0) + w_r(e_1) + \cdots + w_r(e_{k-1})$$

$$w_r(p) = w(e_0) + r(1) - r(0) + w(e_1) + r(2) - r(1) + \cdots + w(e_{k-1}) + r(k) - r(k-1)$$

$$w_r(p) = w(e_0) + w(e_1) + \cdots + w(e_{k-1}) + r(k) - r(0)$$

$$w_r(p) = w(p) + r(k) - r(0)$$

Properties II to IV

- Property II: Retiming does not change the number of delays in a cycle
 - This is a special case of Property I, where $V_k = V_0$
- Property III: Retiming does not alter the iteration bound in a DFG
- Property IV: Adding a constant j to the retiming value of each node does not change the mapping from G to G_r

Retiming Techniques


Cutset Retiming

- **Cutset:** A set of edges if removed, the graph G is partitioned into 2 graphs G_1, G_2 .
- Cutset retiming is done by adding k delays to all the edges in the cutset from G_1 to G_2 , and removing k delays from the edges from G_2 to G_1

$$- \min_{G_1 \xrightarrow{e} G_2} \{w(e)\} \leq k \leq \min_{G_2 \xrightarrow{e} G_1} \{w(e)\}$$


Example 1

$$y(n) = ay(n-2) + by(n-3) + x(n)$$

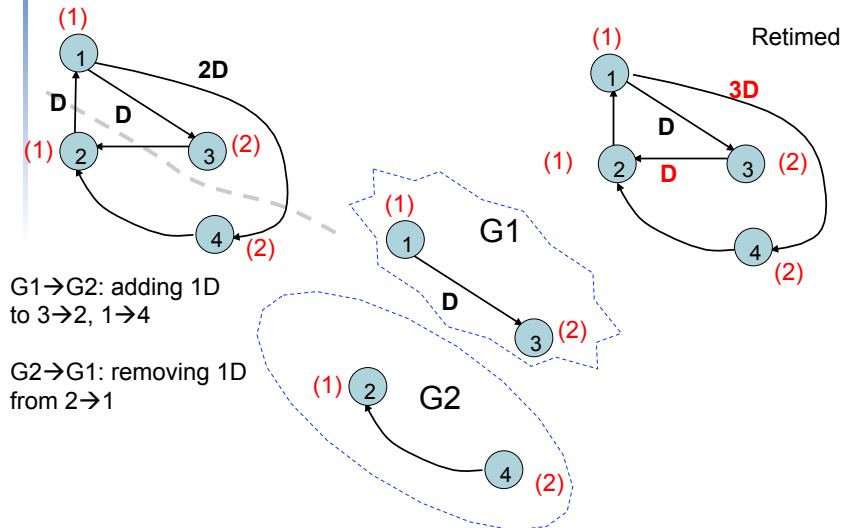


Example 2

$$y(n) = ay(n-2) + by(n-3) + x(n)$$

 

Cutset Retiming: Pipelining

 
- Pipelining is a special case where there are no nodes from G_2 to G_1 (no loops).



K-Slow Transformation

- Replace each delay with N delays

Example:

 


Clock	
0	$A0 \rightarrow B0$
1	$A1 \rightarrow B1$
2	$A2 \rightarrow B2$

$$T_{\text{clk}} = 2ut$$

$$T_{\text{iter}} = 2ut$$

After 2-slow transformation

 


Clock	
0	$A0 \rightarrow B0$
1	
2	$A2 \rightarrow B2$
3	
4	$A4 \rightarrow B4$

$$T_{\text{clk}} = 2ut$$

$$T_{\text{iter}} = 2 \cdot 2ut = 4ut$$

K-Slow Transformation

 - K-slow transformation
 - Input new samples every alternative cycles
 - Null operations account for odd clock cycles.
 - Hardware utilized only 50% time
- Combining K-slow with retiming
 - Hardware utilization = 50%
 - Hardware can be fully utilized if two independent operations are available.




$$T_{\text{clk}} = 1 \text{ ut}$$


$$T_{\text{iter}} = 2 * 1 \text{ ut} = 2 \text{ ut}$$

2-Slow Lattice Filter

- A 100-stage Lattice filter

 


What is the critical path?

 

2-Slow Lattice Filter

- Retimed version

 

Critical path=2 multiplier + 2 adder

If $T_{mul}=2\text{ ut}$, $T_{add}=1\text{ ut}$, then $T_{clk}=6\text{ ut}$, $T_{iter}=2*6=12\text{ ut}$

In original filter, $T_{iter}=105$

Feasible Retiming Solution

- A solution is feasible if all $w_r(e) \geq 0$, i.e.
 $w_r(e) = w(e) + r(V) - r(U) \geq 0$
 $\rightarrow r(U) - r(V) \leq w(e)$ for all edges

Example:

$$r_1 - r_2 \leq 0$$

$$r_3 - r_1 \leq 5$$

$$r_4 - r_1 \leq 4$$

$$r_4 - r_3 \leq -1$$

$$r_3 - r_2 \leq 2$$

Solving Systems of Inequalities

- Draw a constraints graph
 - Draw the node i for each of the N variables $1, 2, \dots, N$
 - Draw the node $N+1$
 - For each inequality $r_i - r_j \leq k$, draw an edge from node $j \rightarrow i$ with weight k
 - For each node $i=1, 2, \dots, N$ draw an edge $N+1 \rightarrow i$ with weight 0
- Solve
 - The system has a solution if the constraints graph has no negative cycle. [Bellman Ford Algorithm](#)
 - One solution is the minimum length from node $N+1$ to i

Activity 1

- Given the following inequalities, draw the constraint graph.

$$r_1 - r_2 \leq 0$$

$$r_3 - r_1 \leq 5$$

$$r_4 - r_1 \leq 4$$

$$r_4 - r_3 \leq -1$$

$$r_3 - r_2 \leq 2$$

Retiming for Clock Period Minimization

Retiming for Clock Period Minimization

- The minimum clock time is the computation time of the critical path.
- Critical path is the path with the longest computation time and **no delay**.
- Retiming could be used to minimize clock period.

Minimize Clock Period

- Minimum feasible clock period of a graph G is $\Phi(G) = \max \{t(p) : w(p) = 0\}$
- $W(U, V)$ is the minimum number of registers on any path from $U \rightarrow V$
- $D(U, V)$ is the maximum computation time among all paths from $U \rightarrow V$ with weight $W(U, V)$

Steps in Minimize Clock Period

1. Let $M = t_{max}n$, where t_{max} is the maximum computation time of any node in G , n = number of nodes in G
2. Form a new graph G' which is the same as G except the edge weights are replaced by $w'(e) = Mw(e) - t(U)$ ($e = U \rightarrow V$), where $t(U)$ is computation time of node U .
3. Solve for all-pairs shortest path on G' (S_{UV})
4. If $U \neq V$, then $W(U, V) = \lceil S_{UV}/M \rceil$ and $D(U, V) = M \times W(U, V) - S_{UV} + t(V)$. $\lceil X \rceil$ denotes the smallest integer not less than X .
5. If $U = V$, $W(U, V) = 0$, $D(U, V) = t(U)$

Steps in Minimize Clock Period


6. Use $W(U, V)$, $D(U, V)$ to find if there a retiming solution such that $\Phi(G) \leq c$ (cycle time).
This is done by constructing the following set of constraints
 - **Feasibility constraints**
 $r(U) - r(V) \leq w(e)$ for every edge in G
 - **Critical path constraint**
 $r(U) - r(V) \leq W(U, V) - 1$ for all nodes U, V in G such that $D(U, V) > c$.
 - If there is a solution to the inequalities (constraints), then the solution is a feasible retiming solution that the circuit can be clocked with period c .

Example

Step 1: find M

$$n=4, t_{\max}=2$$

$$M=2 \times 4=8$$

 


$$y(n)=ay(n-2) + by(n-3) + x(n)$$

Step 2: form new graph G'

$$e = U \rightarrow V$$


$$w'(e)=M \times w(e)-t(U)$$

 

Example

Step 3: Solve all shortest path on G'

S_{UV}	1	2	3	4
1	12	5	7	15
2	7	12	14	22
3	5	-2	12	20
4	5	-2	12	20

 

Example

Steps 4 and 5:
Construct tables for
 $W(U,V)$ and $D(U,V)$

$U \neq V$, then $W(U,V) = \lceil SUV/M \rceil$

$U=V$, $W(U,V)=0$

$W(U,V)$	1	2	3	4
1	0	1	1	2
2	1	0	2	3
3	1	0	0	3
4	1	0	2	0

S_{UV}	1	2	3	4
1	12	5	7	15
2	7	12	14	22
3	5	-2	12	20
4	5	-2	12	20

$D(U,V) = M \times W(U,V) - S_{UV} + t(V)$
 $U=V \quad T(U)$

$D(U,V)$	1	2	3	4
1	1	4	3	3
2	2	1	4	4
3	4	3	2	6
4	4	3	6	2

Example

Step 6: Construct constraints, for $c=3$

- Feasibility constraints


$$r(1) - r(3) \leq 1$$

$$r(1) - r(4) \leq 2$$

$$r(2) - r(1) \leq 1$$

$$r(3) - r(2) \leq 0$$

$$r(4) - r(2) \leq 0$$

 

Example

Critical path constraints

$r(U) - r(V) \leq W(U, V) - 1$ for all
nodes U, V in G
such that $D(U, V) > 3$

$$r(1) - r(2) \leq 0$$

$$r(2) - r(3) \leq 1$$

$$r(2) - r(4) \leq 2$$

$$r(3) - r(1) \leq 0$$

$$r(3) - r(4) \leq 2$$

$$r(4) - r(1) \leq 0$$

$$r(4) - r(3) \leq 1$$

D(U,V)	1	2	3	4
1	1	4	3	3
2	2	1	4	4
3	4	3	2	6
4	4	3	6	2

W(U,V)	1	2	3	4
1	0	1	1	2
2	1	0	2	3
3	1	0	0	3
4	1	0	2	0

Example

- Combine two sets of constraints, we have 12 inequalities.

- Note that there is no overlap between these two sets of constraints

Feasibility constraint

$$r(1) - r(3) \leq 1$$

$$r(1) - r(4) \leq 2$$

$$r(2) - r(1) \leq 1$$

$$r(3) - r(2) \leq 0$$

$$r(4) - r(2) \leq 0$$

Critical path constraint

$$r(1) - r(2) \leq 0$$

$$r(2) - r(3) \leq 1$$

$$r(2) - r(4) \leq 2$$

$$r(3) - r(1) \leq 0$$

$$r(3) - r(4) \leq 2$$


$$r(4) - r(1) \leq 0$$

$$r(4) - r(3) \leq 1$$

 Example


- Solve 12 inequalities
 - Construct constraint graph
 - Find weight matrix W of constraint graph, then solve using Bellman algorithm (Appendix A)

$$W = \begin{bmatrix} 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 1 & 1 & 0 & 1 \\ 2 & 2 & 2 & 0 \end{bmatrix}$$



 Example

- Solution from **Bellman-Ford algorithm**:
- $r(1)=r(2)=r(3)=r(4)=0$, no retiming needed. The graph already has a critical path =3



Redoing for c=2

Critical path constraints

$r(U)-r(V) \leq W(U,V)-1$ for all nodes U, V in G such that $D(U,V) > 2$

$r(1)-r(2) \leq 0$
 $r(2)-r(3) \leq 1$
 $r(2)-r(4) \leq 2$
 $r(3)-r(1) \leq 0$
 $r(3)-r(4) \leq 2$
 $r(4)-r(1) \leq 0$
 $r(4)-r(3) \leq 1$
 $r(1)-r(3) \leq 0$
 $r(1)-r(4) \leq 1$
 $r(3)-r(2) \leq -1$
 $r(4)-r(2) \leq -1$

D(U,V)	1	2	3	4
1	1	4	3	3
2	2	1	4	4
3	4	3	2	6
4	4	3	6	2

Feasibility constraint


$r(1)-r(3) \leq 1$
 $r(1)-r(4) \leq 2$
 $r(2)-r(1) \leq 1$
 $r(3)-r(2) \leq 0$
 $r(4)-r(2) \leq 0$

W(U,V)	1	2	3	4
1	0	1	1	2
2	1	0	2	3
3	1	0	0	3
4	1	0	2	0

For C=2

- Solve 12 inequalities
 - Construct constraint graph
 - Find weight matrix W of constraint graph, then solve using Bellman algorithm (Appendix A)

 $W = \begin{bmatrix} 0 & 1 & 0 & 0 \\ 0 & 0 & -1 & -1 \\ 0 & 0 & 0 & 1 \\ 1 & 2 & 2 & 0 \end{bmatrix}$



For $c=2$

- Bellman algorithm gives the following solution:

$$r(2)=0, r(1)=r(3)=r(4)=-1$$

