

## Chapter Roadmap

- How to design an ALU?
- MIPS datapath
- Pipelining
- Hazards
- Real stuff



Chapter 4 — The Processor — 2

## Introduction

§4.1 Introduction


- CPU performance factors
  - Instruction count
    - Determined by ISA and compiler
  - CPI and Cycle time
    - Determined by CPU hardware
- We will examine two MIPS implementations
  - A simplified version
  - A more realistic pipelined version
- Simple subset, shows most aspects
  - Memory reference: l w, sw
  - Arithmetic/logical: add, sub, and, or, slt
  - Control transfer: beq, j



Chapter 4 — The Processor — 3

## Design of a Simple ALU

- 2 inputs, operation and an output

 

Chapter 4 — The Processor — 4

## Possible Representations

Sign Mag.	Two's Comp.	One's Comp.
	$1000 = -8$	
$1111 = -7$	$1001 = -7$	$1000 = -7$
$1110 = -6$	$1010 = -6$	$1001 = -6$
$1101 = -5$	$1011 = -5$	$1010 = -5$
$1100 = -4$	$1100 = -4$	$1011 = -4$
$1011 = -3$	$1101 = -3$	$1100 = -3$
$1010 = -2$	$1110 = -2$	$1101 = -2$
$1001 = -1$	$1111 = -1$	$1110 = -1$
$1000 = -0$		$1111 = -0$
$0000 = +0$	$0000 = 0$	$0000 = +0$
$0001 = +1$	$0001 = +1$	$0001 = +1$
$0010 = +2$	$0010 = +2$	$0010 = +2$
$0011 = +3$	$0011 = +3$	$0011 = +3$
$0100 = +4$	$0100 = +4$	$0100 = +4$
$0101 = +5$	$0101 = +5$	$0101 = +5$
$0110 = +6$	$0110 = +6$	$0110 = +6$
$0111 = +7$	$0111 = +7$	$0111 = +7$

- Issues:
  - balance
  - number of zeros
  - ease of operations
- Which one is best?  
Why?

## MIPS Representations

- 32-bit signed numbers (2's complement):

```

0000 0000 0000 0000 0000 0000 0000 0000two = 0ten
0000 0000 0000 0000 0000 0000 0001two = + 1ten
0000 0000 0000 0000 0000 0000 0010two = + 2ten maxint
...
0111 1111 1111 1111 1111 1111 1111 1110two = + 2,147,483,646ten
0111 1111 1111 1111 1111 1111 1111 1111two = + 2,147,483,647ten
1000 0000 0000 0000 0000 0000 0000 0000two = - 2,147,483,648ten
1000 0000 0000 0000 0000 0000 0000 0001two = - 2,147,483,647ten
1000 0000 0000 0000 0000 0000 0000 0010two = - 2,147,483,646ten
...
1111 1111 1111 1111 1111 1111 1111 1101two = - 3ten
1111 1111 1111 1111 1111 1111 1111 1110two = - 2ten
1111 1111 1111 1111 1111 1111 1111 1111two = - 1ten minint

```

- What if the bit string represented addresses?  
need operations that also deal with only positive (unsigned) integers

## Two's Complement Operations

- Negating a two's complement number – complement all the bits and then add a 1
  - remember: “negate” and “invert” are quite different!
  - Starting from LSb, all 0's as is, first 1 as is, then invert
  
- Converting n-bit numbers into numbers with more than n bits:
  - MIPS 16-bit immediate gets converted to 32 bits for arithmetic
  - sign extend - copy the most significant bit (the sign bit) into the other bits
 

0010	->	0000 0010
1010	->	1111 1010
  - sign extension versus zero extend (1b vs. 1bu)



## Addition & Subtraction

- Just like in grade school (carry/borrow 1s)
 


0111	0111	0110
+ 0110	- 0110	- 0101
<u>1101</u>	<u>0001</u>	<u>0001</u>
  
- Two's complement operations are easy
  - do subtraction by negating and then adding
 

0111	->	0111
- 0110	->	+ 1010
<u>0001</u>		<u>1 0001</u>
  
- Overflow (result too large for **finite** computer word)
  - e.g., adding two n-bit numbers does not yield an n-bit number
 

0111
+ 0001
<u>1000</u>



## Building a 1-bit Binary Adder

 


A	B	carry_in	carry_out	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$\begin{aligned}
 S &= A \text{ xor } B \text{ xor } \text{carry\_in} \\
 \text{carry\_out} &= A \& B \mid A \& \text{carry\_in} \mid B \& \text{carry\_in} \\
 &\quad (\text{majority function})
 \end{aligned}$$

- ❑ How can we use it to build a 32-bit adder?
- ❑ How can we modify it easily to build an adder/subtractor?



## Building 32-bit Adder

 

❑ Just connect the carry-out of the least significant bit FA to the carry-in of the next least significant bit and connect . . .

- ❑ Ripple Carry Adder (RCA)
  - advantage: simple logic, so small (low cost)
  - disadvantage: slow and lots of glitching (so lots of energy consumption)




## A 32-bit Ripple Carry Adder/Subtractor

- Remember 2's complement is just
  - complement all the bits

control  
(0=add,1=sub) ——————  
B<sub>0</sub> if control = 0,  
!B<sub>0</sub> if control = 1

- add a 1 in the least significant bit
 
$$\begin{array}{r} A \quad 0111 \\ B \quad - 0110 \\ \hline \end{array} \rightarrow \begin{array}{r} 0111 \\ + \\ \hline \end{array}$$




## A 32-bit Ripple Carry Adder/Subtractor

- Remember 2's complement is just
  - complement all the bits

control  
(0=add,1=sub) ——————  
B<sub>0</sub> if control = 0,  
!B<sub>0</sub> if control = 1

- add a 1 in the least significant bit
 
$$\begin{array}{r} A \quad 0111 \\ B \quad - 0110 \\ \hline 0001 \end{array} \rightarrow \begin{array}{r} 0111 \\ + \\ 1 \\ \hline 1001 \end{array}$$




## Overflow Detection and Effects


- Overflow: the result is too large to represent in the number of bits allocated
- When adding operands with different signs, overflow cannot occur! Overflow occurs when
  - adding two positives yields a negative
  - or, adding two negatives gives a positive
  - or, subtract a negative from a positive gives a negative
  - or, subtract a positive from a negative gives a positive
- On overflow, an exception (interrupt) occurs
  - Control jumps to predefined address for exception
  - Interrupted address (address of instruction causing the overflow) is saved for possible resumption
- Don't always want to detect (interrupt on) overflow



 
## A Simple ALU Cell with Logic Op Support




## An Alternative ALU Cell

 


## An Alternative ALU Cell

 

## An Alternative ALU Cell

 


## An Alternative ALU Cell

 

## An Alternative ALU Cell

s0	s1	s2	x	y	z	w
0	0	0	0000	0000	0000	0000
0	0	1	0000	0100	0110	1000
0	1	0	0000	0110	0100	1001
0	1	1	0000	1100	1110	1110
1	0	0	0000	1001	1000	0100
1	0	1	0000	1100	1110	0110
1	1	0	0000	1110	1110	1110
1	1	1	0000	1110	1110	1110


carry\_in

 

## An Alternative ALU Cell

s0	s1	s2	x	y	z	w
0	0	0	0000	0000	0000	0000
0	0	1	0000	0000	0110	0100
0	1	0	0000	1000	1000	1000
0	1	1	0000	1001	1001	0110
1	0	0	0000	1100	1110	1110
1	0	1	0000	1100	1110	1110
1	1	0	0000	1110	1110	1110
1	1	1	0000	1110	1110	1110

carry\_in

 


### The Alternative ALU Cell's Control Codes

s2	s1	s0	c_in	result	function
0	0	0	0	A	transfer A
0	0	0	1	A + 1	increment A
0	0	1	0	A + B	add
0	0	1	1	A + B + 1	add with carry
0	1	0	0	A - B - 1	subt with borrow
0	1	0	1	A - B	subtract
0	1	1	0	A - 1	decrement A
0	1	1	1	A	transfer A
1	0	0	x	A or B	or
1	0	1	x	A xor B	xor
1	1	0	x	A and B	and
1	1	1	x	!A	complement A



### Modifying the ALU Cell for slt

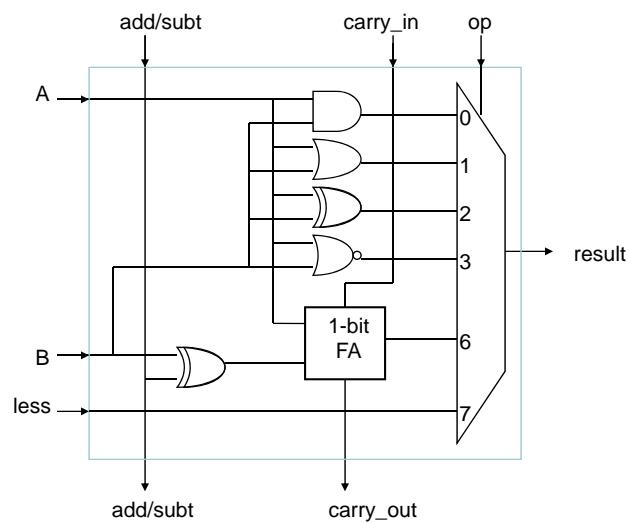


## Overflow Detection

- Overflow occurs when the result is too large to represent in the number of bits allocated
  - adding two positives yields a negative
  - or, adding two negatives gives a positive
  - or, subtract a negative from a positive gives a negative
  - or, subtract a positive from a negative gives a positive
- On your own: **Prove** you can detect overflow by:
  - Carry into MSB xor Carry out of MSB

$$\begin{array}{r}
 0 & 1 & 1 & 1 & 7 \\
 + & 0 & 0 & 1 & 1 \\
 \hline
 0 & 0 & 1 & 1 & 3
 \end{array}
 \quad
 \begin{array}{r}
 1 & 1 & 0 & 0 & -4 \\
 + & 1 & 0 & 1 & 1 \\
 \hline
 1 & 0 & 1 & 1 & -5
 \end{array}$$



### Modifying the ALU for Overflow

 


## Instruction Execution


- PC → instruction memory, fetch instruction
- All but jump, need to access data from a register and use the ALU.
- Depending on instruction class
  - Use ALU to calculate
    - Arithmetic result
    - Memory address for load/store
    - Branch target address    `beq $r1, $r2, LOC`
  - Access data memory for load/store
  - PC ← target address or PC + 4



## CPU Overview

 

## Multiplexers

 


- Can't just join wires together
- Use multiplexers



Chapter 4 — The Processor — 27

## Control

 

Chapter 4 — The Processor — 28

## Logic Design Basics

§4.2 Logic Design Conventions





- Information encoded in binary
  - Low voltage = 0, High voltage = 1
  - One wire per bit
  - Multi-bit data encoded on multi-wire buses
- Combinational element
  - Operate on data
  - Output is a function of input
- State (sequential) elements
  - Store information



Chapter 4 — The Processor — 29

## Combinational Elements



- AND-gate
  - $Y = A \& B$
- Multiplexer
  - $Y = S ? I_1 : I_0$
- Adder
  - $Y = A + B$
- Arithmetic/Logic Unit
  - $Y = F(A, B)$

    

Chapter 4 — The Processor — 30

## Sequential Elements



- Register: stores data in a circuit
  - Uses a clock signal to determine when to update the stored value
  - Edge-triggered: update when Clk changes from 0 to 1

  

Chapter 4 — The Processor — 31

## Sequential Elements


- Register with write control
  - Only updates on clock edge when write control input is 1
  - Used when stored value is required later

  

Chapter 4 — The Processor — 32

## Clocking Methodology

- Combinational logic transforms data during clock cycles
  - Between clock edges
  - Input from state elements, output to state element
  - Longest delay determines clock period

 

Chapter 4 — The Processor — 33

## Building a Datapath


- Datapath
  - Elements that process data and addresses in the CPU
    - Registers, ALUs, mux's, memories, ...
- We will build a MIPS datapath incrementally
  - Refining the overview design

§4.3 Building a Datapath



Chapter 4 — The Processor — 34


## Instruction Fetch

 

Chapter 4 — The Processor — 35

## R-Format Instructions


- Read two register operands
- Perform arithmetic/logical operation
- Write register result    `add $t1, $t2, $t3`

 

Chapter 4 — The Processor — 36

## Load/Store Instructions

- Read register operands
- Calculate address using 16-bit offset
  - Use ALU, but sign-extend offset
- Load: Read memory and update register
- Store: Write register value to memory

 

Chapter 4 — The Processor — 37




## Branch Instructions

- Read register operands
- Compare operands
  - Use ALU, subtract and check Zero output
- Calculate target address
  - Sign-extend displacement
  - Shift left 2 places (word displacement)
  - Add to PC + 4
    - Already calculated by instruction fetch



Chapter 4 — The Processor — 38

## Branch Instructions

 

Chapter 4 — The Processor — 39


## Composing the Elements

- First-cut data path does an instruction in one clock cycle
  - Each datapath element can only do one function at a time
  - Hence, we need separate instruction and data memories
- Use multiplexers where alternate data sources are used for different instructions




Chapter 4 — The Processor — 40

## R-Type/Load/Store Datapath

 

Chapter 4 — The Processor — 41

## Full Datapath

 

Chapter 4 — The Processor — 42

## ALU Control

- ALU used for
  - Load/Store: F = add
  - Branch: F = subtract
  - R-type: F depends on funct field

ALU control	Function
0000	AND
0001	OR
0010	add
0110	subtract
0111	set-on-less-than
1100	NOR

