P 3.3 [a] The 5 k Ω and 7 k Ω resistors are in series. The simplified circuit is shown below:



[b] The 800Ω and 1200Ω resistors are in series, as are the 300Ω and 200Ω resistors. The simplified circuit is shown below:



[c] The 35Ω , 15Ω , and 25Ω resistors are in series. as are the 10Ω and 40Ω resistors. The simplified circuit is shown below:



[d] The 50 Ω and 90 Ω resistors are in series, as are the 80 Ω and 70 Ω resistors. The simplified circuit is shown below:



P 3.4 [a] The 36 Ω and 18 Ω resistors are in parallel. The simplified circuit is shown below:



[b] The 200Ω and 120Ω resistors are in parallel, as are the 210Ω and 280Ω resistors. The simplified circuit is shown below:



[c] The 100 k Ω , 150 k Ω , and 60 k Ω resistors are in parallel, as are the 75 k Ω and 50 k Ω resistors. The simplified circuit is shown below:



[d] The 750Ω and 500Ω resistors are in parallel, as are the 1.5 k Ω and 3 k Ω resistors. The simplified circuit is shown below:



P 3.7 [a] Circuit in Fig. P3.7(a):

$$R_{eq} = ([(15||60) + (30||45) + 20]||50) + 25 + 10 = [(12 + 18 + 20)||50] + 25 + 10$$
$$= (50||50) + 25 + 10 = 25 + 25 + 10 = 60 \Omega$$

Circuit in Fig. P3.7(b) – begin by simplifying the 75Ω resistor and all resistors to its right:

 $[(18+12)\|60+30]\|75 = (30\|60+30)\|75 = (20+30)\|75 = 50\|75 = 30\,\Omega$

Now simplify the remainder of the circuit:

$$R_{eq} = ([(30+20)||50] + (20||60))||40 = [(50||50) + 15]||40 = (25+15)||40$$
$$= 40||40 = 20 \Omega$$

Circuit in Fig. P3.7(c) – begin by simplifying the left and right sides of the circuit:

$$R_{\text{left}} = [(1800 + 1200) \| 2000] + 300 = (3000 \| 2000) + 300 = 1200 + 300 = 1500 \Omega$$
$$R_{\text{right}} = [(500 + 2500) \| 1000] + 750 = (3000 \| 1000) + 750 = 750 + 750 = 1500 \Omega$$

Now find the equivalent resistance seen by the source:

$$R_{\rm eq} = (R_{\rm left} || R_{\rm right}) + 250 + 3000 = (1500 || 1500) + 250 + 3000$$
$$= 750 + 250 + 3000 = 4000 = 4 \ \mathrm{k}\Omega$$

Circuit in Fig. P3.7(d):

$$R_{\rm eq} = ([(750 + 250) || 1000] + 100) || ([(150 + 600) || 500] + 300)$$
$$= [(1000 || 1000) + 100] || [(750 || 500) + 300] = (500 + 100) || (300 + 300)$$
$$= 600 || 600 = 300 \,\Omega$$

[b] Note that in every case, the power delivered by the source must equal the power absorbed by the equivalent resistance in the circuit. For the circuit in Fig. P3.7(a):

$$P = \frac{V_s^2}{R_{\rm eq}} = \frac{30^2}{60} = 15 \ {\rm W}$$

For the circuit in Fig. P3.7(b):

$$P = I_s^2(R_{eq}) = (0.08)^2(20) = 0.128 = 128 \text{ mW}$$

For the circuit in Fig. P3.7(c):

$$P = \frac{V_s^2}{R_{\rm eq}} = \frac{20^2}{4000} = 0.1 = 100 \text{ mW}$$

For the circuit in Fig. P3.7(d):

$$P = I_s^2(R_{eq}) = (0.05)^2(300) = 0.75 = 750 \text{ mW}$$

P 3.12 [a]
$$v_o = \frac{160(3300)}{(4700 + 3300)} = 66 \text{ V}$$

[b] $i = 160/8000 = 20 \text{ mA}$
 $P_{R_1} = (400 \times 10^{-6})(4.7 \times 10^3) = 1.88 \text{ W}$
 $P_{R_2} = (400 \times 10^{-6})(3.3 \times 10^3) = 1.32 \text{ W}$

[c] Since R_1 and R_2 carry the same current and $R_1 > R_2$ to satisfy the voltage requirement, first pick R_1 to meet the 0.5 W specification

$$i_{R_1} = \frac{160 - 66}{R_1}, \quad \text{Therefore, } \left(\frac{94}{R_1}\right)^2 R_1 \le 0.5$$

Thus, $R_1 \ge \frac{94^2}{0.5}$ or $R_1 \ge 17,672 \,\Omega$

Now use the voltage specification:

$$\frac{R_2}{R_2 + 17,672}(160) = 66$$

Thus,
$$R_2 = 12,408 \,\Omega$$

P 3.13
$$4 = \frac{20R_2}{R_2 + 40}$$
 so $R_2 = 10 \Omega$
 $3 = \frac{20R_e}{40 + R_e}$ so $R_e = \frac{120}{17} \Omega$
Thus, $\frac{120}{17} = \frac{10R_L}{100 + R_e}$ so R_I

Thus,
$$\frac{120}{17} = \frac{10R_{\rm L}}{10 + R_{\rm L}}$$
 so $R_{\rm L} = 24\,\Omega$

P 3.16
$$R_{eq} = 10 \| [6+5\|(8+12)] = 10 \| (6+5\|20) = 10 \| (6+4) = 5 \Omega$$

$$v_{10A} = v_{10\Omega} = (10 \text{ A})(5 \Omega) = 50 \text{ V}$$

Using voltage division:

$$v_{5\Omega} = \frac{5 \| (8+12)}{6+5 \| (8+12)} (50) = \frac{4}{6+4} (50) = 20 \text{ V}$$

Thus, $p_{5\Omega} = \frac{v_{5\Omega}^2}{5} = \frac{20^2}{5} = 80 \text{ W}$

P 3.20 [a]



 $20 \text{ k}\Omega + 40 \text{ k}\Omega = 60 \text{ k}\Omega$

 $30 \ \mathbf{k}\Omega \| 60 \ \mathbf{k}\Omega = 20 \ \mathbf{k}\Omega$ $\frac{20,000}{(10,000+20,000)}(180) = 120 \text{ V}$ $v_{o1} =$

$$v_o = \frac{40,000}{60,000} (v_{o1}) = 80 \text{ V}$$

[b]



[c] It removes the loading effect of the second voltage divider on the first voltage divider. Observe that the open circuit voltage of the first divider is

$$v_{o1}' = \frac{30,000}{40,000}(180) = 135 \text{ V}$$

Now note this is the input voltage to the second voltage divider when the current-controlled voltage source is used.





Using voltage division,

$$v_{6k} = \frac{4000}{8000 + 4000} (18) = 6 \text{ V}$$

[b] $v_{5k} = \frac{5000}{5000 + 7000} (6) = 2.5 \text{ V}$

P 3.24 [a] The equivalent resistance of the 100Ω resistor and the resistors to its right is

 $100\|(80+70) = 100\|150 = 60\,\Omega$

Using current division,

$$i_{50} = \frac{(50 + 90 + 60) \|300}{50 + 90 + 60} (0.03) = \frac{120}{200} (0.03) = 0.018 = 18 \text{ mA}$$

[b] $v_{70} = \frac{(80 + 70) \|100}{80 + 70} (0.018) = \frac{60}{150} (0.018) = 0.0072 = 7.2 \text{ mA}$

P 3.28 [a]
$$v_{6k} = \frac{6}{6+2}(18) = 13.5 \text{ V}$$

 $v_{3k} = \frac{3}{3+9}(18) = 4.5 \text{ V}$
 $v_x = v_{6k} - v_{3k} = 13.5 - 4.5 = 9 \text{ V}$
[b] $v_{6k} = \frac{6}{8}(V_s) = 0.75V_s$
 $v_{3k} = \frac{3}{12}(V_s) = 0.25V_s$
 $v_x = (0.75V_s) - (0.25V_s) = 0.5V_s$

P 3.32 Use current division to find the current in the 8Ω resistor. Begin by finding the equivalent resistance of the 8Ω resistor and all resistors to its right:

$$R_{\rm eq} = ([(20||80) + 4]||30) + 8 = 20\,\Omega$$

$$i_8 = \frac{60 \|R_{eq}}{R_{eq}}(0.25) = \frac{60 \|20}{20}(0.25) = 0.1875 = 187.5 \text{ mA}$$

Use current division to find i_1 from i_8 :

$$i_1 = \frac{30 \| [4 + (80 \| 20)]}{30} (i_8) = \frac{30 \| 20}{30} (0.1875) = 0.075 = 75 \text{ mA}$$

Use current division to find $i_{4\Omega}$ from i_8 :

$$i_{4\Omega} = \frac{30\|[4 + (80\|20)]}{4 + (80\|20)}(i_8) = \frac{30\|20}{20}(0.1875) = 0.1125 = 112.5 \text{ mA}$$

Finally, use current division to find i_2 from $i_{4\Omega}$:

$$i_2 = \frac{80||20}{20}(i_{4\Omega}) = \frac{80||20}{20}(0.1125) = 0.09 = 90 \text{ mA}$$

P 3.58 [a] Use the figure below to transform the Y to an equivalent Δ :



$$R_{\rm c} = \frac{(25)(30) + (25)(50) + (30)(50)}{25} = \frac{3500}{25} = 140\,\Omega$$

Replace the Y with its equivalent Δ in the circuit to get the figure below:



Find the equivalent resistance to the right of the 13Ω and 7Ω resistors: $70 \| [(50 \| 116.67) + (20 \| 140)] = 30 \Omega$

Thus, the equivalent resistance seen from the terminals a-b is:

 $R_{\rm ab} = 13 + 30 + 7 = 50\,\Omega$

[b] Use the figure below to transform the Δ to an equivalent Y:





Find the equivalent resistance to the right of the 13Ω and 7Ω resistors: $(50 + 10) ||(25 + 15) + 6 = 30 \Omega$

Thus, the equivalent resistance seen from the terminals a-b is:

 $R_{\rm ab} = 13 + 30 + 7 = 50\,\Omega$

[c] Convert the delta connection $R_1 - R_2 - R_3$ to its equivalent wye. Convert the wye connection $R_1 - R_3 - R_4$ to its equivalent delta.





[c] Now that i_o and i_1 are known return to the original circuit



 $v_2 = (50)(0.048) + (600)(0.096) = 60 \text{ V}$

$$i_2 = \frac{v_2}{100} = \frac{60}{100} = 600 \text{ mA}$$

[d] $v_g = v_2 + 20(0.6 + 0.048) = 60 + 12.96 = 72.96$ V $p_g = -(v_g)(1) = -72.96$ W

Thus the current source delivers 72.96 W.

P 3.67 [a] After making the Y-to- Δ transformation, the circuit reduces to



Combining the parallel resistors reduces the circuit to



Now note: $0.75R + \frac{3RR_{\rm L}}{3R + R_{\rm L}} = \frac{2.25R^2 + 3.75RR_{\rm L}}{3R + R_{\rm L}}$

Therefore
$$R_{\rm ab} = \frac{3R\left(\frac{2.25R^2 + 3.75RR_{\rm L}}{3R + R_{\rm L}}\right)}{3R + \left(\frac{2.25R^2 + 3.75RR_{\rm L}}{3R + R_{\rm L}}\right)} = \frac{3R(3R + 5R_{\rm L})}{15R + 9R_{\rm L}}$$

If
$$R = R_{\rm L}$$
, we have $R_{\rm ab} = \frac{3R_{\rm L}(8R_{\rm L})}{24R_{\rm L}} = R_{\rm L}$

Therefore $R_{\rm ab} = R_{\rm L}$

[b] When $R = R_{\rm L}$, the circuit reduces to

