


EECS2200 Electric Circuits

Chapter 3


Activities

Activity 1

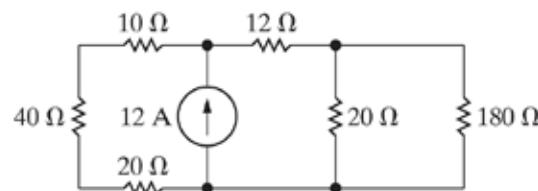- (1) Which of the resistors in the circuit below are connected in series?
- (2) Find the equivalent resistance of the series-connected resistors.




Solution

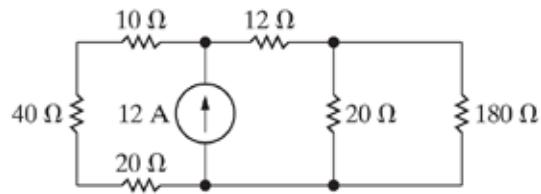


- (1) $10\ \Omega$ and $40\ \Omega$ and $20\ \Omega$.
- (2) $R_{eq} = 10\Omega + 40\Omega + 20\Omega = 70\Omega$

Activity 2

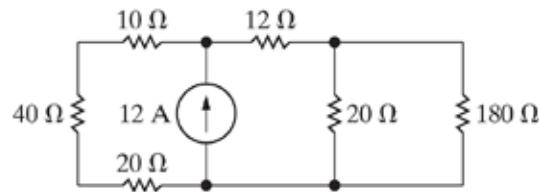- (1) Which of the resistors in the circuit below are connected in parallel?
- (2) Find the equivalent resistance of the parallel-connected resistors.



Solution

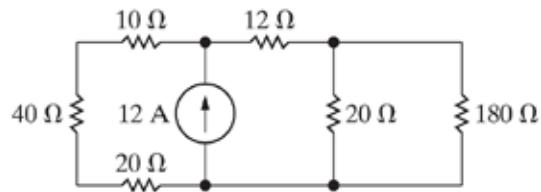


(1) $20\ \Omega$ and $180\ \Omega$.

$$(2) \frac{1}{R_{eq}} = \frac{1}{20} + \frac{1}{180} = \frac{10}{180} = \frac{1}{18} \Rightarrow R_{eq} = 18\Omega$$

Activity 3

Find i_s , i_1 , and i_2

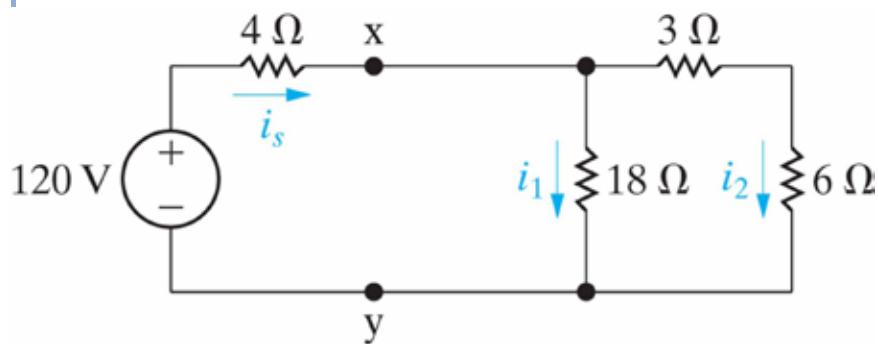

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall


Solution

1. 3Ω and 6Ω are in series, $R_{eq1}=9\Omega$.


2. R_{eq2} and 18Ω are in parallel,

$$\frac{1}{R_{eq2}} = \frac{1}{9} + \frac{1}{18} = \frac{3}{18} = \frac{1}{6}$$

$$\therefore R_{eq2} = 6\Omega$$

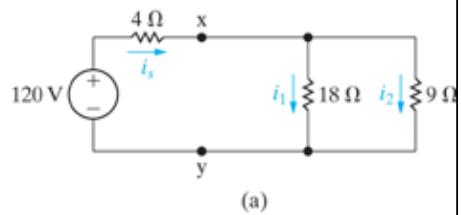

(a)

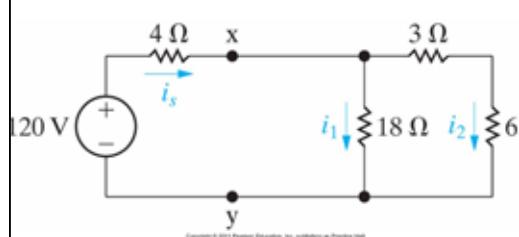

(b)

Copyright ©2015 Pearson Education, All Rights Reserved


Solution

3. $i_s = \frac{120V}{4\Omega + 6\Omega} = 12A$


$$v_{xy} = i_s 6\Omega = 12 * 6 = 72V$$

$$i_1 = \frac{72V}{18\Omega} = 4A$$

$$i_2 = \frac{72V}{9\Omega} = 8A$$

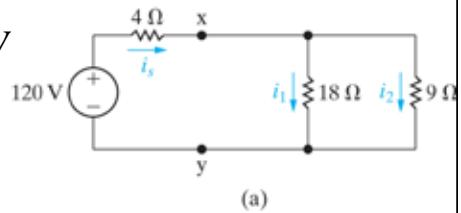

(a)

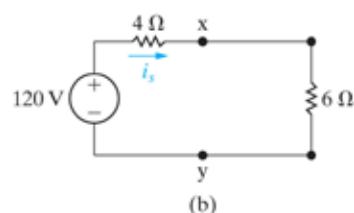


(b)

Copyright ©2015 Pearson Education, All Rights Reserved

Activity 4

Find v_o

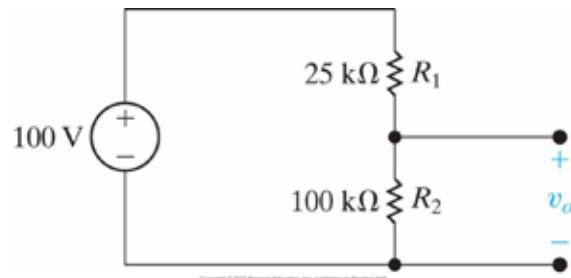- (1) if the load is 10Ω
- (2) If the load is $10 \text{ M } \Omega$




Solution

v_o without load

$$\because R_1 = 25\text{k}\Omega, R_2 = 100\text{k}\Omega, v_s = 100V$$

$$\therefore v_o = \frac{R_2}{R_1 + R_2} v_s = \frac{100k}{25k+100k} 100$$
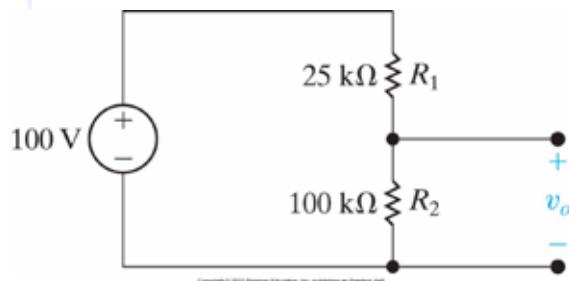
$$v_o = \frac{100k \times 100}{25k+100k} = \frac{10000}{125} = 80V$$




Solution

$$(1) \quad \because R_1 = 25k\Omega, R_2 = 100k\Omega, R_L = 10\Omega, v_s = 100V$$

$$\therefore v_o = \frac{R_2}{R_1(1+R_2/R_L)+R_2} v_s = \frac{100k}{25k(1+100k/10)+100k} 100$$
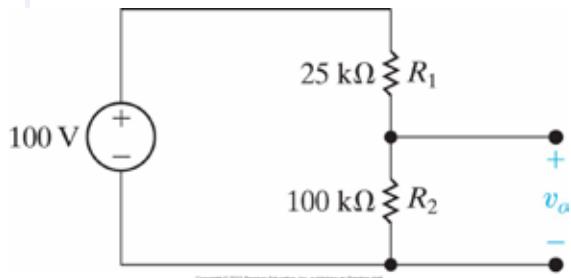
$$v_o = \frac{100k \times 100}{25k \times 10k + 100k} = \frac{10000}{350} = 28.57V$$




Solution

$$(2) \quad \because R_1 = 25k\Omega, R_2 = 100k\Omega, R_L = 10M\Omega, v_s = 100V$$


$$\therefore v_o = \frac{R_2}{R_1(1+R_2/R_L)+R_2} v_s = \frac{100k}{25k(1+100k/10M)+100k} 100$$

$$v_o = \frac{100k \times 100}{25k + 100k} = \frac{10000}{125} = 80V$$

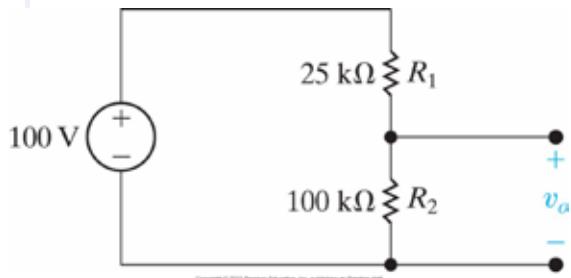

Activity 5

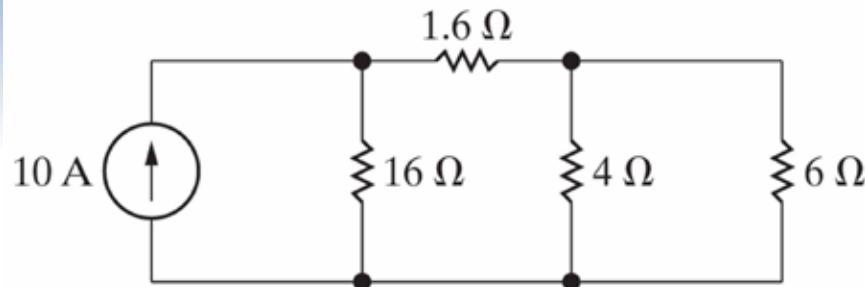Find the power dissipated in the $6\ \Omega$ resistor.





Solution

Find the power dissipated in the $6\ \Omega$ resistor.

$$R_{eq} = 4\Omega // 6\Omega = \frac{4 \times 6}{4 + 6} = 2.4\Omega, i_0 = \frac{16\Omega}{16\Omega + 4\Omega} 10A = 8A$$


$$i_6 = \frac{4\Omega}{4\Omega + 6\Omega} 8A = 3.2A$$

$$p_6 = i_6^2 R_6 = 3.2^2 \times 6 = 61.44W$$

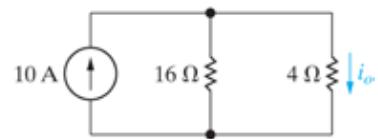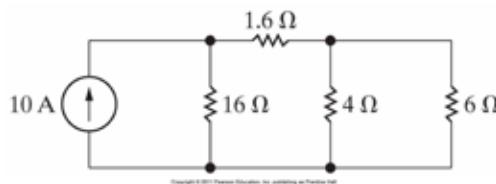

Activity 6

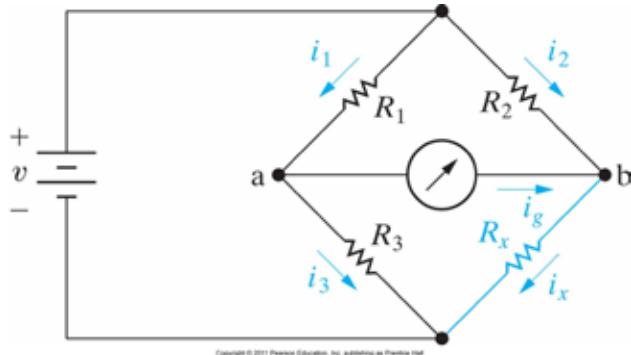Find R_x in a balanced Wheatstone bridge ($i_g = 0$).
Assume R_1 , R_2 , and R_3 are known.



Solution


$$\because i_g = 0 \Rightarrow v_{ab} = 0$$

$$KCL: i_1 = i_3, i_2 = i_x$$

$$KVL: i_3 R_3 = i_x R_x, i_1 R_1 = i_2 R_2$$


$$\Rightarrow i_1 R_3 = i_2 R_x = \frac{R_1}{R_2} i_1 R_x$$

$$\therefore R_x = \frac{R_2}{R_1} R_3$$

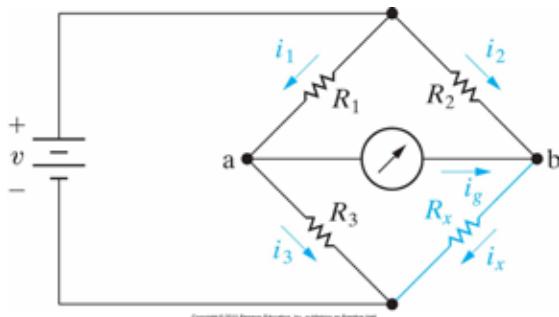

Activity 7

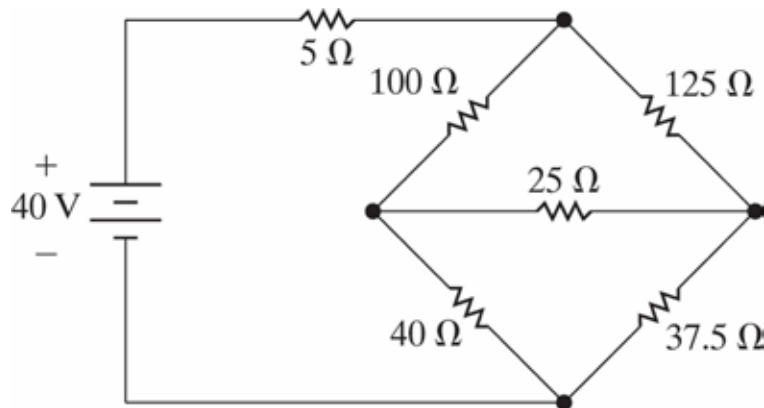Find the current and power supplied by the 40V source .



Solution



1. Replace upper Δ with a Y equivalent.

2. Find R_1 , R_2 , and R_3

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c} = \frac{100 \times 125}{250} = 50\Omega,$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c} = \frac{125 \times 25}{250} = 12.5\Omega,$$
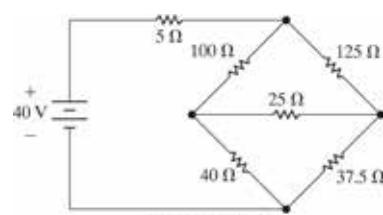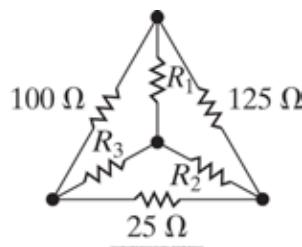
$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c} = \frac{100 \times 25}{250} = 10\Omega$$



Solution

3. Put Y into the circuit, and find the R_{eq}

$$\begin{aligned} R_{eq} &= 5\Omega + 50\Omega + (10\Omega + 40\Omega) // (12.5\Omega + 37.5\Omega) \\ &= 55\Omega + 50\Omega // 50\Omega = 55\Omega + 25\Omega = 80\Omega \end{aligned}$$

$$\therefore i = \frac{40V}{80\Omega} = 0.5A$$

$$p = vi = 40V \times 0.5A = 20W$$

