

EECS2200 Electric Circuits

Chapter 5 Part 1

Activities

Activity 1

Look at the capacitor equation:

$$i(t) = C \frac{dv(t)}{dt}$$

Suppose $v(t)$ is constant, what is the value of $i(t)$?

- A. 0
- B. ∞
- C. a constant


Activity 2

if the voltage drop across the capacitor is constant, its current is 0, so the capacitor can be replaced by:

- A. A short circuit
- B. An open circuit
- C. a constant

Activity 3


Find the voltage, power, and energy

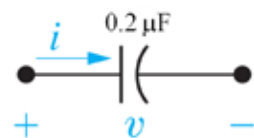

$$i(t) = \begin{cases} 0, & t \leq 0; \\ 5000t \text{ A}, & 0 \leq t \leq 20 \mu\text{s}; \\ 0.2 - 5000t \text{ A}, & 20 \leq t \leq 40 \mu\text{s}; \\ 0, & t \geq 40 \mu\text{s}. \end{cases}$$

Solution
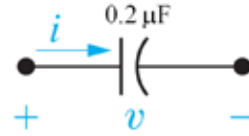
$$i(t) = \begin{cases} 0, & t \leq 0; \\ 5000t \text{ A}, & 0 \leq t \leq 20 \mu\text{s}; \\ 0.2 - 5000t \text{ A}, & 20 \leq t \leq 40 \mu\text{s}; \\ 0, & t \geq 40 \mu\text{s}. \end{cases}$$



For $t < 0$:

$$v(t) = 0 \text{ V}; \quad p(t) = 0 \text{ W}; \quad w(t) = 0 \text{ J}$$

For $0 \leq t \leq 20 \mu\text{s}$:

$$v(t) = \frac{1}{0.2 \mu} \int_0^t 5000x \, dx + v(0) = \frac{1}{0.2 \mu} \frac{5000x^2}{2} \Big|_0^t = 12.5 \times 10^9 t^2 \text{ V}$$

$$p(t) = v(t)i(t) = (12.5 \times 10^9 t^2)(5000t) = 62.5 \times 10^{12} t^3 \text{ W}$$

$$w(t) = \frac{1}{2}(0.2 \mu)(12.5 \times 10^9 t^2)^2 = 15.625 \times 10^{12} t^4 \text{ J}$$

$$\text{At } t = 20 \mu\text{s}, \quad v(20 \mu\text{s}) = 12.5 \times 10^9 (20 \mu)^2 = 5 \text{ V}$$

Solution

$$i(t) = \begin{cases} 0, & t \leq 0; \\ 5000t \text{ A}, & 0 \leq t \leq 20 \mu\text{s}; \\ 0.2 - 5000t \text{ A}, & 20 \leq t \leq 40 \mu\text{s}; \\ 0, & t \geq 40 \mu\text{s}. \end{cases}$$

For $20 \mu\text{s} \leq t \leq 40 \mu\text{s}$:

$$v(t) = \frac{1}{0.2 \mu} \int_{20 \mu}^t (0.2 - 5000x) \, dx + v(20 \mu)$$

$$= \frac{1}{0.2 \mu} \left[0.2x - \frac{5000x^2}{2} \right] \Big|_{20 \mu}^t + 5$$

$$= (10^6 t - 12.5 \times 10^9 t^2 - 10) \text{ V}$$

$$p(t) = v(t)i(t); \quad w(t) = \frac{1}{2} C v(t)^2$$

$$\text{At } t = 40 \mu\text{s}, \quad v(40 \mu\text{s}) = [10^6 (40 \mu) - 12.5 \times 10^9 (40 \mu)^2 - 10] = 10 \text{ V}$$

Solution

$$i(t) = \begin{cases} 0, & t \leq 0; \\ 5000t \text{ A}, & 0 \leq t \leq 20 \mu\text{s}; \\ 0.2 - 5000t \text{ A}, & 20 \leq t \leq 40 \mu\text{s}; \\ 0, & t \geq 40 \mu\text{s}. \end{cases}$$

For $t \geq 40 \mu\text{s}$:


$$v(t) = \frac{1}{0.2 \mu} \int_{40 \mu}^t 0 \, dx + v(40 \mu) = 10 \text{ V}$$

$$p(t) = v(t)i(t) = 0 \text{ W}$$

$$w(t) = \frac{1}{2}(0.2 \mu)(10)^2 = 10 \mu\text{J}$$


During the interval between 0 and $40 \mu\text{s}$, the power is positive (absorbed), energy is stored and “trapped” by the capacitor, so even when the current goes to 0, the voltage stays at 10 V and the energy is non-zero.

Solution

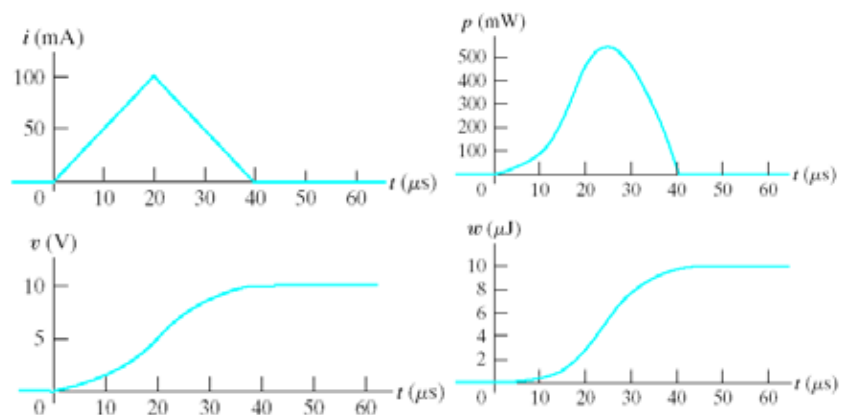

Activity 4

Find $V_c(t)$ for $t \geq 0$

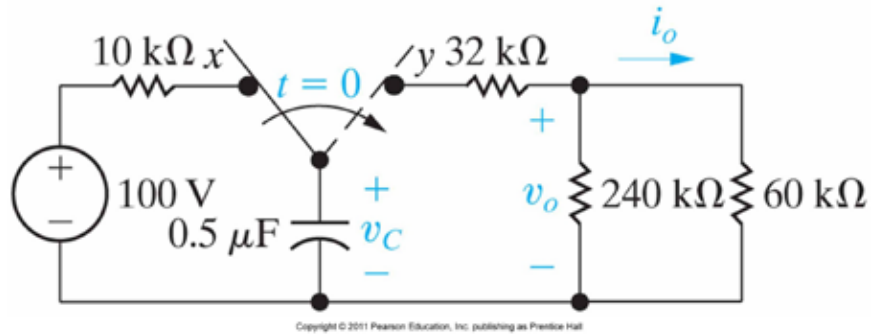


Solution

$$R_{eq} = 32 + 240 // 60 = 80 \text{ k}\Omega$$


$$v_C(t) = 100e^{-(1/RC)t}, \quad \tau = RC = 80 \times 10^3 \times 0.5 \times 10^{-6} = 4 \text{ ms}$$

$$v_C(t) = 100e^{-25t} \text{ V}$$

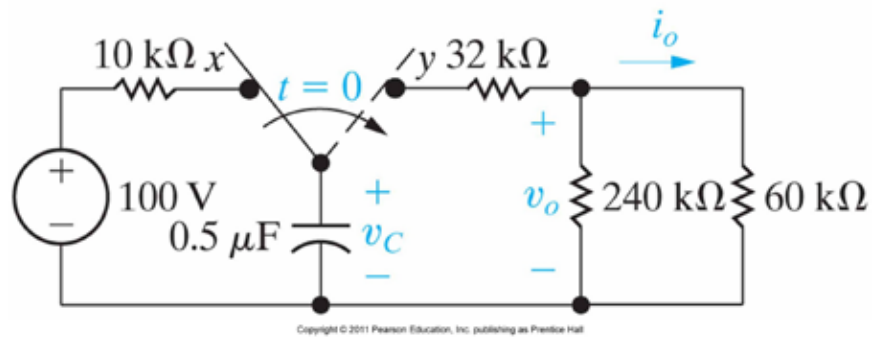


Activity 5

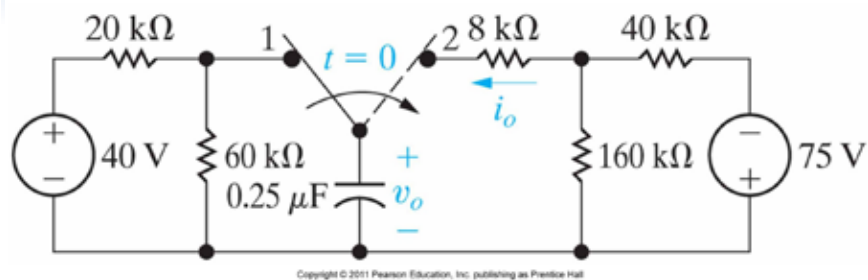The switch has been in position 1 for a long time. At $t=0$, the switch moves to position 2. Find $v_o(t)$ for $t \geq 0$ and $i_o(t)$ for $t \geq 0^+$



Solution

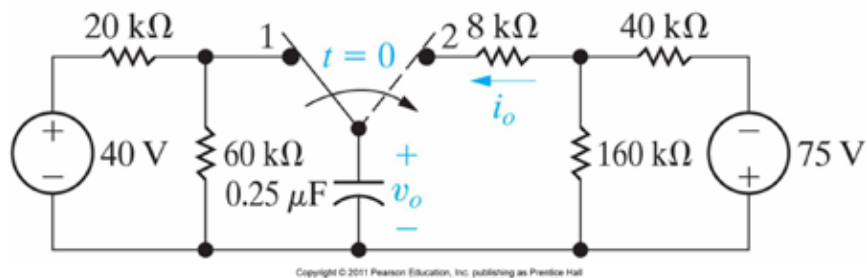
1. Switch was in position 1 for a long time,
 $V_0 = 60 / (20 + 60) * 40V = 30V$ (voltage divider)
2. After switch moves to position 2, the open circuit voltage is:
 $V_{oc} = 160 / (40 + 160) * (-75V) = -60V$



Solution

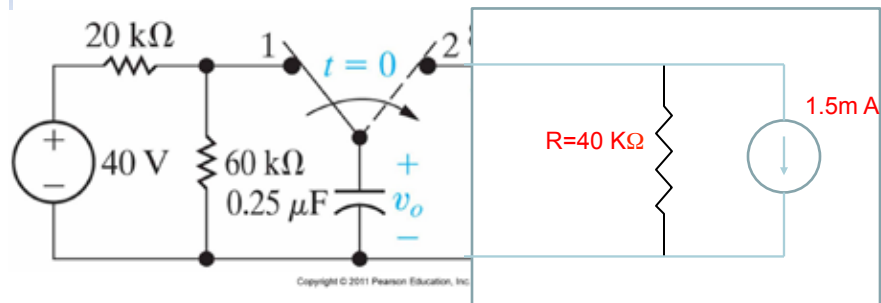3. Replace the right part with a Norton equivalent,

$$V_{oc} = -60V, R_{TH} = 8k + 40k // 160k = 40k\Omega$$




Solution

Since $V_o = 30V$, $I_s R = -60V$, $RC = 10ms$,

$$v_o(t) = I_s R + (V_o - I_s R)e^{-t/RC}$$

$$= -60 + [30 - (-60)]e^{-100t}$$


$$= -60 + 90e^{-100t}$$

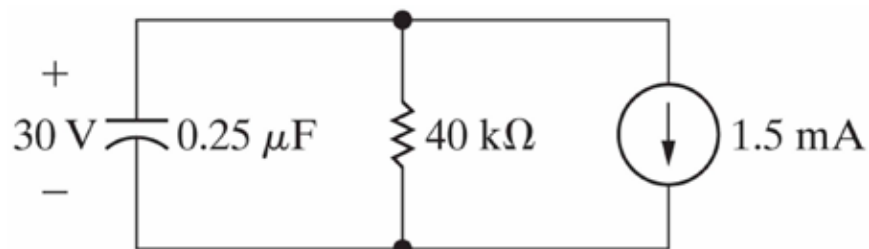

Solution

Since $I_s = -1.5 \text{ mA}$, $V_0/R = 0.75 \text{ mA}$,
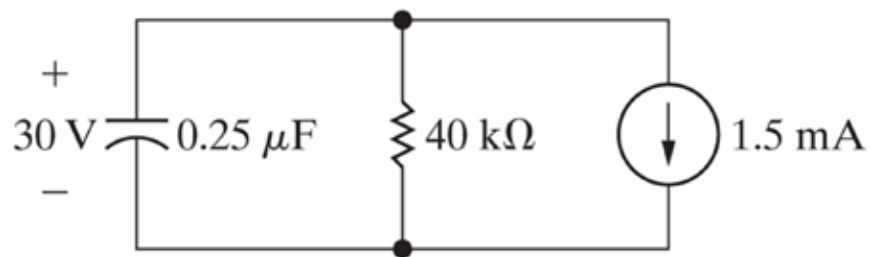
$$\begin{aligned} i(t) &= \left(I_s - \frac{V_0}{R} \right) e^{-t/RC} \\ &= (-1.5 - 0.75) e^{-100t} \\ &= -2.25 e^{-100t} \text{ mA} \end{aligned}$$



Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall