

EECS2200 Electric Circuits

Chapter 5 Part 2

Activities

Activity 1

Look at the inductor equation again:

$$v(t) = L \frac{di(t)}{dt}$$

Suppose $i(t)$ is constant, what is $v(t)$?

- A. L
- B. 0
- C. Undefined

Activity 2


So, if the current in an inductor is constant, its voltage drop is 0, so the inductor can be replaced by:

- A. A short circuit.
- B. An open circuit.
- C. A resistor.

Activity 3

Given the following conditions,

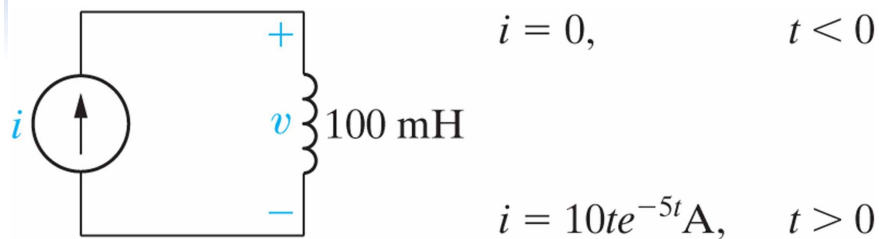
1. Sketch the current waveform.
2. Find $v(t)$ and sketch voltage waveform.



Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Solution

1. $i(t)$ waveform

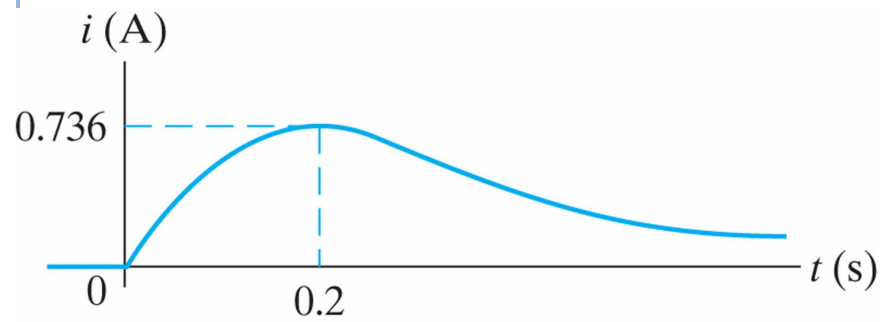


Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Solution

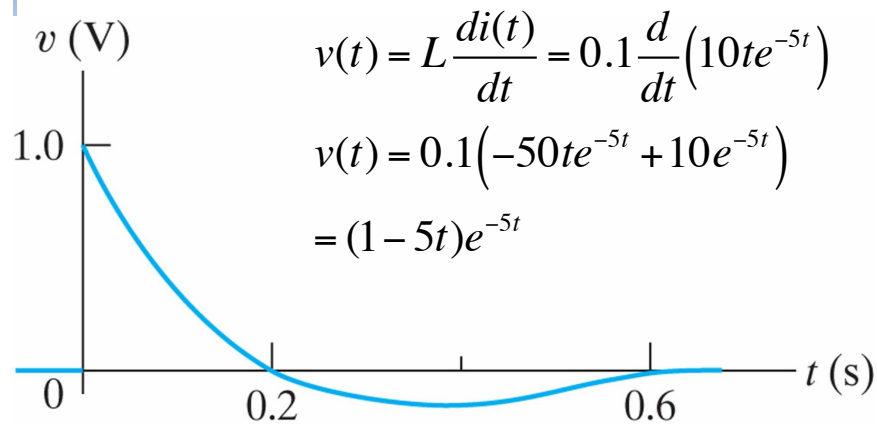2. $v(t)$

$$i(t) = \begin{cases} 0 & t < 0 \\ 10te^{-5t} \text{ A} & t \geq 0 \end{cases}$$



$$v(t) = L \frac{di(t)}{dt} = 0.1 \frac{d}{dt} (10te^{-5t})$$


$$v(t) = 0.1 (-50te^{-5t} + 10e^{-5t})$$

$$= (1 - 5t)e^{-5t}$$

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Activity 4

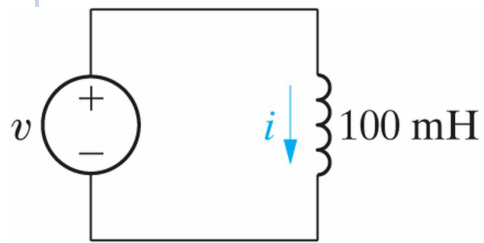1. Sketch the voltage as function of time
2. Find $i(t)$



$$v = 0, \quad t < 0$$


$$v = 20te^{-10t} \text{ V}, \quad t > 0$$

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Solution

1. Sketch $v(t)$

$$v(t) = 20te^{-10t}$$

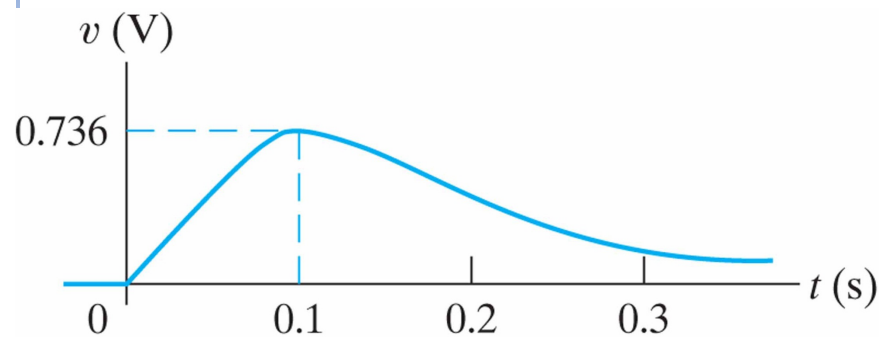


Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Solution

2. Find $i(t)$

$$i(t) = \frac{1}{0.1} \int_0^t 20\tau e^{-10\tau} d\tau = 200 \left[\frac{-e^{-10\tau}}{100} + \tau \right]_0^t$$


$$= 2(1 - 10te^{-10t} - e^{-10t}) A$$

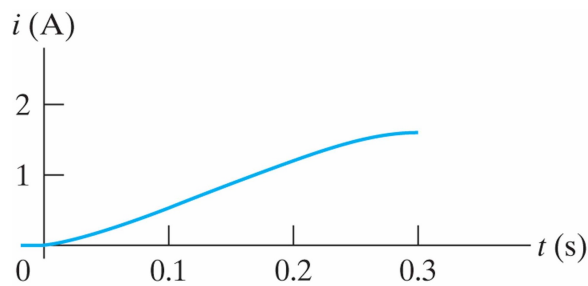

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Activity 5

Write a set of mesh-current equations.

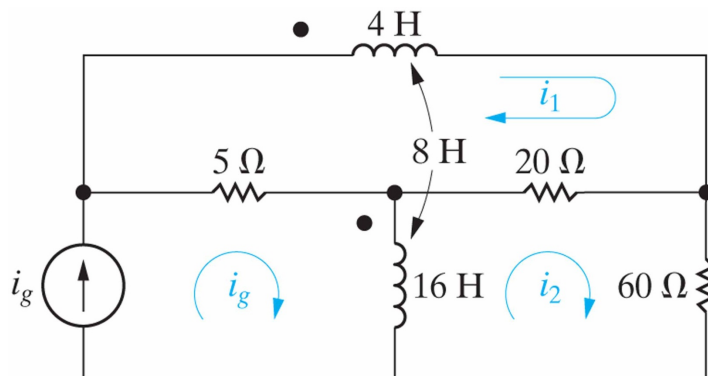


Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Solution

$$4 \frac{di_1}{dt} + 8 \frac{d}{dt}(i_g - i_2) + 20(i_1 - i_2) + 5(i_1 - i_g) = 0$$

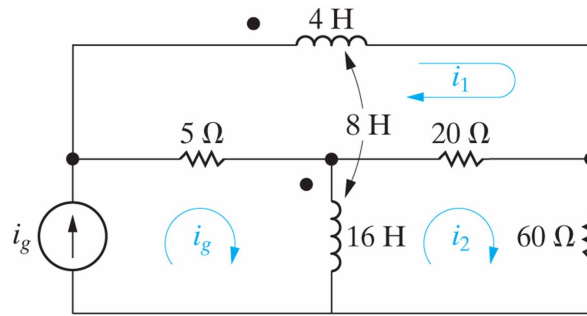
$$20(i_2 - i_1) + 60i_2 + 16 \frac{d}{dt}(i_2 - i_g) - 8 \frac{di_1}{dt} = 0$$



Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Activity 6

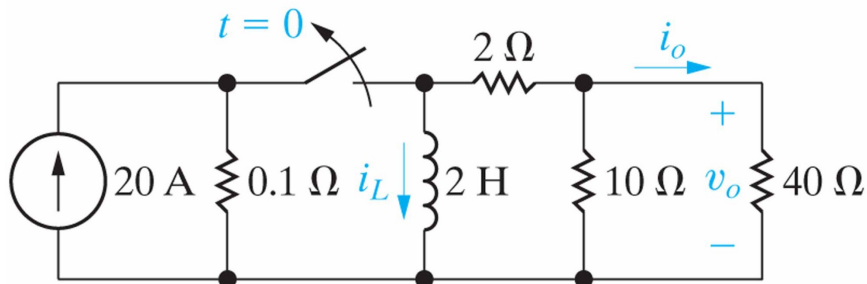The switch has been closed for long time before it is opened at $t=0$. Find $i_L(t)$ for $t \geq 0$.




Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Solution

$$R_{eq} = 2 + 10 // 40 = 10 \Omega, I_0 = 20 \text{ A}, L = 2 \text{ H}$$

$$i(t) = I_0 e^{-(R/L)t}, \quad \tau = \frac{L}{R} \text{ time constant}$$

$$i(t) = 20 e^{-5t}$$

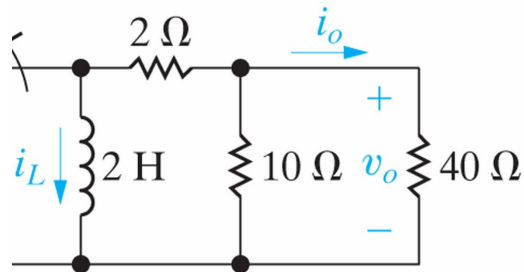


© 2008 Pearson Education, Inc. publishing as Prentice Hall

Activity 7

The circuit we analyzed for the RL natural response problem is shown below, along with the expression for $i(t)$, for $t \geq 0$. What is the value of $i(t)$ as $t \rightarrow \infty$?

- A. 0
- B. I_S
- C. ∞

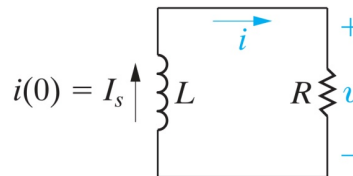


Copyright © 2008 Pearson Education, Inc.

$$i(t) = I_S e^{-(R/L)t}, \quad t \geq 0$$

Activity 8

Now consider what happens to the current as $t \rightarrow \infty$ in the RL step response circuit. First, as $t \rightarrow \infty$, we can replace the inductor by


- A. An open circuit
- B. A short circuit
- C. A resistor

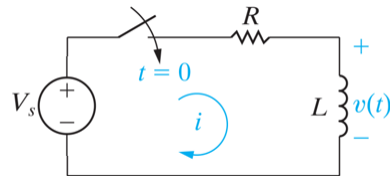

Activity 9


To evaluate the current in the inductor as $t \rightarrow \infty$, close the switch and replace the inductor with a short circuit. The current in the short circuit is

- A. 0
- B. infinite
- C. V_S/R

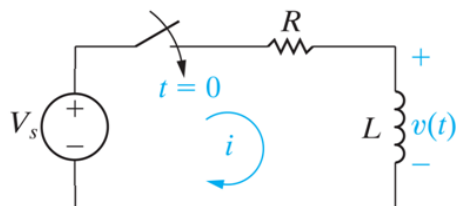

Activity 10

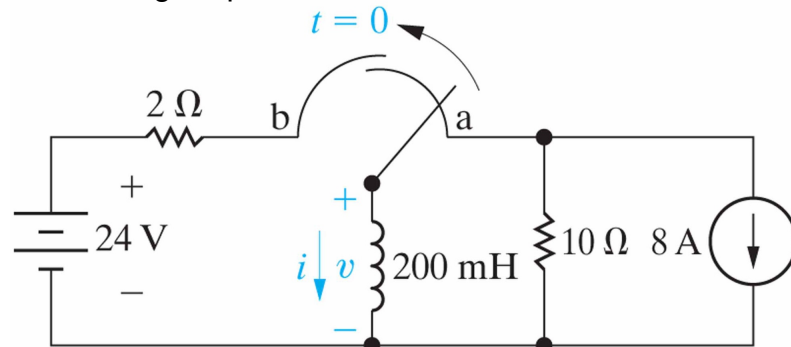1. Find $i(t)$ for $t \geq 0$
2. What is voltage across inductor just after switch has been moved to b.
3. How many ms after the switch has been moved does the inductor voltage equal 24V?



Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall


Solution

Switch at a: $I_0 = -8A$

Switch at b: $I_F = 24/2 = 12A$

$\tau = L/R = 200 / 2 = 100ms$

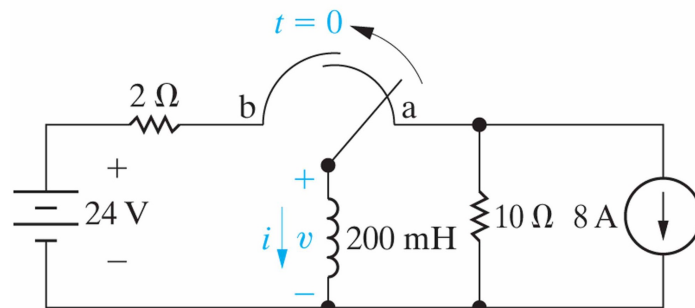$\therefore i(t) = 12 + (-8 - 12)e^{-10t} A$ for $t \geq 0$




Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Solution

$$v(t) = L \frac{di(t)}{dt} = 0.2(-20)(-10) \frac{d}{d(-10t)} e^{-10t}$$

$$\therefore v(t) = 40e^{-10t} \text{ V for } t \geq 0$$


$$v(0^+) = 40 \text{ V}$$

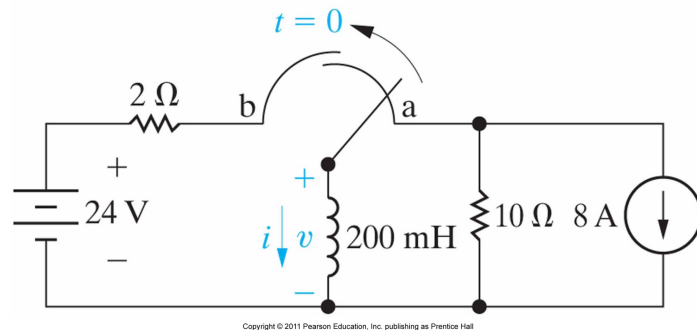


Solution

$$24 = 40e^{-10t}$$
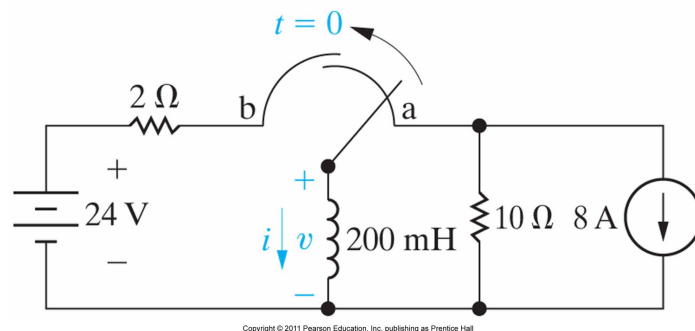
$$t = \frac{1}{10} \ln \frac{40}{24} = 51.08 \text{ ms}$$



Solution

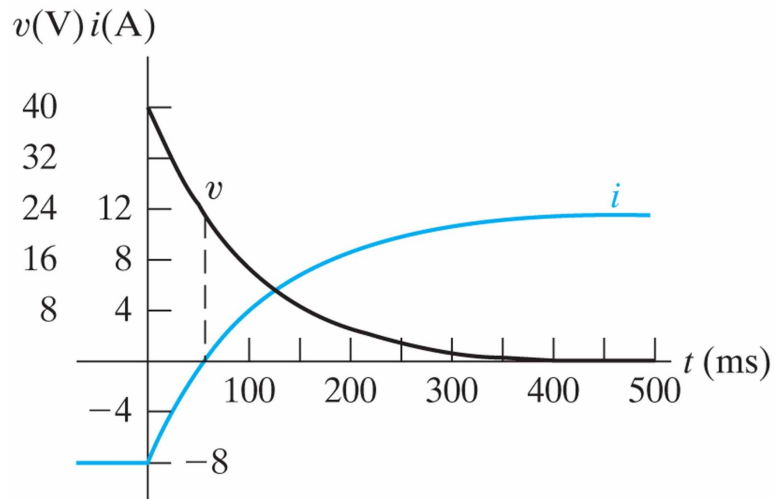

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall