

EECS2200 Electric Circuits

Chapter 6

RLC Circuit Natural and Step Responses

Objectives

- Determine the response form of the circuit
- Natural response parallel RLC circuits
- Natural response series RLC circuits
- Step response of parallel and series RLC circuits

EECS2200 Electric Circuits


Natural Response of Parallel RLC Circuits

Steps in Solving RLC Circuits

- The first step is to write either KVL or KCL for the circuit.
- Take the derivative to remove any integration
- Solve the resulting differential equation

Natural Response of Parallel RLC Circuits

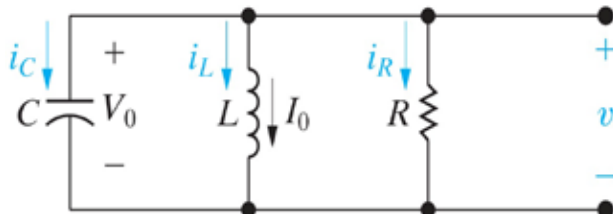The problem – given initial energy stored in the inductor and/or capacitor, find $v(t)$ for $t \geq 0$.




Copyright © 2008 Pearson Prentice Hall, Inc.

Activity 1

It is convenient to calculate $v(t)$ for this circuit because:

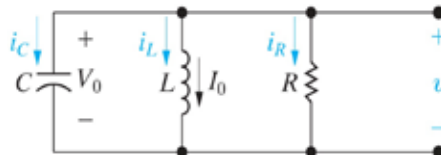- The voltage must be continuous for all time.
- The voltage is the same for all three components.
- Once we have the voltage, it is pretty easy to calculate the branch current.
- All of the above.



Copyright © 2008 Pearson Prentice Hall, Inc.

Natural Response of Parallel RLC Circuits

KCL:
$$C \frac{dv(t)}{dt} + \frac{1}{L} \int_0^t v(x) dx + I_0 + \frac{v(t)}{R} = 0$$

Differentiate both sides to remove the integral:


$$C \frac{d^2v(t)}{dt^2} + \frac{1}{L} v(t) + \frac{1}{R} \frac{dv(t)}{dt} = 0$$

Divide both sides by C to place in standard form:

$$\frac{d^2v(t)}{dt^2} + \frac{1}{LC} v(t) + \frac{1}{RC} \frac{dv(t)}{dt} = 0$$

Natural Response of Parallel RLC Circuits

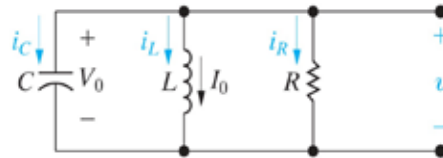The problem – given initial energy stored in the inductor and/or capacitor, find $v(t)$ for $t \geq 0$.



Copyright © 2008 Pearson Prentice Hall, Inc.

Describing equation:
$$\frac{d^2v(t)}{dt^2} + \frac{1}{LC} v(t) + \frac{1}{RC} \frac{dv(t)}{dt} = 0$$

- This equation is
- ✓ Second order
 - ✓ Homogeneous
 - ✓ Ordinary differential equation
 - ✓ With constant coefficients

Natural Response of Parallel RLC Circuits

Describing equation:
$$\frac{d^2v(t)}{dt^2} + \frac{1}{LC}v(t) + \frac{1}{RC}\frac{dv(t)}{dt} = 0$$

The circuit has two initial conditions that must be satisfied, so the solution for $v(t)$ must have two constants. Use

$v(t) = A_1e^{s_1t} + A_2e^{s_2t}$ V; Substitute:

$$(s_1^2 A_1 e^{s_1 t} + s_2^2 A_2 e^{s_2 t}) + \frac{1}{RC}(s_1 A_1 e^{s_1 t} + s_2 A_2 e^{s_2 t}) + \frac{1}{LC}(A_1 e^{s_1 t} + A_2 e^{s_2 t}) = 0$$

$$\Rightarrow [s_1^2 + (1/RC)s_1 + (1/LC)]A_1 e^{s_1 t} + [s_2^2 + (1/RC)s_2 + (1/LC)]A_2 e^{s_2 t} = 0$$

For solution, either $A_1=0$ and $A_2=0$ or the quadratic part is 0. The quadratic part is called Characteristic equation:

$$s^2 + (1/RC)s + (1/LC) = 0$$

Natural Response of Parallel RLC Circuits

The two solutions to the characteristic equation s_1 and s_2 can be calculated using the quadratic formula:

$$s^2 + \left(\frac{1}{RC}\right)s + \left(\frac{1}{LC}\right) = 0;$$

$$s_{1,2} = -\left(\frac{1}{2RC}\right) \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \left(\frac{1}{LC}\right)} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

where $\alpha = \frac{1}{2RC}$ (the neper frequency in rad/s)

and $\omega_0 = \sqrt{\frac{1}{LC}}$ (the resonant radian frequency in rad/s)

Parallel RLC Circuits

$$s_{1,2} = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{1}{2RC} \text{ rad/s}, \quad \omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/s}$$

$$s_{1,2} = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$s_{1,2} = -\xi\omega_0 \pm \omega_0\sqrt{\xi^2 - 1}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}, \quad \xi = \frac{1}{2R}\sqrt{\frac{L}{C}}$$

Neper frequency
radian frequency

Resonant

Damping ratio

Solution to Parallel RLC Circuits

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

- The solution of the differential equation depends on the values of s_1 and s_2 , A_1 and A_2 .
- s_1 and s_2 can be found from the characteristic equation, consider three cases

Case 1 - Overdamping

$\alpha > \omega_0$, $\zeta > 1 \rightarrow$ 2 real roots

$$s_{1,2} = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{1}{2RC} \text{ rad/s}, \quad \omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/s}$$

$$s_{1,2} = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$s_{1,2} = -\xi\omega_0 \pm \omega_0\sqrt{\xi^2 - 1}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}, \quad \xi = \frac{1}{2R}\sqrt{\frac{L}{C}}$$

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

Case 2: Underdamping

$\alpha < \omega_0$, $\zeta < 1 \rightarrow$ a pair of complex roots

$$s_{1,2} = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{1}{2RC} \text{ rad/s}, \quad \omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/s}$$

$$s_{1,2} = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$s_{1,2} = -\xi\omega_0 \pm \omega_0\sqrt{\xi^2 - 1}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}, \quad \xi = \frac{1}{2R}\sqrt{\frac{L}{C}}$$

$$s = -\alpha \pm j\omega_d \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$v(t) = B_1 e^{-\alpha t} \cos(\omega_d t) + B_2 e^{-\alpha t} \sin(\omega_d t)$$

Case 3: Critical Damping

$\alpha = \omega_0$, $\zeta = 1 \rightarrow$ 2 equal roots

$$s_{1,2} = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{1}{2RC} \text{ rad/s}, \quad \omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/s}$$

$$s_{1,2} = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$s_{1,2} = -\xi\omega_0 \pm \omega_0\sqrt{\xi^2 - 1}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}, \quad \xi = \frac{1}{2R}\sqrt{\frac{L}{C}}$$

$$s_1 = s_2 = -\alpha$$

$$v(t) = D_1te^{-\alpha t} + D_2e^{-\alpha t}$$

Solution to Parallel RLC Circuits

$$v(t) = A_1e^{s_1t} + A_2e^{s_2t} \quad \text{Overdamped}$$

$$v(t) = B_1e^{-\alpha t} \cos \omega_d t + B_2e^{-\alpha t} \sin \omega_d t \quad \text{Underdamped}$$

$$v(t) = D_1te^{-\alpha t} + D_2e^{-\alpha t} \quad \text{Critically damped}$$

Determine the Coefficients


- We can calculate them from the *initial conditions*
- Keep in mind voltage across a capacitor and current in an inductor can not change instantaneously

$$v_C(0^-) = v_C(0) = v_C(0^+)$$

$$i_L(0^-) = i_L(0) = i_L(0^+)$$

Activity 2

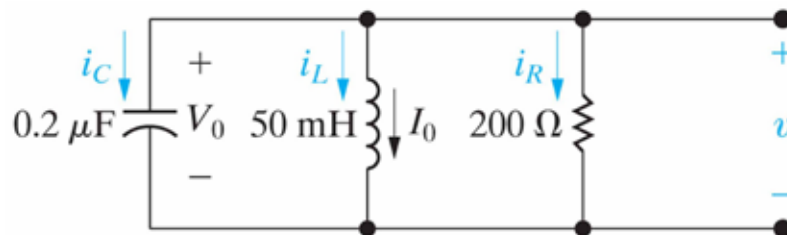Given $v(0^+) = 12\text{V}$ and $i_L(0^+) = 30\text{mA}$,
Find $v(t)$ for $t \geq 0$.



Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Solution

Step 1: determine the solution form.

Given $R=200\Omega$, $C=0.2\mu\text{F}$, $L=50\text{mH}$

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 200 \times 0.2 \times 10^{-6}} = 0.0125 \times 10^6 \text{ rad/s}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{50 \times 10^{-3} \times 0.2 \times 10^{-6}}} = 10^4 \text{ rad/s}$$

$\alpha > \omega_0$ overdamped


$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -1.25 \times 10^4 \pm \sqrt{1.5625 - 1} \times 10^4$$

$$s_1 = -12500 + 7500 = -5000 \text{ rad/s}$$

$$s_2 = -12500 - 7500 = -20000 \text{ rad/s}$$

$$\therefore v(t) = A_1 e^{-5000t} + A_2 e^{-20000t} \text{ V}$$

Solution

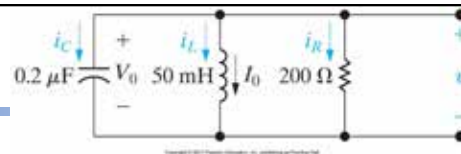

Step 2, find A_1 and A_2

Given $v(0^+) = 12 \text{ V}$, $i_L(0^+) = 30 \text{ mA}$

and $v(t) = A_1 e^{-5,000t} + A_2 e^{-20,000t}$

$$v(0^+) = 12 = A_1 + A_2 \quad (1)$$

KCL: $i_C(0^+) = -i_R(0^+) - i_L(0^+)$, also $i_C(0^+) = C \frac{dv(0^+)}{dt}$

$$C \frac{dv(0^+)}{dt} = -\frac{V_0}{R} - i_L(0^+)$$

$$\begin{aligned} \frac{dv(0^+)}{dt} &= -\frac{V_0}{CR} - \frac{i_L(0^+)}{C} = -\frac{12}{0.2 \times 10^{-6} \times 200} - \frac{30 \times 10^{-3}}{0.2 \times 10^{-6}} \\ &= -0.3 \times 10^6 - 0.15 \times 10^6 = -0.45 \times 10^6 \text{ V/s} \end{aligned}$$

$$\frac{dv(0^+)}{dt} = -450,000 = -5000A_1 - 20,000A_2 \quad (2)$$


Solution

Solve for equations (1) and (2),
 $A_1 = -14V$ and $A_2 = 26V$

$$\therefore v(t) = -14e^{-5,000t} + 26e^{-20,000t}V, \quad t \geq 0$$

Solution


Plot $v(t)$ from 0 to
250ms

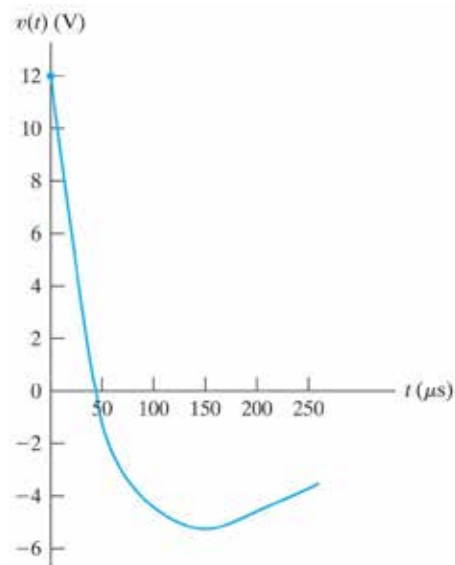

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Activity 3

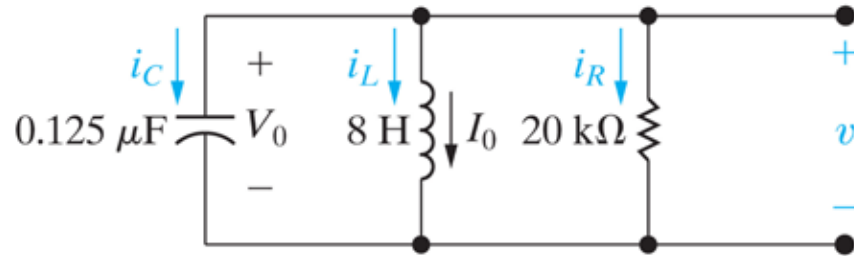Given $V_0=0V$, $I_0=-12.25mA$,
Find $v(t)$ for $t \geq 0$.



Solution

Step 1: determine the solution form.

Given $R=20\text{k}\Omega$, $C=0.125\mu\text{F}$, $L=8\text{H}$

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 20 \times 10^3 \times 0.125 \times 10^{-6}} = 200 \text{ rad / s}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{8 \times 0.125 \times 10^{-6}}} = 10^3 \text{ rad / s}$$

$\alpha < \omega_0$ underdamped

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{10^6 - 4 \times 10^4} = 979.80 \text{ rad / s}$$

$$s_1 = -\alpha + j\omega_d = -200 + j979.80 \text{ rad / s}$$

$$s_2 = -\alpha - j\omega_d = -200 - j979.80 \text{ rad / s}$$

$$v(t) = B_1 e^{-200t} \cos(979.80t) + B_2 e^{-200t} \sin(979.80t)$$

Solution

Step 2, find B_1 and B_2

Given $v_0 = v(0^+) = 0$ V, $i_R = 0 \rightarrow i_C(0^+) = -I_0 = 12.25$ mA

and $v(t) = B_1 e^{-200t} \cos(979.80t) + B_2 e^{-200t} \sin(979.80t)$

$$v(0^+) = B_1 = 0 \quad (1)$$

KCL: $i_C(0^+) = -i_R(0^+) - i_L(0^+)$, also $i_C(0^+) = C \frac{dv(0^+)}{dt}$

$$\frac{dv(0^+)}{dt} = \frac{i_L(0^+)}{C} = \frac{12.25 \times 10^{-3}}{0.125 \times 10^{-6}} = 98000 \text{ V/s}$$

$$B_2 = \frac{dv(0^+)}{dt} / \omega_d = \frac{98000}{979.80} \approx 100 \text{ V} \quad (2)$$

Solution


Solve for equations (1) and (2),

$B_1 = 0$ V and $B_2 = 100$ V

$$v(t) = 100 e^{-200t} \sin(979.80t) \text{ V} \quad t \geq 0$$

Solution


Plot $v(t)$ from 0 to 11ms

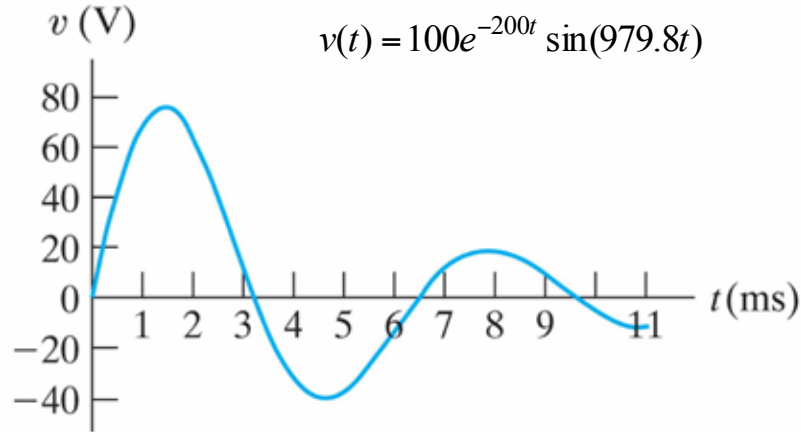

Activity 4

In Activity 4, what is the value of R that results in a critically damped voltage response?

Find $v(t)$ for $t \geq 0$.

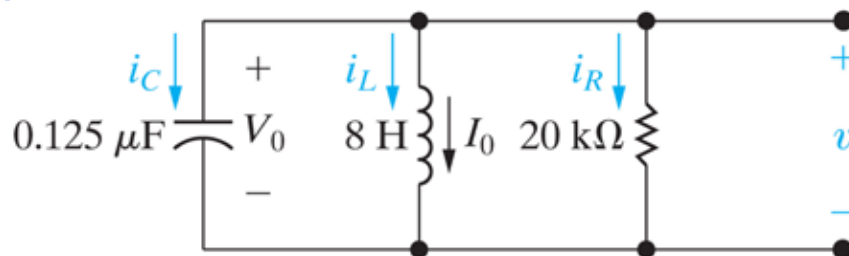

Solution

Step 1: determine the solution form.

Given $C=0.125\mu\text{F}$, $L=8\text{H}$

$$\therefore \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{8 \times 0.125 \times 10^{-6}}} = 10^3 \text{ rad / s}$$

$$\therefore \alpha = \omega_0 = 10^3 = \frac{1}{2RC} \Rightarrow R = \frac{1}{2 \times 10^3 \times 0.125 \times 10^{-6}} = 4\text{k}\Omega$$

$$\therefore v(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$

Solution

Step 2, find D_1 and D_2

Given $v_0 = v(0^+) = 0 \text{ V}$, $dv(0^+)/dt = 98000 \text{ V/s}$



and $v(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$

$$v(0^+) = D_2 = 0 \quad (1)$$

$$\frac{dv(t)}{dt} = D_1 e^{-\alpha t} + D_1 t \frac{e^{-\alpha t}}{-\alpha}$$

$$\frac{dv(0^+)}{dt} = D_1 = 98000 \text{ V} \quad (2)$$
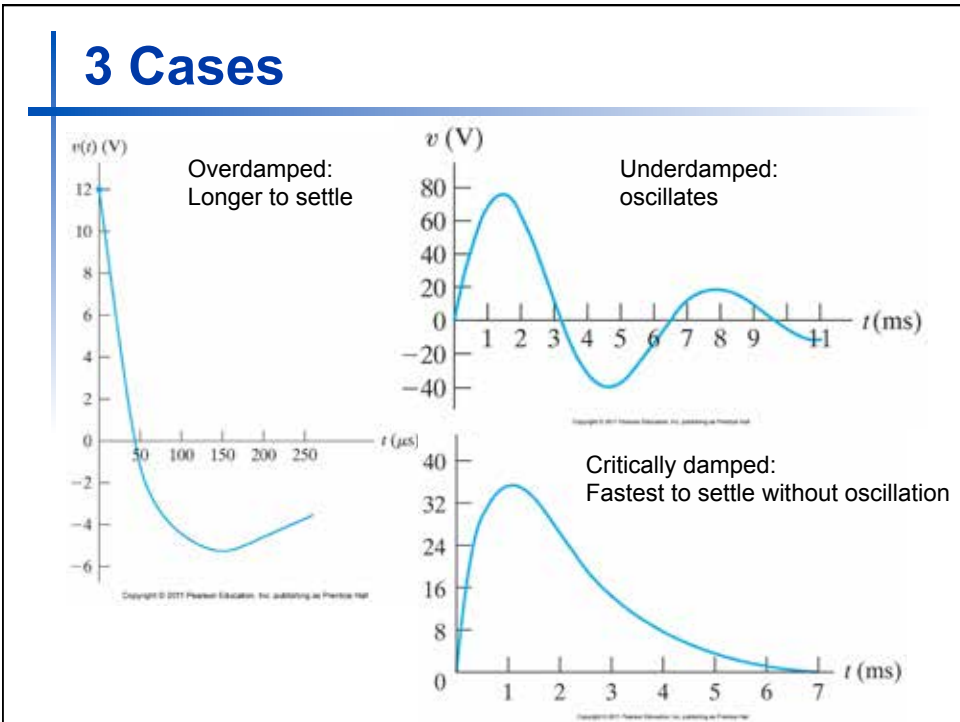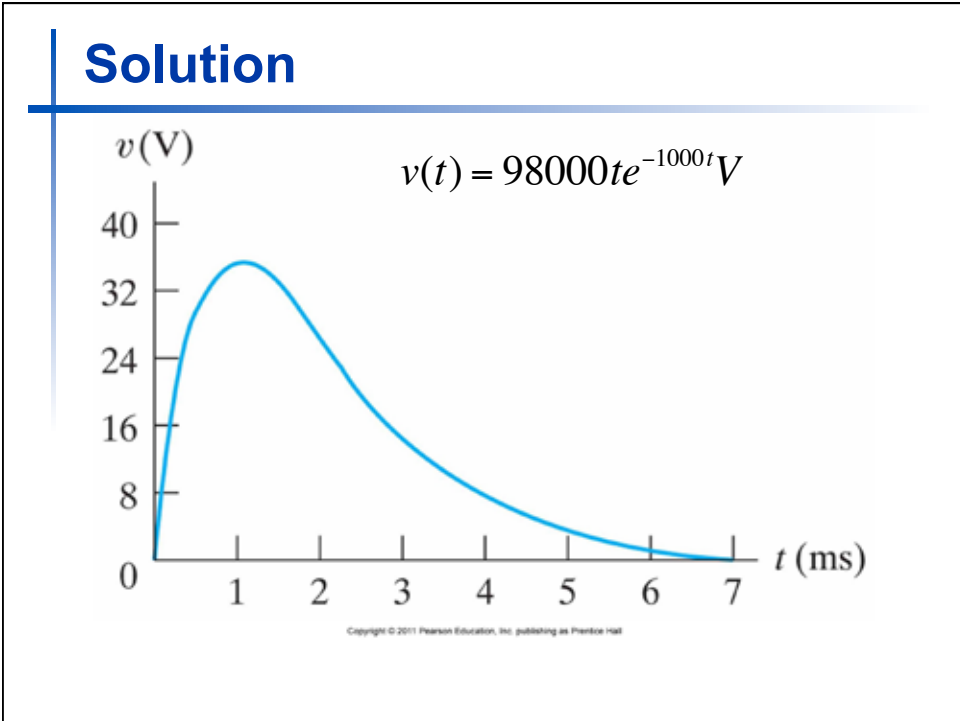
$$\therefore v(t) = 98000 t e^{-1000t} \text{ V} \quad t \geq 0$$



EECS2200 Electric Circuits


Natural Response of Series RLC Circuits

Series and Parallel RLC Circuits

- The difference(s) between the analysis of series RLC circuit and the parallel RLC circuit is/are:
 - A. The variable we calculate.
 - B. The describing differential equation.
 - C. The equations for satisfying the initial conditions

Natural Response of Series RLC Circuits

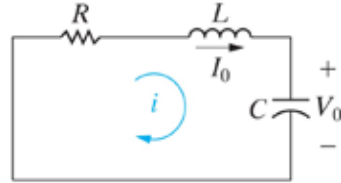The problem – given initial energy stored in the inductor and/or capacitor, find $i(t)$ for $t \geq 0$.



$$\text{KVL: } L \frac{di(t)}{dt} + \frac{1}{C} \int_0^t i(x) dx + V_0 + Ri(t) = 0$$

Differentiate both sides to remove the integral:

$$L \frac{d^2i(t)}{dt^2} + \frac{1}{C} i(t) + R \frac{di(t)}{dt} = 0$$

Divide both sides by L to place in standard form:

$$\frac{d^2i(t)}{dt^2} + \frac{R}{L} \frac{di(t)}{dt} + \frac{1}{LC} i(t) = 0$$

Activity 5

The describing differential equation for the series RLC circuit is

$$\frac{d^2i(t)}{dt^2} + \frac{R}{L} \frac{di(t)}{dt} + \frac{1}{LC} i(t) = 0$$

Therefore, the characteristic equation is

A. $s^2 + (1/RC)s + 1/LC = 0$

B. $s^2 + (R/L)s + 1/LC = 0$

C. $s^2 + (1/LC)s + 1/RC = 0$

Natural Response of Series RLC Circuits

The two solutions to the characteristic equation can be calculated using the quadratic formula:

$$s^2 + (R/L)s + (1/LC) = 0$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{R}{2L} \quad (\text{the neper frequency in rad/s})$$

$$\omega_0 = \sqrt{\frac{1}{LC}} \quad (\text{the resonant radian frequency in rad/s})$$


Natural Response of Series RLC Circuits

The solution are in the same form as in the parallel RLC circuits:

$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$	Overdamped
$i(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$	Underdamped
$i(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$	Critically damped

Activity 6

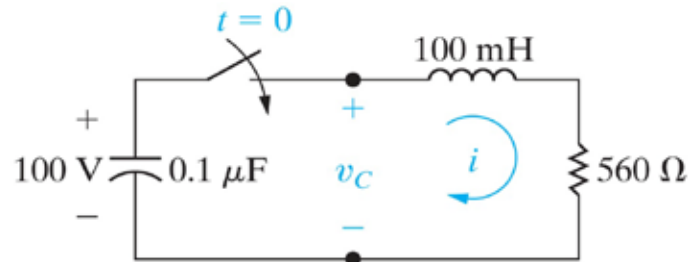The capacitor is charged to 100 V and at $t = 0$, the switch closes. Find $i(t)$ for $t \geq 0$.



Copyright © 2008 Pearson Prentice Hall, Inc.

Solution


$$\alpha = \frac{R}{2L} = \frac{560}{2(0.1)} = 2800 \text{ rad/s}$$

$$\omega_0 = \sqrt{\frac{1}{LC}} = \sqrt{\frac{1}{(0.1)(0.1\mu)}} = 10,000 \text{ rad/s}$$

$\alpha^2 < \omega_0^2$ so this is the underdamped case!

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 9600 \text{ rad/s}$$
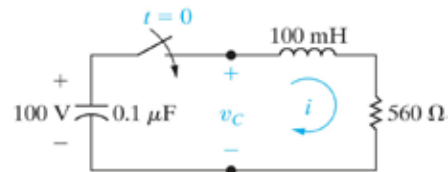
$$i(t) = B_1 e^{-2800t} \cos 9600t + B_2 e^{-2800t} \sin 9600t \text{ A}, t \geq 0$$



Copyright © 2008 Pearson Prentice Hall, Inc.


Solution

$$i(t) = B_1 e^{-2800t} \cos 9600t + B_2 e^{-2800t} \sin 9600t \text{ A}, t \geq 0$$

Now we must use the coefficients in the equation to satisfy the initial conditions in the circuit :

$$i(t)|_{t=0} \text{ in the equation} = i(t)|_{t=0} \text{ in the circuit}$$

$$\left. \frac{di(t)}{dt} \right|_{t=0} \text{ in the equation} = \left. \frac{di(t)}{dt} \right|_{t=0} \text{ in the circuit}$$

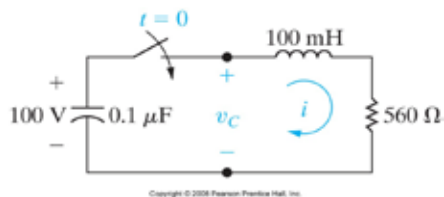


Solution

$$i(t) = B_1 e^{-2800t} \cos 9600t + B_2 e^{-2800t} \sin 9600t \text{ A}, t \geq 0$$

Equation: $i(0) = B_1$ (same as the parallel case!)

Circuit: $i(0) = I_0 = 0$

$$\Rightarrow B_1 = 0$$

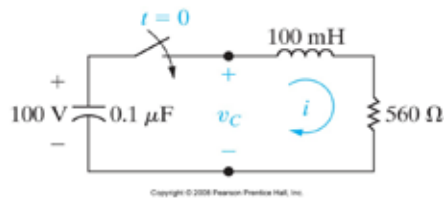


Solution

Equation: $\frac{di(0^+)}{dt} = -\alpha B_1 + \omega_d B_2$ (same as the parallel case!)

Circuit: $L \frac{di(0^+)}{dt} = V_0 \Rightarrow \frac{di(0^+)}{dt} = \frac{V_0}{L} = \frac{100}{100 \times 10^{-3}} = 1000 \text{ A/s}$

$\therefore B_1 = 0 \Rightarrow \frac{di(0^+)}{dt} = \omega_d B_2 = 9600 B_2 = 1000 \Rightarrow B_2 = 0.104$

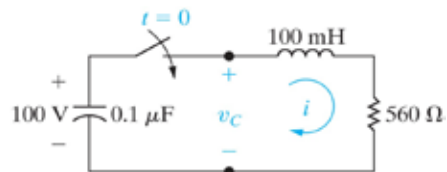
$\therefore i(t) = 0.104 e^{-2800t} \sin 9600t \text{ A}, t \geq 0$



EECS2200 Electric Circuits

Step Response of RLC Circuits

Step Response of RLC Circuit

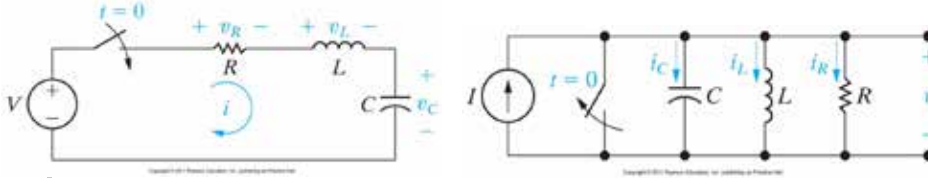

$$\begin{aligned}
 v_L + v_C + v_R &= V \\
 L \frac{di}{dt} + v_C + iR &= V \\
 i &= C \frac{dv_C}{dt} \\
 LC \frac{d^2 v_C}{dt^2} + v_C + RC \frac{dv_C}{dt} &= V \\
 \frac{d^2 v_C}{dt^2} + \frac{R}{L} \frac{dv_C}{dt} + \frac{v_C}{LC} &= \frac{I}{LC}
 \end{aligned}$$

$$\begin{aligned}
 i_L + i_C + i_R &= I \\
 i_L + C \frac{dv}{dt} + \frac{v}{R} &= I \\
 v &= L \frac{di_L}{dt} \\
 LC \frac{d^2 i_L}{dt^2} + \frac{L}{R} \frac{di_L}{dt} + i_L &= I \\
 \frac{d^2 i_L}{dt^2} + \frac{1}{RC} \frac{di_L}{dt} + \frac{i_L}{LC} &= \frac{I}{LC}
 \end{aligned}$$

Step Response of RLC Circuits

- A topic for a course in Math.
- Generally speaking, the solution of a second-order DE with a constant driving force equals the forced response plus the a response function identical to the natural response.

$$i = I_f + \left\{ \begin{array}{l} \text{function of the same form} \\ \text{as natural response} \end{array} \right\}$$

$$v = V_f + \left\{ \begin{array}{l} \text{function of the same form} \\ \text{as natural response} \end{array} \right\}$$

- I_f or V_f is the non-zero final value.

EECS2200 Electric Circuits


Step Response for Parallel RLC Circuits

Step Response of a Parallel *RLC Circuit*

$i_L(t) = I_f + A_1 e^{s_1 t} + A_2 e^{s_2 t}$	Overdamped
$i_L(t) = I_f + B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$	Underdamped
$i_L(t) = I_f + D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$	Critically damped

Step Response of RLC Circuit


As $t \rightarrow \infty$:

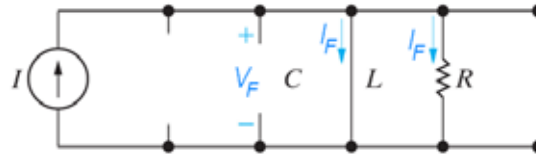

The only component whose final value is NOT zero is the inductor, whose final current is the current supplied by the source.


Activity 7

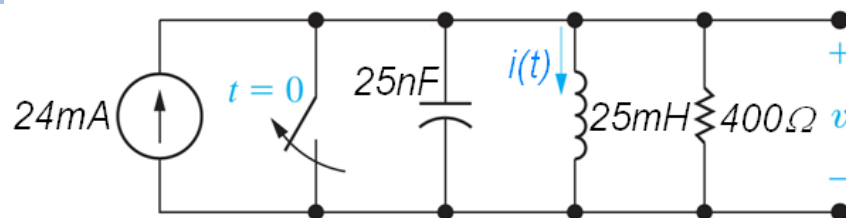There is no initial energy stored in this circuit; find $i(t)$ for $t \geq 0$.



Solution

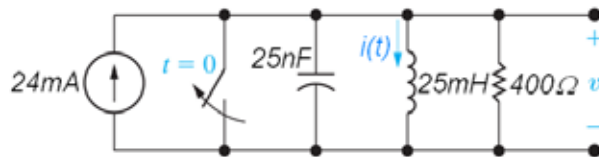
The problem – there is no initial energy stored in this circuit; find $i(t)$ for $t \geq 0$.




To begin, find the initial conditions and the final value. The initial conditions for this problem are both zero; the final value is found by analyzing the circuit as $t \rightarrow \infty$.

Solution

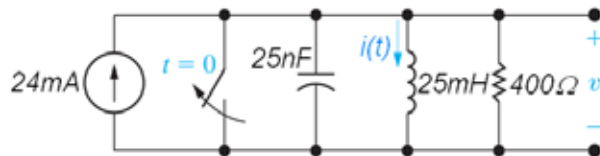The problem – there is no initial energy stored in this circuit; find $i(t)$ for $t \geq 0$.



$t \rightarrow \infty$:

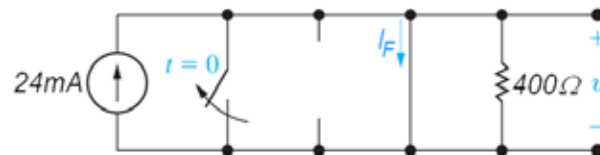

$$I_F = 24\text{mA}$$


Solution

Next, calculate the values of α and ω_0 and determine the form of the response:

$$\alpha = \frac{1}{2RC} = \frac{1}{2(400)(25\text{n})} = 50,000 \text{ rad/s}$$

$$\omega_0 = \sqrt{1/LC} = \sqrt{1/(25\text{m})(25\text{n})} = 40,000 \text{ rad/s}$$

Overdamped

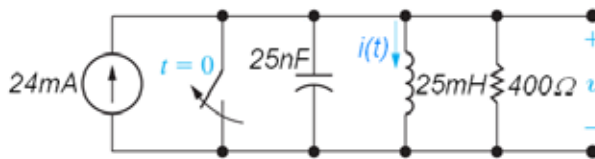

Solution


Since the response form is overdamped, calculate the values of s_1 and s_2 :

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -50,000 \pm \sqrt{50,000^2 - 40,000^2}$$

$$= -50,000 \pm 30,000 \text{ rad/s}$$

$$\therefore s_1 = -20,000 \text{ rad/s} \text{ and } s_2 = -80,000 \text{ rad/s}$$
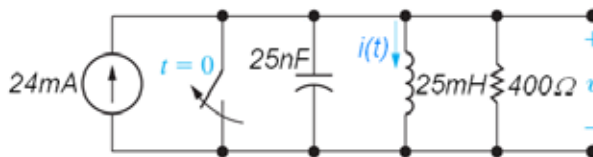
$$\Rightarrow i_L(t) = 0.024 + A_1 e^{-20,000t} + A_2 e^{-80,000t} \text{ A, } t \geq 0$$



Solution

$$i_L(t) = 0.024 + A_1 e^{-20,000t} + A_2 e^{-80,000t} \text{ A}, t \geq 0$$

Next, set the values of $i(0)$ and $di(0)/dt$ from the equation equal to the values of $i(0)$ and $di(0)/dt$ from the circuit.

From the equation: $i_L(0) = 0.024 + A_1 + A_2$

From the circuit: $i_L(0) = I_0 = 0$

From the equation: $\frac{di_L(0)}{dt} = -20,000A_1 - 80,000A_2$

From the circuit: $\frac{di_L(0)}{dt} = \frac{v_L(0)}{L} = \frac{V_0}{L} = 0$


Solution

Solve: $0.024 + A_1 + A_2 = 0$

and $-20,000A_1 - 80,000A_2 = 0$


$\therefore A_1 = -32 \text{ mA}; \quad A_2 = 8 \text{ mA}$

$\Rightarrow i_L(t) = 24 - 32e^{-20,000t} + 8e^{-80,000t} \text{ mA}, t \geq 0$

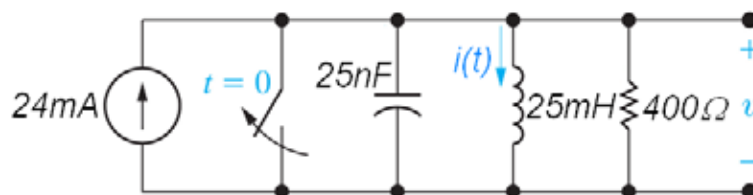

Activity 8

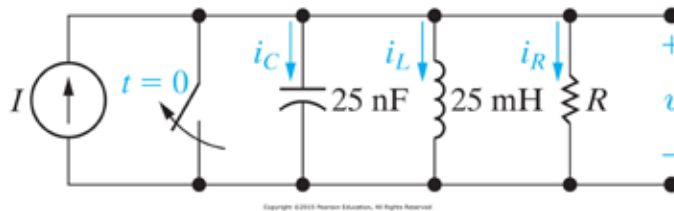If the resistor value is changed to 625Ω , find $i(t)$ for $t \geq 0$.



Solution

$$\because R = 625\Omega, C = 25\text{nF},$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2(625)(25\text{n})} = 32,000 \text{ rad/s}$$

$$\omega_0 = \sqrt{1/LC} = \sqrt{1/(25\text{m})(25\text{n})} = 40,000 \text{ rad/s}$$

$$\alpha < \omega_0 \Rightarrow \text{Underdamped}$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{(16 - 10.24) \times 10^8} = 24000 \text{ rad/s}$$

$$s_1 = -32000 + j24000 \text{ rad/s}$$

$$s_2 = -32000 - j24000 \text{ rad/s}$$

$$i_L(t) = I_f + B_1 e^{-32000t} \cos(24000t) + B_2 e^{-32000t} \sin(24000t)$$

Solution

Next, set the values of $i(0)$ and $di(0)/dt$ from the equation equal to the values of $i(0)$ and $di(0)/dt$ from the circuit.

$$i_L(0) = 0.024 + B_1 = 0$$

$$\frac{di_L(0)}{dt} = \omega_d B_2 - \alpha B_1 = 0$$


$$B_1 = -24mA, B_2 = 32mA$$

$$i_L(t) = 24 - 24e^{-32000t} \cos(24000t)$$

$$-32e^{-32000t} \sin(24000t)mA \quad t \geq 0$$

Activity 9

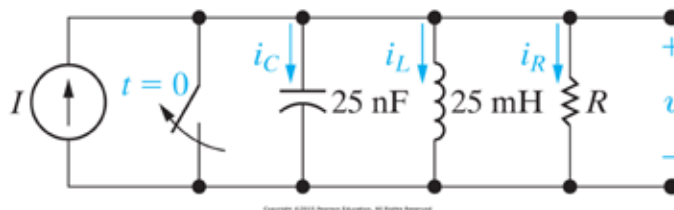If the resistor value in is changed to 500Ω , find $i(t)$ for $t \geq 0$.



Solution

$$\because R = 500\Omega, C = 25nF,$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2(500)(25n)} = 40,000 \text{ rad/s}$$

$$\omega_0 = \sqrt{1/LC} = \sqrt{1/(25m)(25n)} = 40,000 \text{ rad/s}$$

$$\alpha = \omega_0 \Rightarrow \text{Critically damped}$$

$$s_1 = s_2 = -\alpha = -40000 \text{ rad/s}$$

$$i_L(t) = I_f + D_1te^{-40000t} + D_2e^{-40000t}$$

Solution

Next, set the values of $i(0)$ and $di(0)/dt$ from the equation equal to the values of $i(0)$ and $di(0)/dt$ from the circuit.

$$i_L(0) = 0.024 + D_2 = 0$$

$$\frac{di_L(0)}{dt} = D_1 - \alpha D_2 = 0$$

$$D_1 = -960000 \text{ mA/s}, D_2 = -24 \text{ mA}$$

$$i_L(t) = 24 - 960000te^{-40000t} - 24e^{-40000t} \text{ mA} \quad t \geq 0$$

Plot Responses of 3 Cases

The overdamped, underdamped, and critically damped responses of Activities 7-9 are given below:

Overdamped:

$$i_L(t) = 24 - 32e^{-20,000t} + 8e^{-80,000t} \text{ mA}, t \geq 0$$

Underdamped:


$$i_L(t) = 24 - 24e^{-32000t} \cos(24000t)$$

$$- 32e^{-32000t} \sin(24000t) \text{ mA}, t \geq 0$$

Critically damped:

$$i_L(t) = 24 - 960000te^{-40000t} - 24e^{-40000t} \text{ mA}, t \geq 0$$

The current plots

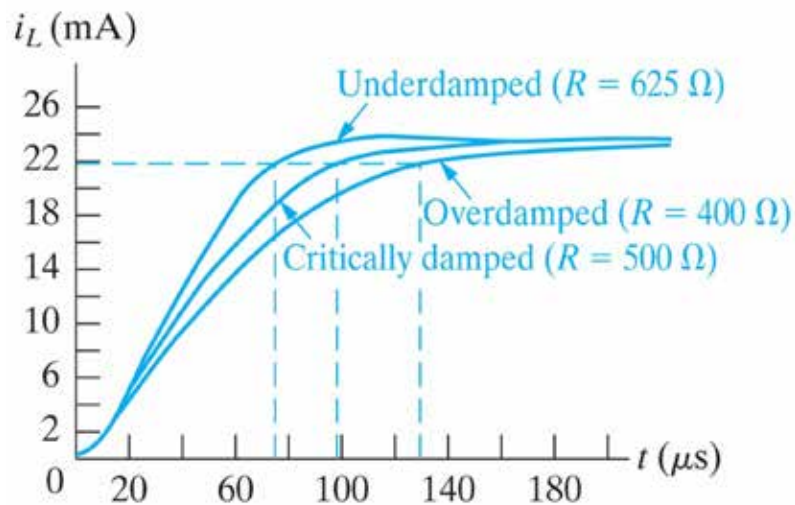

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

EECS2200 Electric Circuits


Step Response for Series RLC Circuits

Step Response of a Series *RLC Circuit*


$v_c = V_f + A_1 e^{s_1 t} + A_2 e^{s_2 t}$	Overdamped
$v_c = V_f + B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$	Underdamped
$v_c = V_f + D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$	Critically damped

Step Response for Series RLC Circuit

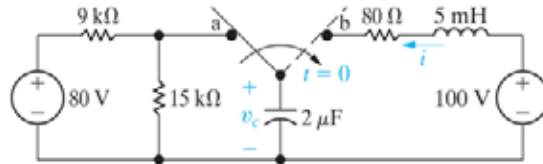The problem –
find $v_c(t)$ for $t \geq 0$.




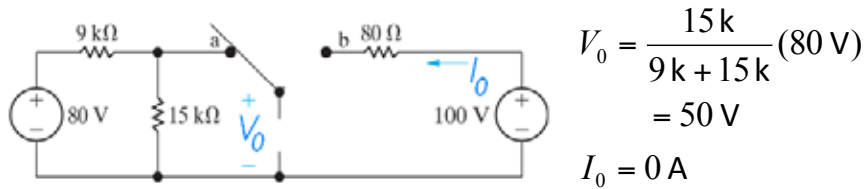Find the initial conditions by analyzing the circuit for $t < 0$:



Step Response for Series RLC Circuit

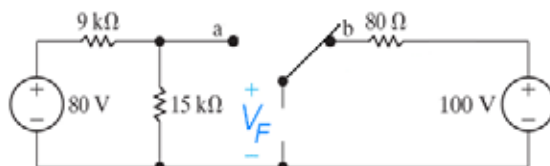Find the final value of the capacitor voltage
by analyzing the circuit as $t \rightarrow \infty$:



$$V_F = 100\text{V}$$

Step Response for Series RLC Circuit


Use the circuit for $t \geq 0$ to find the values of α and ω_0 :

$$\alpha = R/2L = 80/2(0.005) = 8000 \text{ rad/s}$$

$$\begin{aligned} \omega_0 &= \sqrt{1/LC} = \sqrt{1/(0.005)(2\mu)} \\ &= 10,000 \text{ rad/s} \end{aligned}$$

$$\alpha^2 < \omega_0^2 \quad \Rightarrow \quad \text{underdamped}$$
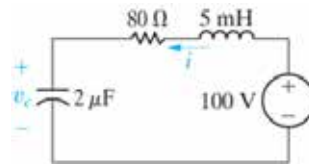
$$\begin{aligned} \omega_d &= \sqrt{\omega_0^2 - \alpha^2} = \sqrt{10,000^2 - 8000^2} \\ &= 6000 \text{ rad/s} \end{aligned}$$



Step Response for Series RLC Circuit

Write the equation for the response and solve for the unknown coefficients:

$$v_C(t) = 100 + B_1 e^{-8000t} \cos 6000t + B_2 e^{-8000t} \sin 6000t \text{ V}, t \geq 0$$

$$v_C(0) = V_F + B_1 = V_0 \quad \therefore \quad 100 + B_1 = 50$$

$$\frac{dv_C(0)}{dt} = -\alpha B_1 + \omega_d B_2 = \frac{I_0}{C} \quad \therefore \quad -8000B_1 + 6000B_2 = 0$$

$$\Rightarrow \quad B_1 = -50 \text{ V}, \quad B_2 = 66.67 \text{ V}$$

$$v_C(t) = 100 - 50e^{-8000t} \cos 6000t + 66.67e^{-8000t} \sin 6000t \text{ V}, t \geq 0$$

