

EECS2200 Electric Circuits

Chapter 8 Part 2

Sinusoidal Steady State Power Calculation


EECS2200 Electric Circuits

Complex Power

Complex Power

Complex power is the complex sum of average power and reactive power, or:

$$S = P + jQ = |S| \angle \theta_{pf}$$

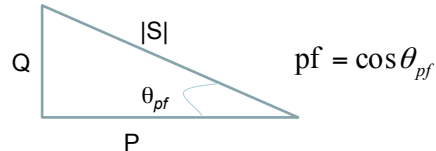


Notes:

- $|S|$ is apparent power
- θ_{pf} is the power factor angle
- Units for both complex power and apparent power are volt-amperes [VA]

Complex Power

- Apparent power $|S|$

$$|S| = \sqrt{P^2 + Q^2}$$

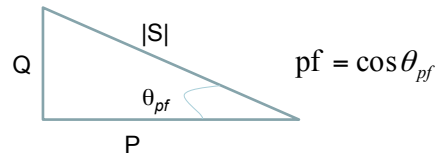


- Power factor angle

$$\frac{Q}{P} = \frac{(V_m I_m / 2) \sin(\theta_v - \theta_i)}{(V_m I_m / 2) \cos(\theta_v - \theta_i)} = \tan(\theta_v - \theta_i) = \tan \theta_{pf}$$

Activity 1

The power triangle that characterizes the impedance in a circuit is shown below. In its simplest form, the impedance is


- A. Purely resistive
- B. RL
- C. RC
- D. Purely capacitive

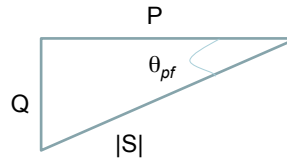

Activity 2

The power triangle shown here represents the power for which type of load?

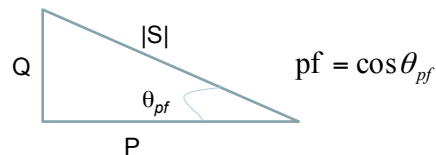- A. Purely resistive
- B. RL
- C. RC
- D. Can't tell from the triangle



Example

An electrical motor operates at 240 V rms.
The average power is 8 kW at a lagging power factor of 0.8.

- Calculate the complex power of the motor.
- Calculate the impedance of the motor.

Solution

A. Calculate the complex power

Given power factor is lagging, the load is inductive, i.e. $Q > 0$.

$$\theta_{pf} = \cos^{-1} pf = \cos^{-1} 0.8 = 36.87^\circ$$

$$P = 8000$$


$$Q/8000 = \tan 36.87^\circ$$

$$\Rightarrow Q = 6000 \text{ var}$$

$$|S| = \sqrt{P^2 + Q^2} = \sqrt{8000^2 + 6000^2}$$

$$= 10,000 \text{ VA}$$
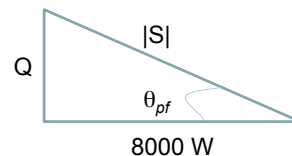
$$S = 8000 + j6000 \text{ VA} = 10,000 \angle 36.87^\circ \text{ VA}$$



Solution

B. Calculate the load impedance

How to find the load impedance, let's start from its definition.

$$Z_L = \frac{\mathbf{V}_L}{\mathbf{I}_L} = \frac{|\mathbf{V}_L|}{|\mathbf{I}_L|} \angle(\theta_v - \theta_i) = \frac{|\mathbf{V}_L|}{|\mathbf{I}_L|} \angle \theta_{pf} = \frac{|\mathbf{V}_L|}{|\mathbf{I}_L|} \angle 36.87^\circ$$

$$|\mathbf{V}_L| = 240 \text{ V}_{rms} \quad \text{but what about} \quad |\mathbf{I}_L| = I_{rms} ?$$

$$P = V_{rms} I_{rms} \text{ pf} \quad \Rightarrow \quad I_{rms} = \frac{P}{V_{rms} \text{ pf}} = \frac{8000}{(240)(0.8)} = 41.67 \text{ A}_{rms}$$

$$\therefore |Z_L| = \frac{V_{rms}}{I_{rms}} = \frac{240}{41.67} = 5.76 \Omega \quad \Rightarrow \quad Z_L = 5.76 \angle 36.87^\circ \Omega = 4.61 + j3.46 \Omega$$

EECS2200 Electric Circuits

Power Calculation

Power calculation


$$S = (V_m I_m / 2) \cos(\theta_v - \theta_i) + j(V_m I_m / 2) \sin(\theta_v - \theta_i)$$

$$S = \frac{V_m I_m}{2} [\cos(\theta_v - \theta_i) + j \sin(\theta_v - \theta_i)]$$

$$S = \frac{V_m I_m}{2} e^{j(\theta_v - \theta_i)} = \frac{V_m I_m}{2} \angle(\theta_v - \theta_i)$$

$$S = V_{rms} \angle \theta_v \times I_{rms} \angle -\theta_i$$
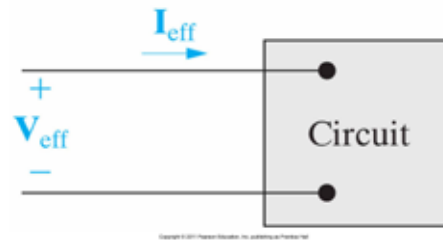
$$S = \mathbf{V}_{rms} \mathbf{I}_{rms}^* = \frac{1}{2} \mathbf{V} \mathbf{I}^*$$



Alternative Forms of Complex Power


$$S = \mathbf{V}_{rms} \mathbf{I}_{rms}^*, V_{rms} = \mathbf{I}_{rms} Z$$

$$\rightarrow S = \mathbf{I}_{rms}^* \mathbf{I}_{rms} Z = |\mathbf{I}_{rms}|^2 Z$$

$$S = |\mathbf{I}_{rms}|^2 (R + jX) = |\mathbf{I}_{rms}|^2 R + j |\mathbf{I}_{rms}|^2 X = P + jQ$$


$$\rightarrow P = |\mathbf{I}_{rms}|^2 R = \frac{1}{2} I_m^2 R$$

$$\rightarrow Q = |\mathbf{I}_{rms}|^2 X = \frac{1}{2} I_m^2 X$$

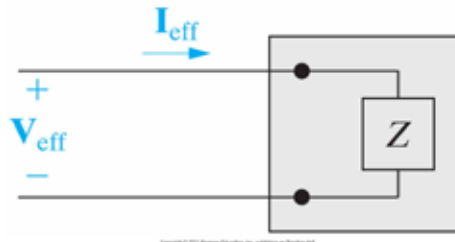

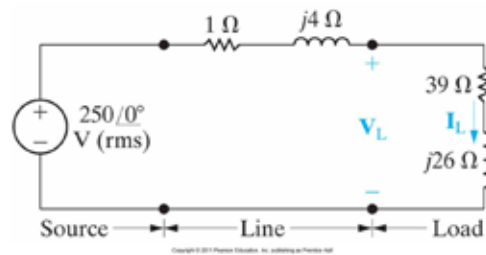Example

- Find \mathbf{I}_L and \mathbf{V}_L
- Calculate \mathbf{S} supplied by the source
- Calculate \mathbf{S} delivered to the load
- Calculate \mathbf{S} delivered to the line



Solution


Find \mathbf{I}_L and \mathbf{V}_L

$$\mathbf{I}_L = \frac{250\angle 0^\circ}{(1 + j4) + (39 + j26)} = \frac{250\angle 0^\circ}{40 + j30}$$

$$= (4 - j3) \text{ A} = 5\angle -36.87^\circ \text{ A (rms)}$$

$$\mathbf{V}_L = (39 + j26)\mathbf{I}_L$$

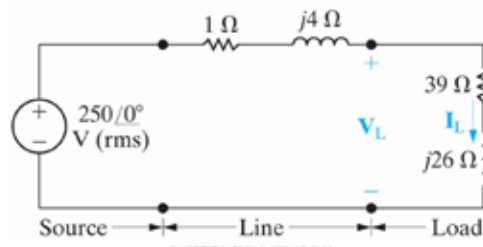
$$= (234 - j13) = 234.36\angle -3.18^\circ \text{ V (rms)}$$



Solution

Calculate S delivered to the load
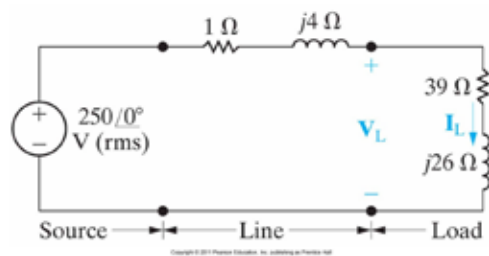
$$S = \mathbf{V}_L \mathbf{I}_L^* = (234 - j13)(4 + j3) = 975 + j650 \text{ VA}$$




Solution

Calculate S delivered to the line

$$P = |\mathbf{I}_{rms}|^2 R = 5^2 \times 1 = 25 \text{ W}$$

$$Q = |\mathbf{I}_{rms}|^2 X = 5^2 \times 4 = 100 \text{ VAR}$$


$$S = 25 + j100 \text{ VA}$$

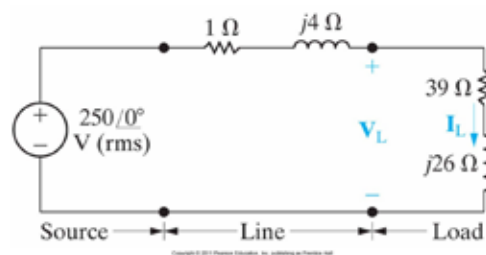

Solution


Calculate S supplied by the source

$$\begin{aligned} S &= S_{load} + S_{line} = 975 + j650 + 25 + j100 \\ &= 1000 + j750 \text{ VA} \end{aligned}$$

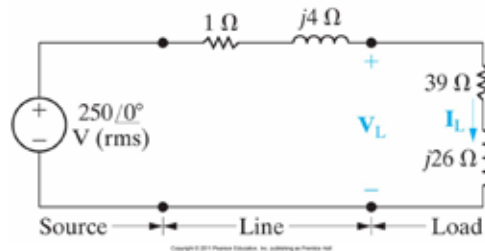

Activity 3

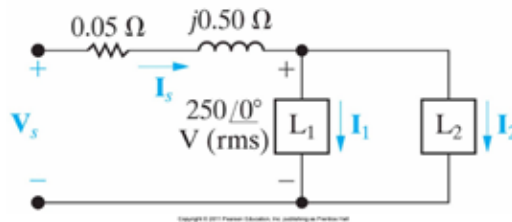Load 1 absorbs an average power of 8 kW and leading pf 0.8. Load 2 absorbs 20 kVA at lagging pf 0.6. Assume effective values for all.



- Find the pf of the 2 loads in parallel.
- Find magnitude of I_s and the apparent power to supply the load.
- Assuming 60 Hz, what is the capacitor required to correct the power factor

Solution

1. Find pf of 2 loads in parallel

$$\mathbf{I}_s = \mathbf{I}_1 + \mathbf{I}_2$$


$$S = 250\mathbf{I}_s^* = 250(\mathbf{I}_1 + \mathbf{I}_2)^* = 250\mathbf{I}_1^* + 250\mathbf{I}_2^* = S_1 + S_2$$

$$pf_1 = \cos \theta_1 = 0.8 \rightarrow \theta_1 = -36.87^\circ, \sin \theta_1 = -0.6$$

$$pf_2 = \cos \theta_2 = 0.6 \rightarrow \theta_2 = 53.13^\circ, \sin \theta_2 = 0.8$$

$$S_1 = P_1 + jQ_1 = 8000 + j \frac{8000 \times (-0.6)}{0.8} = 8000 - j6000 \text{ VA}$$
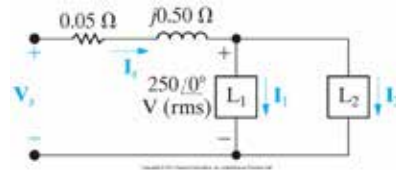
$$S_2 = P_2 + jQ_2 = 20000 \times 0.6 + j20000 \times 0.8 \\ = 12000 + j16000 \text{ VA}$$



Solution


$$\therefore S_1 = 8000 - j6000 \text{ VA}, S_2 = 12000 + j16000 \text{ VA}$$

$$\therefore S = 20000 + j10000 \text{ VA}$$

$$\mathbf{I}_s^* = \frac{S}{250} = \frac{20000 + j10000}{250} = 80 + j40 \text{ A}$$

$$\mathbf{I}_s = 80 - j40 \text{ A} = 89.44 \angle -26.57^\circ \text{ A}$$
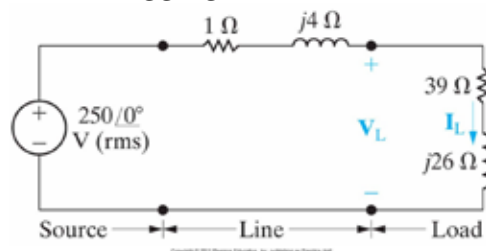
$$pf = \cos(0 - (-26.57^\circ)) = 0.8944 \text{ lagging}$$



Solution


2. Find magnitude of I_s and apparent power,

$$\therefore \mathbf{I}_s = 80 - j40 \text{ A}$$

$$\therefore |\mathbf{I}_s| = |80 - j40| = \sqrt{80^2 + 40^2} = 89.44 \text{ A}$$


$$\therefore S = 20000 + j10000$$

$$\therefore |S| = |20000 + j10000| = \sqrt{20000^2 + 10000^2} = 22.36 \text{ KVA}$$

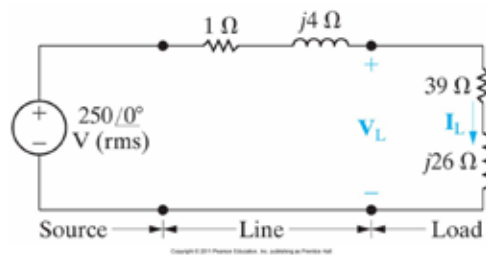


Solution

Using power triangle

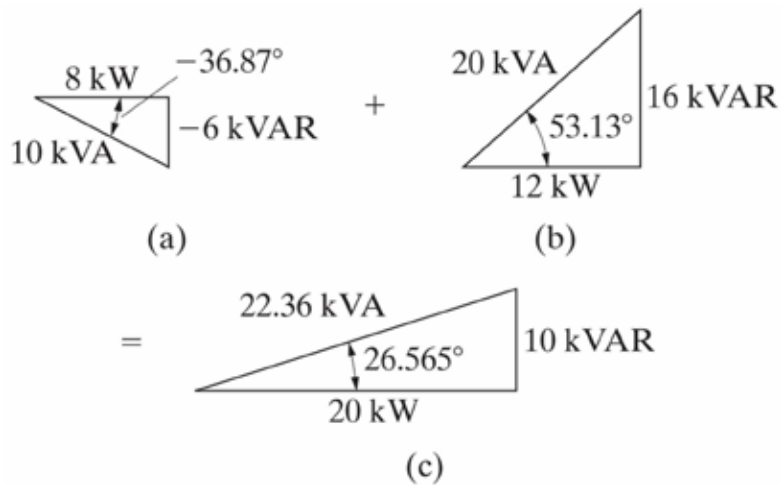

Solution

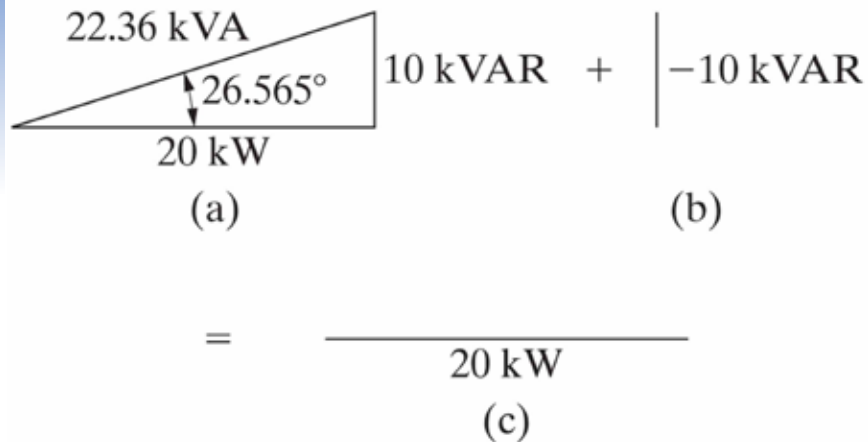3. Assuming 60 Hz, what is the capacitor required to correct the power factor



Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Solution

3. Assuming 60 Hz, what is the capacitor required to correct the power factor


$$Q = \frac{|V_{eff}|^2}{X} = -10000$$

$$X = \frac{250^2}{-10000} = -6.25\Omega, X = \frac{-1}{\omega C}$$

$$C = \frac{-1}{\omega X} = \frac{-1}{2\pi fX} = \frac{1}{2 \times 3.1416 \times 60 \times 6.25} = 424.4\mu F$$

Example: Power Balance

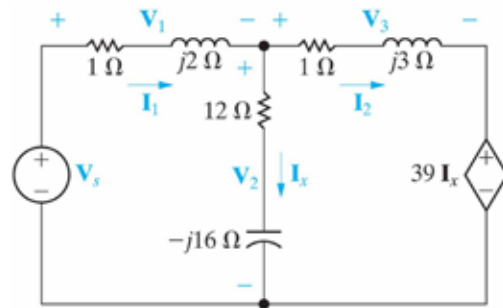- A. Find the total average and reactive power delivered to each impedance.
- B. Find the average and reactive powers for each source.



$$\begin{aligned} \mathbf{V}_s &= 150 \angle 0^\circ \text{ V} \\ \mathbf{V}_1 &= (78 - j104) \text{ V} & \mathbf{I}_1 &= (-26 - j52) \text{ A} \\ \mathbf{V}_2 &= (72 + j104) \text{ V} & \mathbf{I}_x &= (-2 + j6) \text{ A} \\ \mathbf{V}_3 &= (150 - j130) \text{ V} & \mathbf{I}_2 &= (-24 - j58) \text{ A} \end{aligned}$$

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall


Solution: Power Balance

- A. Find the total average and reactive power delivered to each impedance.

$$\begin{aligned} S_1 &= \frac{1}{2} \mathbf{V}_1 \mathbf{I}_1^* = \frac{1}{2} (78 - j104)(-26 - j52) \\ &= 1690 + j3380 \text{ VA} \end{aligned}$$

$$\begin{aligned} S_2 &= \frac{1}{2} \mathbf{V}_2 \mathbf{I}_x^* = \frac{1}{2} (72 + j104)(-2 + j6) \\ &= 240 - j320 \text{ VA} \end{aligned}$$
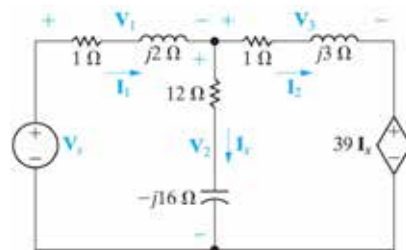
$$\begin{aligned} S_3 &= \frac{1}{2} \mathbf{V}_3 \mathbf{I}_2^* = \frac{1}{2} (150 - j130)(-24 + j58) \\ &= 1970 + j5910 \text{ VA} \end{aligned}$$



$$\begin{aligned} \mathbf{V}_s &= 150 \angle 0^\circ \text{ V} \\ \mathbf{V}_1 &= (78 - j104) \text{ V} & \mathbf{I}_1 &= (-26 - j52) \text{ A} \\ \mathbf{V}_2 &= (72 + j104) \text{ V} & \mathbf{I}_x &= (-2 + j6) \text{ A} \\ \mathbf{V}_3 &= (150 - j130) \text{ V} & \mathbf{I}_2 &= (-24 - j58) \text{ A} \end{aligned}$$

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Solution: Power Balance

B. Find the average and reactive powers for each source.


$$S_s = -\frac{1}{2} \mathbf{V}_s \mathbf{I}_1^* = -\frac{1}{2} (150)(-26 - j52)$$

$$= 1950 - j3900 \text{ VA}$$

$$S_x = \frac{1}{2} (39 \mathbf{I}_x) \mathbf{I}_2^*$$

$$= \frac{1}{2} (-78 + j234)(-24 + j58)$$

$$= -5850 - j5070 \text{ VA}$$

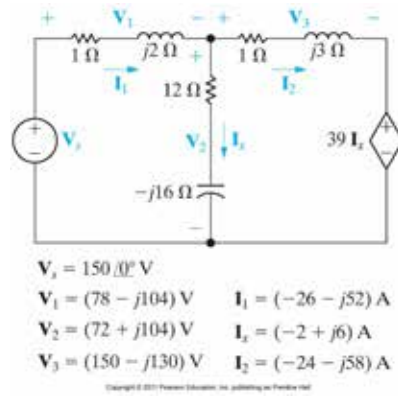

Solution: Power Balance

Verify power balance:

1. Total power absorbed by the passive impedances and the independent source.

$$P_{\text{absorbed}} = P_1 + P_2 + P_3 + P_s = 1690 + 240 + 1970 + 1950 = 5850 \text{ W}$$

2. Total power delivered (by dependent source)

$$P_{\text{delivered}} = P_x = -5850 \text{ W}$$

$$P_{\text{absorbed}} = P_{\text{delivered}}$$

3. Reactive power absorbed:

$$Q_{\text{absorbed}} = Q_1 + Q_3 = 3380 + 5910 = 9290 \text{ VAR}$$

4. Reactive power delivered:


$$Q_{\text{delivered}} = Q_2 + Q_s + Q_x = 320 + 3900 + 5070 = 9290 \text{ VAR}$$

$$Q_{\text{absorbed}} = Q_{\text{delivered}}$$

Maximum Power Transfer

Maximum Power Transfer

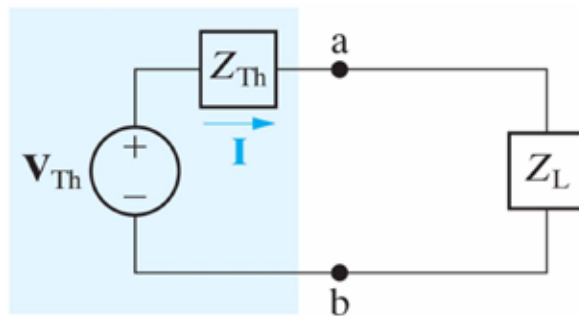- Assume the source is replaced by its Thevenin equivalent circuits.
- V_{TH} , Z_{TH} and a load or Z_L is connected



Copyright © 2011 Pearson Education, Inc. publishing as Pearson Hall

Maximum Power Transfer

$$I = \frac{V_{TH}}{(R_{TH} + R_L) + j(X_{TH} + X_L)}$$

$$P = |I|^2 R_L$$

$$P = \frac{|V_{TH}|^2 R_L}{(R_{TH} + R_L)^2 + (X_{TH} + X_L)^2}$$

$$\frac{\partial P}{\partial R_L} = 0, \frac{\partial P}{\partial X_L} = 0$$

$$X_L = X_{TH}, R_L = \sqrt{R_{TH}^2 + (X_L + X_{TH})^2}$$

$$Z_L = Z_{TH}^*$$


Restriction on Z_L

- R_L and X_L may be restricted to a limited range of values.
 - Set X_L as near to $-X_{TH}$ as possible
 - Set R_L as close to $R_L = \sqrt{R_{TH}^2 + (X_L + X_{TH})^2}$ as possible
- The magnitude of Z_L can be varied but its phase angle cannot.
 - Set $|Z_L| = |Z_{TH}|$

Example

Determine Z_L that results in maximum average power transferred to Z_L .

Find the maximum average power.

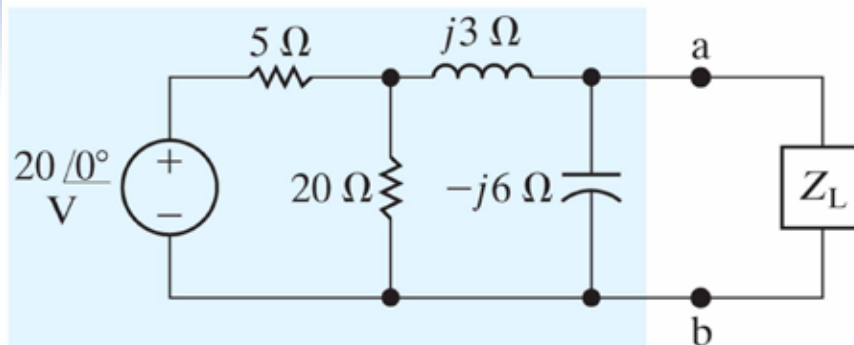

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall


Solution

A. Determine the Z_L .

First, perform source transformation, then calculate V_{Th}

$$V_{Th} = \frac{-j6}{4 + j3 - j6} \times 16 = \frac{16(18 - j24)}{25} = \frac{96}{5}(0.6 - j0.8)$$
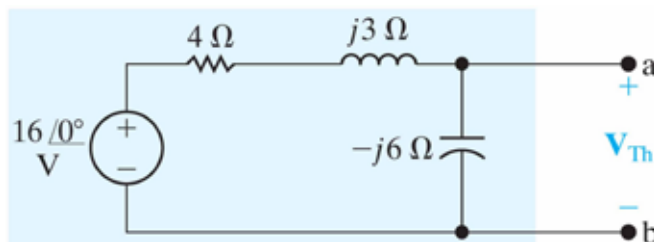
$$= 19.2 \angle -53.13^\circ = 11.52 - j15.36V$$



Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall


Solution

A. Determine the Z_L .

Calculate Z_{Th} , deactivate voltage source

$$Z_{Th} = (4 + j3) // (-j6) = \frac{(4 + j3)(-j6)}{4 + j3 - j6} = \frac{6(24 - j7)}{25}$$

$$= 5.76 - j1.68\Omega$$

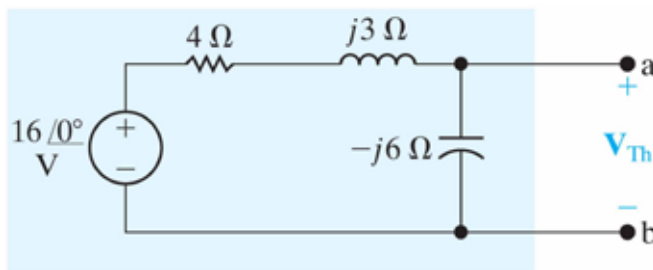


Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Solution

$$\therefore Z_{Th} = 5.76 - j1.68\Omega$$
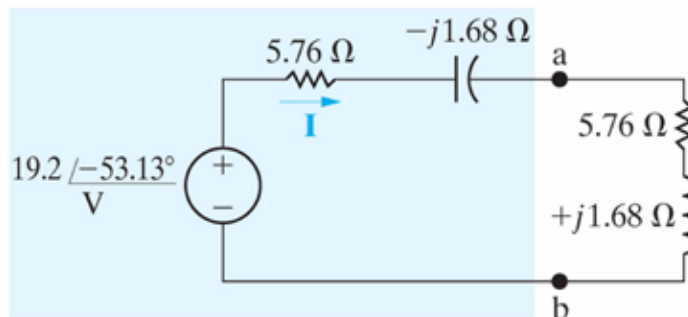
$$\therefore Z_L = Z_{Th}^* = 5.76 + j1.68\Omega$$




Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Solution

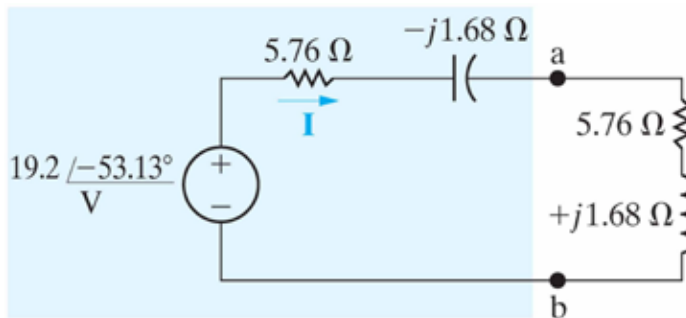B. Find the maximum power

$$I_{eff} = \frac{19.2 / \sqrt{2}}{5.76 + 5.76} \text{ A}$$

$$P = I_{eff}^2 (5.76) = \frac{19.2^2}{2 \times 4 \times 5.76} = 8 \text{ W}$$




Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Example: Load with Restriction

A. Find Z_L for maximum average power.

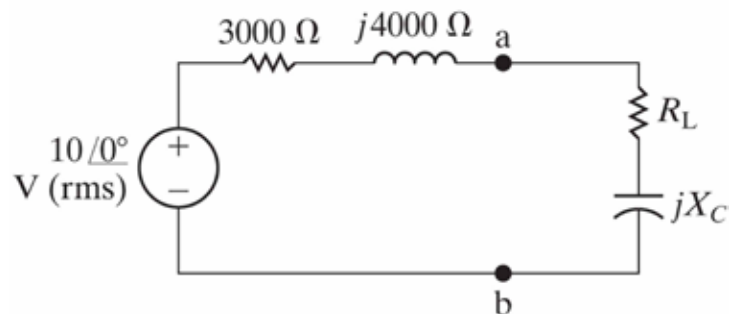B. If R_L can be varied from 0 to 4000Ω and X_C is restricted to $0 \sim -2000\Omega$, what settings of R_L and X_C transfer the most average power?



Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Solution: Load with Restriction


A. Find Z_L for maximum average power.

$$\therefore Z_{Th} = (3000 + j4000)\Omega$$

$$\therefore Z_L = Z_{Th}^* = 3000 - j4000\Omega$$

$$I_{eff} = \frac{10}{2 \times 3000} A$$
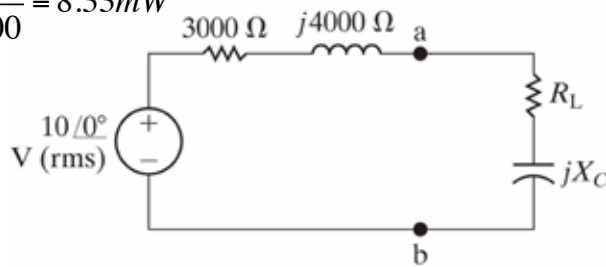
$$P_{max} = \frac{I_{eff}^2}{3000} = \frac{10^2}{4 \times 3000} = 8.33mW$$



Copyright © 2011 Pearson Education, Inc. publishing as Pearson Hall


Solution: Load with Restriction

B. If R_L can be varied from 0 to 4000 ohm and X_C is restricted to 0~-2000ohm, what settings of R_L and X_C transfer the most average power?

First, set X_L as close to -4000Ω as possible, $X_L = -2000\Omega$

$$R_L = \sqrt{R_{Th}^2 + (X_L + X_{Th})^2} = \sqrt{3000^2 + (-2000 + 4000)^2} = 3605.55\Omega$$

$$Z_L = 3605.55 - j2000\Omega$$

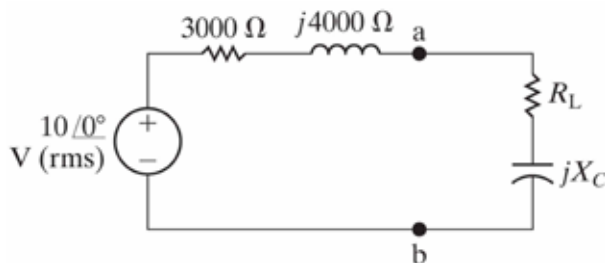

Copyright © 2011 Pearson Education, Inc. publishing as Pearson Hall


Solution: Load with Restriction

B. If R_L can be varied from 0 to 4000 ohm and X_C is restricted to 0~-2000ohm, what settings of R_L and X_C transfer the most average power?


First, set X_L as close to -4000Ω as possible, $X_L = -2000\Omega$

$$I_{eff} = \frac{10\angle 0^\circ}{6605.55 + j2000} = 1.4489\angle -16.85^\circ \text{ mA}$$
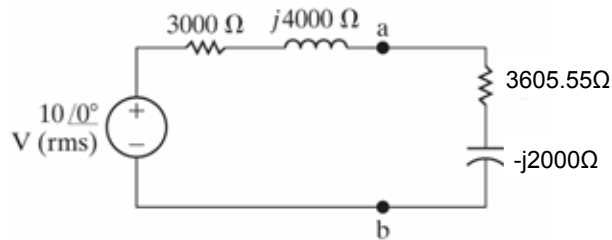
$$P = (1.4489\angle -16.85^\circ)^2 \times 3605.55 \approx 7.57 \text{ mW}$$




A Handheld Hair Dryer

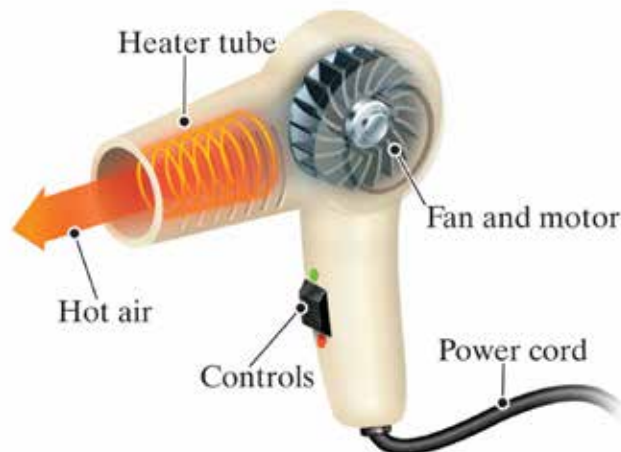


Copyright © 2011 Pearson Education, Inc. publishing as Pearson Hall

A circuit diagram for the hair dryer

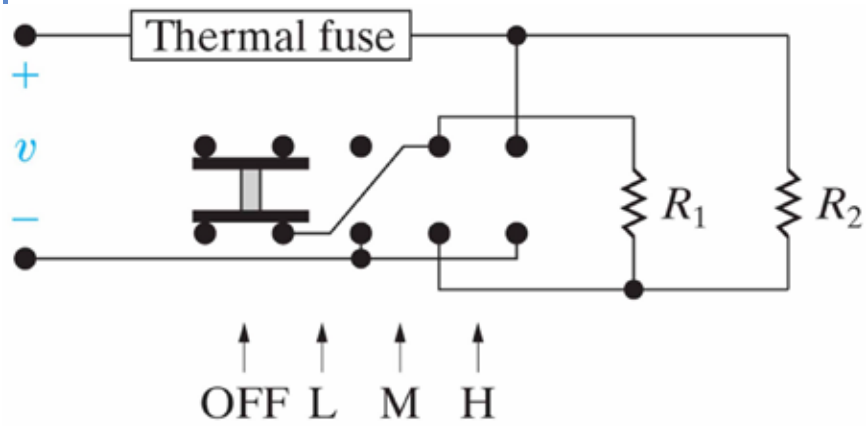


Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Equivalent Circuit

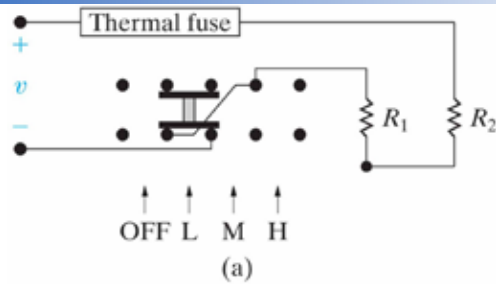


(a)

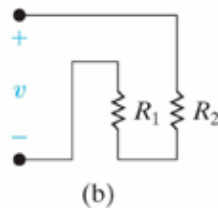

(b)


Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Equivalent Circuit

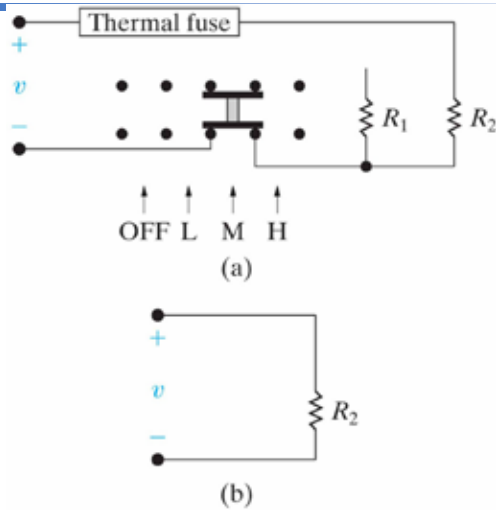

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Equivalent Circuit

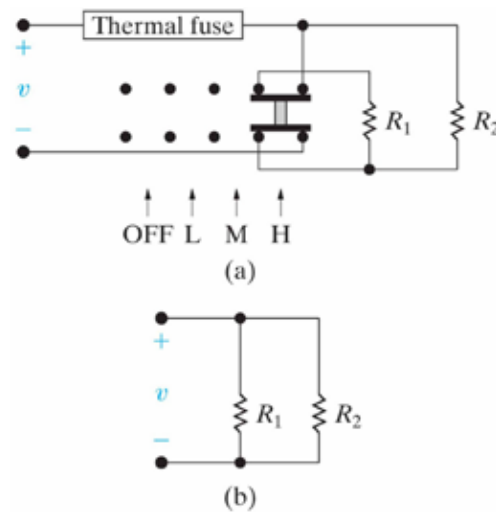

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall