

EECS2200 Electric Circuits

Chapter 8 Part 3

Sinusoidal Steady State Power Calculation

EECS2200 Electric Circuits

Transformer

Analysis of Linear Transformer Circuit

$$V_s = I_1(Z_s + R_1 + j\omega L_1) - I_2 j\omega M$$


$$0 = -j\omega M I_1 + I_2(R_2 + j\omega L_2 + Z_L)$$

$$j\omega M I_1 = I_2(R_2 + j\omega L_2 + Z_L)$$

$$I_2 = \frac{j\omega M I_1}{(R_2 + j\omega L_2 + Z_L)}$$

$$Z_{11} = Z_s + R_1 + j\omega L_1$$

$$Z_{22} = Z_L + R_2 + j\omega L_2$$

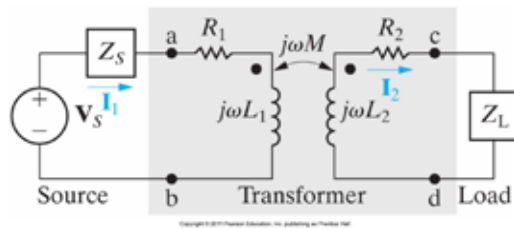

Analysis of Linear Transformer Circuit


$$V_s = I_1(Z_s + R_1 + j\omega L_1) - I_2 j\omega M$$

$$0 = -j\omega M I_1 + I_2(R_2 + j\omega L_2 + Z_L)$$

$$I_1 = \frac{Z_{22}}{Z_{11}Z_{22} + \omega^2 M^2} V_s$$

$$I_2 = \frac{j\omega M}{Z_{22}} I_1 = \frac{j\omega M}{Z_{11}Z_{22} + \omega^2 M^2} V_s$$
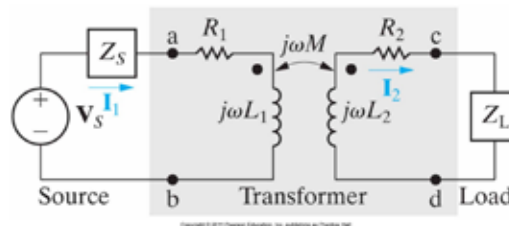
$$\frac{V_s}{I_1} = Z_{\text{int}} = Z_{11} + \frac{\omega^2 M^2}{Z_{22}}$$




Analysis of Linear Transformer Circuit

$$Z_{ab} = Z_{\text{int}} - Z_s = Z_{11} + \frac{\omega^2 M^2}{Z_{22}} - Z_s$$

$$= Z_s + R_1 + j\omega L_1 + \frac{\omega^2 M^2}{Z_{22}} - Z_s$$

$$= R_1 + j\omega L_1 + \frac{\omega^2 M^2}{Z_{22}}$$

Reflected Impedance

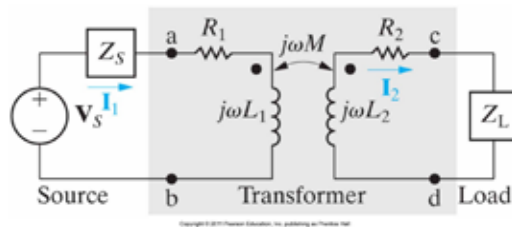

Reflected Impedance


$$Z_{\text{reflected}} = \frac{\omega^2 M^2}{Z_{22}}$$

$$Z_{\text{reflected}} = \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L}$$

$$Z_{\text{reflected}} = \frac{\omega^2 M^2}{R_2 + j\omega L_2 + R_L + j\omega X_L}$$

$$Z_{\text{reflected}} = \frac{\omega^2 M^2}{(R_2 + R_L) + j\omega(L_2 + X_L)}$$

$$Z_{\text{reflected}} = \frac{\omega^2 M^2}{|Z_{22}|^2} [(R_2 + R_L) - j\omega(L_2 + X_L)]$$

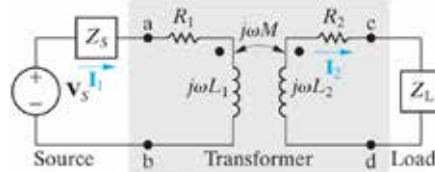

The complex conjugate of the self impedance of the secondary circuit scaled by a factor

Example

The parameters of a linear transformer are $R_1=200\Omega$, $R_2=100\Omega$, $L_1=9H$, $L_2=4H$, $k=0.5$. The transformer couples an impedance consists of an 800Ω resistor in series with a $1\mu F$ capacitor to a sinusoidal voltage source. The $300V(\text{rms})$ source has an internal impedance of $500+j100\Omega$ and a frequency of 400 rad/s .

Note: $M = k\sqrt{L_1 L_2}$

- Construct a frequency-domain equivalent circuit.
- Find the impedance seen looking into the primary terminals of the transformer.
- Find the Thevenin equivalent with respect to the terminals of load.

Solution


- Frequency domain equivalent circuit.

Given: $R_1=200\Omega$, $R_2=100\Omega$, $L_1=9H$, $L_2=4H$, $k=0.5$, $C=1\mu F$, $\omega=400\text{rad/s}$

$$j\omega L_1 = j400 \times 9 = j3600\Omega, j\omega L_2 = j400 \times 4 = j1600\Omega$$

$$M = k\sqrt{L_1 L_2} = 0.5\sqrt{9 \times 4} = 3H, j\omega M = j400 \times 3 = j1200\Omega$$
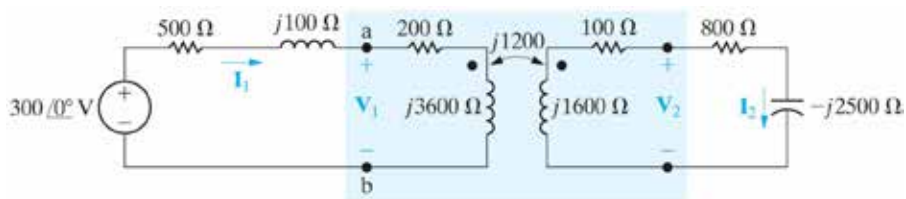
$$\frac{1}{j\omega C} = -j \frac{10^6}{400 \times 1} = -j2500\Omega$$




Solution

B. Find the Thevenin equivalent.

$$V_{Th} = V_2 = I_2 Z_{22} = \frac{j\omega M}{Z_{22}} I_1 Z_{22} = j\omega M I_1 = j1200 I_1$$

$$I_1 = \frac{300 \angle 0^\circ}{700 + j3700} = 79.67 \angle -79.29^\circ \text{ mA}$$
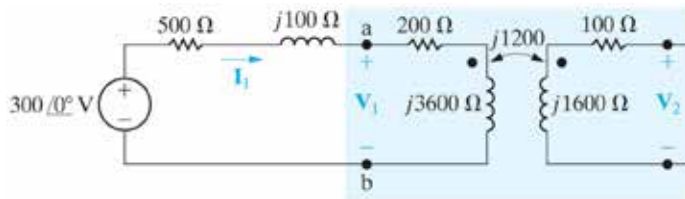
$$\therefore V_{Th} = j1200 \times 79.67 \angle -79.29^\circ \times 10^{-3} = 95.60 \angle 10.71^\circ \text{ V}$$



Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall


Solution

The Thevenin impedance will be equal to the impedance of secondary winding plus the impedance reflected from the primary when the voltage source is replaced by a short-circuit.

$$\begin{aligned} R_{Th} &= R_2 + j\omega L_2 + \frac{\omega^2 M^2}{|Z_{11}|^2} \\ &= 100 + j1600 + \frac{(1200)^2}{|700 + j3700|^2} (700 - j) \\ &= 171.09 + j1224.26 \Omega \end{aligned}$$

Solution


The Thevenin equivalent circuit

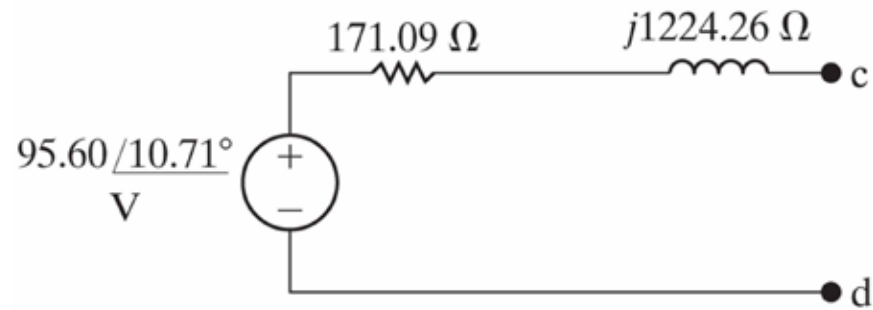

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Ideal Transformer

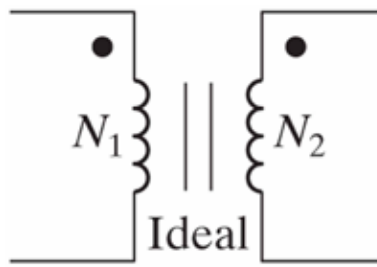- Two magnetically coupled coils having N_1 and N_2 turns, respectively, and exhibiting three properties
 - The coefficient of coupling is unity ($k=1$)
 - The self-inductance of each coil is infinite ($L_1=L_2=\infty$)
 - The coil losses are negligible.




Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall





Voltage and Current Ratio

■ Voltage ratio: $\frac{V_1}{N_1} = \frac{V_2}{N_2}$

■ Current ratio: $I_1 N_1 = I_2 N_2$

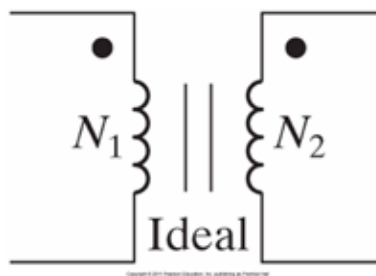


Polarity of the Voltage and Current

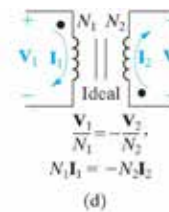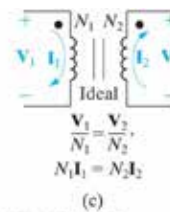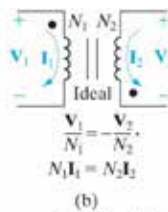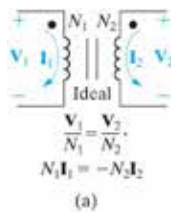

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

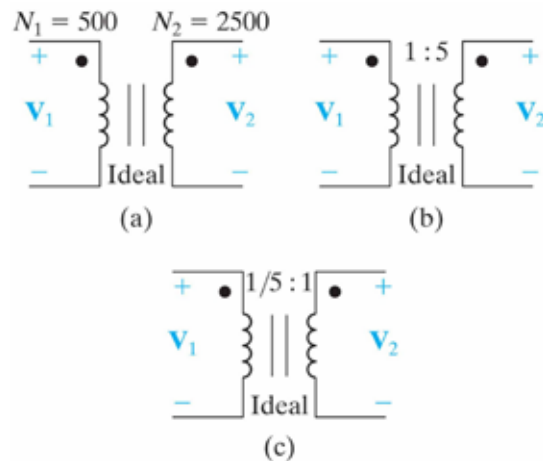Example

- Three ways to show that the turns ratio of an ideal transformer is 5.




Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Example


Transfer the following circuit to phasor domain circuit

Given $V_s = 2500 \cos(400t)$ V

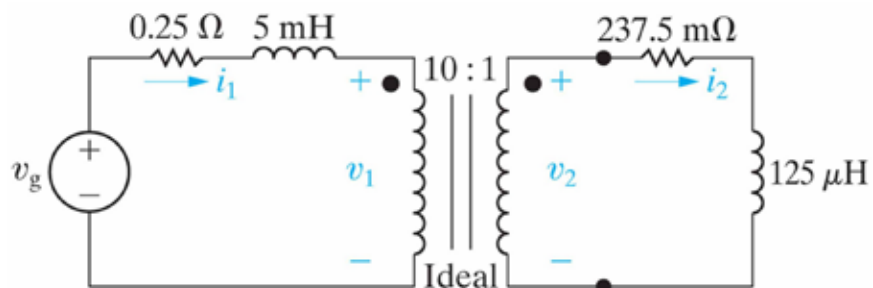

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall


Example: Phasor Domain Circuit

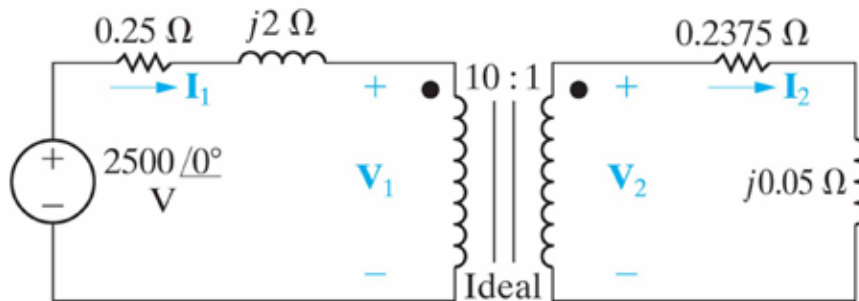

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Activity: Max Power Transfer

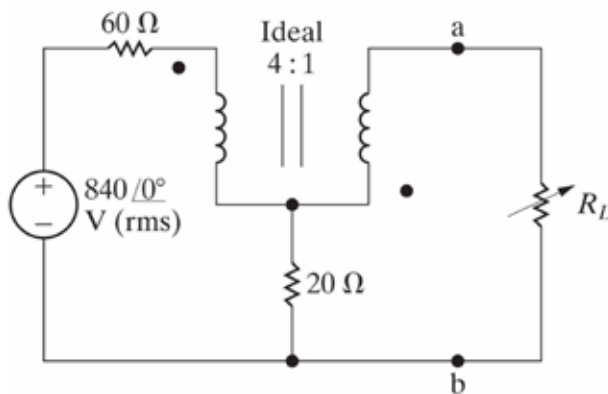The variable resistor is adjustable until maximum average power is delivered to R_L . What is the value of R_L ?



Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Solution

First find the Thévenin equivalent.

For ideal transformer, we have:


$$V_2 = \frac{1}{4}V_1, \quad I_1 = -\frac{1}{4}I_2$$

Open circuit $I_2=0$, so $I_1=0$

$$\therefore V_1 = 840\angle 0^\circ \text{ V}$$

$$\therefore V_2 = \frac{1}{4}V_1 = 210\angle 0^\circ \text{ V}$$
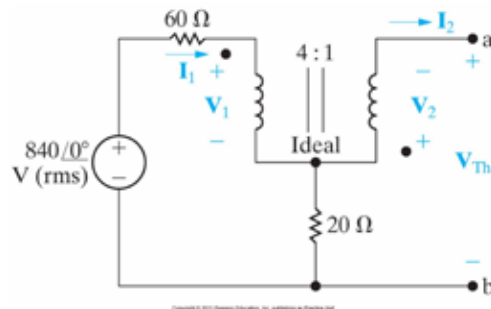
$$V_{Th} = -V_2 = -210\angle 0^\circ \text{ V}$$



Solution


To find the Thévenin impedance, short-circuit "ab" to calculate I_2 .

$$\begin{cases} 840\angle 0^\circ = 60I_1 + V_1 + 20(I_1 - I_2) \\ 0 = 20(I_2 - I_1) + V_2 \end{cases}$$

Note: $I_1 = -\frac{1}{4}I_2$


$$\begin{cases} 840\angle 0^\circ = -40I_2 + V_1 \\ 0 = 25I_2 + \frac{V_1}{4} \end{cases}$$
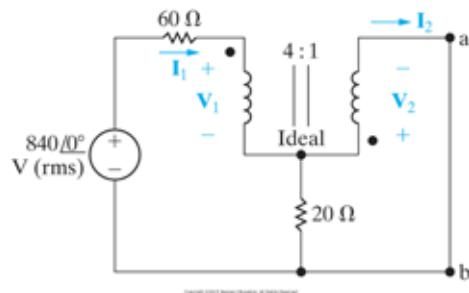
$$I_2 = -6\text{ A} \rightarrow R_{Th} = \frac{V_{Th}}{I_2} = \frac{-210\angle 0^\circ}{-6} = 35\Omega$$



Solution

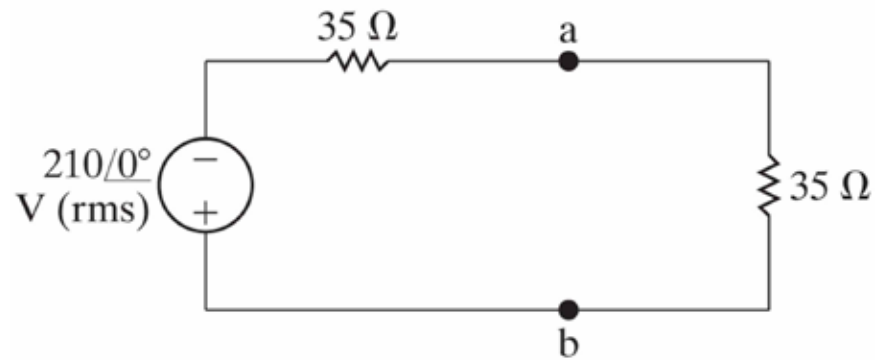Max power will be delivered to R_L when R_L equals to 35Ω



Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall