

EECS220 Summary

Chapter 1

- Standardized prefixes – p, n, u,m, k, M
- Definitions of current, voltage, and power
- Ideal basic circuit element
- Reference polarity – passive sign convention

Chapter 2

- Independent and dependent sources
- Ohm's Law
- KCL and KVL

Chapter 3

- Resistors in series and parallel connections
- Voltage and current dividers
- Delta-to-Wye

Chapter 4

- Definitions of essential node, essential path, mesh, planar circuit
- Simultaneous equations, $\#Eq = \#unknown$
- Node-voltage method, 2 special cases, supernode concept
- Mesh-current method, supermesh concept
- Source transformation
- Thevenin and Norton equivalent circuits
- Superposition
- Maximum power transfer condition

Node-Voltage Method

- Based on writing KCL equations at essential nodes
- Solves for node voltages
- The “recipe”:
 1. Identify the essential nodes
 2. Pick a reference node
 3. Label remaining essential nodes with voltage values
 4. Write a KCL equation at each non-reference essential node
 5. Put equations in standard form and solve
 6. Check your solutions by balancing power
 7. Calculate quantities of interest


Mesh-Current Method

- Uses KVL equations around meshes
- Solves directly for currents
- Special cases for dependent sources and for current sources in a mesh
- The “recipe”:
 1. Identify the meshes
 2. Label each with a mesh current
 3. Write a KVL equation around each mesh
 4. Put equations in standard form and solve
 5. Check your solutions by balancing power
 6. Calculate quantities of interest

Chapter 5


- Definitions of capacitor, inductor(transformer)
- C and L in series and parallel connections
- Definitions of natural and step responses
- Time constants
- Natural responses of RC and RL circuits
- Step responses of RC and RL circuits

Inductor and Capacitor comparison

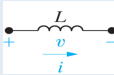	Inductor	Capacitor
Symbol		
Units	Henries [H]	Farads [F]
Describing equation	$v(t) = L \frac{di(t)}{dt}$	$i(t) = C \frac{dv(t)}{dt}$
Other equation	$i(t) = \frac{1}{L} \int_{t_o}^t v(\tau) d\tau + i(t_o)$	$v(t) = \frac{1}{C} \int_{t_o}^t i(\tau) d\tau + v(t_o)$
Initial condition	$i(t_o)$	$v(t_o)$
Behavior with const. source	If $i(t) = I$, $v(t) = 0$ → short circuit	If $v(t) = V$, $i(t) = 0$ → open circuit
Continuity requirement	$i(t)$ is continuous so $v(t)$ is finite	$v(t)$ is continuous so $i(t)$ is finite


Inductor and Capacitor comparison

	Inductor	Capacitor
Power	$p(t) = v(t)i(t) = Li(t) \frac{di(t)}{dt}$	$p(t) = v(t)i(t) = Cv(t) \frac{dv(t)}{dt}$
Energy	$w(t) = \frac{1}{2} Li(t)^2$	$w(t) = \frac{1}{2} Cv(t)^2$
Initial energy	$w_o(t) = \frac{1}{2} Li(t_o)^2$	$w_o(t) = \frac{1}{2} Cv(t_o)^2$
Trapped energy	$w(\infty) = \frac{1}{2} Li(\infty)^2$	$w(\infty) = \frac{1}{2} Cv(\infty)^2$
Series-connected	$L_{eq} = L_1 + L_2 + L_3$ $i_{eq}(t_o) = i(t_o)$	$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$ $v_{eq}(t_o) = v_1(t_o) + v_2(t_o) + v_3(t_o)$
Parallel-connected	$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$ $i_{eq}(t_o) = i_1(t_o) + i_2(t_o) + i_3(t_o)$	$C_{eq} = C_1 + C_2 + C_3$ $v_{eq}(t_o) = v(t_o)$

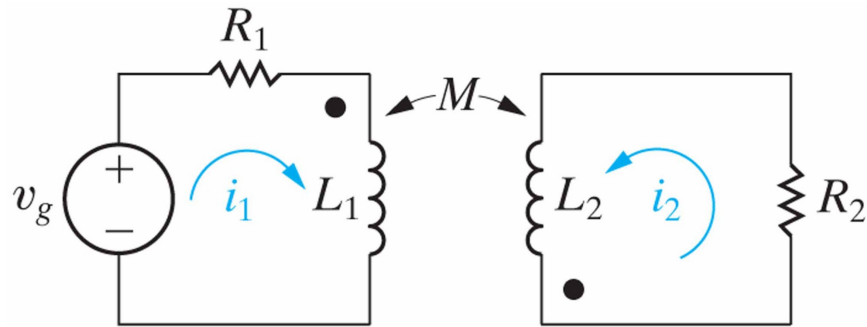

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

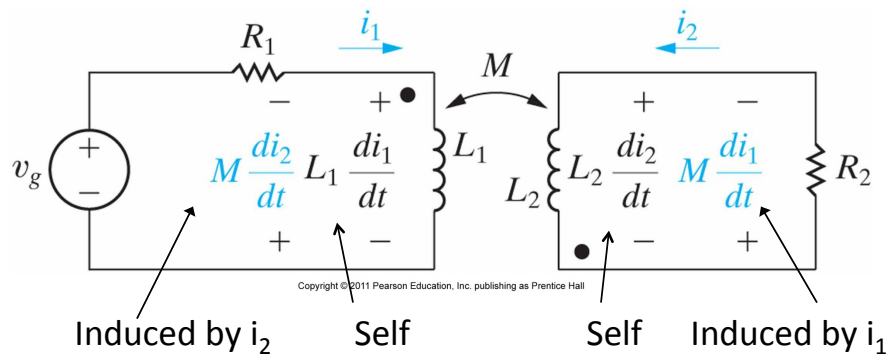Dot Convention: When the reference direction for a current entering (leaving) the dotted terminal in a coil, the reference polarity of the voltage that it induces in the other coil is positive (negative) at its dotted terminal.



Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

$$\begin{aligned}
 -v_g + i_1 R_1 + L_1 \frac{di_1}{dt} - M \frac{di_2}{dt} &= 0 \\
 i_2 R_2 + L_2 \frac{di_2}{dt} - M \frac{di_1}{dt} &= 0
 \end{aligned}$$

RL/RC Natural Response

1. Identify the variable of interest (hint – it's the variable that must be continuous in the circuit):
 - For RL, $i(t)$ through L
 - For RC, $v(t)$ across C
2. Find the initial value of this variable, either $i(0) = I_o$ or $v(0) = V_o$
 - From the problem statement.
 - By analyzing the circuit for $t < 0$, with L replaced by a short circuit or C replaced by an open circuit

RL/RC Natural Response

3. Find the time constant, τ
 - $\tau_{RL} = L/R_{eq}$ or $\tau_{RC} = R_{eq}C$
 - Note that R_{eq} is the equivalent resistance as seen from the inductor or capacitor for $t \geq 0$
4. Write the expression for the variable of interest:

$$x(t) = X_o e^{-t/\tau}, \quad t \geq 0$$
5. Use simple circuit analysis to calculate any other requested variables.

RL/RC Step (Natural) Response

1. Identify the variable of interest (hint – it's the variable that must be continuous in the circuit):
 - For RL, $i(t)$ through L
 - For RC, $v(t)$ across C
2. Find the initial value of this variable, either $i(0) = I_o$ or $v(0) = V_o$
 - From the problem statement
 - By analyzing the circuit for $t < 0$, with L replaced by a short circuit or C replaced by an open circuit

RL/RC Step (Natural) Response

3. Find the final value of this variable, either $i(\infty) = I_F$ or $v(\infty) = V_F$
 - If there is no source in the circuit as $t \rightarrow \infty$, the final value is 0 – this is the natural response problem!
 - Otherwise, analyze the circuit as $t \rightarrow \infty$, with L replaced by a short circuit or C replaced by an open circuit
4. Find the time constant, τ
 - $\tau_{RL} = L/R_{eq}$ or $\tau_{RC} = R_{eq}C$
 - Note that R_{eq} is the equivalent resistance as seen from the inductor or capacitor for $t \geq 0$

RL/RC Step (Natural) Response

5. Write the expression for the variable of interest:

$$x(t) = X_F + (X_o - X_F)e^{-t/\tau}, \quad t \geq 0$$

6. Use simple circuit analysis to calculate any other requested variables.

Chapter 6

- Forms of response of RLC circuits:
underdamped, critically damped, overdamped
- Natural response of parallel RLC circuits
- Natural response of series RLC circuits
- Step response of parallel and series RLC circuits

Natural Response of Parallel & Series RLC Circuits

The solutions are in the same form for parallel and series RLC circuits:

$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$	Overdamped
$v(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$	Underdamped
$v(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$	Critically damped

$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$	Overdamped
$i(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$	Underdamped
$i(t) = D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$	Critically damped

Series and Parallel RLC Circuits

- The difference(s) between the analysis of series RLC circuit and the parallel RLC circuit is/are:
 - A. The variable we calculate.
 - B. The describing differential equation.
 - C. The equations for satisfying the initial conditions

Step Response of RLC Circuits

- Generally speaking, the solution of a second-order DE with a constant driving force equals the forced response plus the a response function identical to the natural response.

$$i = I_f + \left\{ \begin{array}{l} \text{function of the same form} \\ \text{as natural response} \end{array} \right\}$$

$$v = V_f + \left\{ \begin{array}{l} \text{function of the same form} \\ \text{as natural response} \end{array} \right\}$$

- I_f or V_f is the non-zero final value.

Chapter 7

- Phasor transform and inverse phasor transform
- Impedance of R, L, C – R: I & V in-phase, L: I lags V by 90° , C: I leads V by 90°
- Phasor domain representation
- Sinusoid steady-state analysis
- Source transformation
- Thevenin equivalent

Phasor Domain Representation

- In the time domain
 - Ohm's law (only for resistors): $v = Ri$
 - KVL (around a loop): $v_1 + v_2 + \dots + v_n = 0$
 - KCL (at a node): $i_1 + i_2 + \dots + i_n = 0$
 - These three laws lead to all other time-domain circuit analysis techniques
- In the phasor domain
 - Ohm's law (for R, L, C): $\mathbf{V} = \mathbf{Z}\mathbf{I}$
 - KVL (around a loop): $\mathbf{V}_1 + \mathbf{V}_2 + \dots + \mathbf{V}_n = 0$
 - KCL (at a node): $\mathbf{I}_1 + \mathbf{I}_2 + \dots + \mathbf{I}_n = 0$
 - These three laws mean we can use all time-domain circuit analysis techniques in the phasor domain!

Steps in ACSS Analysis:

1. Redraw the circuit (the phasor transform does not change the components or their connections).
2. Phasor transform all known $v(t)$ and $i(t)$.
3. Represent unknown voltages and currents with V and I .
4. Replace component values with impedance (Z) values.
5. Use any circuit analysis method(s) to write equations and solve them with a calculator.
6. Inverse-transform the result, which is a phasor, back to the time domain.

Chapter 8

- Instantaneous power, average power, reactive power, complex power (power triangle)
- Power factor
- RMS values for power calculation
- Maximum average power transfer to the load (un-restricted and restricted)
- Transformer – reflected impedance, ideal transformer

Resistive, Inductive, Capacitive Circuits

- Resistors $P > 0, Q = 0$
 - Resistors absorb real power and have no reactive power
- Inductors $P = 0, Q > 0$
 - Inductors absorb reactive power and have no real power
- Capacitors $P = 0, Q < 0$
 - Capacitors generate reactive power and have no real power