


EECS2200 Electric Circuits

Chapter 4

Activities


Activity 1

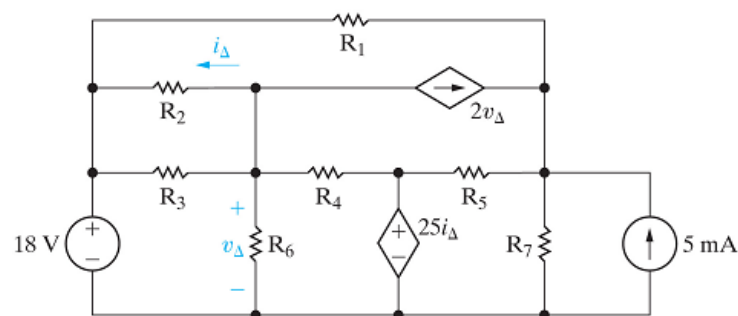How many essential nodes does this circuit have?




Solution

- 5 essential nodes

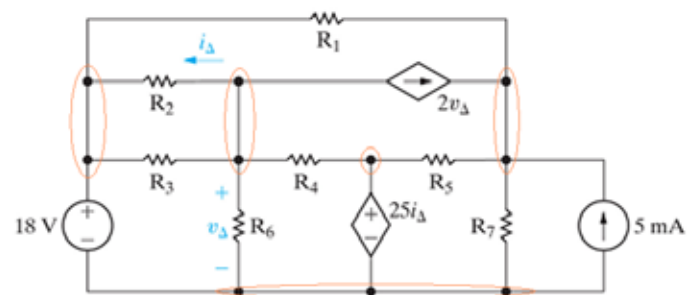


Activity 2

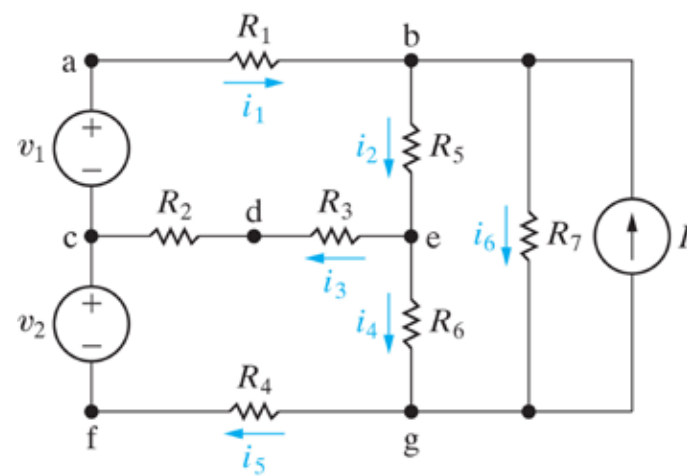Write simultaneous equations for below circuit.




Solution

- Need 6 equations for 6 unknown

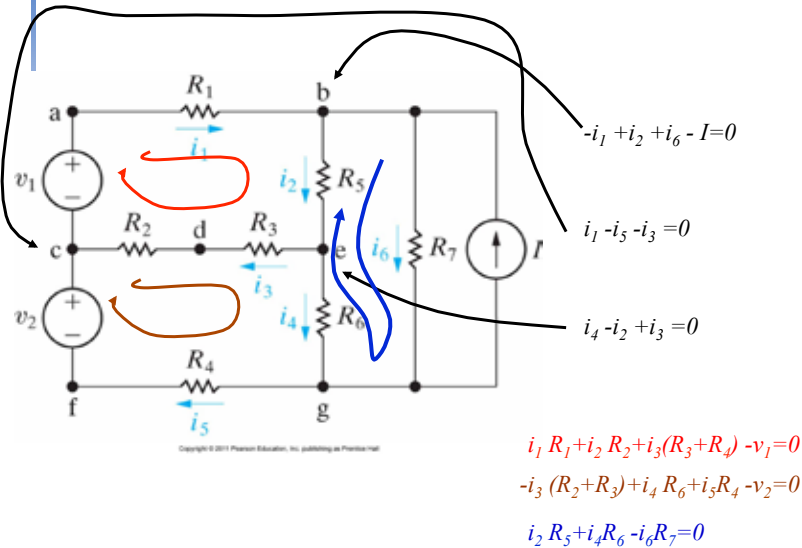


Activity 3

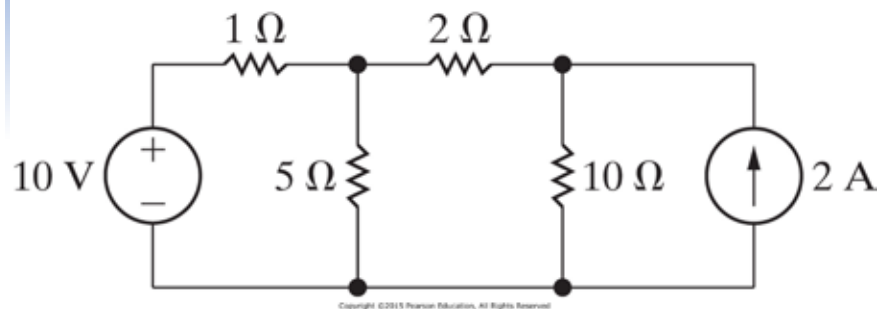Find voltages and currents for each resistor.



Solution

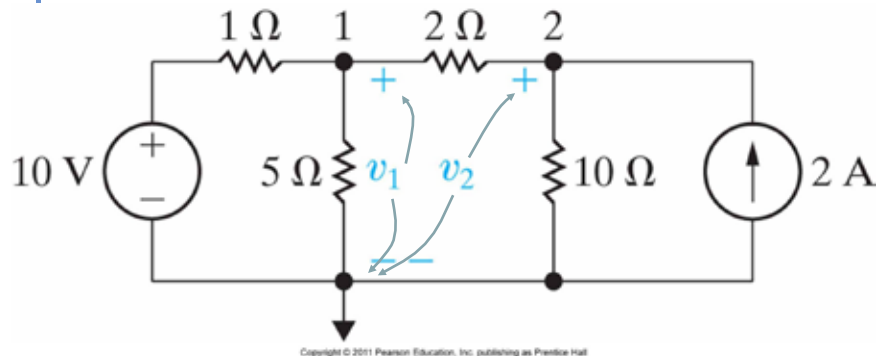

$$-\frac{10 - v_1}{1} + \frac{v_1}{5} + \frac{v_1 - v_2}{2} = 0 \quad -\frac{v_1 - v_2}{2} + \frac{v_2}{10} - 2 = 0$$

Solution

$$(1) -\frac{10 - v_1}{1} + \frac{v_1}{5} + \frac{v_1 - v_2}{2} = 0 \Rightarrow 10v_1 - 100 + 2v_1 + 5v_1 - 5v_2 = 0$$

$$(2) -\frac{v_1 - v_2}{2} + \frac{v_2}{10} - 2 = 0 \Rightarrow 5v_2 - 5v_1 + v_2 - 20 = 0$$


$$\begin{cases} 17v_1 - 5v_2 = 100 \\ -5v_1 + 6v_2 = 20 \end{cases}$$

$$\begin{cases} 102v_1 - 30v_2 = 600 \\ -25v_1 + 30v_2 = 100 \end{cases} \Rightarrow 77v_1 = 700$$

$$\therefore v_1 = 9.09V, v_2 = 10.91V$$

Activity 4

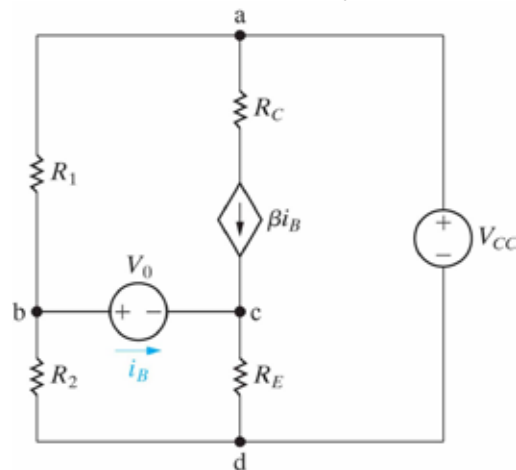Use supernode concept to find i_B .
(Same circuit as in Chapter 2 Activity 10)




Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Chapter 2 Activity 10

The circuit represents a common configuration encountered in the analysis and design of transistor amplifiers. Assume that the values of R_1 , R_2 , R_C , R_E , V_{CC} and V_0 are known.

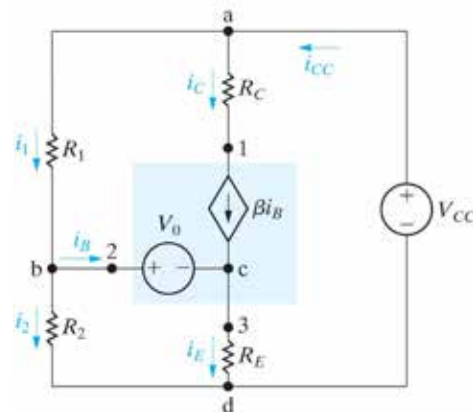Find i_B in terms of the circuit element values.



Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Chapter 2 Solution

Apply KCL to nodes a, b, c, and 1, we have:

$$(1) \quad i_1 + i_C - i_{CC} = 0$$

$$(2) \quad i_B + i_2 - i_1 = 0$$

$$(3) \quad i_E - i_B - i_C = 0$$

$$(4) \quad i_C = \beta i_B$$

Apply KVL to 2 loops bcdb and badb, we have:

$$(5) \quad V_0 + i_E R_E - i_2 R_2 = 0$$

$$(6) \quad -i_1 R_1 + V_{CC} - i_2 R_2 = 0$$

Chapter 2 Solution

Solve Eq.(6) for i_1 and substitute i_1 into Eq. (2)

$$i_1 = \frac{V_{CC} - i_2 R_2}{R_1}$$

$$\frac{V_{CC} - i_2 R_2}{R_1} = i_B + i_2 \Rightarrow i_2 = \frac{V_{CC} - i_B R_1}{R_1 + R_2}$$

Substitute i_2 to Eq.(5), solve for i_E

$$\frac{V_0 + i_E R_E}{R_2} = \frac{V_{CC} - i_B R_1}{R_1 + R_2} \Rightarrow i_E = \left(\frac{(V_{CC} - i_B R_1) R_2}{(R_1 + R_2) R_E} - \frac{V_0}{R_E} \right)$$

Chapter 2 Solution


Substitute i_E into Eq. (3), and use Eq.(4) to eliminate i_C in Eq.(3), we have:

$$\frac{(V_{CC} - i_B R_1) R_2}{(R_1 + R_2) R_E} - \frac{V_0}{R_E} = i_B (1 + \beta)$$

$$\therefore i_B = \frac{V_{CC} R_2 / (R_1 + R_2) - V_0}{R_1 R_2 / (R_1 + R_2) + (1 + \beta) R_E}$$


Solution

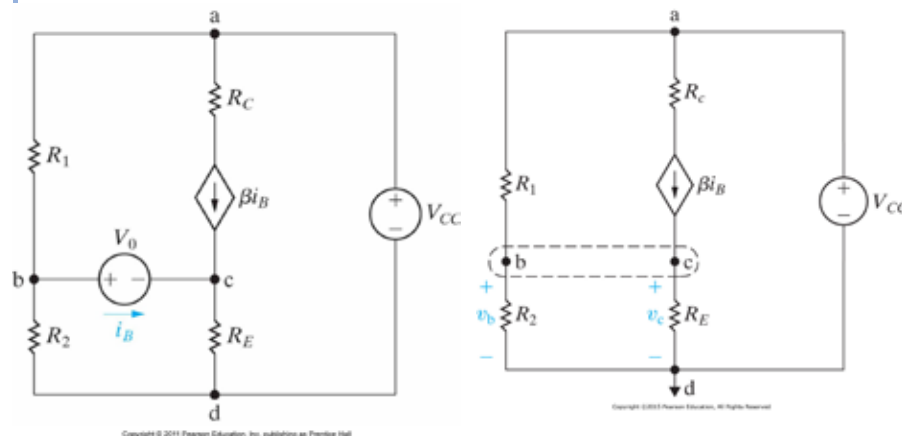- Apply supernode concept to nodes b and c.



Solution

Write KCL at supernode:

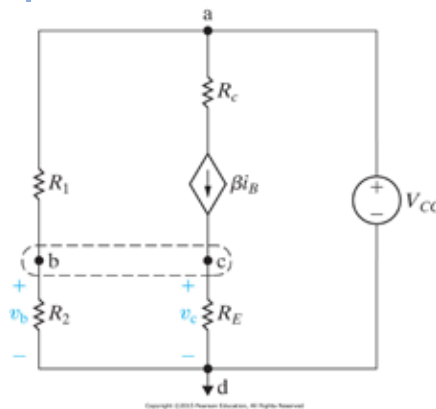

$$\frac{v_b - V_{CC}}{R_1} + \frac{v_b}{R_2} + \frac{v_c}{R_E} - \beta i_B = 0$$

Need 2 more equations
to get rid of v_c and v_b

$$v_b - v_c = V_o$$

$$v_c = (i_B + \beta i_B) R_E$$

Solution

Solve 3 equations for i_B :
(compared to 6 equations in Chapter 2)

$$\frac{v_c + V_o - V_{CC}}{R_1} + \frac{v_c + V_o}{R_2} + \frac{v_c}{R_E} - \beta i_B = 0$$


$$\Rightarrow \frac{(R_1 + R_2)v_c + (R_1 + R_2)V_o - R_2V_{CC}}{R_1R_2} + i_B + \beta i_B - \beta i_B = 0$$

$$\Rightarrow (R_1 + R_2)(1 + \beta)i_B R_E + R_1R_2i_B = R_2V_{CC} - (R_1 + R_2)V_o$$

$$\Rightarrow i_B = \frac{R_2V_{CC} - (R_1 + R_2)V_o}{R_1R_2 + (R_1 + R_2)(1 + \beta)R_E} = \frac{(R_2V_{CC})/(R_1 + R_2) - V_o}{R_1R_2/(R_1 + R_2) + (1 + \beta)R_E}$$

Activity 5

- Find currents in i_1 , i_2 , and i_3 .

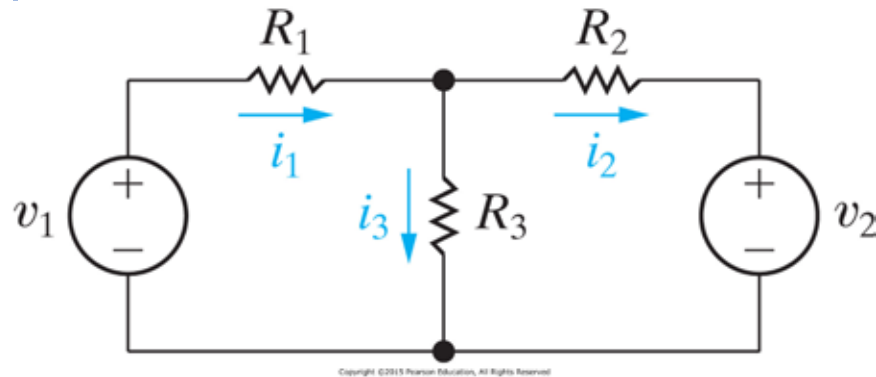


Solution

- Use mesh-current method, there are two meshes for two KVL equations


$$i_a R_1 + R_3(i_a - i_b) = v_1$$

$$R_3(i_b - i_a) + i_b R_2 = -v_2$$

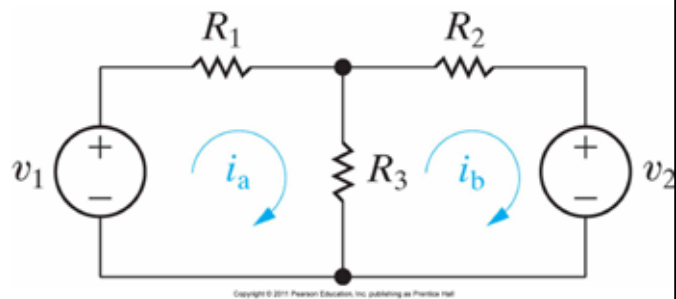


Activity 6

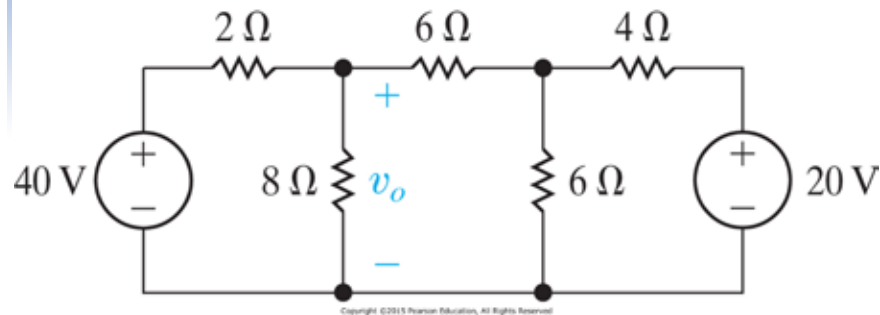- Use the mesh-current method to determine the power associated with each voltage source in the circuit.



Solution

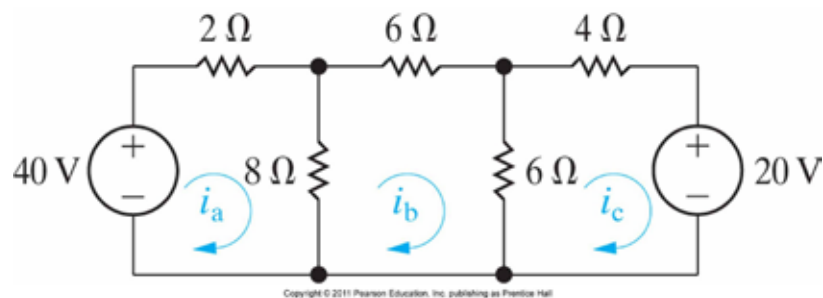

$$2i_a + 8(i_a - i_b) - 40 = 0$$

$$6i_b + 6(i_b - i_c) + 8(i_b - i_a) = 0$$

$$4i_c + 20 + 6(i_c - i_b) = 0$$

Solution


$$\begin{cases} 2i_a + 8(i_a - i_b) - 40 = 0 \\ 6i_b + 6(i_b - i_c) + 8(i_b - i_a) = 0 \\ 4i_c + 20 + 6(i_c - i_b) = 0 \end{cases}$$

$$\begin{cases} 10i_a - 8i_b = 40 \\ -8i_a + 20i_b - 6i_c = 0 \\ -6i_b + 10i_c = -20 \end{cases} \Rightarrow \begin{cases} i_a = 5.6A \\ i_b = 2.0A \\ i_c = -0.8A \end{cases}$$

$$p_{40V} = -40i_a = -224W, p_{20V} = 20i_c = -16W$$


Activity 7

- Find i_B .

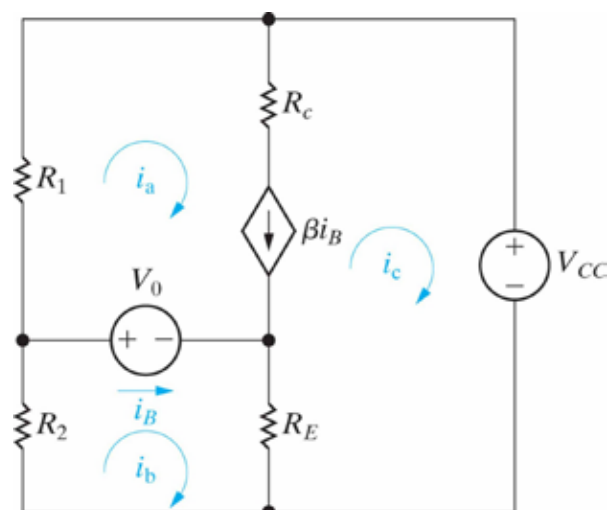

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Solution

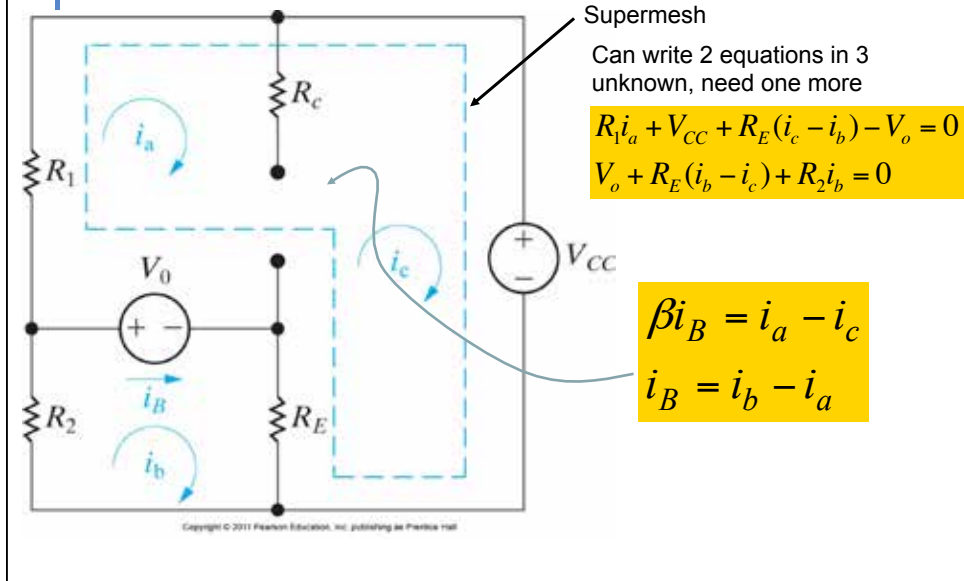

Solution

$$\begin{cases} \beta i_B = i_a - i_c \\ i_B = i_b - i_a \end{cases} \Rightarrow (1 + \beta) i_B = i_b - i_c$$

$$\begin{cases} R_1 i_a + V_{CC} + R_E (i_c - i_b) - V_o = 0 \\ V_o + R_E (i_b - i_c) + R_2 i_b = 0 \end{cases} \Rightarrow \begin{cases} -R_1 R_2 i_a + R_2 R_E (i_b - i_c) = R_2 V_{CC} - R_2 V_o \\ R_1 R_2 i_b + R_1 R_E (i_b - i_c) = -R_1 V_o \end{cases}$$


$$\Rightarrow R_1 R_2 (i_b - i_a) + (R_1 + R_2) R_E (1 + \beta) i_B = R_2 V_{CC} - (R_1 + R_2) V_o$$

$$\Rightarrow \frac{R_1 R_2 i_B}{(R_1 + R_2)} + R_E (1 + \beta) i_B = \frac{R_2 V_{CC}}{(R_1 + R_2)} - V_o$$

$$\therefore i_B = \frac{R_2 V_{CC} / (R_1 + R_2) - V_o}{R_1 R_2 / (R_1 + R_2) + R_E (1 + \beta)}$$


Activity 8

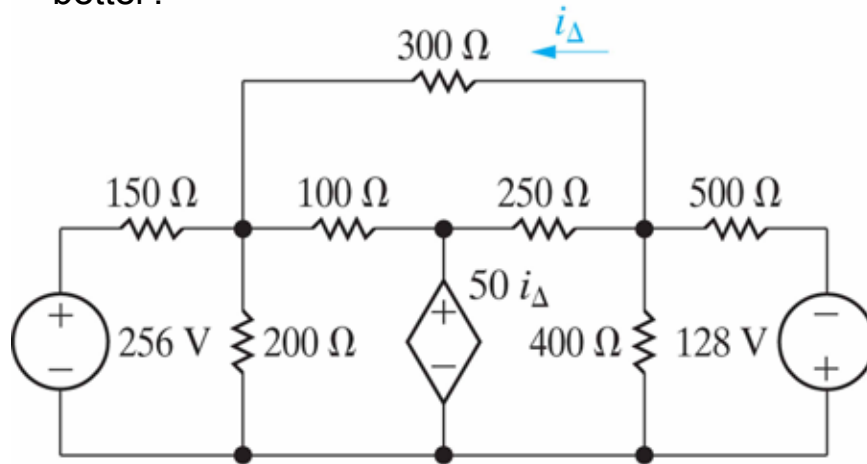Find power in the $300\ \Omega$ resistor, which method is better?




Solution

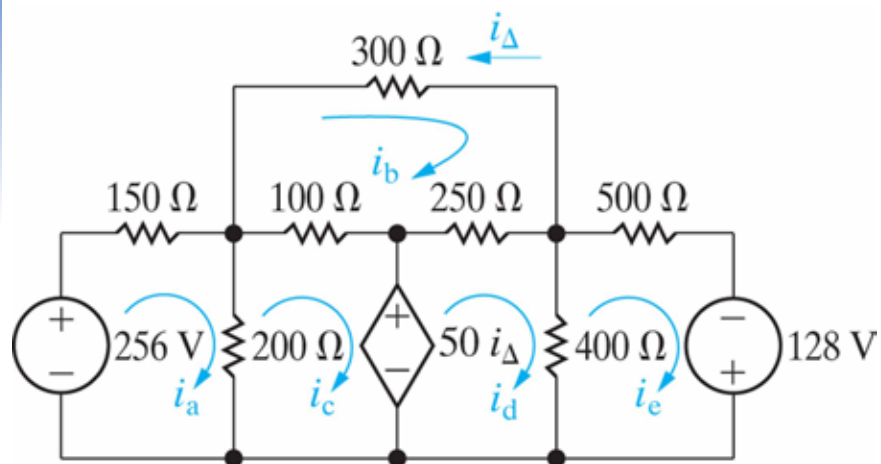- Mesh-current: 5 equations (note that $i_{\Delta} = -i_b$)




Solution

- Node voltages: 4 nodes, need only 3 equations

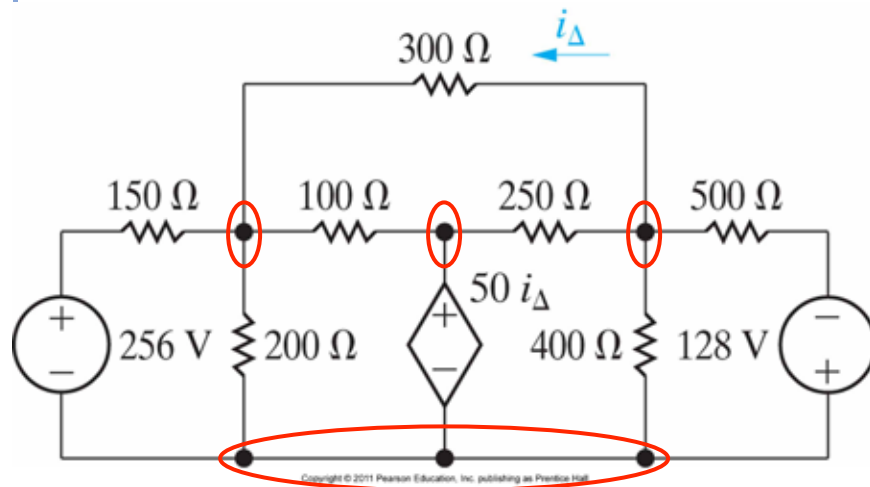

Method 1

Supernode:

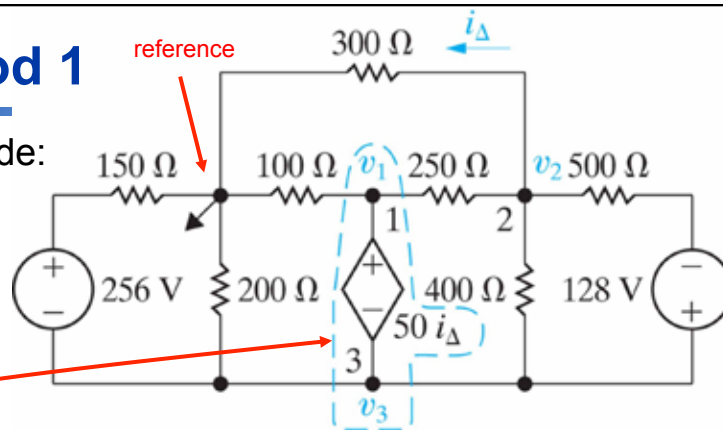


$$\frac{v_1}{100} + \frac{v_3}{200} + \frac{v_3 + 256}{150} + \frac{v_1 - v_2}{250} + \frac{v_3 - v_2}{400} + \frac{v_3 - 128 - v_2}{500} = 0$$

$$\frac{v_2 - v_1}{250} + \frac{v_2 + 128 - v_3}{500} + \frac{v_2 - v_3}{400} + \frac{v_2}{300} = 0 \quad \text{At node 2}$$

$$v_1 - v_3 = 50i_\Delta = 50 \frac{v_2}{300} \quad \text{Constraint at supernode}$$

Method 2

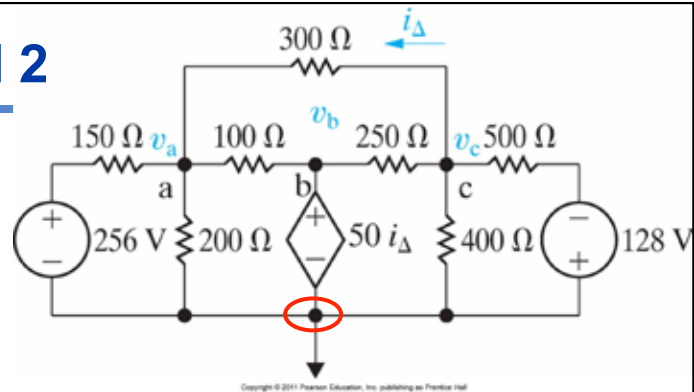

$$\frac{v_a}{200} + \frac{v_a - 256}{150} + \frac{v_a - v_b}{100} + \frac{v_a - v_c}{300} = 0$$

Node a

$$\frac{v_c - v_b}{250} + \frac{v_c}{400} + \frac{v_c + 128}{500} + \frac{v_c - v_a}{300} = 0$$

Node c

$$v_b = 50i_{\Delta} = 50 \frac{v_c - v_a}{300}$$



Constraint at supernode

Solution

- For both methods, the power dissipated by 300Ω resistor, is 16.57W.

Activity 9



Are these 2 circuits equivalent?

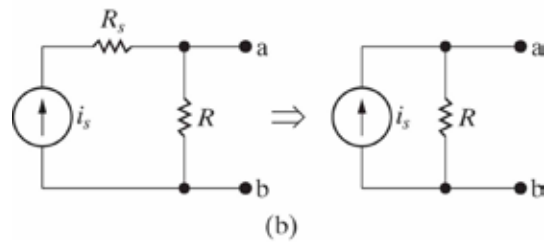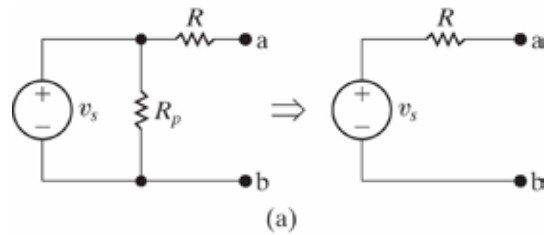

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Solution

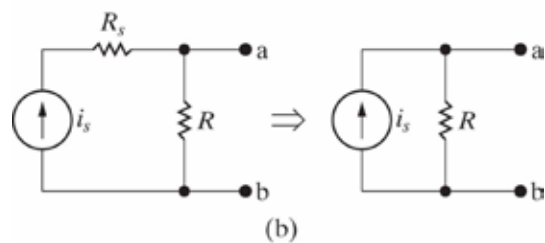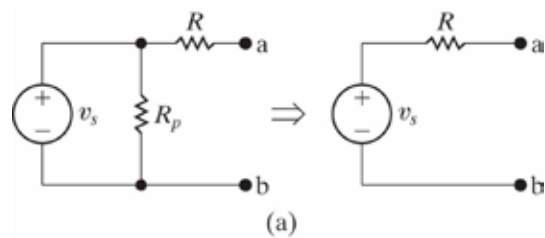
They are equivalent with respect to terminals a and b.



Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Activity 10

- Find Thevenin equivalent

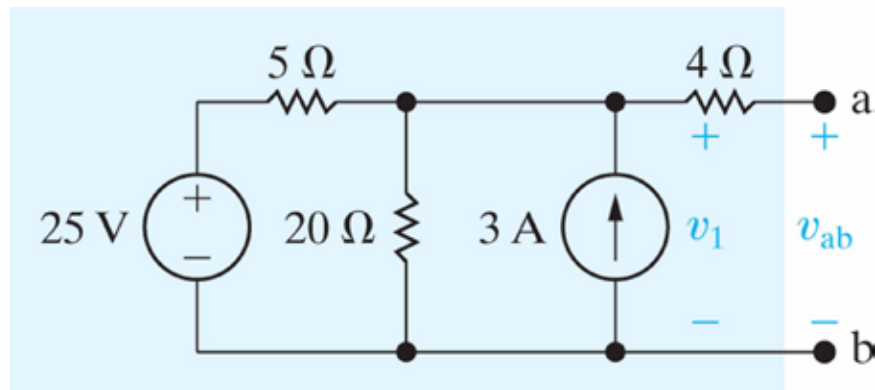


Solution

- Find v_{ab} using node voltage.

$$3 + \frac{25 - v_1}{5} = \frac{v_1}{20} \Rightarrow v_1 = 32V$$

$$\therefore v_{th} = v_1 = 32V$$

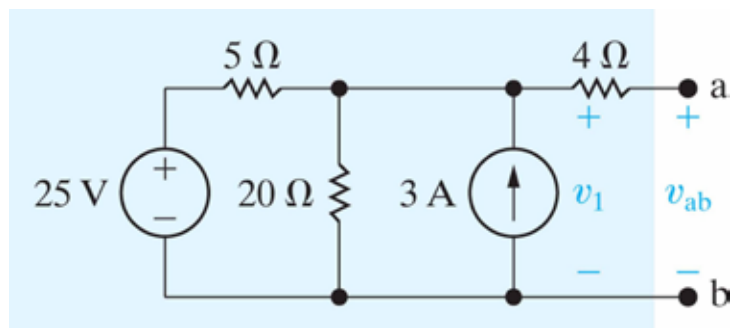


Solution

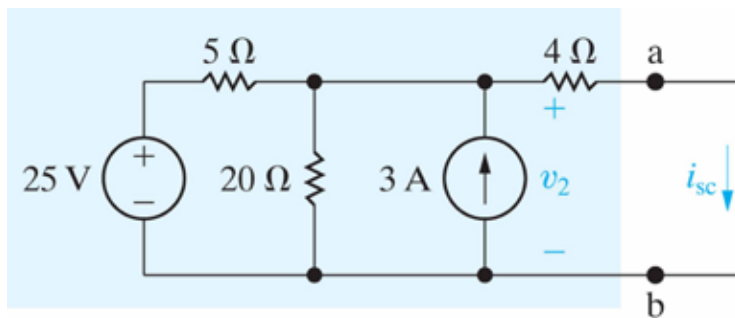2. find the short circuit current.

$$\frac{v_2 - 25}{5} + \frac{v_2}{20} + \frac{v_2}{4} - 3 = 0 \Rightarrow v_2 = 16V$$


$$i_{sc} = \frac{v_2}{4} = 4A \Rightarrow R_{th} = \frac{V_{th}}{i_{sc}} = \frac{32}{4} = 8\Omega$$



Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Activity 11


Find the Thevenin equivalent.

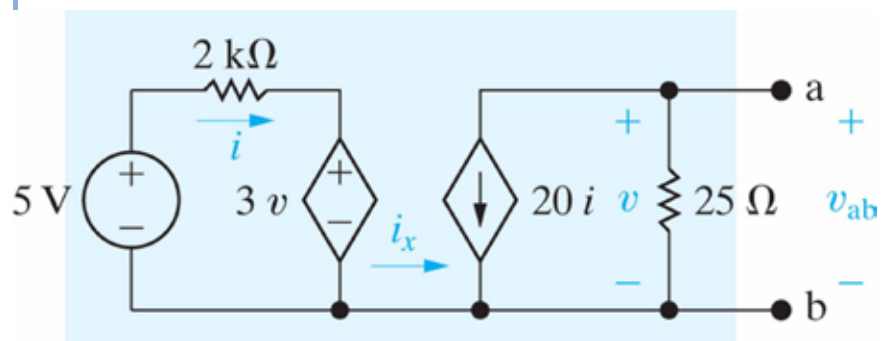

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Solution

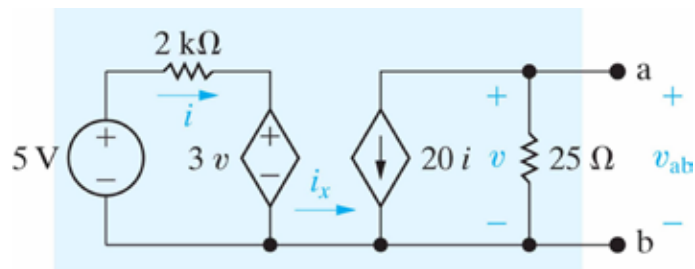
- Note that $i_x = 0$ (why?)
- KCL at node "a": $20i + \frac{v}{25} = 0 \Rightarrow v = -500i$
- KVL at left loop: $5 = 2000i + 3v = 500i \Rightarrow i = 10\text{mA}, v = V_{th} = -5\text{V}$
- Short circuit a and b, $v = 0 \Rightarrow 3v = 0, i = 5/2000 = 2.5\text{mA}$
 $i_{sc} = -20i = -50\text{mA} \Rightarrow R_{th} = V_{th}/i_{sc} = 100\Omega$



Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Activity 12

Find i_B

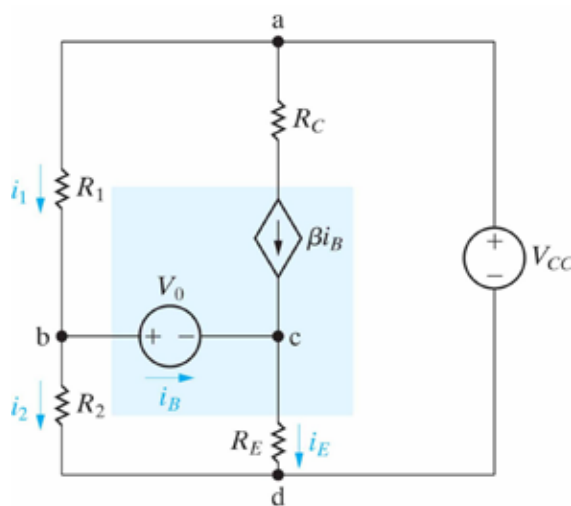


Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

Solution

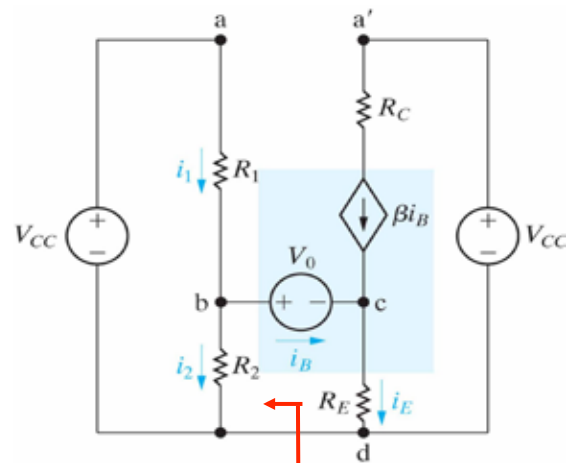1. Redraw it.
2. Find V_{TH} , R_{TH}

$$V_{TH} = \frac{R_2}{R_1 + R_2} V_{CC}$$

$$R_{TH} = R_1 // R_2 = \frac{R_1 R_2}{R_1 + R_2}$$




Find Thevenin
Equivalent

Solution

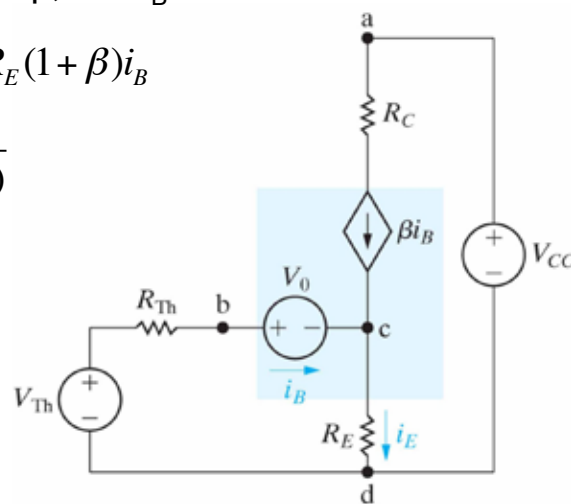3. KVL to the left loop, find i_B

$$V_{TH} = R_{TH} i_B + V_o + R_E (1 + \beta) i_B$$

$$i_B = \frac{V_{TH} - V_o}{R_{TH} + R_E (1 + \beta)}$$



Solution

4. Substitute V_{TH} and R_{TH} into i_B


$$i_B = \frac{V_{TH} - V_o}{R_{TH} + R_E(1 + \beta)}, V_{TH} = \frac{R_2 V_{CC}}{R_1 + R_2}, R_{TH} = \frac{R_1 R_2}{R_1 + R_2}$$

$$\therefore i_B = \frac{R_2 V_{CC} / (R_1 + R_2) - V_o}{R_1 R_2 / (R_1 + R_2) + R_E(1 + \beta)}$$

Activity 13


In the circuit below, the load resistor is matched to the Thevenin resistance, how much power is absorbed by the load resistor?

- A. 100 W
- B. 50 W
- C. 20 W
- D. 10 W

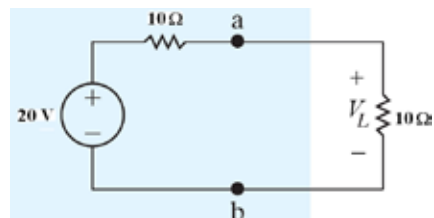

Activity 14

- Find i_2

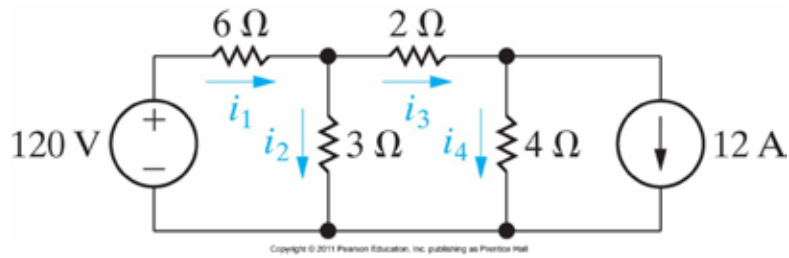



Solution

Deactivated current source

$$R_{total} = 6 + \frac{3 \times 6}{3 + 6} = 8 \Omega$$

$$i'_1 = \frac{120}{8} = 15 A$$
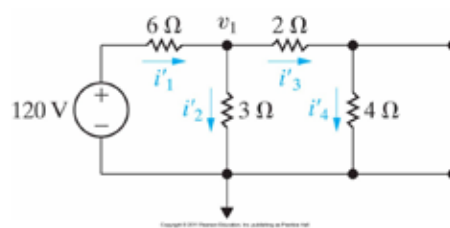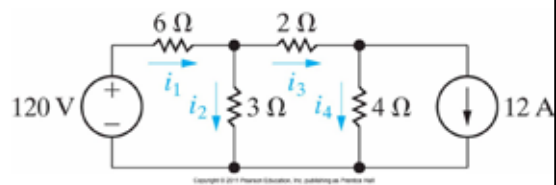
$$i'_2 = \frac{6}{3 + 6} \times 15 = 10 A$$



Solution



Deactivated voltage source

$$R_{6//3+2} = \frac{6 \times 3}{6 + 3} + 2 = 4 \Omega$$

$$i_3'' = \frac{12}{2} = 6 A, i_4'' = -6 A$$


$$i_2'' = -6 \times \frac{6}{3 + 6} = -4 A$$

$$i_2 = i_2' + i_2'' = 10 - 4 = 6 A$$

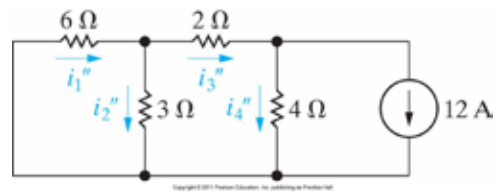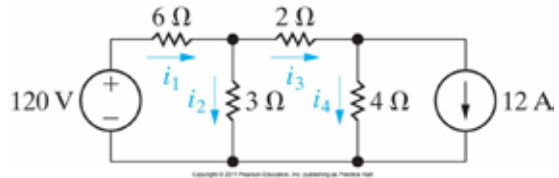

Activity 15

Find v_o using superposition

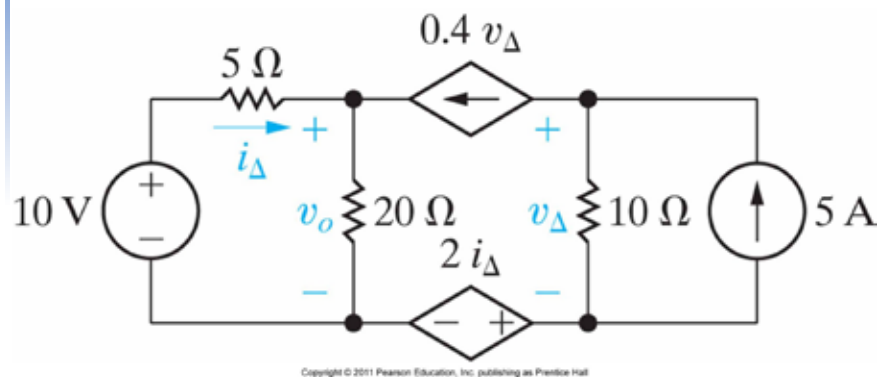


Solution

Deactivate current source

$$\text{KCL at right node: } \frac{v_{\Delta}'}{10} + 0.4v_{\Delta}' = 0 \Rightarrow v_{\Delta}' = 0$$
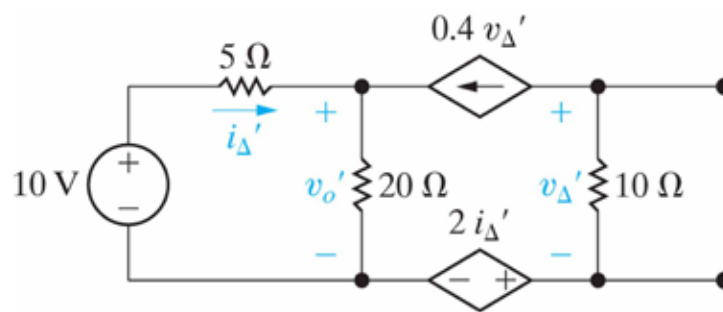
$$\text{Voltage divider: } v_o' = \frac{20}{5+20} \times 10 = 8V$$



Solution

Deactivate voltage source

$$\text{KCL at node a: } \frac{v_o''}{20} + \frac{v_o''}{5} - 0.4v_{\Delta}'' = 0 \Rightarrow 5v_o'' - 8v_{\Delta}'' = 0$$

$$\text{KCL at node b: } 0.4v_{\Delta}'' + \frac{v_b - 2i_{\Delta}''}{10} - 5 = 0 \Rightarrow 4v_{\Delta}'' + v_b - 2i_{\Delta}'' = 0$$

$$v_b = 2i_{\Delta}'' + v_{\Delta}'' \Rightarrow v_{\Delta}'' = 10V, v_o'' = 16V$$

$$v_o = v_o' + v_o'' = 8 + 16 = 24V$$

