

Q1. Multiple choice questions [10 marks]

- (1) D
- (2) C
- (3) B
- (4) E

Q2.

- (a) 3 essential nodes
- (b) 2, 3/4, 5/6/7/8
- (c) 4 meshes
- (d) one supernode 2 and 3/4
- (e) Using supernode concept at Nodes 2 and 3, we have:

$$\frac{V_2 - 5}{R_1} + \frac{V_2}{R_2} + \frac{V_2 - V_3}{R_3} + \frac{V_3}{R_4} + \frac{V_3 - V_2}{R_3} - 10mA = 0$$

$$\text{KVL in loop 23762: } V_3 - V_2 = 14500i_x = 14500 \frac{V_2}{R_2}$$

Write above two equations in standard form:

$$\frac{V_2 - 5}{5k} + \frac{V_2}{1k} + \frac{V_3}{10k} = 10mA \rightarrow 12V_2 + V_3 = 110$$

$$V_3 - V_2 = 14500i_x = 14500 \frac{V_2}{R_2} \rightarrow 15.5V_2 - V_3 = 0$$

Or:

Without using supernode concept, we can write two KCLs at Node 2 and 3.

$$\text{At Node 2: } \frac{V_2 - 5}{R_1} + \frac{V_2}{R_2} + \frac{V_2 - V_3}{R_3} + i = 0$$

$$\text{At Node 3: } -i + \frac{V_3}{R_4} + \frac{V_3 - V_2}{R_3} - 10mA = 0$$

Note: i is the current flow through dependent source.

$$\text{KVL in loop 23762: } V_3 - V_2 = 14500i_x = 14500 \frac{V_2}{R_2}$$

Above three equations lead to two standard form equations:

$$\frac{V_2 - 5}{5k} + \frac{V_2}{1k} + \frac{V_3}{10k} = 10mA \rightarrow 12V_2 + V_3 = 110$$

$$V_3 - V_2 = 14500i_x = 14500 \frac{V_2}{R_2} \rightarrow 15.5V_2 - V_3 = 0$$

(f) $i_x = 4\text{mA}$

Q3.

- (1) Equivalent capacitance: $0.12\mu\text{F}$
- (2) Time constant: 1.2ms
- (3) Voltage between nodes a and b

$$V(t) = 10e^{-\frac{5t \times 10^3}{6}} \text{V}$$

(4)

$$P = 4e^{-\frac{5t \times 10^3}{3}} \text{mW}$$