

Q1.

- (1) C
- (2) D
- (3) A
- (4) B

Q2.

- (a) 3 essential nodes
- (b) 2, 3, 4/5/6
- (c) 3 meshes
- (d) One supermesh for nodes 2 and 3
- (e) Using supermesh concept at Nodes 2 and 3, we have:

$$\begin{cases} I_1 R_1 + (I_1 - I_2) R_2 + 5 = 0 \\ (I_2 - I_1) R_2 + I_3 R_3 + 10 = 0 \\ i_x = I_1 - I_2 = I_3 - I_2 \end{cases}$$
$$\rightarrow \begin{cases} 5 I_1 - I_2 = -0.005 \\ -I_1 + I_2 + 2 I_3 = -0.010 \\ I_1 - I_3 = 0 \end{cases}$$

Or:

Without using supermesh concept, we can write 3 KVLs (assuming the voltage across dependent source is  $V_x$ ).

$$\begin{cases} I_1 R_1 + (I_1 - I_2) R_2 + 5 = 0 \\ (I_2 - I_1) R_2 - V_x + 10 = 0 \\ I_3 R_3 + V_x = 0 \\ i_x = I_1 - I_2 = I_3 - I_2 \end{cases}$$

- (f)  $i_x = 5 \text{ mA}$

Q3.

- (1) Equivalent inductance: 0.12mH
- (2) Time constant: 6  $\mu\text{s}$
- (3) Voltage between nodes "a" and "b"

$$V(t) = 40e^{-\frac{t \times 10^6}{6}} \text{ V}$$

- (4) Power dissipated:

$$P = 80e^{-\frac{t \times 10^6}{3}} \text{ W}$$