

Solution for Quiz3

Paper A

Q1.
V1 n0 0 DC 20
R1 n0 n1 5K
R2 n1 n2 3K
R3 n2 0 2K
C1 n1 0 0.2u
.END

Q2.

- (1). 100mA and 0V;
- (2). 110mA;
- (3). Critically damped;
- (4). $I(t) = -1000te^{-10^5t} - 0.01e^{-10^5t} + 0.11$

Paper B

Q1.
V1 n0 0 DC 20
R1 n0 n1 1K
R2 n1 n2 2K
R3 n1 0 5k
L1 n2 0 10m
.END

Q2.

- (1). 120mA and 0;
- (2). 100mA;
- (3). Underdamped;
- (4). $I(t) = 0.02e^{-31250t}\cos(39031t) + 0.016e^{-31250t}\sin(39031t) + 0.1$