

York University

Department of Electrical Engineering and Computer Science

Introduction to Simulation in Cadence

EECS 4612

Winter 2024-2025



Introduction

This tutorial will guide you through the steps of creating a library, designing schematics, running simulations, and drawing layouts in Cadence. Follow the steps closely to familiarize yourself with the tool.

Starting Up Cadence

If you want to run cadence through your laptop or a EECS Windows PC:

Go to Remote Lab (<https://remotelab.eecs.yorku.ca/>).

Use your EECS account to log in.

Select Remote Desktop (Crimson) or choose from one of the available "rl" hosts (rl01-rl25).

If you want to run Cadence through an EECS Linux PC:

You just need to login using your EECS account.

Once logged in, open a terminal and execute the following command create a folder in your home directory:

```
*****
```

```
mkdir ~/EECS4612
```

```
*****
```

then change the created directory using this command:

```
*****
```

```
cd EECS4612
```

```
*****
```


now to run cadence enter following command and press enter:

```
*****
```

```
gpd45
```

```
*****
```

 
Note: It is always recommended to run Cadence inside the created directory
Wait for the software to open (CIW window).



Creating a New Library in Cadence

Open the Library Manager:

 In the CIW window, go to the top menu and select Tools > Library Manager. This will launch the Library Manager window.



Create a New Library:

In the Library Manager, go to File > New > Library.


In the New Library window, enter the desired name for your library. For this tutorial, we will use "Test1".

Click OK to proceed.


Attach to an Existing Technology File:

After clicking OK, a window labeled Technology File for New Library will appear.

Select Attach to an existing techfile and click OK.

  **Select the Technology File:**

In the Attach Design Library to Technology File window, select the technology file (for example, gpdk180).




Click OK.

Note: In This tutorial gpdk180 is used. But in EECS4612 we work with 45nm technology- gpdk45. So, when you want to choose attached technology you have to select gpdk45. In future steps, whenever gpdk180 is mentioned, you must replace it with gpdk45.

Confirm Library Creation:

The new library should now appear in the Library Manager.

 
Your library is now ready to use with the attached technology file.




Creating a Schematic

Create a New Cell View:

 In the Library Manager, select your library (e.g., "Test1") and navigate to File > New > Cell View. In the Create New File window, enter a name for your design in the Cell Name field. We'll call it " Sch1".



 Click OK to open the Virtuoso Schematic Editor.



Design in the Schematic Editor:

Familiarize yourself with the menu and hotkeys. For instance:

Press I to add components (instances).

Press W to draw wires.


Press Q to modify properties of components.

Add Components:


Press I to open the Add Instance window (or follow this: create > instance).

Select the library (gpd180 for transistors), cell (e.g., nmos), and view (e.g., symbol).

 Place the component in the schematic. For instance, place an NMOS transistor.



 Note: In gpd45 you will see different type of transistors. For your project you should use **nmos1v** and **pmos1v**.



Use **analogLib** library for components like voltage sources, ground, and others.

Modify Component Properties:

After placing a component, select it and press Q to modify its properties, such as W and L of transistors and DC voltages of a voltage source.

Connect Components:

Press W to wire your components. Click on a component terminal (indicated by red squares) and connect it to other components.

Add Pins:

Use Create > Pin to add pins for input, output, or supply.

Use input and output for regular connections and InputOutput for supply nodes like vdd and gnd!

The image displays three sequential screenshots of the "Create Pin" dialog box in Cadence, illustrating different pin configurations.

First Screenshot: The "Names" field contains "In". The "Direction" dropdown menu is open, showing options: input, output, inputOutput, switch, jumper, tristate, and unused. "input" is currently selected.

Second Screenshot: The "Names" field contains "Out". The "Direction" dropdown is set to "output". The "Usage" dropdown is set to "schematic". The "Signal Type" dropdown is set to "signal". There are two unchecked checkboxes at the bottom: "Expand busses" and "Place multiple pins".


Third Screenshot: The "Names" field contains "AVDD AVSS". The "Direction" dropdown is set to "inputOutput". The "Usage" dropdown is set to "schematic". The "Signal Type" dropdown is set to "signal". There are two unchecked checkboxes at the bottom: "Expand busses" and "Place multiple pins".

Label Wires:

Press L to label wires. Enter a name in the Names field and click on the wire you want to put label on it.

Check and Save:

 
After designing your schematic, click the Check and Save button (a box with a check mark) to verify connections and save your work.



Running a Simulation (DC, AC, Transient, ...)

Launch ADE (Analog Design Environment):

 
Open the simulation environment via Launch > ADE L



Note: If a popup window appears and asks you about the License just press **Always**.

Set up transistor model libraries:

Via Setup > Model Libraries and set the section to **tt**

 **DC Analysis:**

Open the Choosing Analyses window via Analyses > Choose and select dc.

Check the Save DC Operating Point option and click OK.

AC Analysis:

In the same Choosing Analyses window, select ac and configure the settings as needed.

Transient Analysis:

Select tran from the analysis options, set the stop time, and choose moderate accuracy.

Ensure Enable is checked.

Choosing Analyses -- ADE L (2) [X]

Analysis

☒ tran ☐ dc ☐ ac ☐ noise

☐ xf ☐ sens ☐ dcmatch ☐ acmatch

☐ stb ☐ pz ☐ lf ☐ sp

☐ envlp ☐ pss ☐ pac ☐ pstb

☐ pnoise ☐ pxf ☐ psp ☐ qpss

☐ qpac ☐ qpnoise ☐ qpxf ☐ qpssp

☐ hb ☐ hbac ☐ hbstb ☐ hbnoise

☐ hbasp ☐ hbx

Transient Analysis

Stop Time

Accuracy Defaults (errpreset)

☐ conservative ☐ moderate ☐ liberal

☐ Transient Noise

Dynamic Parameter ☐

Enabled

Options...

OK Cancel Defaults Apply Help

Run the Simulation:

Click the Run button (green traffic light) to start the simulation.

Viewing Results:

Use the Results menu to view:

DC Voltages via Annotate > DC Node Voltages.

AC Voltage vs Frequency via Direct Plot > Main Form.



Alternatively, use the Results Browser to explore and manipulate the data.

Example: Inverter design and characterizing

Test Bench Setup:

a- Transient Analysis

  Create a schematic like the following picture. You can add **vdc** source and **vpulse** from **analogLib** library.



Select **vpulse** component on schematic and then press ‘Q’ for edit object properties:

Parameter	Value	Toggle
Number of noise/freq pairs	0	off
DC voltage		off
AC magnitude		off
AC phase		off
XF magnitude		off
PAC magnitude		off
PAC phase		off
Voltage 1	0 V	off
Voltage 2	1.8 V	off
Period	1u s	off
Delay time	500n s	off
Rise time		off
Fall time		off
Pulse width		off
Temperature coefficient 1		off
Temperature coefficient 2		off
Nominal temperature		off
Type of rising & falling edge		off

Buttons: OK, Cancel, Apply, Defaults, Previous, Next, Help

Then do the same thing for the **vdc** source and set VDC value to 1.1V.

Note: The nominal VDD in gpdk45 technology is 1.1 V. So, you must set the VDD value to 1.1 V. Also, in vpulse you need to set high voltage to 1.1 V.

Simulation Setup:

- ADE > Analyses > choose – Choose transient analysis and set stop time to reasonable value based on input pulse period.
- Select the outputs you want to plot after simulation (Outputs > to be plotted > select on design)

OR using Output > Direct Plot > Transient > Selecting on the schematic > press Esc (after running)

- **Run**

Choosing Analyses -- ADE L (2)

Analysis

☒ tran	☐ dc	☐ ac	☐ noise
☐ xf	☐ sens	☐ dcmatch	☐ acmatch
☐ stb	☐ pz	☐ lf	☐ sp
☐ envlp	☐ pss	☐ pac	☐ pstb
☐ pnoise	☐ pxf	☐ psp	☐ qpss
☐ qpac	☐ qpnoise	☐ qpxf	☐ qpssp
☐ hb	☐ hbac	☐ hbstb	☐ hbnoise
☐ hbsp	☐ hbxf		

Transient Analysis

Stop Time

Accuracy Defaults (errpreset)

☐ conservative ☐ moderate ☐ liberal



☐ Transient Noise

Dynamic Parameter ☐


Enabled ☒

Options...

OK Cancel Defaults Apply Help

  


Transient Result:

 

b-Vin Sweep (Plotting Vout Vs Vin):

Test Bench Setup:

 

Set up a DC analysis and sweep Vin in the configuration menu (Select Component Parameter > Select Component > Click on "V4" Dc Voltage Source).

Choosing Analyses -- ADE L (3) x

☐ stb	☐ pz	☐ lf	☐ sp
☐ envlp	☐ pss	☐ pac	☐ pstb
☐ pnoise	☐ pxf	☐ psp	☐ qpss
☐ qpac	☐ qpnoise	☐ qpxf	☐ qpssp
☐ hb	☐ hbac	☐ hbstb	☐ hbnoise
☐ hbsp	☐ hbxf		

DC Analysis

Save DC Operating Point ☒

Hysteresis Sweep ☐


Sweep Variable

☐ Temperature	Component Name
☐ Design Variable	Select Component
☒ Component Parameter	Parameter Name
☐ Model Parameter	

Sweep Range

☒ Start-Stop	Start	Stop
☐ Center-Span		

Sweep Type

 

Choosing Analyses -- ADE L (3) ✕

DC Analysis

Save DC Operating Point ☒

Hysteresis Sweep ☐

Sweep Variable

☐ Temperature

☐ Design Variable

☒ Component Parameter

☐ Model Parameter

Component Name

Select Component

Parameter Name

Sweep Range

☒ Start-Stop

Start Stop

☐ Center-Span

Sweep Type

Linear

☒ Step Size

☐ Number of Steps

Add Specific Points ☐


Add Points By File ☐

Enabled ☒

Options...


OK Cancel Defaults Apply Help

Run.

 


c- Vin Sweep (Plotting Vout Vs Vin) + PMOS Transistor Width Sweep:


Setting up the schematic

 


 
Inserting Wp variable: Right Click in the *Design Variable* window




 Copy From Cellview and import 1u as the initial value of the Wp variable.




  Sweep Wp (1um to 10um) from Tools > Parametric Analysis and Run



 

 
As the V_{in} and V_{out} are defined by setting the outputs (To be plotted) the figure will show output for V_{in} and Wp sweep.




Power Consumption

To evaluate the power consumption of a circuit in Cadence, it is essential to analyze both static and dynamic components to ensure optimal performance and efficiency. To do so, the following steps should be taken:

- Output > save all

 

 
- Select all and apply.
- Run the simulation
- From the plotted figure follow **windows > Assistants > Browser**



Select dcOp

Right click on pwr(W) > calculator

Send to ADL (Highlighted button)

 

Now, power consumption can be observed on ADE through any simulation.

ADE L (2) - LAB2 3_1_Amp schematic

Launch Session Setup Analyses Variables Outputs Simulation Results Tools Help

cadence

Design Variables

Name	Value
1 lb	10u

Analyses

Type	Enable	Arguments
1 dc	☒	t
2 tran	☒	0 1m liberal
3 ac	☒	10 10G Automatic Start-Stop

Outputs

Name/Signal/Expr	Value	Plot	Save	Save Options
1 Avd	wave	☒	☐	
2 Avcm	wave	☒	☐	
3 CMRR	wave	☒	☐	
4 getData("pwr" ?result ...	158.851u	☒	☐	

Plot after simulation: Auto Plotting mode: Replace

Drawing a Layout


Create a Layout:

In the schematic: Lunch > Layout XL


Or in the Library Manager, select your library and create a new cell view, choosing layout as the view type.

Display Option:

Press “E” and change display option as:

 

 Note: for the gpd45 set Minor spacing = 0.001, Major Spacing = 0.005, X Snap Spacing = 0.001 and Y Snap Spacing = 0.001.



Add Instances:

Place transistors and other components in the layout editor using Create > Instance. Or select the components from the schematic using Connectivity > generate > Selected from Source and click on the instance in the schematic view.

Draw Metal Layers:

Use Create > Shape > Path to draw metal connections. First, select metal1 in the LSW window, and adjust the width with Q.

Run DRC/LVS (Design Rule Check and Layout vs. Schematic):

Verify your layout using Pegasus > Run DRC and Run LVS to ensure it follows design rules.